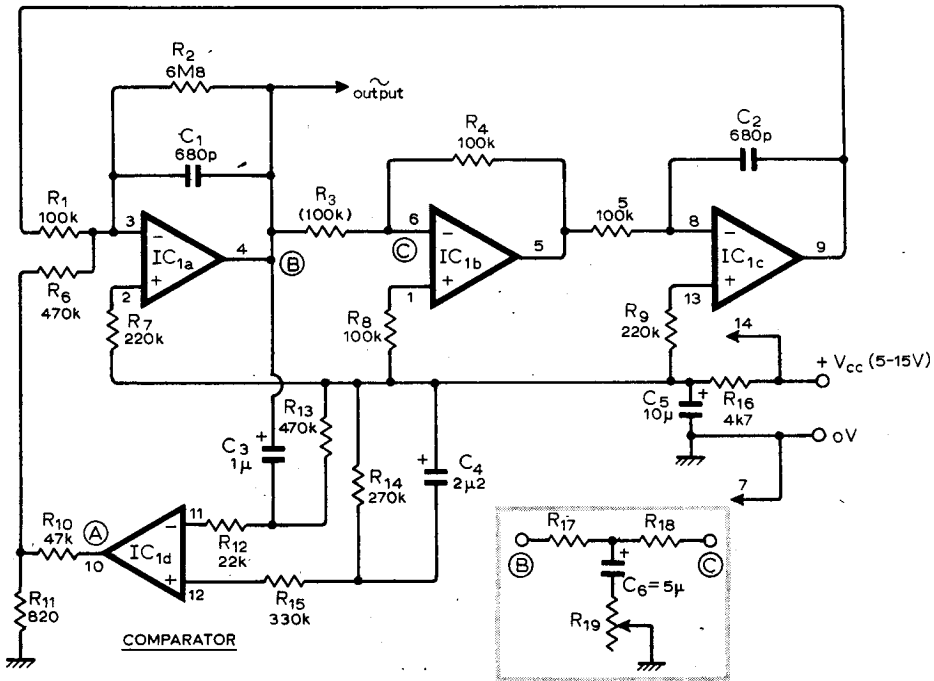


Sine oscillator uses c.d.a.

The circuit, new in realization but not in principle, produces moderately low-distortion sinewaves (typically 0.5% t.h.d.) which have negligible amplitude bounce on changing frequency. Further advantages are the ability to alter frequency with a single component and the low cost of the quad differential amplifier (LM3900N).

When the supply is switched on the comparator output initially goes to $+V_{cc}$; after about a second C_4 has charged and the output rapidly slews to 0V. This shocks the bandpass filter, formed by the two integrators IC_{1a} , IC_{1c} , and the inverting amplifier IC_{1b} , and causes it to ring. The resultant sinewave causes the comparator to produce a square wave which



is fed back into the loop to sustain oscillation. Sinewave amplitude is stabilized by virtue of the constant square wave input and is typically $0.25V_{cc}$ pk-pk, its purity being proportional to filter Q .

Frequency of oscillation (2.34kHz) and $Q(62)$ are:

$$2\pi f = \sqrt{\frac{R_4}{C_1 R_1 C_2 R_5 R_3}} \quad Q = \omega C_1 R_2$$

Note that owing to the internal compensation of the amplifiers significant Q -

enhancement occurs at frequencies greater than a few kHz and this may lead to oscillation of the filter itself.

To vary the frequency the inset network can be used in place of R_3 , the effective impedance being

$$R_{13} = R_{17} + R_{18} + \frac{R_{17} R_{18}}{R_{19}}$$

T. J. M. Rossiter,
Corpus Christi College,
Cambridge.