

# wireless world circard

## Set 13: Alarm circuits

Rather than dwelling on circuit techniques, the background article brings the concept of data domains to the fore. This interesting approach is an adaptation of that by Malmstadt and Enke, referenced in the article. Card 9, on signal domain conversion, loosely connects with the theme in presenting voltage-to-current and voltage-to-frequency converters and their converse.

Transducer circuits included in this set measure pressure and temperature on card 10, displacement, velocity and acceleration on card 12, and light on card 1. Another important group of circuits, for sensing variations in conductance, is applied to flame, smoke and gas detection on card 1, and as a water-level or moisture-sensitive alarm on cards 10 & 11. Most resistance sensors are bridge circuits, of course, & card 2 shows some useful variants, including a bridge/amplifier combination with both input and output referred to earth. The security alarm of card 11 is one application of the bridge. Cards 4 & 5 are of simple hysteretic level sensors.

Information on driving filament lamps and relays is provided on card 8, while card 4 gives various output stage configurations. Further load-driving circuits can make direct use of the 555—see cards 3 & 5, which also detail other uses of the i.c.

|   |    |
|---|----|
| Flame, smoke and gas detectors                      | 1  |
| Bridge circuits                                     | 2  |
| Time delay and generator circuits                   | 3  |
| Level sensing and load driving                      | 4  |
| Applications of 555 timer                           | 5  |
| Frequency sensing alarm                             | 6  |
| Digital alarm annunciators                          | 7  |
| Filament lamps and relays                           | 8  |
| Signal domain conversion                            | 9  |
| Pressure, temperature and moisture-sensitive alarms | 10 |
| Security, water level and automobile alarms         | 11 |
| Electromechanical alarms                            | 12 |

# Alarm circuits

In this topic the viewpoint changes. Previously in Circards, circuits have been described as separate entities, with the articles laying a foundation, and the cards showing the practical alternatives. The dilemma is that the title used here, though commonly applied to the topic, can be misleading. This is because so many "alarm circuits" have several identifiable sub-sections each of which can be readily classified under headings such as those of previous series e.g. Schmitt trigger and astable circuits. Even heading this article "Alarm systems" might confuse since it could convey the idea of a conglomeration of alarms.

A typical alarm arrangement is shown in block diagram form in Fig. 1. An alarm signal is required from some output transducer when the signal from an input transducer indicates a particular fault condition. The intervening blocks are required to process the signal representing the fault condition, to detect a particular voltage/current level which is an analogue of the input parameter, and to deliver power to the output transducer. Before considering each of these sub-sections individually, there is a general principle which can be very helpful in considering such systems—the concept of data domains.

## Data domains

Information on physical systems is obtainable in the form of physical quantities such as force, distance, energy. The required information may often have to be obtained by monitoring some more complex property involving a function of the more common parameters. In few cases is the information in such a form that it can be conveyed and displayed directly. It has to be transmitted through some medium or series of media first. To the practising engineer the medium is not the message but rather the barrier that hinders the appearance of that message.

In passing through these media the information takes on new forms or dimensions. For each new set of dimensions we may postulate a domain in which the data exists. Within that domain there may take place further conversions without going outside the domain. Thus the first main division is between inter-domain and intra-domain conversions. The division is arbitrary since the selection of domain interfaces is arbitrary. One possible division is discussed below but readers may have their own ideas on this.\*

For the purpose of this article, the domains are determined by the following considerations: is the data (a) continuous or discontinuous and (b) instantaneous or

not. These conditions applied to electrical phenomena provide us with four domains. In addition there is the much larger physical domain ( $P$ ) containing all non-electrical data. For other disciplines it is this domain that would be sub-divided into more convenient packages, as for example the heat/light/sound divisions of physics. The electrical domains are thus

|               | Instantaneous | Non-instantaneous |
|---------------|---------------|-------------------|
| Continuous    | $A$           | $t$               |
| Discontinuous | $D_p$         | $D_s$             |

An  $A$  or amplitude function e.g. voltage/current/resistance, is an electrical signal precisely and continuously related to some other function which may or may not be within the  $A$  domain itself. It has an instantaneous value which is a measure of some property of the unknown. An example is the electrical resistance thermometer where the resistance ( $A$  domain) is a continuously variable function of the instantaneous temperature ( $P$  domain) i.e. a  $P-A$  domain conversion occurs.

A  $t$  function is also continuously variable, but to represent the data a finite time must elapse i.e. it is not instantaneous. This property should not be confused with the finite delays imposed by the physical limitations of systems, which prevent the instantaneous change in an  $A$  function. A  $t$  function will have corresponding delays in responding to changes in the data, but even with a fixed input requires a finite time to complete the conversion. An example is an oscillator whose frequency is proportional to a voltage. To determine that frequency at least one period must elapse (often many) and the data conversion is non-instantaneous. Such a voltage-controlled oscillator is performing an  $A-t$  conversion, the amplitude of the output waveform being irrelevant as all the data resides in the time-function.

Conversions may take place through more than one domain, and the shortest route in a system is not necessarily the best. If we wish, for example, to convert from temperature to frequency (a  $P-t$  conversion)

we can do so by constructing an oscillator whose frequency is temperature dependent†, or we can use a thermocouple to generate a direct voltage that, amplified, controls a v.c.o. The latter can be considered as a  $P-A-A-t$  conversion with the voltage amplifier being an  $A-A$  converter i.e. input and output both existing in the amplitude or  $A$  domain. Better linearity of frequency against temperature could be achieved in this second approach.

Where the data is required in digital i.e. discontinuous form, a similar distinction can be made as to whether the data appears simultaneously at input and output (within the delay constraints mentioned above) or whether a finite time is required for the data conversion. The two categories resulting are the parallel and series modes respectively ( $D_p$  and  $D_s$ ). They may also be thought of as a spatial and temporal ordering of the data—a pulse train representing the data in serial form conveys that information correctly regardless of the frequency if the order pattern is correct. In a digital voltmeter the data might be converted into serial form following an initial voltage-to-frequency/time conversion, while it would be stored and displayed in parallel form. The data domain conversion pattern would then be  $A-t-D_s-D_p$ .

Within each domain, there may be a great variety of possible forms for the data, and multiple conversions can and do take place. Even a "simple" amplifier may have individual stages best viewed as  $V-I$  and  $I-V$  converters, while a voltage amplifier can be regarded as a  $V-V$  converter.

## Transducers

These are the interfaces between the physical ( $P$ ) and electrical domains ( $A$ ,  $t$ ,  $D_p$ ,  $D_s$ ). The range and variety is too large to cover in such an article as this, but some obvious

\*This approach was prompted by the excellent book "Digital Electronics for Scientists" by Malmstadt & Enke (Benjamin) which proposed a slightly different division.

†This can also be considered as a hidden form of  $P-A-t$  conversion since the temperature affects some  $A$  parameter such as  $R$ ,  $C$  etc.

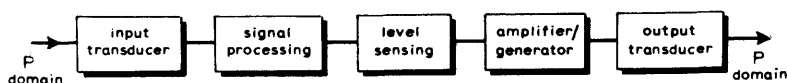


Fig. 1. Typical alarm circuit with input and output transducers.

examples are worth discussing. If an electrical conductor is subject to temperature variations its conductivity will vary. For metallic conductors the temperature coefficient of resistance is normally positive and the characteristic is sufficiently well-defined to allow precision thermometers to be based on it (platinum resistance thermometers). For semiconductors the coefficient may be negative or positive and of much greater magnitude though generally less well defined. This makes devices such as thermistors, which depend on this property, particularly useful in alarm circuits as a relatively sharp transition takes place in the resistance value and switching of a load is simplified.

If such a resistance which depends on a physical parameter is incorporated in a bridge circuit (Fig. 2) then by suitable selection of the other resistors the critical resist-

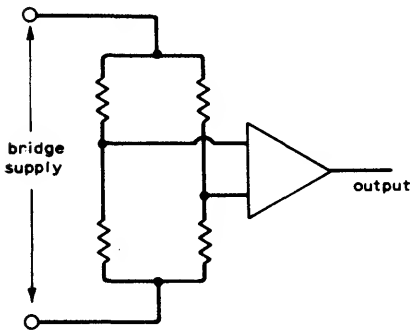


Fig. 2. Bridge circuit for including a sensing resistor.

ance value of the transducers may be made to correspond to the bridge balance point. Any high gain differential input amplifier may be used to detect this change of polarity about the balance point, providing a large output swing. Addition of positive feedback provides hysteresis, minimizing the output switching that would occur from noise or other stray input signals, when close-to-balance comparators or general-purpose operational amplifiers may be satisfactory in such applications.

Other physical parameters may affect the resistance of particular conductors and semiconductors. For example a polycrystalline film of cadmium sulphide in darkness has a very high resistance ( $> 1M\Omega$ ), while exposure to sunlight may drop that resistance to a few hundred ohms. Where the changes are as extreme as this, the variable resistance could simply be placed in series

with a supply voltage and the load to provide a direct if somewhat imprecise alarm.

Other semiconductors when exposed to particular gaseous impurities show similar large variations in resistance and are now used in gas and smoke detectors, though they require a separate power source to raise their operating temperature. Even the basic resistance thermometer mentioned above can be adapted to detect other physical parameters; for example the flow of air or other fluid across a heated filament removes the heat more rapidly causing the resistance to fall. Thus detection of fluid velocity is a possibility.

Other transducers give a voltage or current that is a function of a physical parameter; the e.m.f. of a thermocouple and the current flow in a reverse-biased photodiode are examples. Yet others may involve the variation of electrical parameters such as capacitance or inductance, coupling between coils, etc. In such cases a common alternative to the bridge technique, still viable with the substitution of a.c. drive to the bridge, is to make the frequency of an oscillator depend on the variation of the reactance used, and follow the oscillator by some form of frequency-sensitive switch.

Following the input transducer the signal may need to be amplified, filtered or modified (domain conversion of some form) in some signal-processing stage prior to being fed to a level-sensing stage. In some cases the two functions can be combined, as operational amplifiers having very high gain can suffice. If the output of the level-sensing device is insufficient in magnitude to drive the required load then a further power stage may have to be substituted (Fig. 1).

Additionally it may be required to cause this output signal to be an audible tone or an interrupted voltage for flashing a lamp. Either case could require an astable oscillator or similar form of generator (Fig. 3). A monostable circuit may be interposed to delay the onset of the alarm output for some period after the appearance of the fault signal and logic gating would be added in more complex systems to generate alarm outputs that depend on a particular combination of input parameters.

Thus most alarm systems can be broken down into simpler blocks and the block diagram of a burglar alarm could be identical with that for a circuit intended to sense icy conditions on a road. By appreciating and making use of this principle, it is often possible to make very economical designs of alarm circuits by adapting the best individual blocks from previously published alarm circuits. The major design problem is then that of making the blocks compatible in respect of supply voltage load requirements and the like.


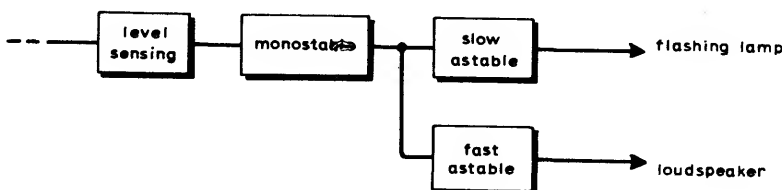


Fig. 3. Arrangement for operating a lamp and/or loudspeaker.

## Flame, smoke and gas detectors

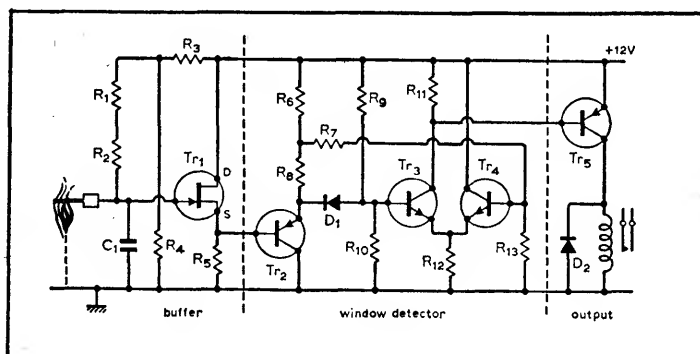

## Component values


Tr<sub>1</sub>: TIS34Tr<sub>2</sub>: BC126Tr<sub>3</sub>: BC125Tr<sub>4</sub>: BC125Tr<sub>5</sub>: BC126D<sub>1</sub>: 1N914D<sub>2</sub>: 1N4002C<sub>1</sub>: 1nFR<sub>1</sub>, R<sub>2</sub>: 15MΩR<sub>3</sub>: 2.2kΩR<sub>4</sub>: 12kΩR<sub>5</sub>: 6.8kΩR<sub>6</sub>: 1.5kΩR<sub>7</sub>, R<sub>9</sub>: 12kΩR<sub>8</sub>: 820ΩR<sub>10</sub>: 15kΩR<sub>11</sub>: 2.7kΩR<sub>12</sub>: 4.7kΩR<sub>13</sub>: 22kΩ

Semiconductors not critical but TIS34 may need selection because of parameter spread.

## Flame detector

A flame offers a low conductance path to ground. In series with R<sub>1</sub>, R<sub>2</sub>, that conductance defines a range of potentials on the gate of Tr<sub>1</sub>, that leaves the emitter of Tr<sub>2</sub> at a high enough potential to keep D<sub>1</sub> out of conduction, but not so high as to bring Tr<sub>4</sub> into conduction via R<sub>7</sub>. Hence Tr<sub>3</sub>, Tr<sub>5</sub> conduct holding on the relay—interlocked with the supply for fail-safe operation. If the flame is extinguished Tr<sub>1</sub> gate goes high, driving Tr<sub>4</sub> on via Tr<sub>2</sub>, R<sub>7</sub>. This removes the

drive from Tr<sub>3</sub>, Tr<sub>5</sub> and the relay. A short circuit to ground at the input reduces the base potential of Tr<sub>2</sub> bringing D<sub>1</sub> into conduction and cutting off Tr<sub>3</sub> and hence the output. The mid-section of the circuit offers a window action with the relay being held on for a restricted range of flame resistances, higher and lower values giving drop-out. The resistance is high requiring a high input resistance buffer; the output is conventional.

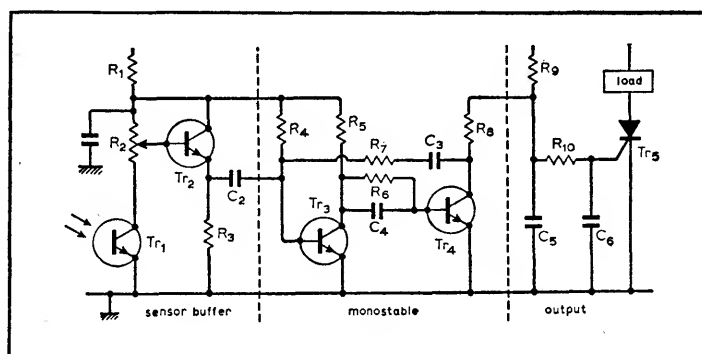
Tr<sub>1</sub>: LS400Tr<sub>2-4</sub>: 2N712Tr<sub>5</sub>: C106FR<sub>1</sub>: 1kΩR<sub>2</sub>, R<sub>9</sub>: 100kΩR<sub>3</sub>: 15kΩR<sub>4</sub>: 470kΩR<sub>5-7</sub>, R<sub>10</sub>: 10kΩR<sub>8</sub>: 3.9kΩC<sub>1</sub>: 16μFC<sub>2</sub>, C<sub>4</sub>: 22nFC<sub>3</sub>: 0.1μFC<sub>5</sub>: 50μFC<sub>6</sub>: 4.7nF

Transistor types not critical.

## Smoke detector

When detecting the interruption of light by smoke, to avoid the effects of ambient illumination, etc., the light beam may be chopped at source and the resulting a.c. from Tr<sub>1</sub> above used via buffer Tr<sub>2</sub> to trigger the monostable circuit around Tr<sub>3</sub>, Tr<sub>4</sub>. This prevents the potential

applied to R<sub>10</sub> from rising sufficiently to fire the thyristor. If the load is a horn having an interrupter switch in series with its coil, the thyristor can cease conduction on removal of the gate drive (alternatively a.c. drive to the load would be required).

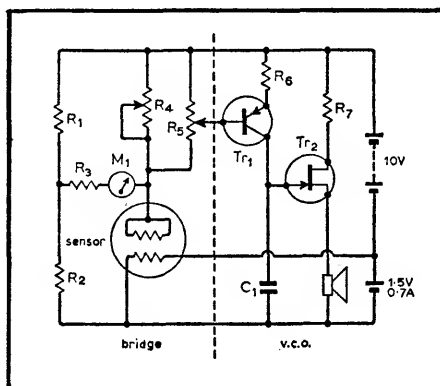Tr<sub>1</sub>: BC126Tr<sub>2</sub>: TIS43C<sub>1</sub>: 0.22μF

LS: 8 to 80Ω


R<sub>1</sub>: 470ΩR<sub>2</sub>: 3.3kΩR<sub>3</sub>, R<sub>4</sub>: 10kΩR<sub>5</sub>: 100kΩR<sub>6</sub>, R<sub>7</sub>: 1kΩ

## Gas detector

A particular gas-sensor (TGS from Figaro Engineering, Shannon, Ireland) has two fine wires embedded in a semiconductor. One is used to heat the material, with the resistance between it and the second being reduced on the absorption of deoxidizing gas or smoke. The sensor is sensitive to concentrations of <0.1%, with resistance falling from many tens of kilohms to as low as 1kΩ at high gas concentrations. Response is non-linear and with a recovery time in excess of one minute. Bridge unbalance is

detected on M<sub>1</sub> and though repeatable has to be interpreted qualitatively unless special calibration procedures are available. When the unbalance brings Tr<sub>1</sub> into conduction, C<sub>1</sub> charges until the unijunction Tr<sub>2</sub> fires and the cycle recommences. The audible note in the loudspeaker rises from a succession of clicks to a continuous tone as the gas concentration increases. A Schmitt trigger would allow relay drive, while the audible alarm could be transferred to the flame-detector circuit, for example.

## Bridge circuits

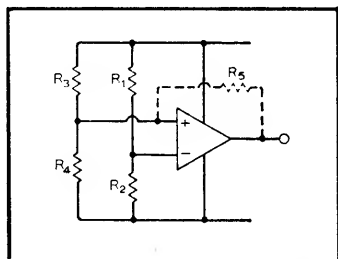

### Components

ICs: 741,  $V_s \pm 15V$   
 $R_1$  to  $R_4$ :  $10k\Omega$ ,  $R_5$ :  $1M\Omega$   
 Bridge voltage:  $1.5V$  (Fig. 2)

### Circuit description

Three bridge configurations are shown. In each case the bridge is composed of four resistors,  $R_1$  to  $R_4$ , and the circuits are basically Wheatstone bridges with balance occurring for  $R_1/R_2 = R_3/R_4$ . Substitution of impedances  $Z_1$  to  $Z_4$  would leave the balance requirements unchanged, and other variants such as the Wien bridge can be produced. For resistive elements it may be possible to supply the bridge and amplifier from a common d.c. supply and a high-gain op-amp detects departure from balance. A small amount of positive feedback via  $R_5$  helps reduce jitter in the output when close to balance, but gives hysteresis to the balance sensing.

● If a separate supply is required for the bridge, one bridge balance point may be grounded, removing the need for high common-mode rejection for the amplifier (Fig. 2). The errors in all these circuits include voltage offset of the amplifier, 1 to 5mV for untrimmed general-purpose op-amps, and input currents/offset, 10nA to  $1\mu A$  for conditions as before. For balance

detection to within 0.1% this implies bridge voltages in excess of 1V and currents of up to 1mA.

● By opening the bridge and embedding the amplifier in the network as shown, balance is achieved for the same relationship between the resistances, but with input and output both with respect to ground.

Fig. 3 has an output that is a linear function of the departure of  $R_2$  from the balance condition ( $R_1, R_3, R_4$  assumed constant as reference resistors). For d.c. applications the input may be one or other of the supply voltages. In all cases best sensitivity is achieved for  $R_1/R_2 \rightarrow 1$ . If the resistor whose value is being sensed has to have a low resistance, power wastage is avoided by keeping the other pairs of resistances high.

● Another method of achieving input and output as ground-referred signals, is to use an amplifier with push-pull outputs and single-ended input. A simple case is the single transistor, Fig. 4, where the power supply, if properly by-passed, closes the bridge when used for a.c.

measurement/sensing. The example shown would pass all frequencies except the notch frequency by  $1/2\pi RC$ , though with appreciable attenuation near the notch.

● For many purposes, the availability of a centre-tapped supply provides a "phantom-bridge" action. If the ratio of positive to negative supplies remains constant then taking one input of the sense amplifier to the centre-tap leaves only a half-bridge externally. Used for example with photodiodes, the output voltage is proportional to the unbalance currents in the diodes, i.e., to the degree of unbalance in the illumination of the diodes. Because the diodes act as constant-current devices the circuit Fig. 5, is much more tolerant of drift in the centre-tap than for purely resistive elements. The negative feedback gives a linear output-unbalance characteristic. Reversal of the amplifier input terminals would give positive feedback, introducing a switching action and hysteresis as in the first diagram.

● Some i.c.s have internal potential dividers which can effectively form part of a

bridge. The 555 timer, for example, has its two comparators tapped at  $\frac{1}{3}$  and  $\frac{2}{3}$  of the supply voltage via a resistor chain with very good stability to the ratio of their values; the absolute values are not important for such an application (Fig. 6). The lower-threshold detector ("trigger") when held high prevents any output change (input 1 is assumed high) regardless of the status of the reset terminal. The reset terminal regains control only when the trigger input falls below the level accurately defined by the potential divider. With the trigger taken from an external potential divider containing the required sensing element the bridge—balance sensing can be obtained.

### Further reading

Markus, J. (ed.), *Bridge circuits*, in *Electronics Circuits Manual*, McGraw-Hill, 1971, pp. 84-9.

Graeme, Tobey & Huelsman, *Operational Amplifiers*, McGraw-Hill, 1971.

### Cross references

Set 1, cards 9 & 10.  
 Set 9, cardr 1 & 11.  
 Set 13, cards 1 & 3.

Fig. 2

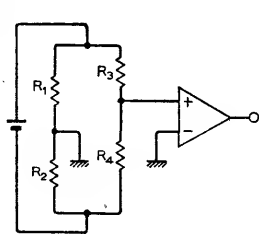


Fig. 3

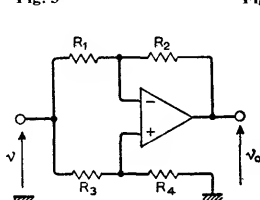


Fig. 4

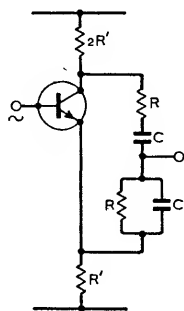


Fig. 5


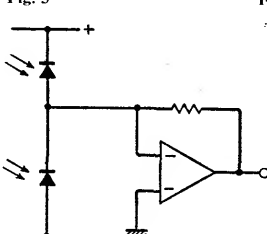
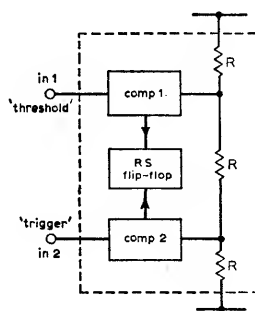
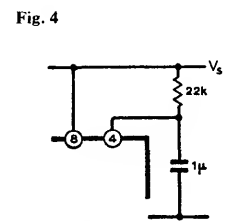
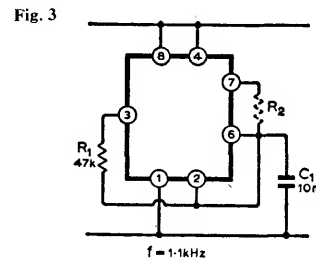
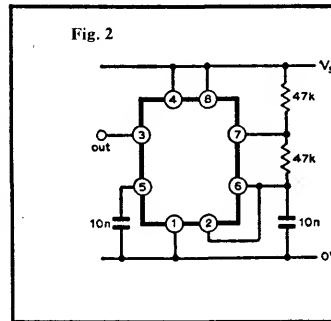


Fig. 6

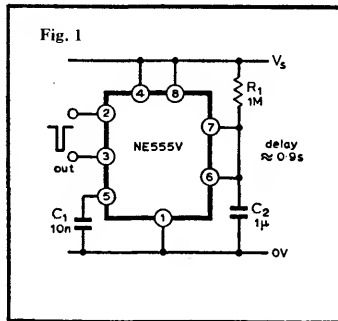

## Time delay and generator circuits

**Circuit description**

An i.c. such as the 555, with internal comparators driving a set-reset flip-flop offers great flexibility in the design of alarm systems. With pin 2 high, the capacitor is held low via pin 7. A negative-going edge on 2 allows  $R_1$  to charge  $C_2$  until the potential on 6 passes  $2V_S/3$ , when the original state is restored.

- Linking the inputs of the two comparators (2 and 6) to the discharge path (7) causes the potential at the common point to cycle between  $V_S/3$  and  $2V_S/3$ , set by an internal Potential-divider (Fig. 2). For both circuits the output has switching characteristics comparable to a t.t.l. gate because of a similar totem-pole output stage. An audible alarm is available by connecting a loudspeaker (3–25Ω) between  $V_S$  and pin 3. If  $V_S$  is +5V, the on/off condition of the alarm may be controlled by driving pin 4 from the output of a t.t.l. gate.

- An astable can also be constructed by feedback from the output to the paralleled comparator inputs. When the

output is high,  $C_1$  is charged (Fig. 3) through  $R_7$  until the upper threshold is passed; the output switches low and  $C_1$  is discharged until the trigger value set by pin 2 is passed. Timing is set by the less well-defined output amplitude, and the frequency is less stable than the basic circuit. Addition of  $R_2$  varies mark-space ratio.

- If the reset terminal 4 is coupled to an RC network (Fig. 4), then a time-delay can be introduced at switch-on, before which firing of the circuit as a monostable cannot be achieved.

- A monostable using c.m.o.s. inverters can use very high-value resistors, giving time delays of  $> 1s$  with capacitors of  $< 1\mu F$ . In Fig. 5, a short-duration excursion of the input from + to ground sets the output to zero for the monostable period (about 3s) because the output of the first inverter is high, as is the input of the second until  $R_2$  can pull the gate down by charging  $C_1$ . The high impedance makes such monostables useful as touch-operated circuits.

- A related astable circuit Fig. 6

shows an additional resistor  $R_1$  which isolates  $C_1$  from the rapid charge/discharge imposed by the gate protection diodes in both these circuits. The resistor improves the timing stability.

- The output stage of an astable/monostable circuit is important where high voltage/current/power is required. For the 555 timer, the output stage is similar to the typical t.t.l. output (Fig. 7), but with a Darlington-connected top section. The positive output is thus at least 1V below supply while the low output can be to within 0.1V of ground at low currents. Above 50mA the voltage drops may reach 2V and 1V respectively.





- For some applications the open-collector output of t.t.l. devices such as SN7401 gives convenient driving of loads, while other devices such as SN7406 will withstand collector-emitter voltages of up to 30V. (Fig. 8).

**Further reading**


Three articles, by Robbins, Orrel and De Kold, in *Electronics*, 21 June, 1973, pp. 128-32.

Application note for XR-2556 timing circuit, Exar, 1973.

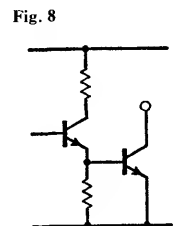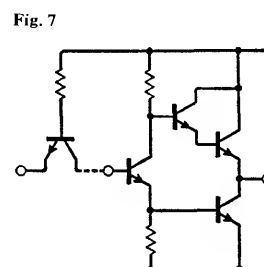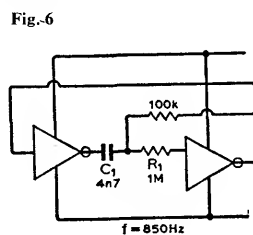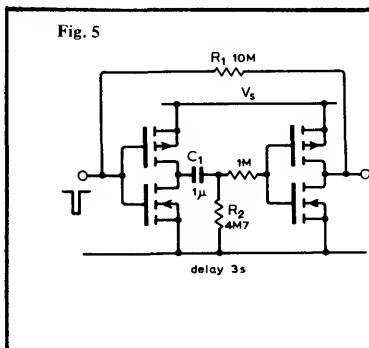**Cross references**  
Set 3, card 9.  
Set 13, card 5.



Level sensing and load driving

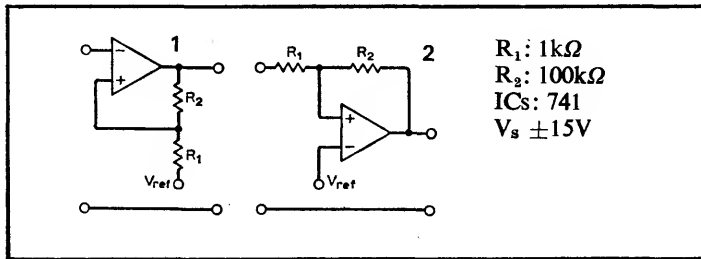


$R_1$ :  $1k\Omega$   
 $R_2$ :  $100k\Omega$   
 ICs: 741  
 $V_s \pm 15V$

Circuit description

The basic level-sensing circuits shown may be used with or without positive feedback, to obtain an output change as the input passes a defined level or levels. For  $R_2 \rightarrow \infty$ ,  $R_1 \rightarrow 0$ , amplifier gain determines the range of input voltages for which the output is not switched hard to one or other extreme. (Typically 1 to 20mV for comparators, required to operate at high speeds; 0.1 to 5mV for op-amps where accuracy of level-sensing makes their slower operation an acceptable penalty.) Hysteresis introduced by positive feedback allows the circuit to latch into a final state after the first excursion through a given level, provided the input cannot reverse its sense sufficiently to pass back through the other switching level. These circuits can thus perform the combined functions of level-sensing and set-reset action required in many alarms if for example the signal initiating the set action, while the reset action is a negative-going pulse over-riding the

former, e.g., a resistor taken from the non-inverting input to the negative rail.

- An adaptation of the output stage shown in Fig. 5 gives an output when the p.d. across either  $R_1$  or  $R_2$  exceeds about 0.6V. In the former case this corresponds to a positive input voltage defining sufficient positive supply current via  $R_3$ , i.e.,  $V_{in}R_1/R_3 \approx 0.6V$ . Similarly a negative input voltage switches the output via  $Tr_1$ . The switching action is not particularly sharp as it uses only the gains of the transistors.
- A standard window comparator gives sharper switching but requires two amplifiers/comparators and still requires an additional transistor if an output swing comparable to supply voltage is required, e.g. for efficient switching of lamps relays, etc. particularly at higher currents.
- A previously-described output stage (set 2) gives push-pull drive using one op-amp as driver. Resistors  $R_1$ ,  $R_3$  are selected to keep  $Tr_1$ ,  $Tr_2$  out of conduction in quiescent state. The op-amp is

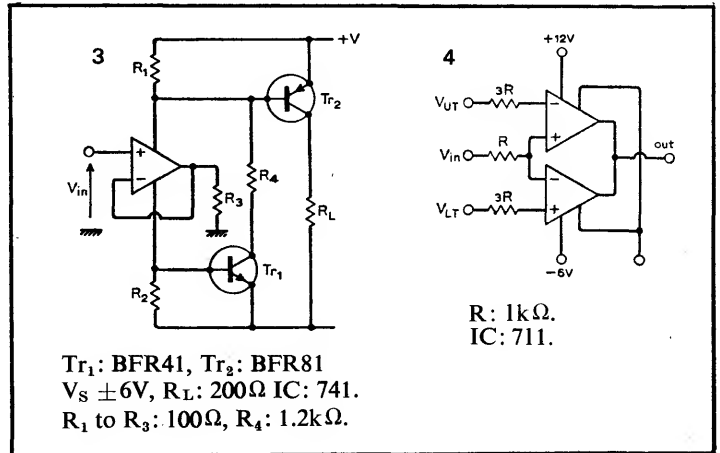

$Tr_1$ : BFR41,  $Tr_2$ : BFR81  
 $V_s \pm 6V$ ,  $R_L$ :  $200\Omega$  IC: 741.  
 $R_1$  to  $R_3$ :  $100\Omega$ ,  $R_4$ :  $1.2k\Omega$ .

$R$ :  $1k\Omega$ .  
 IC: 711.

used in any of the sensing/oscillating modes that result in p.d.s across  $R_3$  sufficient to drive  $Tr_1, Tr_2$  into conduction. Either may be used alone for driving lamps, relays, or the circuit as shown may be capacitively coupled to a loudspeaker for a.c. power drive.


- An output stage using a bridge configuration requires antiphase switching at the inputs, but gives a load voltage whose peak-peak value is twice the supply voltage. This is equally applicable to audio alarms or to driving of servo systems for which it was designed.
- Complementary m.o.s. buffers may be used to drive complementary output transistors as shown and with the aid of an additional inverter a similar stage provides a bridge output. The transistor base current is limited to a few milliamperes but in all these output

stages, short-duration current spikes may occur during the output transitions. Diode protection against inductive voltage spikes as in Fig. 5 should be used for loudspeaker, relay and solenoid loads.

- Any of the output transistors may in principle be replaced by the compound transistor pairs if higher peak currents are needed. To reduce the above requirements it is worth considering the use of f.e.t. devices as the input transistor of the pair.

Further reading

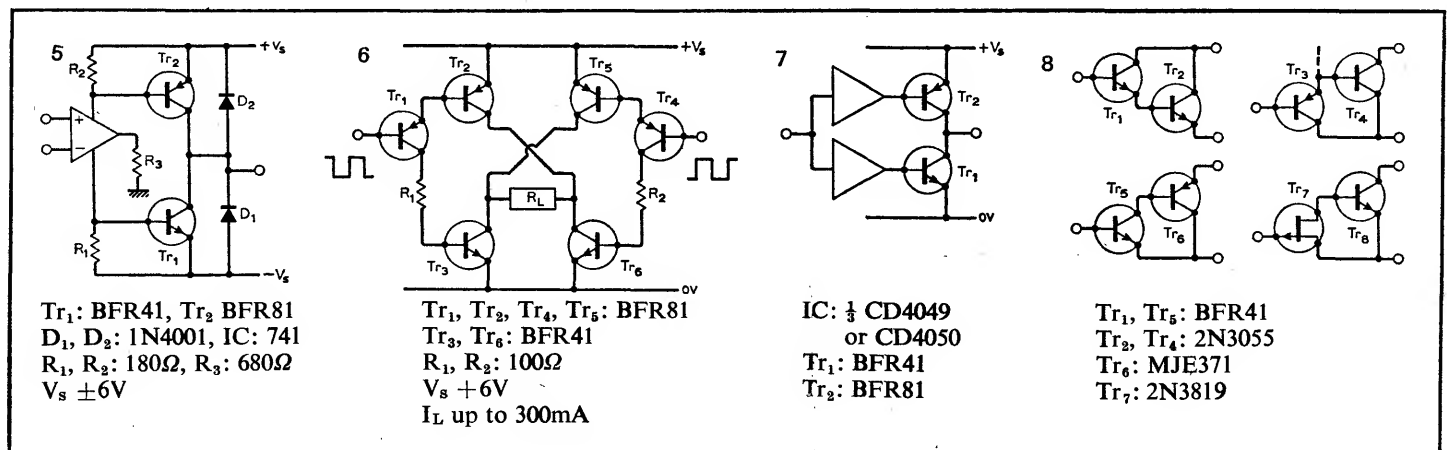Electronic Circuits Manual (Markus, McGraw-Hill, 1971): Main circuits—pp. 1-6; lamp control circuits—pp. 344-9; trigger circuits—pp. 889-907. Linear Integrated Circuits Handbook, Marconi-Elliott, pp. 165-170. Industrial Circuits Handbook, SGS-Fairchild, pp. 6-13.





$Tr_1$ : BFR41,  $Tr_2$ : BFR81  
 $D_1, D_2$ : 1N4001, IC: 741  
 $R_1, R_2$ :  $180\Omega$ ,  $R_3$ :  $680\Omega$   
 $V_s \pm 6V$

$Tr_1, Tr_2, Tr_4, Tr_5$ : BFR81  
 $Tr_3, Tr_6$ : BFR41  
 $R_1, R_2$ :  $100\Omega$   
 $V_s + 6V$   
 $I_L$  up to 300mA

IC:  $\frac{1}{3}$  CD4049  
 or CD4050  
 $Tr_1$ : BFR41  
 $Tr_2$ : BFR81

$Tr_1, Tr_5$ : BFR41  
 $Tr_2, Tr_4$ : 2N3055  
 $Tr_6$ : MJE371  
 $Tr_7$ : 2N3819

## Applications of 555 timer

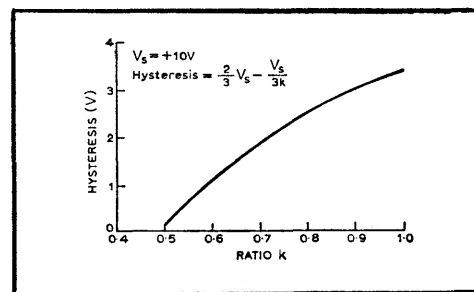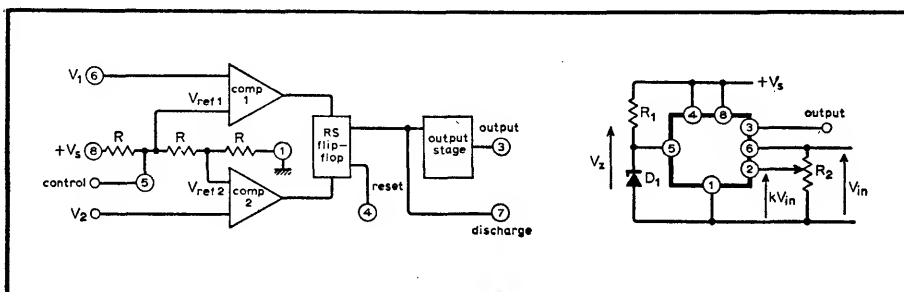

## Typical performance

IC: NE555V (Signetics),  $V_S$  +10V.

$R_1$ : 2.2k $\Omega$ ,  $R_2$ : 10k $\Omega$ .

$k=0.6$ ,  $D_1$ : 5.6-V Zener diode.

Upper set point: 5.7 ( $V_Z$ ).

Lower set point: 4.75V ( $V_Z/2k$ ).

Output swing: 9V for  $R_L \geq 250\Omega$ .

If  $R_1$ ,  $D_2$  omitted,  $V_{ref1} = 2V$ ,

$V_{ref2} = V$  and set points become

$2V$  and  $V/k$ .

## Circuit description

The 555, designed as a timing circuit with either monostable or astable operation, has internal circuit functions that allow it to be used for many other purposes. In alarm systems, the power output stage that permits currents of either polarity of up to 200mA (though 50mA minimizes voltage losses) means that lamps and relays can be driven quite readily. When used as an astable circuit the output square wave can be applied to a loudspeaker to give an audible alarm, while a voltage fed to the control terminal modulates the frequency for warble or two-tone effects. As a monostable circuit it can be used to provide delays from microseconds to minutes, allowing, for example, a warning alarm to be held for a defined period of time after the appearance of the condition being detected. In such cases the condition (closure of a switch in a burglar alarm for example) is converted into a negative-going pulse, applied to the trigger input. A further application for the device involves the controlled hysteresis provided by the two comparators biased from an internal potential divider. With  $V_1 > V_{ref1}$  the output is driven negative via the flip-flop which ignores any further excursions of  $V_1$  about  $V_{ref1}$  in either sense. When  $V_2$  falls below  $V_{ref2}$  the flip-flop is reset, the output converted positive. In the astable

circuit  $V_1 = V_2$ ,  $V_{ref1} = 2V_S/3$ ,  $V_{ref2} = V_S/3$  and the capacitor is charged and discharged between  $V_S/3$  and  $2V_S/3$ .

## Component changes

IC: Motorola MC1455.

Separate comparators could be used with independent reference voltages or a single comparator with hysteresis defined by feedback—see Series 2.

$V_S$ : 4.5 to 18V. At low voltages the saturation voltages at the output may not allow adequate drive to electromechanical/filament lamp loads.

$R_1$ ,  $D_1$ : Any network to provide constant voltage at control input. Voltage may be to within 1V of common line or positive supply, but for optimum performance should be close to  $2V_S/3$ .

$R_2$ : 1k to 1M $\Omega$ . At low values, excessive loading of source; at high values inaccuracies due to threshold current of up to 0.25 $\mu$ A.

## Circuit modifications

● Use as battery charger illustrates method well (Fig. 1). Upper threshold when  $k_1 V_L = V_Z$ ; lower threshold when  $k_2 V_L = V_Z/2$ . When upper threshold is exceeded output at pin 3 reverse-biases diode  $D_2$  and battery discharges into load when present. As voltage  $V_L$  falls below lower threshold, voltage at pin 3 rises and charges battery through limiting resistor  $R_2$ . Hysteresis may be reduced towards zero for  $V_Z/k_1 \rightarrow V_Z/2k_2$ .


● To increase hysteresis, the potential at pin 5 may be reduced following a transition through the upper threshold. This may be done as in Fig. 2 by using output pin 3 via a diode—both thresholds are varied if the diode is replaced by a resistor.

● The increased swing simplifies the triggering of a following 555 used as a Schmitt trigger, as the capacitor voltage in Fig. 2 can approach zero.

Complete alarm systems can be based on such circuits combining level sensing, time delays and waveform generation, as well as audible alarms.

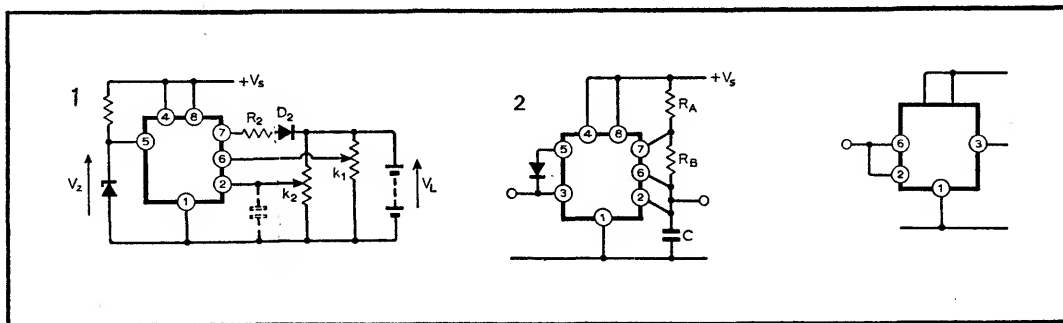
## Further reading

Four articles, by De Kold, McGowan, Harvey & Pate, in *Electronics*, 21 June 1973, pp. 128–32.





## Frequency sensing alarm

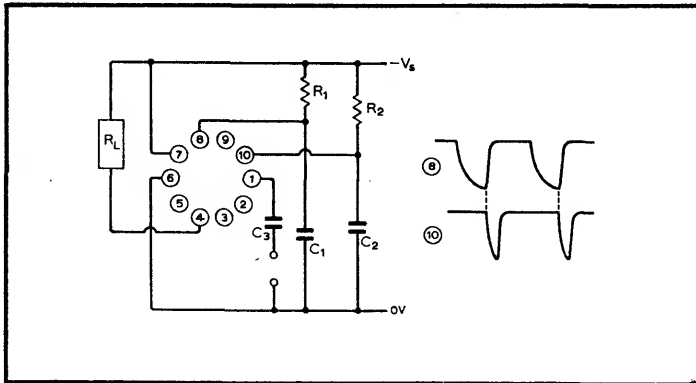

## Circuit description

The circuit is a monolithic m.o.s. i.c. which uses external RC elements to fix the frequencies at which the circuit provides a switching action. It does so via two separate switching times defined by  $C_1R_1$  and  $C_2R_2$ , as from a pair of monostable circuits with the second time interval being initiated at the end of the first. The input may be a repetitive signal of arbitrary waveform, provided the amplitude is in excess of 100mV pk-pk (though it should not exceed 20V pk-pk). Internally this is presumably squared by a Schmitt type of circuit to trigger the monostables. Three distinct conditions may exist; if the period of the received signal is  $t = 1/f$  and the two delays are  $t_1 = k/C_1R_1$   $t_2 = k/C_2R_2$ , then  $t < t_1$ ,  $t_1 < t < t_1 + t_2$ ,  $t > t_1 + t_2$ . These conditions are distinguished by additional internal circuitry that allows sensing of frequencies above a given datum or within a given band with a switched output that can be made to latch on or off, toggle at a lower frequency ( $f/20$ ), and hold on during signal failure or for temporary interruptions of the signal. The upper frequency in the band mode or the datum in the datum mode is set by  $t_1$  and the lower band-frequency by  $t_1 + t_2$ . The circuit provides frequency-sensing function similar to comparators, Schmitt-triggers and window-comparators.

## Component changes

Vs: -12 to -22V some samples operate with reduced accuracy down to -8V.  
 Vin: 0.1 to 20V pk-pk.  
 freq. set points: 0.01Hz to 50kHz.  
 response time: within 5 to 10 cycles of receipt of correct frequency.  
 $R_1, R_2$ : 100k to 1M $\Omega$ .  
 $C_1, C_2$ : 250pF to 1 $\mu$ F.  
 $C_3$ : 10nF to 1 $\mu$ F (not critical).

## Circuit modifications

● As the lower frequency in the band mode is affected by time constant  $C_2R_2$  in the original circuit while the upper frequency is not, variation of  $R_2$  increases the band by variation of its lower bound only. For  $C_1 = C_2 = C$ , variation in the tapping point of  $R_C$  in (a) at left leaves the sum of the time constants unchanged at  $(R_A + R_B + R_C)C$ , i.e., it is the lower frequency that remains constant while the upper frequency is changed.  
 ● Variation in both frequencies while retaining a reasonably constant ratio of  $f_2:f_1$  (the

## Typical performance

IC: FX101 (Consumer Microcircuits) -12V supply, -3mA + load current.  
 Vin: 250mV pk-pk to pin 1.  
 $R_1, R_2$ : 470k $\Omega$ .  
 $C_1$ : 22nF,  $C_2$ : 10nF,  $C_3$ : 0.1 $\mu$ F.  
 Ground pins: 2, 3, 9.  
 Output on for:  $f > 150$ Hz ( $f \approx 1/0.6C_1R_1$ ).  
 Pin 1 signal input.  
 2 grounded, holds switch state during signal loss.  
 open, switch off.  
 ground via 'C', switch off after signal break of

200ms/ $\mu$ F for 'C'.

3 ground, circuit automatically resets on change off.  
 open, switch latches when turned off.  
 5 link to 8, switch latches when turned on. Ground 3.  
 link to 8 via 'C', hysteresis in datum point of 'C'/ $C_1 \times 100\%$ .  
 9 ground, datum mode, switches on for  $f > f_1$ .  
 open, band mode, on for  $f_1 > f > f_2$ .  
 link to pin 5, output toggles at  $f/20$  when in band.

equivalent of a constant Q), can be achieved by varying the common bias applied to the resistors. If strong dependence on supply voltage is to be avoided the bias voltage should be supply-proportional as in (b).


● Constant-current sources allow linear control of period against a separate reference voltage, which may be supply-proportional (centre).  
 ● Filament lamps may be driven via an additional transistor, currents up to 100mA or so being provided by circuit on right. Direct drive of reed relays, i.e.ds is possible though current is marginal.

## Further reading


Volk, A. M. Two i.c. digital filter varies passband easily, *Electronics*, 15 Feb. 1973, p. 106.  
 McKinley, R. J., Versatile digital circuit filters highs, lows or bands. *Electronics*, 21 June 1971, p. 66.  
 FX101: Consumer Microcircuits data sheet D/026.

## Cross references

Set 1, cards 6 & 7.

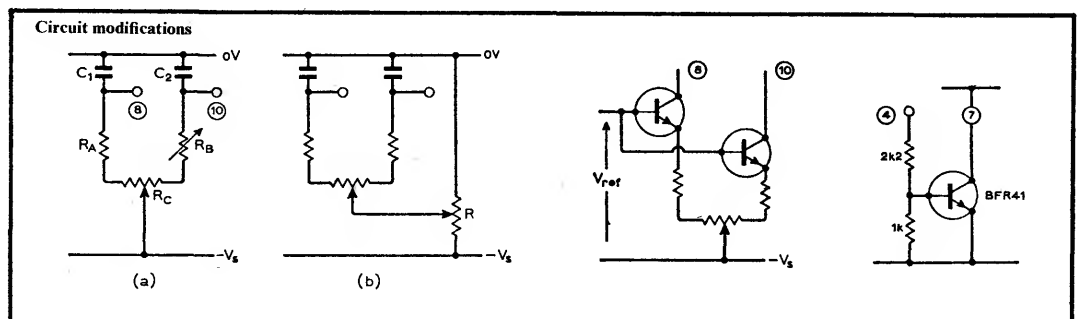

## Digital alarm annunciators

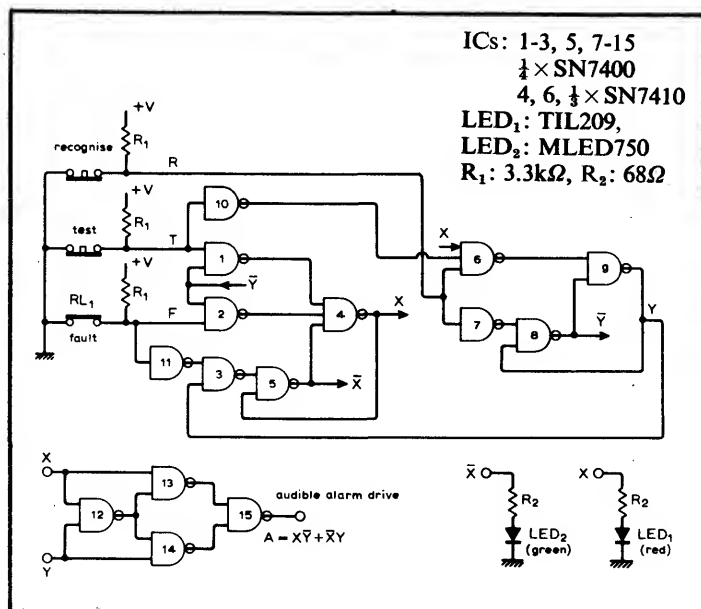

### Circuit function


It is assumed that a fault condition is the opening of relay contact  $RL_1$ , though any other sensor that maintains the NAND-gate input terminal at a low ('0') level is adequate. A fault will turn off a "safe" green light and illuminate a "danger" red light, and operate an audible alarm. When the "recognize" push-button is depressed, the red light stays on, but the alarm is silenced. When the fault clears, the alarm is restarted, the green light comes on and the red light goes off. The "recognize" button is again pushed to reset circuit to its normal state.

### Circuit operation

Consider the circuit in its normal state where inputs  $R$ ,  $T$  and  $F$  are at zero volts (or binary zero), i.e.  $R=T=F=0$  and  $X=0$  ( $\bar{X}=1$ ),  $Y=0$  ( $\bar{Y}=1$ ) and hence  $LED_1$  is energized (green) and  $LED_2$  (red) is off.
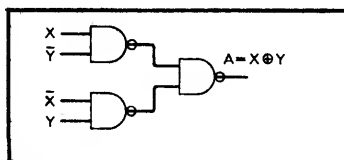
### Circuit modification

As  $X$ ,  $\bar{X}$ ,  $Y$ ,  $\bar{Y}$  are available, the exclusive-OR function of  $A$  can be obtained as shown.




If a fault occurs,  $RL_1$  opens,  $F$  goes high (or binary one), i.e.  $F=1$ , causing  $X=1$  ( $\bar{X}=0$ ), but the state of  $Y$  (and  $\bar{Y}$ ) remains as before. Hence  $A=1$ , and triggers audible alarm. Pushing the recognize button causes  $R=1$ , and as  $F=1$ ,  $T=0$ , then  $Y=1$  ( $\bar{Y}=0$ ), but  $X$  does not change.  $LED_1$  remains on, but  $A=0$ , and alarm stops. This state will be maintained until the fault is cleared.

When the fault is cleared,  $R=F=T=0$ ,  $Y$  does not change, but  $X=0$  ( $Y=\bar{X}=1$ ,  $X=\bar{Y}=0$ ). Hence  $LED_2$  is illuminated,  $A=1$ , and the alarm operates.

Final recognition of the fault clearance is obtained from  $R=1$ , which will return circuit to its normal state, i.e. for  $R=1$ ,  $F=T=0$ ,  $Y=0$  and  $X=0$ . Depression of the test button will check  $LED_1$  and the alarm, when started from normal state with  $LED_2$  on.
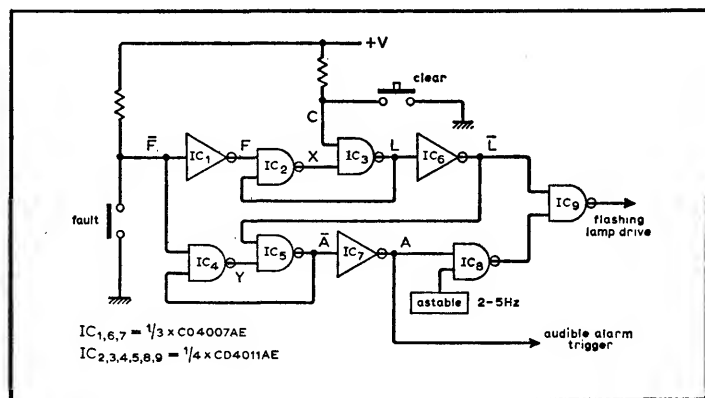
### Further reading


Zissos, D., Logic Design Algorithms, Oxford 1972.


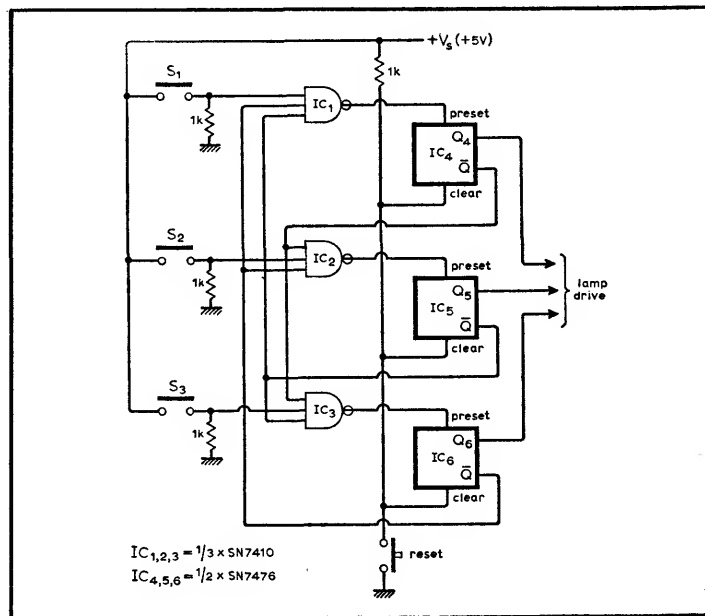
### Circuit description

Complementary-m.o.s. devices may be used in the circuit above to minimize stand-by power consumption. Normal safe condition obtains with  $L=A=0$ ,  $\bar{F}=1$ . When the fault-switch closes,  $F \rightarrow 1$  and since  $L$  is already low,  $X \rightarrow 0$ . Memory circuit  $IC_2$ ,  $IC_3$  does not change. Also since  $\bar{F}=0$ ,  $Y \rightarrow 1$ , and hence  $\bar{A}$  is forced to zero, therefore  $A=1$ . This transition may be used to switch an audible alarm.

Simultaneously the oscillator gate is opened which will cause lamp flashing at a rate determined by the astable frequency. If the fault is rectified, the alarm condition is maintained until the clear button is pressed causing  $C$  to below. Hence  $L \rightarrow 1$ , and will latch in this condition via memory circuit  $IC_2$  and  $IC_3$ . Also  $\bar{L}=0$ , thus  $A=0$ , this condition being maintained via  $IC_4$  and  $IC_5$ , and the alarm is silenced.



### Circuit description

Arrangement right allows detection of first-fault occurrence from three sensors  $S_1$ ,  $S_2$ ,  $S_3$ , this number being restricted by the number of inputs available per NAND-gate. Outputs  $Q_4$ ,  $Q_5$ ,  $Q_6$  are set to zero when the reset button is depressed. The  $\bar{Q}$  output of each flip-flop is applied to the other

two NAND gates, but not to the one associated with itself. Hence two of the three inputs of each gate are high. If  $S_2$  closes, for example,  $IC_2$  output goes low, and this negative-going edge being applied to  $IC_5$  preset terminal sets  $Q_5=1$  (and hence  $\bar{Q}=0$ ). Therefore  $IC_1$  and  $IC_3$  are now inhibited and cannot respond to a fault condition.

## Filament lamps and relays

Fig. 1

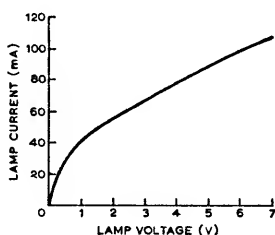


Fig. 2


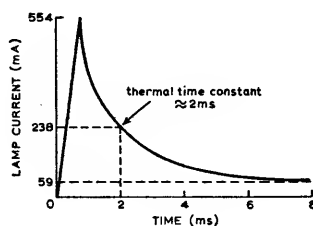


Fig. 3

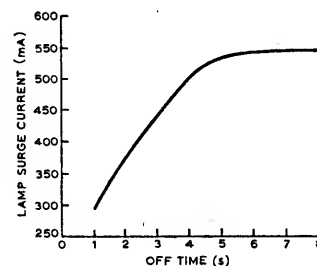

Filament lamps are widely used as visual alarm indicators and often connected in the collector-emitter circuit of a bipolar transistor that is switched on and saturated under alarm conditions. These lamps have a positive temperature coefficient of resistance with a large difference of resistance between the cold and hot states—see graph 1 which is typical for a 6V, 100mA panel lamp. When switched on across a voltage source, a large current surge flows in the lamp, and switching transistor, which then decays exponentially to its normal or rated value in the hot state. This surge may be ten times the rated current, or even higher, shortens the life of the lamp, may destroy the switching transistor or blow the power supply fuse. graph 2 shows the typical initial surge current characteristic of a 6V, 60mA panel lamp having a thermal time constant of about 2ms.

When lamps are used as flashing alarms, the initial surge current is as shown in graph 2 but the surge current on successive pulses depends on the thermal time constant and the time between flashes. Graph 3 shows the typical variation in surge current when a 6V, 60mA panel lamp is switched on for 5 s then off for  $t_{off}$  seconds.

If the p.d. applied to the lamp is gradually increased the current rises in a controlled manner to its normal operating value, prolonging the life of the lamp and reducing the probability of transistor damage. A simple arrangement is shown Fig. 4, where  $Tr_2$  is normally held on

and saturated with a low value of  $V_{CE(sat)}$  holding  $Tr_1$  and the lamp off. Under alarm conditions, the base drive to  $Tr_2$  is removed and the capacitor charges through  $R_B$ . The base voltage of  $Tr_1$  rises exponentially so that the lamp surge current is avoided.

To prevent damage to  $Tr_1$  should the lamp become short-circuited, a resistor  $R_C$  could be included in  $Tr_1$ 's free collector, but this would reduce the lamp voltage in normal operation. Circuit Fig. 5 shows a modification that allows an almost normal lamp voltage and also limits the short-circuit current to the desired value by using only a small  $R_C$  value and a saturating transistor  $Tr_3$ . Relays are used to actuate alarm devices that need to be isolated from their control circuitry for various reasons such as their current, voltage or power requirements being incompatible with the electronic circuitry. Circuit Fig. 6, of a commonly-used relay drive circuit which takes into account both the resistive and inductive

properties of the relay coil.

When actuated, the steady-state coil current is fixed by the coil resistance and supply voltage, but when  $Tr_1$  is turned off the inductance of the coil causes the collector voltage to rise towards a level greatly exceeding  $V_{CC}$  if the protective diode  $D_1$  were omitted. Diode  $D_1$  allows  $V_{CE}$  to rise only slightly above  $V_{CC}$  before the diode conducts to dissipate the energy stored in the relay coil. When  $Tr_1$  turns on  $D_1$  is reverse-biased and does not affect the operation. The diode must be able to withstand a reverse voltage slightly greater than  $V_{CC}$  and be able to conduct the relay-coil discharge current for a brief time. Transistor  $Tr_1$  must have a  $V_{CE}$  rating exceeding  $V_{CC}$  and be capable of carrying the relay operating current.

If a relay is required to operate when an input level exceeds a certain predetermined value, it may be included in a Schmitt trigger circuit; e.g., the relay coil and protective diode could replace  $R_4$  in the basic circuit of series 2, card 2.

If the alarm indication uses a l.e.d. or alpha-numeric array of l.e.d.s consult series 9, cards 2, 5 & 6.

## Further reading

Shea, R. F. (Ed.), *Amplifier Handbook*, section 31-6, McGraw-Hill, 1966.  
Egan, F. (Ed.), 400 ideas for design, vol. 2, pp. 18/9, Hayden, 1971.  
Cleary, J. F. (Ed.), *Transistor Manual*, pp. 202, General Electric Co. of New York, 1964.  
*Industrial Circuit Handbook*, section 2, SGS-Fairchild, 1967.

## Cross references

Series 2, card 2.  
Series 9, cards 2, 5 & 6.  
Series 13, cards 4 & 7.

Fig. 4

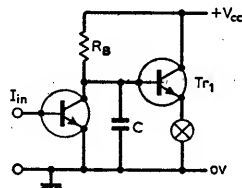


Fig. 5


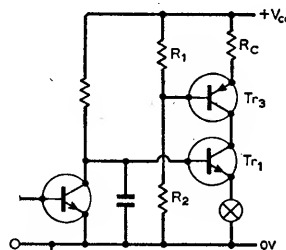
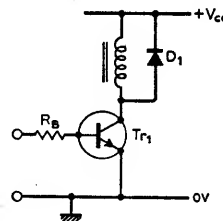


Fig. 6

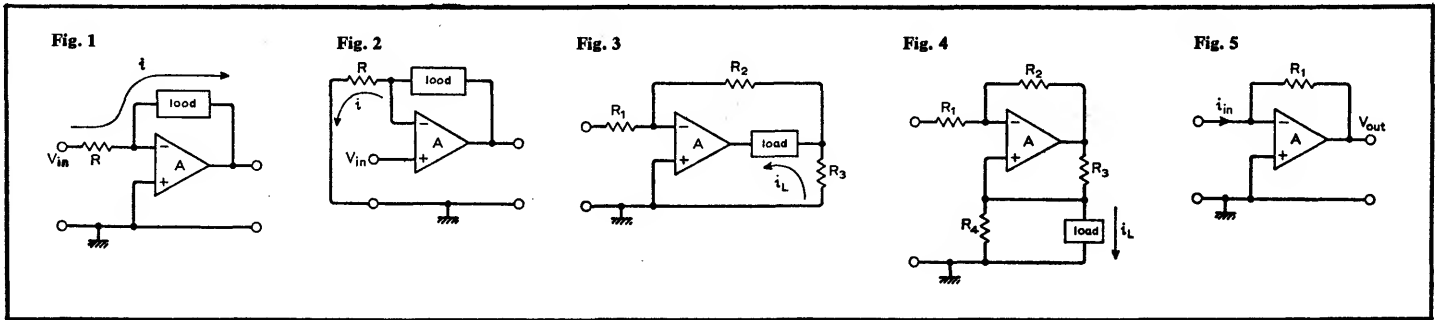

## Signal domain conversion

**Voltage-to-current conversion**

It is often required to supply signals to relatively long transmission lines in which case the signal is more convenient in current form rather than as a voltage. Thus, voltage-to-current converters are useful and may be realized using operational amplifiers especially if the load is floating. Figs. 1 & 2 show the more common forms the former being an inverting type and the latter non-inverting. In both Figs,  $i = V_{in}/R$  and is independent of the load impedance, but the source and operational amplifier must be able to supply this load current in Fig. 1, whereas little source current is needed in Fig. 2 due to the high input impedance of the amplifier. Fig. 3 shows another floating-load V-to-I converter which requires little source current if  $R_1$  is large and allows  $i_L$  to be scaled with  $R_3$ , the operational amplifier supplying the whole of the load current;  $i_L = V_{in}(1/R_1 + R_2/R_1R_3)$ . The circuit of Fig. 4 is suitable for V-to-I conversion when the load is grounded. When  $R_1R_3 = R_2R_4$  the load current is  $i_L = -V_{in}/R_4$  and the current source impedance seen by the load very high.

**Current-to-voltage conversion**

If a device is best operated when fed from a voltage source but the available signal is in the form of a current, a current-to-voltage converter will be required, one example being shown in Fig. 5. Current is fed to the summing junction of the operational amplifier which is a virtual earth so that current source sees an almost-zero load.

Input current flows through  $R_1$  producing an output voltage of  $V_{out} = -R_1$  volts/amp. The only conversion error is due to the bias current of the operational amplifier which is algebraically summed with  $i_{in}$ . The output impedance is very low due to the use of almost 100% feedback.

**Voltage-to-frequency conversion**

Many voltage-to-frequency converters exist, the circuit complexity often being a guide to the degree of linearity and maximum operating frequency. Fig. 6 shows one form of V-to-f converter (a v.c.o.) suitable for use at frequencies below about 10kHz, each amplifier being of the current-differencing LM3900 type. Amplifier  $A_1$  is connected as an integrator with  $A_2$  acting as a Schmitt trigger which senses the output from  $A_1$  and controls the state of  $Tr_1$  which either shunts the input current through  $R_2$  to ground, making  $V_{out1}$  run down linearly, or allows it to enter  $A_1$  causing

$V_{out1}$  to rise linearly with  $R_1 = 2R_2$ . So  $V_{out1}$  is a triangular wave and  $V_{out2}$  a square wave having a frequency that is linearly dependent of  $R_1$ ,  $C_1$  and the threshold levels selected for the Schmitt trigger.

**Frequency-to-voltage conversion**

Diode-pump, transistor-pump and op-amp pump circuits are widely used for low-cost frequency to voltage conversion. Another circuit, using a single LM3900 quad current-differencing amplifier package, is the phase-locked loop shown in Fig. 7 which uses the v.c.o. of Fig. 6. Amplifier  $A_3$  is in the LM3900 package used as a phase comparator having a pulse-width modulated output depending on the phase difference between  $V_{in}$  and  $V_{out2}$  of the v.c.o. Resistor  $R_8$  and  $C_2$  form a simple low-pass filter which makes the d.c. output vary in the range  $+V$  to  $+V/2$  as the phase difference changes from  $180^\circ$  to  $0^\circ$ . This direct voltage controls the

frequency of the v.c.o. and its lock range may be increased by using the fourth amplifier in the package as a d.c. amplifier between the filter and the integrator. Centre-frequency of the p.l.l. is about 3kHz with:  $R_1, R_3$  1M $\Omega$ ;  $R_2$  510k $\Omega$ ;  $R_4, R_5, R_9, R_6$  30k $\Omega$ ;  $R_5, R_6$  1.2M $\Omega$ ;  $R_7$  62k $\Omega$ ;  $C_1$  1nF;  $C_2$  100nF;  $V = +4$  to  $+36V$ .

**Further reading**

Graeme, J. G. & Tobey, G. E. Operational Amplifiers, chapter 6, McGraw-Hill, 1971. Linear Applications—application notes AN20 and AN72, National Semiconductor, 1973.

**Cross references**

Set 3, cards 3, 5 & 10. Set 13, cards 1 & 6.

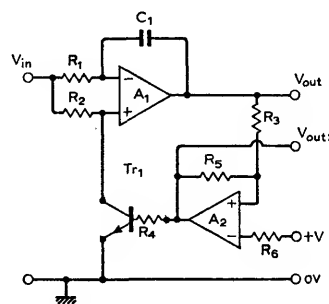


Fig. 6


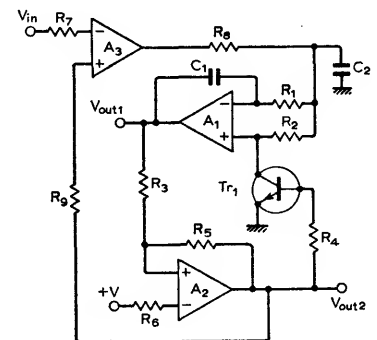


Fig. 7

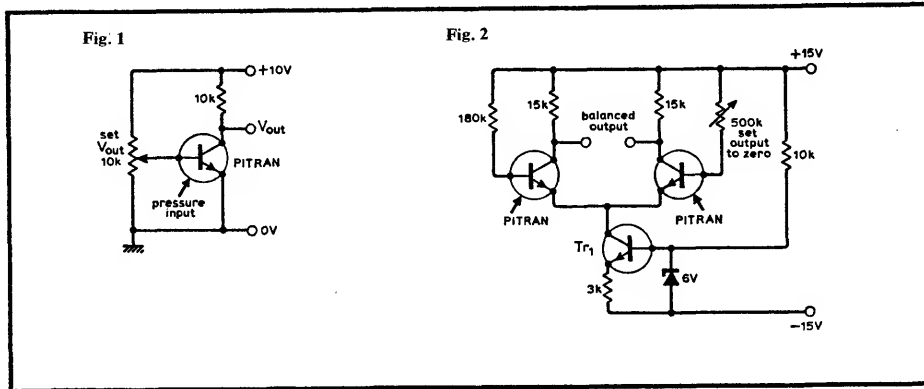Pressure, temperature and moisture-sensitive alarms



Pressure-sensitive alarm

A pressure-sensitive alarm may be made using a specially-modified transistor known as the Pitran. It is a planar n-p-n transistor having a diaphragm mounted in the top of its metal can which is mechanically coupled to its base-emitter junction. When a pressure is applied to the diaphragm a reversible charge is produced in the transistor characteristics. The mechanical pressure input can be used to directly modulate the electrical output of the transistor which may be fed to the alarm circuitry, e.g., via a comparator or Schmitt trigger which switches state when the input pressure to the Pitran either exceeds or falls below some critical level. The Pitran may be connected as a single-ended-input single-ended-output stage, as shown in Fig. 1 or as a differential-input balanced-output stage, Fig. 2. Conventional transistor circuit design techniques may be used for the Pitran stages. Linear output voltages of up to one-fifth of the total supply voltage are obtainable.

Temperature-sensitive alarm

Circuit Fig. 3, shows the input circuitry of an alarm which may be operated by the output signal from the operational amplifier when the temperature monitored by the probe transistor exceeds a pre-determined value. The temperature-sensing transistor is a low-cost n-p-n type that can produce a resolution of less than 1 deg C in a temperature range of 100 deg C. If the operating

current of the probe transistor is made proportional to temperature, the non-linearity of its base-emitter voltage may be minimized, being less than 2mV in the temperature range -55 to +125°C. Zener diodes set the input voltage to 1.2V and this is applied through R<sub>2</sub> to fix the operating current of the probe transistor. Resistor R<sub>4</sub> may be adjusted to make amplifier's output zero at 0°C and R<sub>5</sub> is used to calibrate the output voltage to 100mV/deg C, or any other scaling factor, independently of the V<sub>out</sub>=0 condition. R<sub>1</sub>, R<sub>3</sub> 12kΩ; R<sub>2</sub> 3kΩ; R<sub>4</sub> 5kΩ; R<sub>5</sub>, R<sub>6</sub> 100kΩ; D<sub>1</sub>, D<sub>2</sub> LM113; Tr<sub>1</sub> 2N2222; A<sub>1</sub> LM112; V±15V.

Moisture-sensitive alarm


A low-cost audible alarm which operates when the electrodes of the input sensor become damp due to increase in humidity, direct contact with water, rain or snow is shown in

Fig. 4. The sensor is conveniently made from parallel-strip printed circuit board or commercial equivalent, so that increase in moisture at the strips produces a very small current to Tr<sub>1</sub> base via R<sub>1</sub> which forms a high-gain compound pair with Tr<sub>2</sub> which switches hard on. Transistors Tr<sub>3</sub> and Tr<sub>4</sub> form the audible alarm multivibrator, that acts as a load on the compound pair, having a repetition rate determined by the C<sub>1</sub>R<sub>3</sub> time constant. A piercing note at about 2.5kHz is produced with R<sub>1</sub>, R<sub>2</sub> 100kΩ; R<sub>3</sub> 1kΩ; C<sub>1</sub> 10nF; Tr<sub>1</sub>, Tr<sub>2</sub>, Tr<sub>4</sub> ZTX300; Tr<sub>3</sub> OC71; LS 8-Ω loudspeaker; V+9V. A flashing display with a rate of about 2Hz may be obtained by replacing the loudspeaker with a 6V, 60mA panel lamp and changing the values of R<sub>2</sub> to 470kΩ and C<sub>1</sub> to 2.2μF.


Further reading

Tingay, E. The Pitran—a new concept in pressure measure-

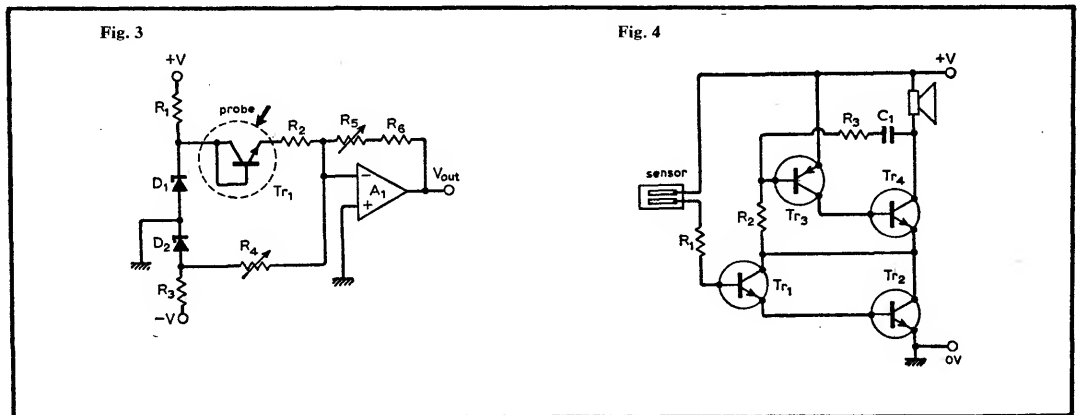ment, *International Marketing News*, p. 8, 1970. Linear Applications—application notes AN31, AN56 and AN72, National Semiconductor, 1973. Brown, F. Rain warning alarm, *Everyday Electronics*, pp. 208-11, 1972.


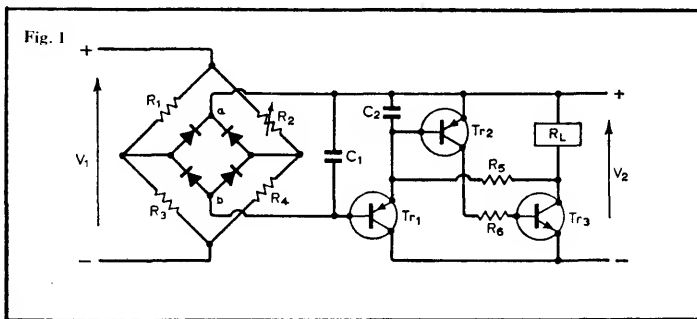
## Security, water level and automobile alarms



## Component values

$R_1, R_4$ : 150k $\Omega$   
 $R_3$ : 200k $\Omega$   
 $R_2$ : 250k $\Omega$  variable  
 $R_5$ : 27k $\Omega$   
 $R_6$ : 470 $\Omega$   
 $C_1, C_2$ : 0.33 $\mu$ F  
 $Tr_1, Tr_2$ : BC126  
 $Tr_3$ : BFR41 or BFY52  
 Diodes 0A81  
 $V_1$ : 18V  
 $V_2$ : 9V

## Circuit description

Component  $R_3$  is the resistance in the search loop which if obtained using two 100k $\Omega$  resistors allows one to include switches either in series with the loop or in parallel with either resistor, or both. In the latter case changing a switch condition from open to closed in the parallel case and from closed to open in the series case can give rise to either a positive voltage or a negative voltage being applied to the diode bridge; the bridge is, of course, balanced initially. The diode bridge being a full wave rectifier will apply a negative  $V_{ba}$  to the following circuit in either case. The bridge resistors are large valued to minimize current drain from the battery but require that the following circuit have a large input resistance. Hence the buffer  $Tr_1$  is employed.

When  $V_{ba}$  goes negative,  $Tr_1$  and with it  $Tr_2$ , conducts. Transistor  $Tr_2$  then drives  $Tr_3$  which is a higher power device capable of drawing a relay coil to produce the warning signal. At the same time when  $Tr_3$  conducts, the collector of  $Tr_3$  goes negative and hence via positive feedback through  $R_5$  the base of  $Tr_2$  remains negative, even if  $V_{ba}$  is set back to zero. Hence, a latching action is obtained, which keeps the warning signal on. The warning signal will only be removed if the power supply is removed.

Capacitors  $C_1$  and  $C_2$  are required to prevent spurious pulses from triggering the alarm, in the case of  $C_1$ , and to prevent switching transients

from triggering the alarm when the alarm is being reset, in the case of  $C_2$ .

## Brake light monitor (Fig. 2.)

Both of the identical counterwound coils are wound round the reed relay. Hence the relay switch will only close, giving a dashboard warning, if either of the brake lights fails either with an open circuit or short circuit.

## Water level alarm

Fig. 3 circuit is designed to produce a note from the loudspeaker when the sensor input terminals are shorted. As such it can be used for many applications apart from suggested water level/rain alarm. When the input terminals are shorted base drive to  $Tr_1$  via  $R_1$  is obtained, and the supply voltage is switched to the unijunction relaxation oscillator comprising  $Tr_2$ ,  $R_2$ ,  $R_3$  and  $C$  (card 4, series 3). A train of pulses of period mainly determined by the product  $R_2C$  is then presented to the base of  $Tr_3$ , thereby producing

pulses of current through the loudspeaker. The loudspeaker alarm note can be altered by altering the product  $R_2C$ . Considerable effective output can be obtained by selecting the note to correspond to the resonant frequency of speaker. In practice the alarm will sound for any resistance between zero and five megohms. The quiescent current of the unit is of the order of nanoamps so that battery life is many months even if the unit is switched off. Provision to test the battery condition is made by switch position 2 which should cause  $Tr_1$  to switch on the oscillator provided the battery is in good condition.

For water level sensing two conducting rods spaced an inch, or less, apart and positioned at the required level is all that is required.

For a rain alarm two rods separated by some blotting paper will suffice. When the blotting paper becomes wet contact between the rods is made, the alarm sounds and the washing is saved once more

(provided the missus isn't away shopping).

## Component changes

Resistor  $R_1$  may be any value up to 5M $\Omega$  provided a true shorting of the sensor input terminals is obtainable. The  $R_2C$  product is dictated by the pitch of the note required. Resistor  $R_3$  should be much less than  $R_2$ , e.g.,  $R_2/10$ .

## Further reading

Andrews, J. Security Alarm, *Practical Electronics*, 1973, p. 338.  
 Moorshead, H. Rain & Water Level Alarm, *Practical Electronics*, 1971, p. 820.  
 Morum, S. W. F., Brake Light Monitor, *Practical Electronics*, 1973, p. 588.

## Component values

$R_1$ : 100k $\Omega$   
 $R_2$ : 3.3k $\Omega$   
 $R_3$ : 270 $\Omega$   
 $C$ : 0.5 $\mu$ F  
 $Tr_1, Tr_3$ : 2N2926 (G)  
 $Tr_2$ : 2N2646  
 LS: 8- $\Omega$  loudspeaker  
 Supply voltage: 9V


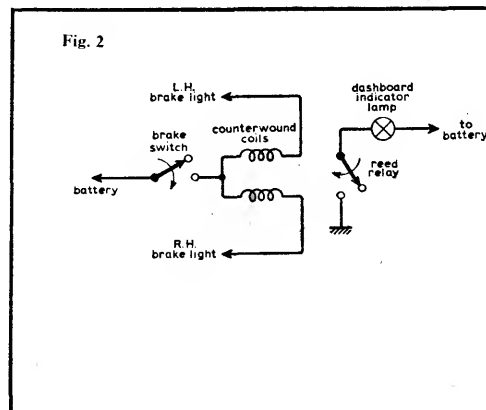



Fig. 3

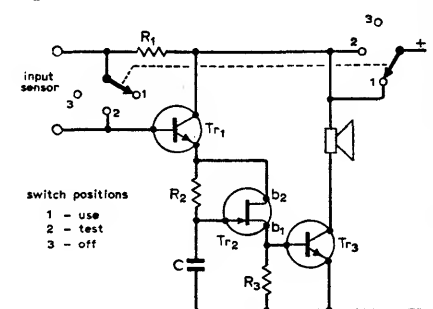
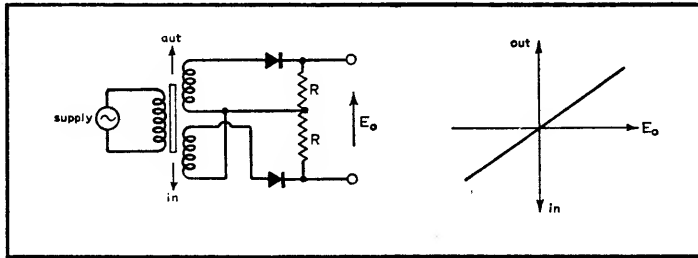
## Electromechanical alarms

Electromechanical transducers are obtainable in a wide variety of types: they may be d.c. or a.c., resistive, reductive or capacitive, contacting or non-contacting, analogue or digital, linear or angular, etc. Insofar as most alarm systems use a comparator (cross ref. 1) to

compare the signal with a reference and as d.c. signals are easily compared we shall assume here that any a.c. systems are followed by signal conditioning equipment which includes a rectifier (cross ref. 2) of some sort so that the effective output is d.c.



### Displacement Alarms

Circuit shows a reductive displacement transducer, of the differential transformer type, followed by a demodulator to provide the d.c. output shown in graph. The core, which is shown in its zero output position, is attached to the member whose displacement is required. The core is generally made from high permeability ferromagnetic material so that flux linkages with and hence the e.m.f.s of the secondary coils are highly dependent on the position of the core relative to the coils. Reluctive transducers generally have a displacement span of

between 0.01 and 120in, in rectilinear form, and between 0.05 and 90° in angular form. As the induced e.m.f.s are proportional to frequency, very sensitive systems can be made at high frequencies. Capacitive transducers are used in situations where very small displacements have to be measured and/or non-contacting measurement has to be performed. Photoelectric/digital measurements (again non-contacting) are used when high accuracy is required, although fairly low cost versions can be constructed if accuracy is not essential.

### Velocity alarm


Linear velocity transducers are most commonly used in the vibrations field where the displacement of the member whose velocity is required is small. Essentially, they consist of a coil moving in a permanent magnetic field, the coil e.m.f. being proportional to the speed. As a large proportion of the speed producing systems are driven by motors one can generally obtain information on linear speed from a knowledge of angular speed. This can be obtained by various types of a.c. or d.c. tachometers, but with the increasing use of digital instrumentation, toothed rotor,

photoelectric and similar systems are becoming increasingly common. Diagram shows basis of operation of the toothed rotor tachometer and the corresponding output when the rotor is rotated by the shaft of a motor. The output waveform is obtained because of the changing flux pattern caused by the changing magnetic circuit. If the output signal is fed to a zero crossing comparator (cross refs. 1, 3) or to a Schmitt trigger (cross ref. 1) one will then obtain a train of pulses, each pulse representing the passage of a rotor tooth past the permanent magnet. Obviously the pulse frequency is
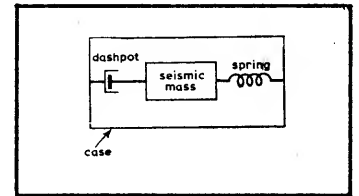
### Acceleration alarm

Acceleration transducers all have one feature in common, viz. the seismic mass, M. The basic acceleration transducer is shown below. The case of the system is attached to the body whose acceleration is required. Due to a constant acceleration the seismic mass exerts a force  $M\alpha$  which in the steady state will stretch or compress the spring by an amount  $x$  where  $M\alpha = Kx$ , K being the spring constant. The dashpot simply provides damping whilst the mass is moving. If we know M and K then a measure of  $x$  gives a signal proportional to the acceleration. This can be done by any displacement transducer of suitable dimensions and sensitivity. Frequently, however, the spring arrangement is a leaf spring arrangement with strain gauges attached. The spring deflection gives rise to changes in resistance in the strain gauges which if connected in a Wheatstone bridge circuit gives a voltage proportional to the deflection and, hence, to the acceleration. As the Wheatstone bridge can be supplied from a d.c. source there is no need for rectifiers before feeding to a comparator. Strain gauge bridges usable up to 750Hz have been built.

For higher frequencies piezoelectric crystals replace the spring. The crystal produces a




charge or voltage across its terminals when subjected to the stress of the seismic mass under acceleration. However, the output impedance of the crystal is large and amplifiers with an input impedance in excess of 500M $\Omega$  typically have to be used. Furthermore, the cable between the crystal and the amplifier requires to have low capacitance and to be free from friction induced noise. On the other hand very large accelerations (> 100g) can be measured and they can be used over a large temperature range (570°C for a lead metaniobate crystal).

### Further reading

H. N. Norton, Handbook of Transducers for Electronic Measuring Systems, Prentice-Hall.  
Considine, Encyclopedia of Instrumentation and Control, McGraw-Hill.
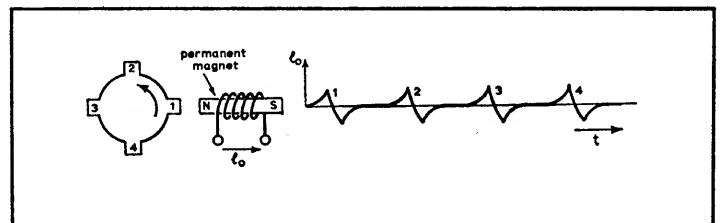
### Cross references


Set 2, Comparators and Schmitts.  
Set 4, A.C. Measurements.  
Set 13, card 4.



proportional to the shaft speed. If the train of pulses is then fed to a frequency-to-voltage converter a direct voltage proportional to shaft speed is obtained and this can be fed to a comparator to give an alarm if it exceeds a pre-determined level. Because the number of teeth on the toothed rotor can easily be varied, the

range of speeds measurable by this technique is extremely large. Further, the rotor can easily be constructed in any workshop, no great precision being required for many applications. Bolt heads on a coupling between two shafts often suffice as the toothed rotor.

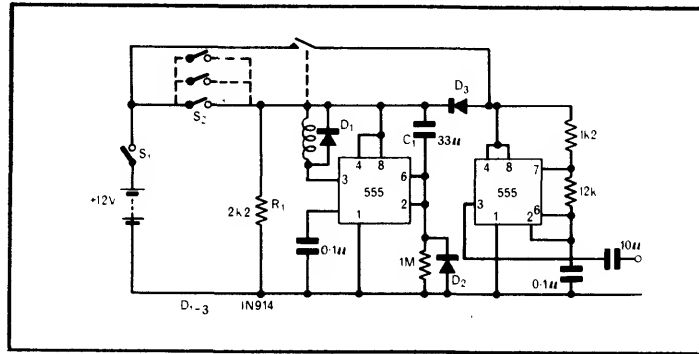1. The ability of the 555 timer to act as a monostable or astable and to deliver sufficient power to drive a loudspeaker directly is put to use in this burglar alarm. Switch  $S_1$  is closed arming the circuit, with  $S_2$  consisting of a number of normally-closed switches each detecting an entry point. If any of these switches is allowed to close by an opened window, etc. the relay is activated and power is applied to both monostable and astable. The audio output can be accompanied by a visual output via a second relay contact. The circuit



remains latched by the relay throughout the monostable delay, further variation in  $S_2$  having no effect. The alarm ceases at the end of the


selected delay ( $\sim 12s$  is given in the source article) regardless of  $S_2$ , but is re-triggerable once  $S_2$  has been opened and the stored charge in  $C_1$  has

been dissipated through  $D_2$ ,  $R_1$ , i.e. the alarm operates for only one cycle. No standby current flows as the contacts of  $S_2$  are normally open. Frequency of oscillation of the astable section is around 1kHz and transformer coupling to a low resistance loudspeaker is suggested in the article.

#### Reference

Long, J. D. Burglar alarm is effective, yet simple and inexpensive, *EDN*, 1974, Dec. 20, pp. 50/1.

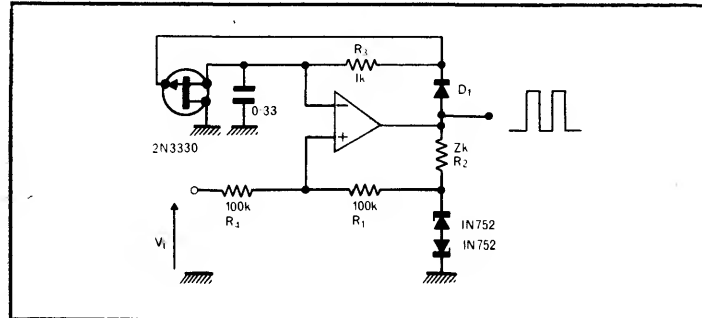2. Positive feedback around an operational amplifier may be used to provide either astable or Schmitt characteristics. This novel circuit combines both while needing only one operational amplifier. When the op-amp output is low  $D_1$  is reverse biased and  $R_3$  provides the f.e.t. with a zero gate-source voltage. Hence the f.e.t. shorts out the capacitor grounding the inverting input. As the input voltage increases, it overcomes the effect of the negative voltage across the zeners, raising the non-inverting input above



zero. The op-amp output swings positive, reverse-biasing the f.e.t. gate source and allowing the capacitor to charge positively. This


continues until the inverting input rises to equal the now positive potential on the non inverting input. At this point the op-amp output

switches back to its negative state and the capacitor discharges, with the cycle recommencing. The reference article gives equations representing the circuit performance and indicates that 0.1% stability of trip-point is achievable, though the frequency of oscillation is determined only to within about 30%.

#### Reference

Graeme, J. Voltage comparator circuit gives audio alarm when tripped, *Electronic Design*, 1975, May 10, p. 148.

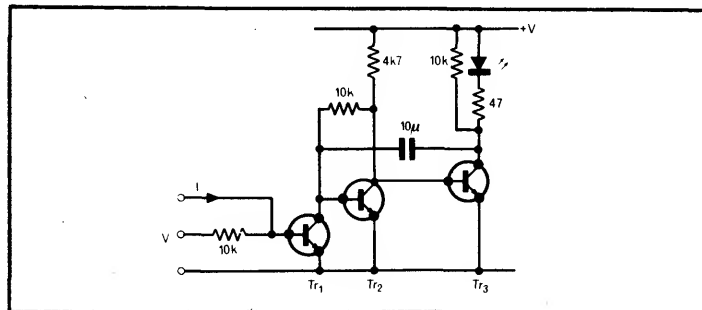3. The circuit is an astable gated by a single transistor that can be driven from a small positive current or from a low voltage ( $> 0.6V$ ), including the output of t.t.l., c.m.o.s. etc. Alternatively  $Tr_1$  can be replaced by an open-collector t.t.l. gate. The novel property of this astable that it drives an l.e.d. from a low voltage supply with the l.e.d. permanently on for input level high and flashing at, say, 1-10Hz depending on choice of



$C$  for input level low. This allows a single l.e.d. to act as the on-off indicator for a

battery instrument as a supply voltage of 2V is sufficient to initiate conduction; the same

l.e.d. acts as the visual indicator of a fault condition if that fault is converted into a low voltage/current to drive  $Tr_1$ . In the quiescent state the l.e.d. current may be typically 20mA. The three transistors may be any general purpose silicon devices including those from such multi-transistor packages as CA3046, CA3086, etc. The other two transistors in such a case are usable as part of a Schmitt trigger or amplifier stage.