


## Non-inverting comparator with hysteresis circuit

### Design Goals

Output		Hysteresis	Thresholds		Supply	
$V_o = \text{HIGH}$	$V_o = \text{LOW}$	$V_{\text{HYS}}$	$V_{\text{H}}$	$V_{\text{L}}$	$V_{\text{cc}}$	$V_{\text{ee}}$
$V_i > V_{\text{H}}$	$V_i < V_{\text{L}}$	400mV	1.7V	1.3V	3V	0V
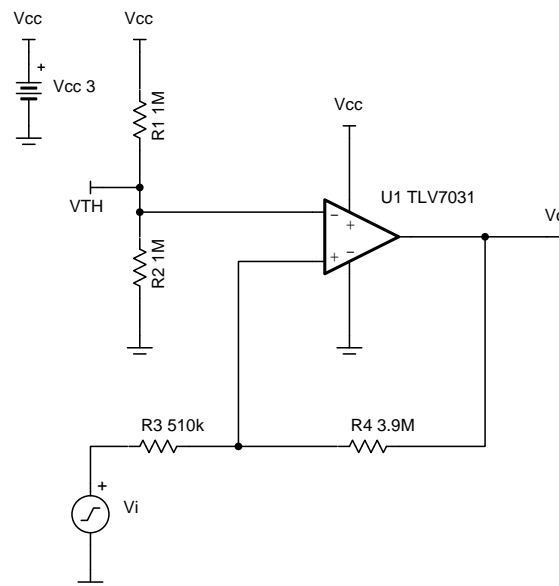
### Design Description

Comparators are used to differentiate between two different signal levels. When setup in a non-inverting fashion, the comparator output will be a digital high if the analog input is above a selected threshold. With noise, signal variation, or a slow-moving signal at the comparison threshold, undesirable transitions at the output can be observed. Setting upper and lower hysteresis thresholds eliminates these undesirable output transitions caused by the noise. This circuit example will focus on the steps required to design the positive feedback resistor network required to obtain the necessary hysteresis for a non-inverting comparator application.




### Design Notes


1. Achieving balanced hysteresis will depend on the size of hysteresis and the threshold voltage to  $V_{\text{cc}}$  ratio.
2. In comparison to the inverting comparator circuit, this example has a lower impedance seen at the inputs.
3. The accuracy of the hysteresis threshold voltages are related to the tolerance of the resistors used in the circuit, the selected comparator's input offset voltage specification, and any internal hysteresis already applied to the device.
4. For the TLV7031,  $V_{\text{OH}}$  is approximately 200mV below  $V_{\text{cc}}$  and  $V_{\text{OL}}$  is approximately 250mV above  $V_{\text{ee}}$ .
5. The TLV7031 has a push-pull output stage, so no pull-up resistor is needed.

### Design Steps

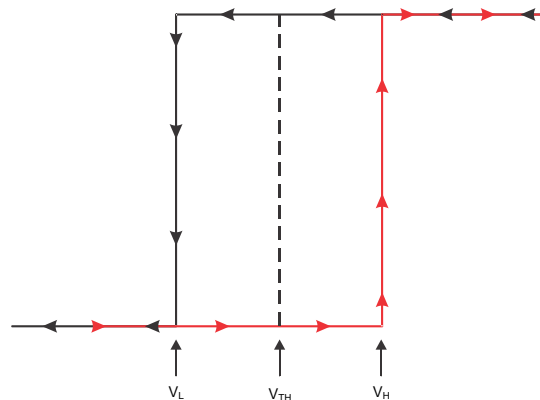1. Select  $R_1$ . This can be a high resistance value due to the very low input bias current caused by the CMOS input of the device.  
 $R_1 = 1\text{M}\Omega$  (Standard Value)
2. Solve for  $R_3$ . A common practice is to select  $R_3$  to be the impedance seen at the inverting pin to provide input bias current cancellation. Since  $R_2$  is not known, approximate  $R_3$ . Here  $V_{TH}$  is expected to be 50% of  $V_{CC}$ .  
 $R_3 = R_1 \parallel R_2 \cong \frac{1}{2}R_1 = 500\text{k}\Omega$   
 $R_3 = 510\text{k}\Omega$  (Standard Value)
3. Observe the feedback resistor network in the two possible output states: Low and High. Note that the input signal plays a role in determining the hysteresis. The hysteresis eye diagram follows.



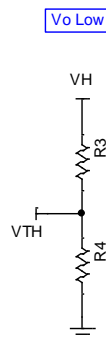
4. Derive the equation for  $V_H$ , the voltage that the input signal must rise to for the output to switch high. Set the voltage at the non-inverting pin to be equal to  $V_{TH}$ . This ensures the correct hysteresis window will be achieved.



$$V_H = R_3 \times \frac{V_{TH}}{R_4} + V_{TH}$$

5. Derive the equation for  $V_L$ , the voltage that the input signal must drop to for the output to switch low. Again, set the voltage at the non-inverting pin to be equal to  $V_{TH}$ .

Vo High

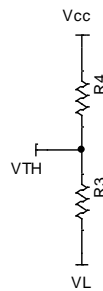

6. For push-pull outputs.

$$V_L = \frac{V_{TH} \times (R_3 + R_4) - V_{cc} \times R_3}{R_4}$$

7. If the comparator in use has an open-drain or open-collector output stage, then the pull-up resistor,  $R_{pu}$ , will be in series with  $R_3$  and  $R_4$ . The following equation is true if  $V_{pu} = V_{cc}$ . Do note that for some applications, the pull-up resistor could be ignored in the  $V_L$  equation since the eventual feedback resistor value could be significantly larger (ideally 10 times larger) than the pull-up resistor.

$$V_L = \frac{V_{TH} \times (R_{pu} + R_4) - (V_{cc} - V_{TH}) \times R_3}{R_4 + R_{pu}}$$

8. If  $V_{pu} \neq V_{cc}$ , then use the following equation for  $V_L$ .

$$V_L = \frac{V_{TH} \times (R_{pu} + R_4) - (V_{pu} - V_{TH}) \times R_3}{R_4 + R_{pu}}$$

9. Derive the equation for  $V_{HYS}$ .

$$V_{HYS} = V_H - V_L = V_{cc} \times \frac{R_3}{R_4}$$

10. Solve for  $R_4$ .

$$R_4 = \frac{V_{cc}}{V_{HYS}} \times R_3 = \frac{3V}{0.4V} \times 510k\Omega = 3.83M\Omega$$

$$R_4 = 3.9M\Omega \text{ (Standard Value)}$$

11. Use the  $V_H$  equation found in step 4 to now solve for  $V_{TH}$ .

$$V_{TH} = \frac{R_4 \times V_H}{R_3 + R_4} = \frac{3.9M\Omega \times 1.7V}{510k\Omega + 3.9M\Omega} = 1.50V$$


12. Verify the  $V_{TH}$  value with the  $V_L$  equation found in step 6.

$$V_{TH} = \frac{R_4 \times V_H}{R_3 + R_4} = \frac{3.9M\Omega \times 1.7V}{510k\Omega + 3.9M\Omega} = 1.50V$$

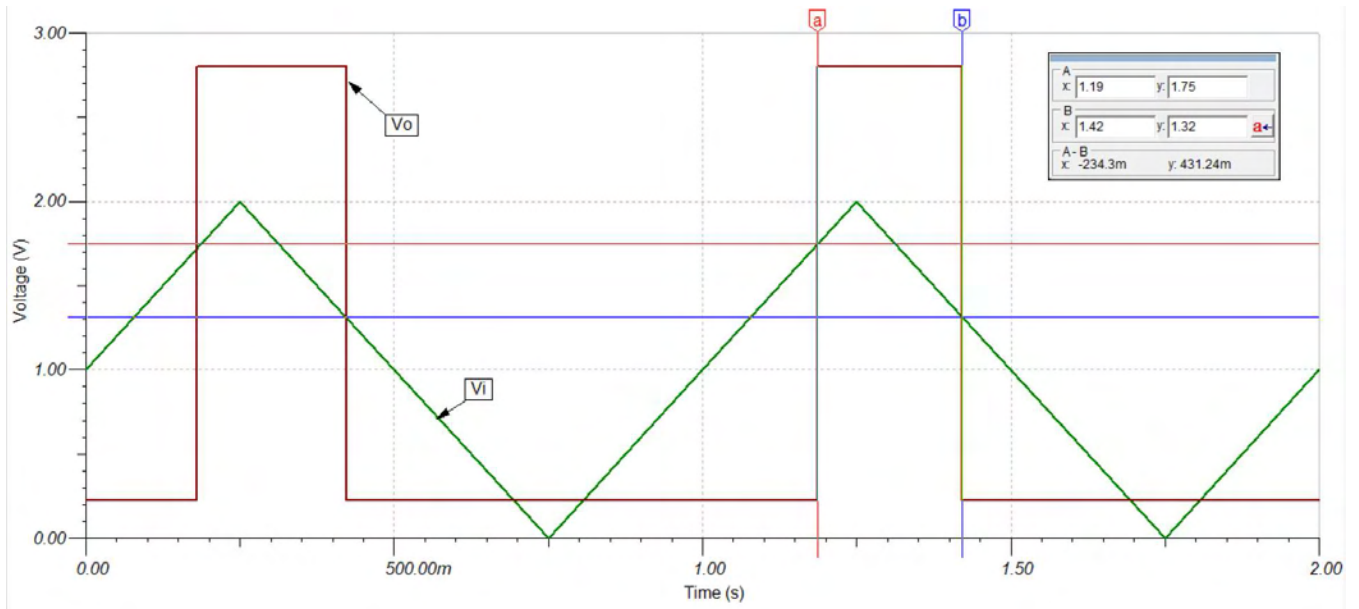13. Solve for  $R_2$  based on the calculated threshold voltage,  $V_{TH}$ .

$$R_2 = \frac{R_1 \times V_{TH}}{V_{cc} - V_{TH}} = \frac{1M\Omega \times 1.5V}{3V - 1.5V} = 1M\Omega$$

Design Simulations  
Transient Simulation Results



## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See Circuit SPICE Simulation File [SLVMCR2](#).

For more information on many comparator topics including hysteresis, propagation delay and input common mode range please see [training.ti.com/ti-precision-labs-op-amps](http://training.ti.com/ti-precision-labs-op-amps).

## Design Featured Comparator

TLV7031	
<b>Output Type</b>	Push-Pull
<b>V<sub>cc</sub></b>	1.6V to 6.5V
<b>V<sub>inCM</sub></b>	Rail-to-rail
<b>V<sub>os</sub></b>	±100µV
<b>V<sub>HYS</sub></b>	7mV
<b>I<sub>q</sub></b>	335nA/Ch
<b>t<sub>pd</sub></b>	3µs
<b>#Channels</b>	1
	<a href="http://www.ti.com/product/tlv7031">www.ti.com/product/tlv7031</a>

## Design Alternate Comparator

TLV1701	
<b>Output Type</b>	Open Collector
<b>V<sub>cc</sub></b>	2.2V to 36V
<b>V<sub>inCM</sub></b>	Rail-to-rail
<b>V<sub>HYS</sub></b>	N/A
<b>V<sub>os</sub></b>	±500µV
<b>I<sub>q</sub></b>	55µA/Ch
<b>t<sub>pd</sub></b>	560ns
<b>#Channels</b>	1, 2, 4
	<a href="http://www.ti.com/product/tlv1701">www.ti.com/product/tlv1701</a>