

designideas

EDITED BY BRAD THOMPSON
AND FRAN GRANVILLE

READERS SOLVE DESIGN PROBLEMS

Op amp can source or sink current

Alfredo H Saab and Steve Logan,
Maxim Integrated Products Inc, Sunnyvale, CA

When you design for electronics applications, such as sensor or amplifier bias supplies or special waveform generators, a controlled constant-current source or sink circuit can serve as a useful building block. These circuits exhibit high dynamic-output impedance and deliver relatively large currents within an allowed range of compliance voltage. You can implement a constant-current circuit with an op amp and a discrete external transistor, but you can also design a bipolar version of a current source or sink around a single op amp and a few resis-

tors (Figure 1). The constant-current sink circuits in Figure 1a through Figure 1c offer various compromises between precision, dynamic impedance, and compliance range.

The circuit in Figure 1d describes a bipolar current source with a simpler feedback configuration than that of the usual Howland-current pump, which requires positive feedback and presents variable input impedance. Figure 1e shows a constant-current source. All of these circuits exhibit excellent linearity of output current with respect to input voltage.

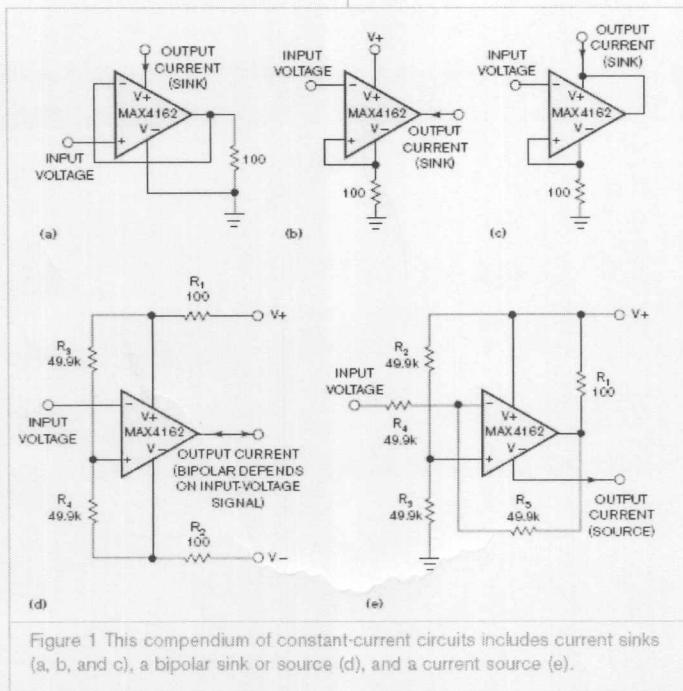


Figure 1 This compendium of constant-current circuits includes current sinks (a, b, and c), a bipolar sink or source (d), and a current source (e).

DIs Inside

76 Simple digital filter
cleans up noisy data

78 Single switch selects
one of three signals

80 Low-cost audio filter
suppresses noise and hum

82 Microprocessor's single-
interrupt input processes
multiple external interrupts

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

The output from the circuit in Figure 1a includes an uncertainty due to the op amp's quiescent current, which adds to the calculated output current. For example, in most applications, you can neglect the MAX4162 op amp's quiescent current of approximately 25 μ A. The circuit in Figure 1b behaves similarly, but its quiescent current subtracts from the ideal output-current value. The circuit in Figure 1c provides a current sink with no quiescent-current error, and the circuit in Figure 1d presents a bipolar output—that is, it sinks or sources current—depending on the polarity of the input voltage. Its performance depends on close matching for the resistor pairs R_1 and R_2 , and R_3 and R_4 and good tracking of the positive- and negative-power-supply voltages. Any difference between the absolute values of the supply voltages appears as an offset current at 0V input voltage. To achieve insensitivity to power-supply-voltage variations, the current-source circuit in Figure 1e requires close matching of resistor pairs R_2 and R_3 and R_4 and R_5 .

You can use the following equations to calculate output currents for the cir-

designideas

circuits in Figure 1. Note that $R_{LOAD} = 100\Omega$ in these examples. In Figure 1a, $I_{OUT} = -V_{IN}/R_{LOAD} + 25\ \mu\text{A}$; in Figure 1b, $I_{OUT} = -V_{IN}/R_{LOAD} - 25\ \mu\text{A}$; in Figure 1c, $I_{OUT} = -V_{IN}/R_{LOAD}$; in Figure 1d, $I_{OUT} = -2 \times V_{IN}/R_{LOAD}$; and, in Figure 1e, $I_{OUT} = V_{IN}/R_{LOAD}$. The equation for circuit 1d assumes perfect match-

es—that is, $R_3 = R_4$, $R_1 = R_2$, and $V_+ = V_-$. It also assumes that R_4 is much greater than R_1 .

For a fixed value of output current in each of the five circuits in Figure 1, the graphs of Figure 2 show the circuits' dynamic impedance and range of useful output voltage (current compli-

ance). The graphs show a high nominal output current of 5 mA to better display the higher end of the current-amplitude range. Depending on your application, you can optimize each circuit's dynamic impedance and current range through a judicious choice of op amps and resistor values.EDN

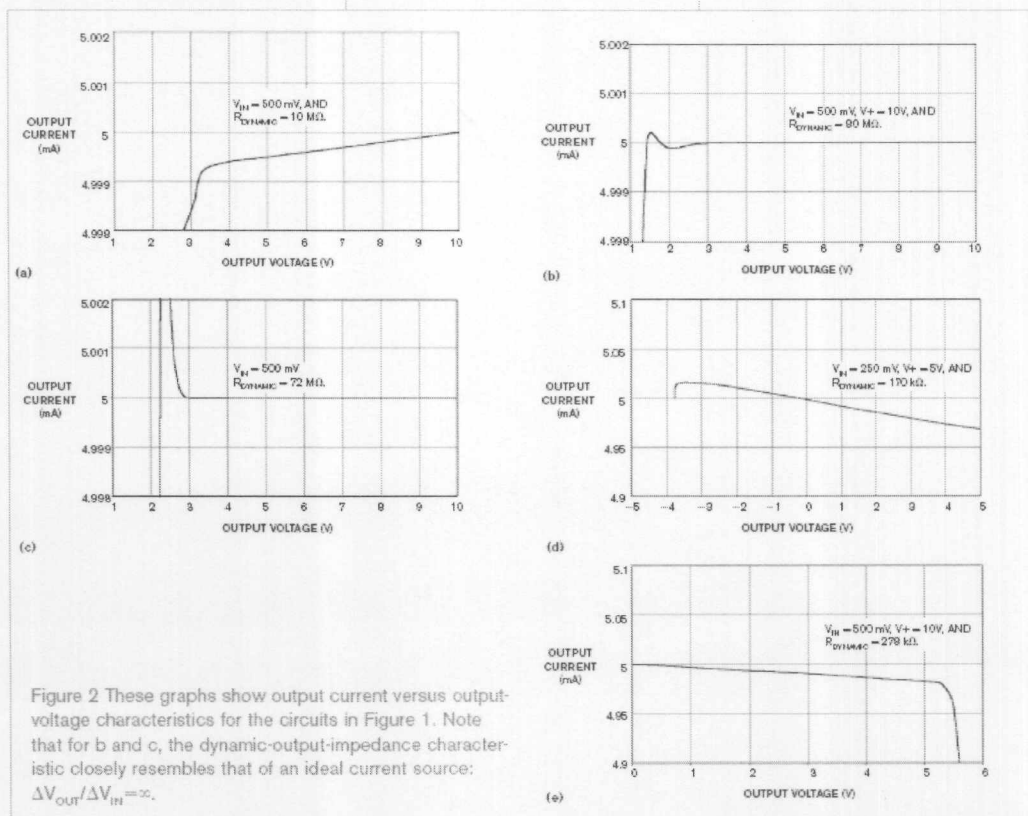


Figure 2 These graphs show output current versus output-voltage characteristics for the circuits in Figure 1. Note that for b and c, the dynamic-output-impedance characteristic closely resembles that of an ideal current source: $\Delta V_{OUT}/\Delta V_{BI} = \infty$.

Simple digital filter cleans up noisy data

Richard Rice, Oconomowoc, WI

Many systems use an ADC to sample analog data that temperature and pressure sensors produce. Sometimes, system noise or other fac-

tors cause the otherwise slowly fluctuating data to "jump around." To reduce higher frequency noise, designers often install an analog RC (resistor-capaci-

tor) lowpass filter between the sensor and the analog-to-digital-conversion stage. However, this approach is not always ideal or practical. For example, a long time constant of minutes would require very large values for R and C.

Figure 1 shows an analog RC lowpass filter and its design equations. As an alternative, you can clean up noisy signals that remain within the ADC's lin-