

THAT Corporation

Department Engineering

Subject ***Analog Secrets Your
Mother Never Told You***

Name Les Tyler, Gary Hebert,
Ros Bortoni, Bob Moses

Address 123rd AES Convention
New York, October 2007

Seminar Outline

- New ICs
- Microphone preamplifiers
- Log math
- Balanced outputs
- Q & A
- Door prizes!

THAT Corporation

Department Engineering

Chapter ***New ICs***

Name Bob Moses

Address 123rd AES Convention
New York, October 2007

New ICs

- THAT 2162 Dual VCA
 - Pre-trimmed
 - Current-in, current-out
 - VCAs are completely independent
 - QSOP-16 package
 - \$2.98 (1,000's) -- \$1.49 per channel
 - Samples available now
 - Production quantities this quarter (4Q07)

New ICs

- THAT 1280-Series
Dual Balanced Line Receiver
 - Three gain versions
 - THAT 1280: 0dB (pin compatible w/ TI INA2134)
 - THAT 1283: ± 3 dB
 - THAT 1286: ± 6 dB (pin compatible w/ TI INA2137)
 - SO-14 package
 - \$1.98 (1,000's) -- \$0.99/channel
 - Samples available now
 - Production quantities this quarter (4Q07)

THAT Corporation

Department Engineering


Chapter ***Mic Preamps***

Name Rosalfonso "Ros" Bortoni

Address 123rd AES Convention
New York, October 2007

Mic Preamp - Highlights

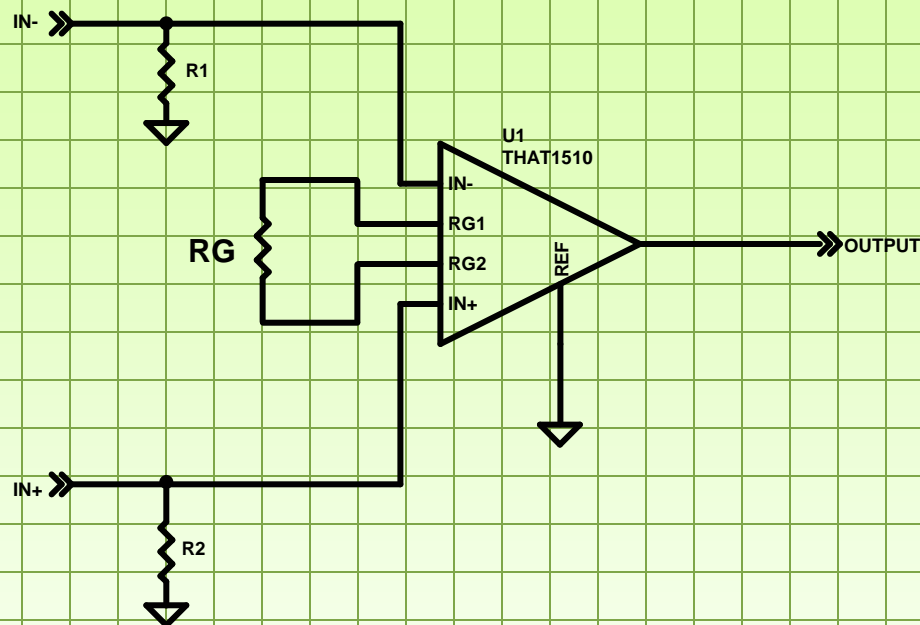
- One chip solution
 - Wide gain range
 - High bandwidth
 - Low noise
 - Low power



- Two gain options
 - 1510: $G = 1 + 10k/R_g$ (0dB min)
 - 1512: $G = 0.5 + 5k/R_g$ (-6dB min)
 - Accepts +24dBu @ +/- 15V rails

Continuously Adjustable Gain Mic Preamp

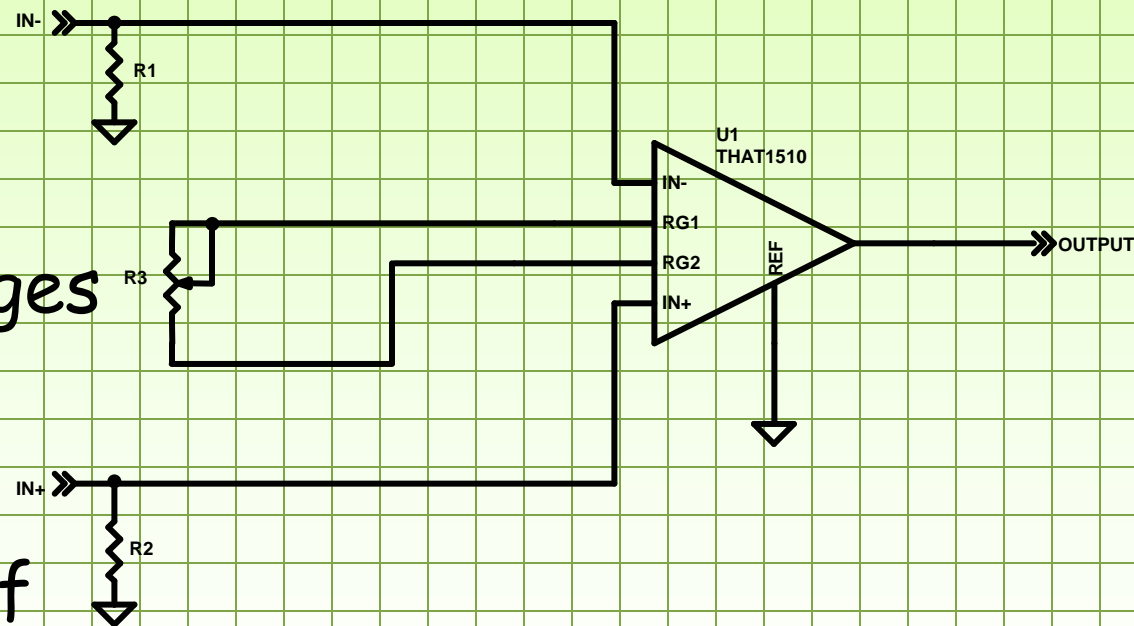
- Uses potentiometer (R3) to control gain
- 60dB+ gain range
- Output dc offset changes with gain
- Will thump if changed quickly



Cure Thump with a Capacitor


- C1 avoids output dc variations
- Sets dc gain to 1

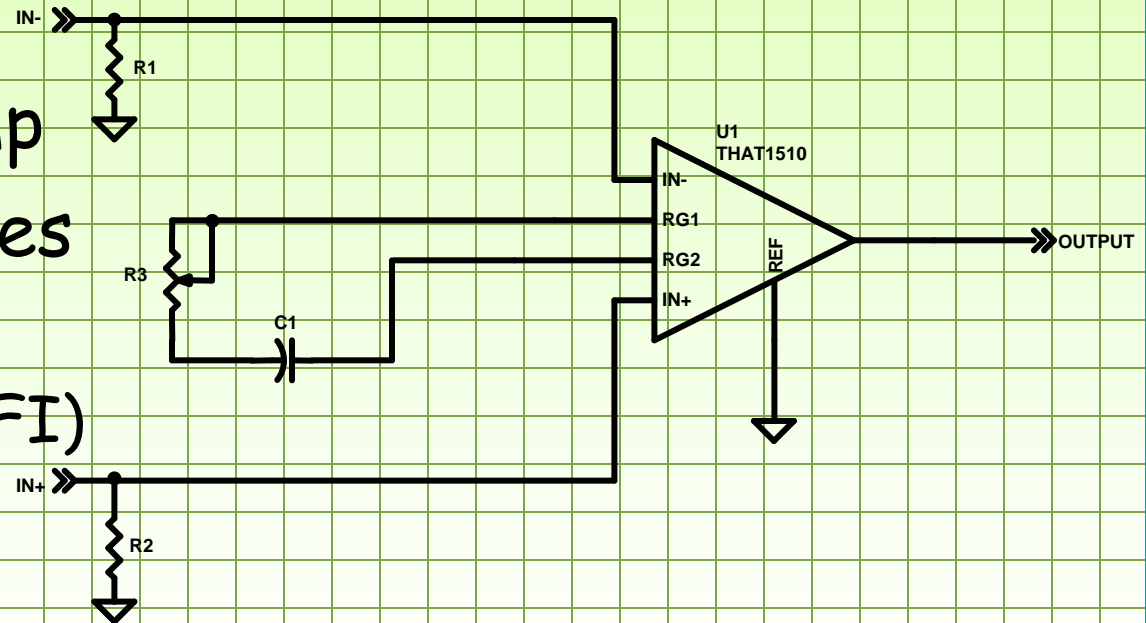- Avoids thump
- Disadvantages
 - + PCB Area
 - Antenna (RFI)
 - Cost of cap



Switched Gain Mic Preamp

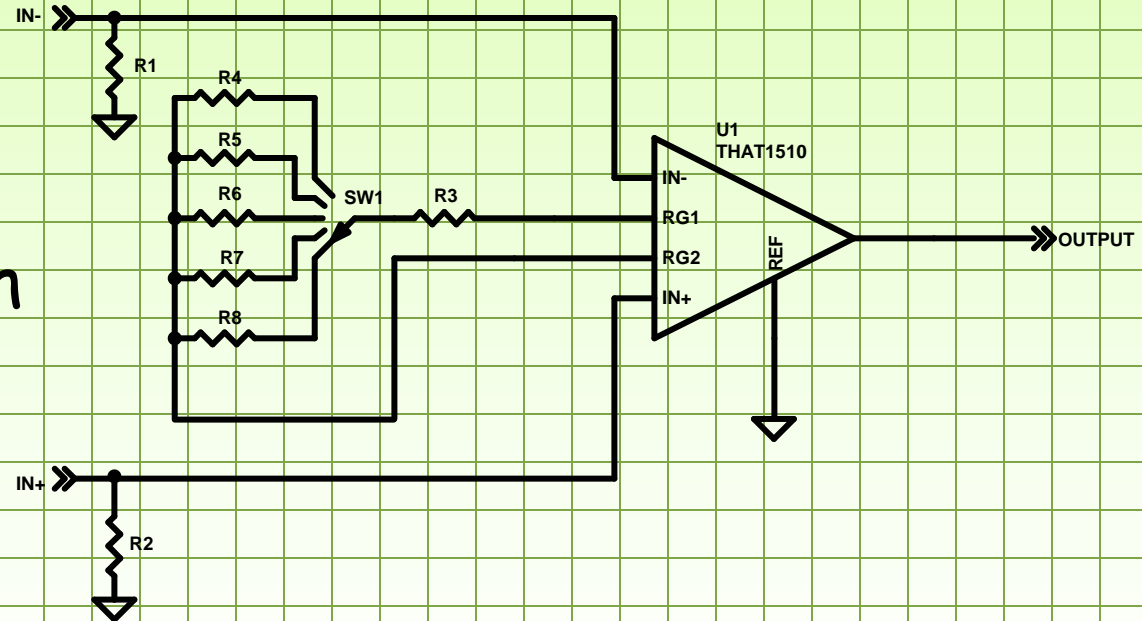- Uses switches to control gain
- 60dB+ gain range
- Output dc offset still changes with gain




- Will click when gain is changed

Cure Click with a Capacitor

- C1 avoids output dc variations
- Sets dc gain to 1

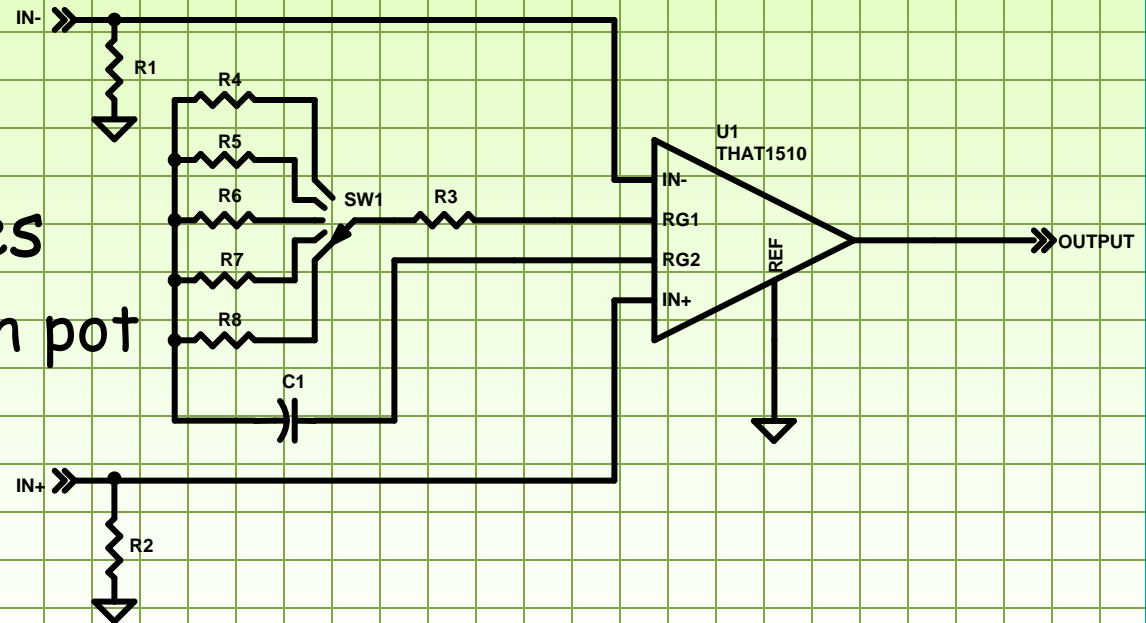- Avoids click
- Disadvantages
 - Same as with pot




Mic Preamps - Choosing the Cap

- First, choose minimum R_g based on max gain
- Second, choose highest allowed LF cutoff
- Then: $C_g = 1 / (2\pi f R_g)$
- For max gain = +60dB & LF cutoff = 5Hz
 - For 1510: $R_g = 10\Omega$, $C_g \cong 3300\mu\text{F}$
 - For 1512: $R_g = 5\Omega$, $C_g \cong 6800\mu\text{F}$
- For max gain = +40dB & LF cutoff = 5Hz
 - For 1510: $R_g = 100\Omega$, $C_g \cong 330\mu\text{F}$
 - For 1512: $R_g = 50\Omega$, $C_g \cong 680\mu\text{F}$
- Etc.

Mic Preamp with Output Servo

- Reduces steady-state output offset
- Doesn't fix transient offset

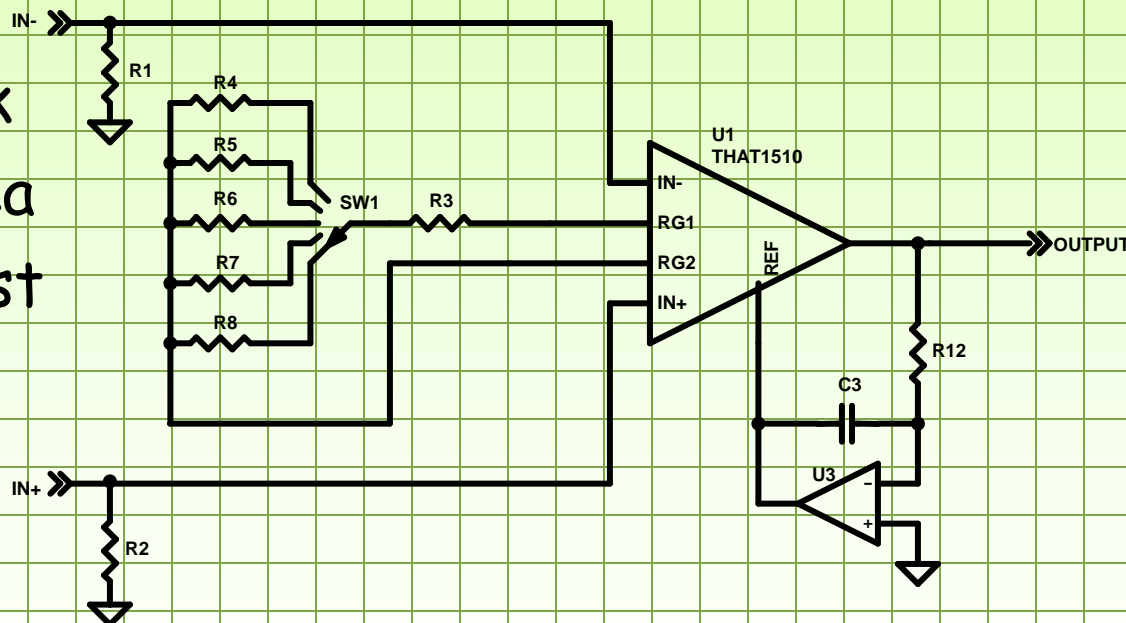- Likely to click
- Adds PCB area
- Increases cost




Mic Preamp with Input Servo

- Reduces steady-state output offset
- Reduces transient offset, too


- Requires high-performance opamp

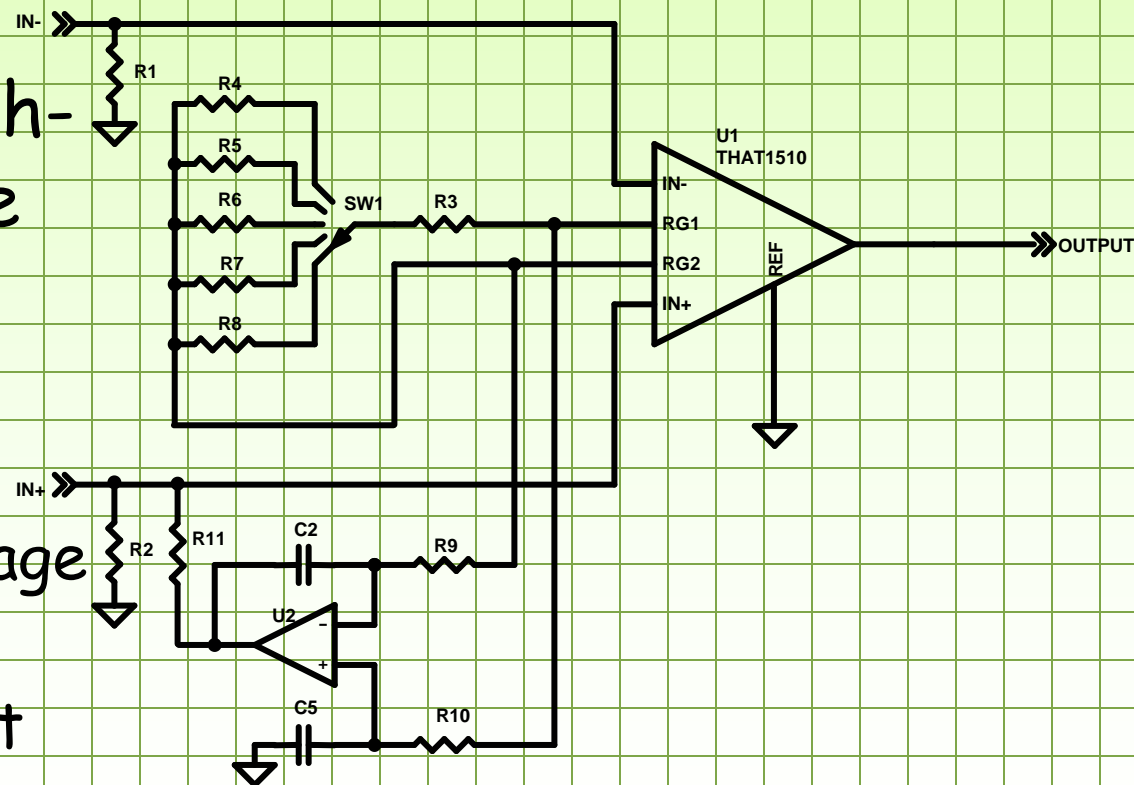- Low input offset voltage
- Low input bias current



Recommended Circuit for Digital Control

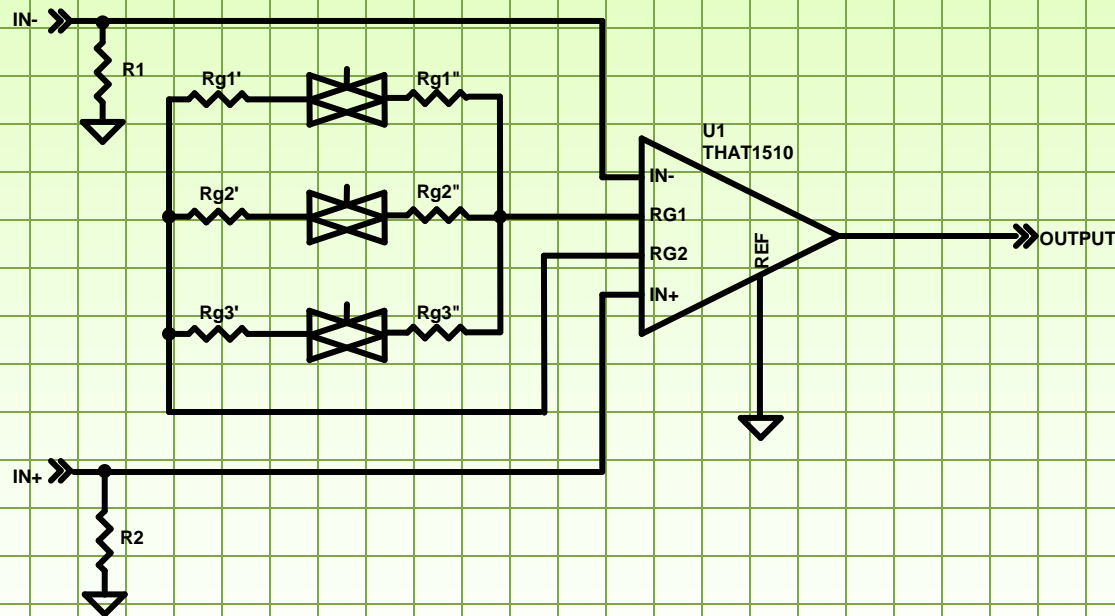
- Use C-MOS switches to change R_g
- Splitting R_g to minimize charge injection (pops)




- 1512 lowers charge injection pop by 6dB

Unbalanced Capacitance at Rg1, Rg2

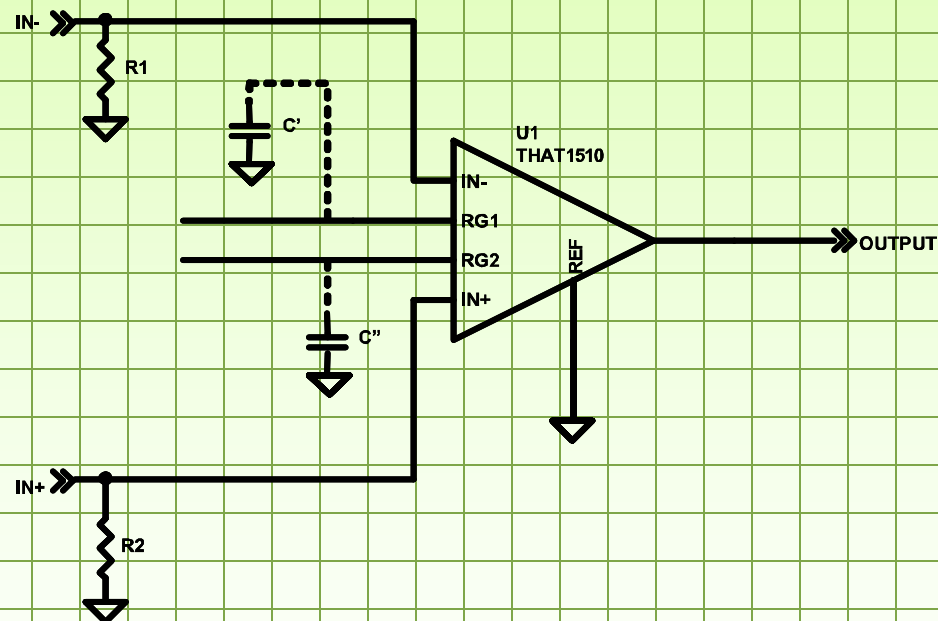
- Lowers CMRR @ HF
- Caused by
 - PCB stray capacitances
 - Different loading on Rg1 vs Rg2
- Effect is surprisingly large



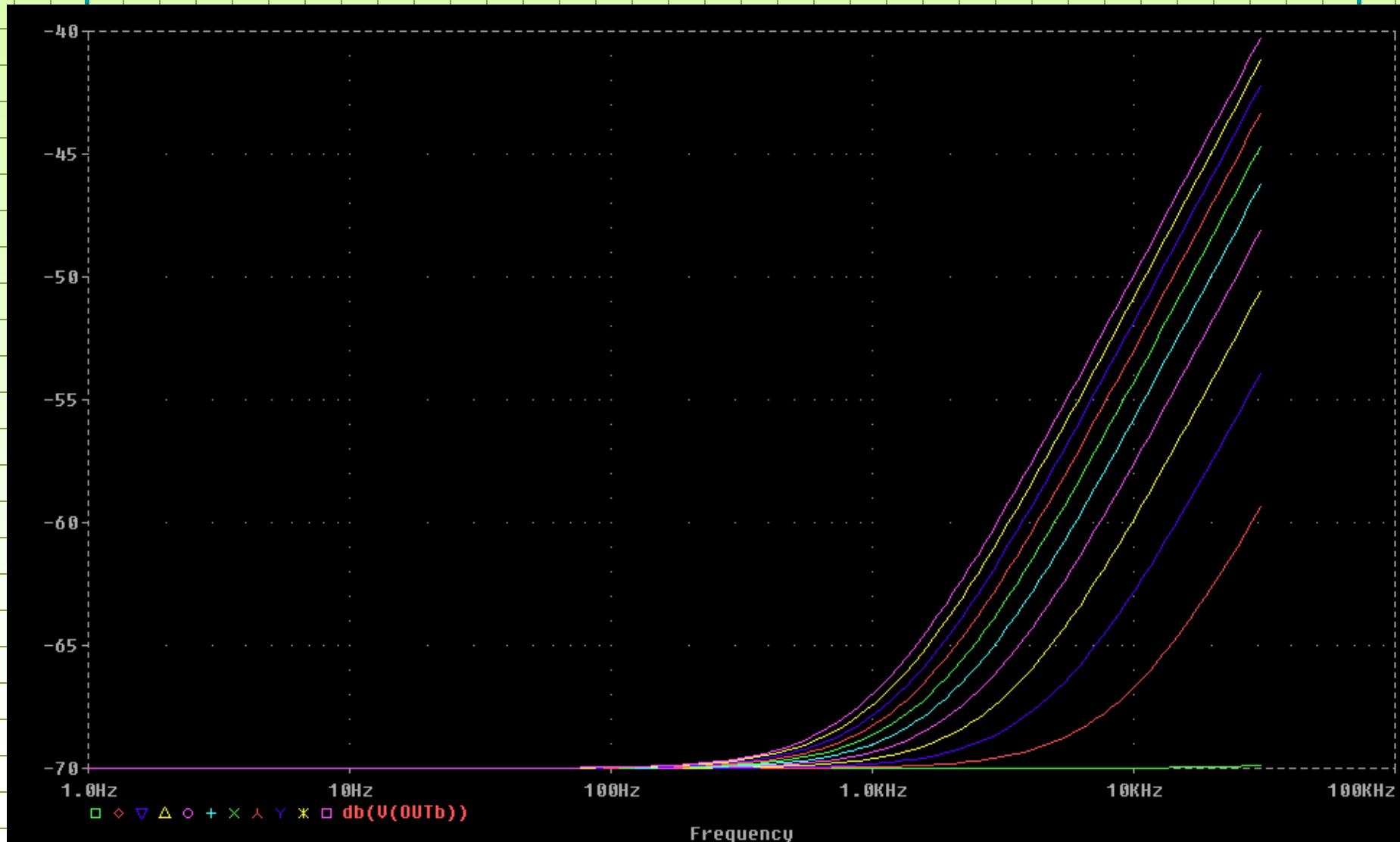Common-Mode Gain vs. Freq., 1~10pf Imbalance



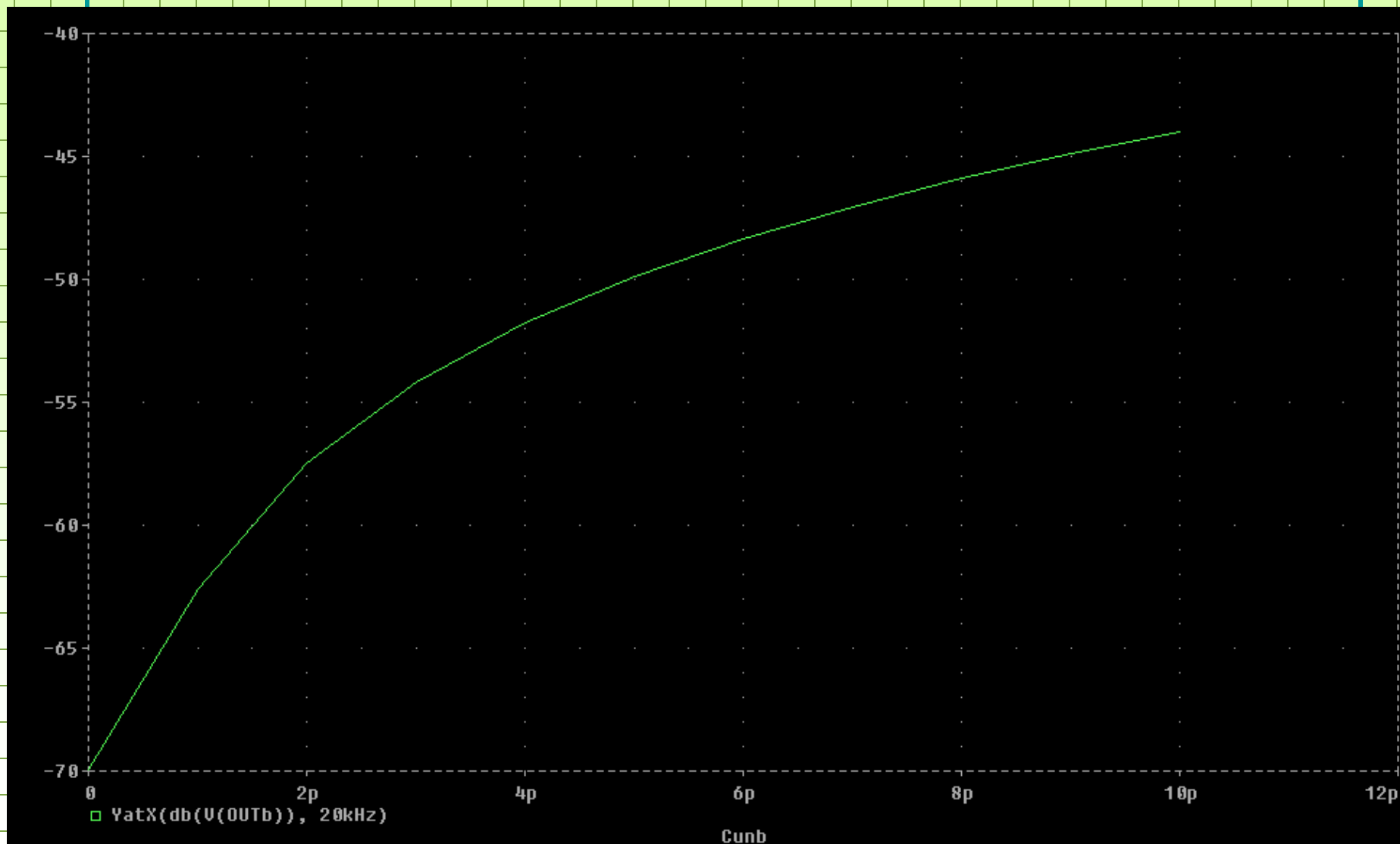Common-Mode Gain vs. Capacitive Imbalance, 20kHz



THAT Corporation

Department Engineering

Chapter *VCA/RMS & Log Math*

Name Les Tyler



Address 123rd AES Convention
New York, October 2007

THAT VCAs, RMS, & Log Math

- (Very) basic Voltage Controlled Amplifiers (VCAs)
- (Very) basic RMS Detectors
- (Very) basic Analog Engines®
- Cool "log math" simplifies designs using the above




Blackmer® VCAs Offer "Deci-Linear" Control

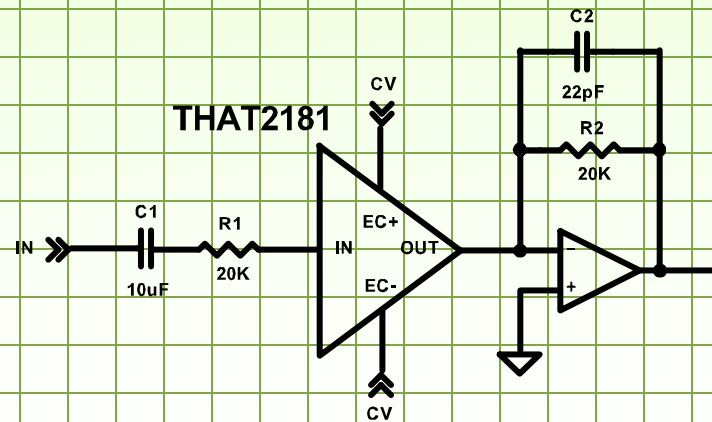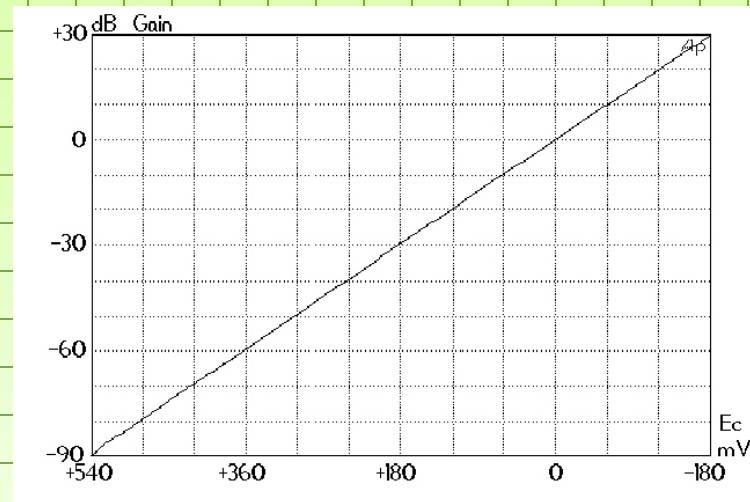- *Linear* control voltage causes *Exponential* gain (direct dB control)
- Typically -100~+40dB
- ~ ±6mV per dB gain
- Positive- & negative-sense control ports
- Current in & out
- Singles: 2180/1-series
 - SO-8 & SIP-8
- Dual: 2162
 - QSOP-16





THAT Level Detectors Are "Deci-Linear"

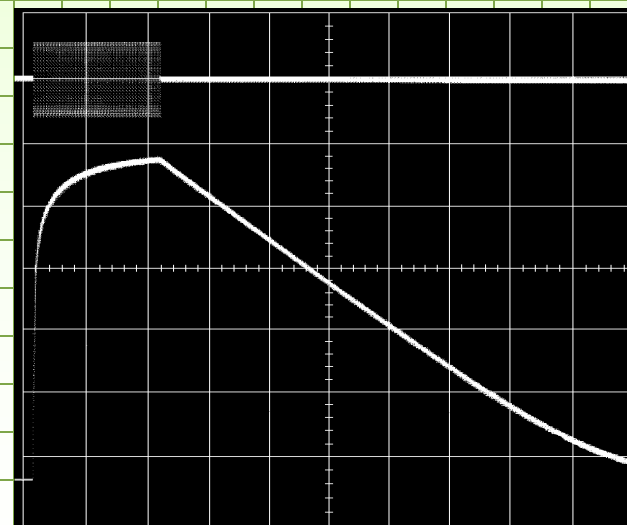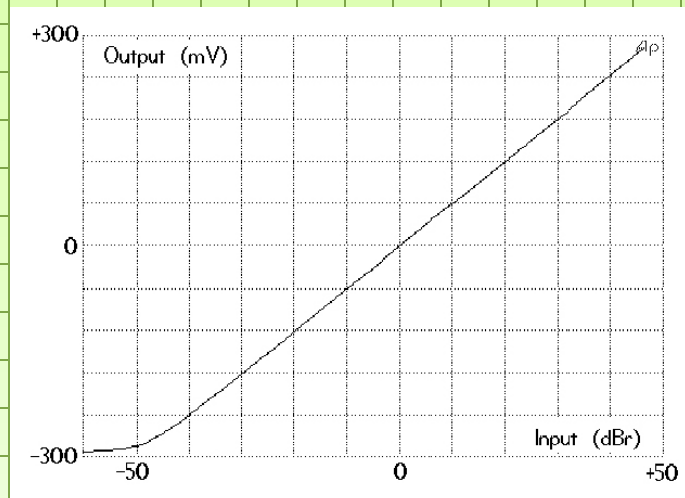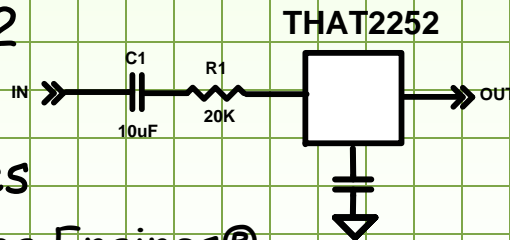- Logarithmic output Voltage (direct dB) reading
- Good linearity over >60dB
- Current in, voltage out
- RMS-responding
- Time response mimics ear's time-weighting
 - Less sensitive to phase shifts than peak or average.
- Single: 2252
 - SIP-8
- SO-packages
 - See Analog Engines®



Analog Engines®: VCAs + RMS Detector

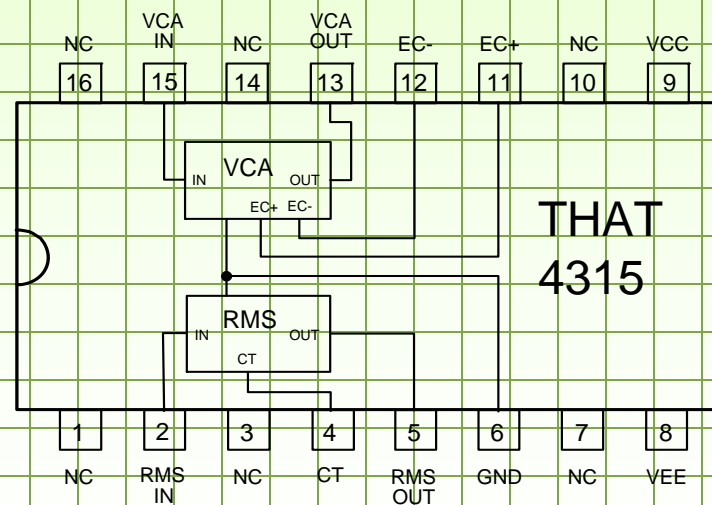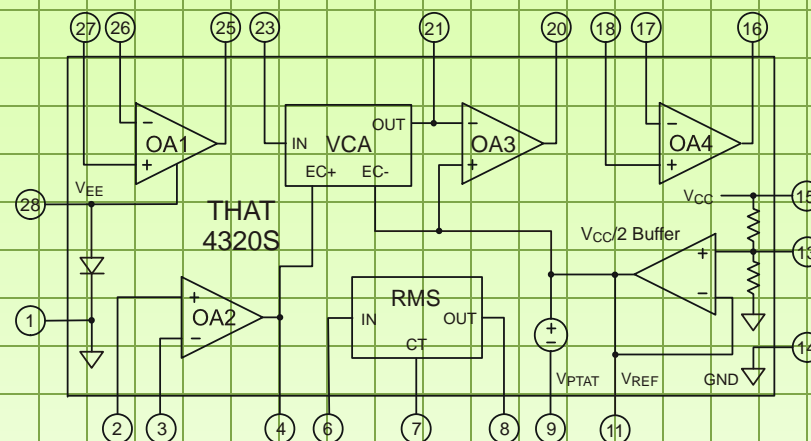- Compressor/limiter on a single chip
- Versatile 4320/4301
 - Includes several opamps and other useful stuff
- Basic 4305/4315
 - Just VCA and RMS detector
- 4301/4305
 - High voltage ($\pm 15V$)
- 4315/4320
 - Low voltage, low power (+5V, 1.6mA)



Analog Engines® Are Deci-Linear, Too

- VCAs offer Deci-Linear control law
 - Direct dB control of gain
- Detectors offer Deci-Linear output law
 - Direct dB reading of RMS level
- Makes designing complex dynamics processors easy
 - Compressors/Limiters
 - Expanders/Gates
- Feedforward possible
 - VCA control law matches RMS-detector output law
- Deci-Linear characteristic makes "log-math" useful for side chain design
- Easily produces repeatable, predictable results

Linear Math Approach

- VCA gain law: $A_V = e^{\frac{-E_C}{2V_T}}$
- Detector output law: $V_{OUT} = 2V_T \ln(V_{inrms})$
- "Linear" math leads to exponentials & logs
- Combining these two *theoretically* predicts gain trajectory
- But, do you really want to deal with this math?


"Log Math" Approach

- Express signal levels as their dB levels
- Express all gains in dB
- VCA gain law: $A_{db} = -166.7E_c$
- Detector output law: $V_{OUT} = 0.006 \text{ dB}_{RMS}$
- "Log" math reduces the exponentials and logs to simple, linear relationships
- Much easier to deal with!

Feedforward Processors - Log Math

- We can combine the previous two equations, and get:
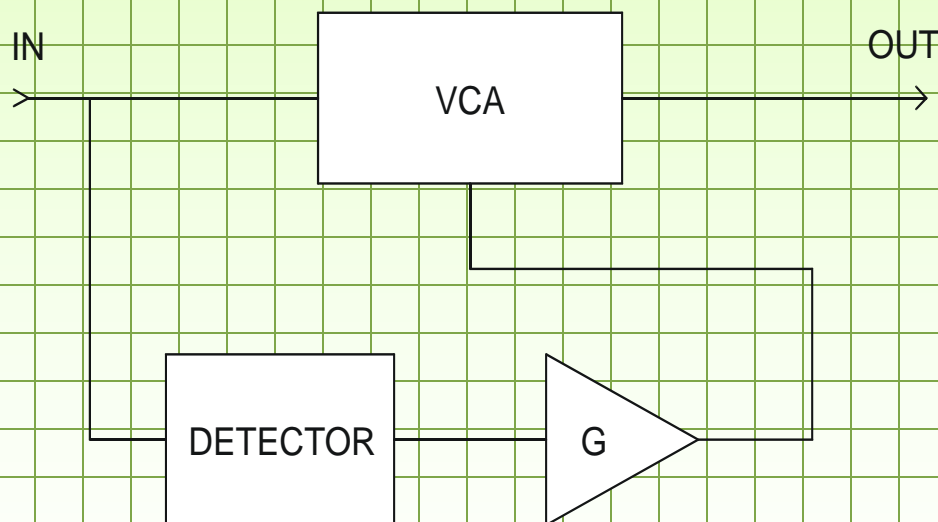
$$\text{dB}_{OUT} = \text{dB}_{IN} + [-166.7 \cdot (G \cdot 0.006 \text{ dB}_{IN})] = (1 - G) \text{dB}_{IN}$$



- Compression (Expansion) ratio is:

$$\frac{\text{dB}_{IN}}{\text{dB}_{OUT}} = \frac{1}{(1 - G)}$$
- Sign of gain determines compress or expand
- Lots of variations possible
 - Infinite compression
 - Negative compression

Feedback Processors - Log Math

- The VCA control voltage depends on the detector's level reading and G :


$$E_c = G \cdot 0.006 \text{ dB}_{OUT}$$

- But, the output signal depends on the input and the VCA gain:

$$\text{dB}_{OUT} = \text{dB}_{IN} + [166.7 \cdot (G \cdot 0.006 \text{ dB}_{OUT})] = \text{dB}_{IN} - G \text{ dB}_{OUT}$$

- Combining and rearranging, we can solve for the Compression (or Expansion) ratio:

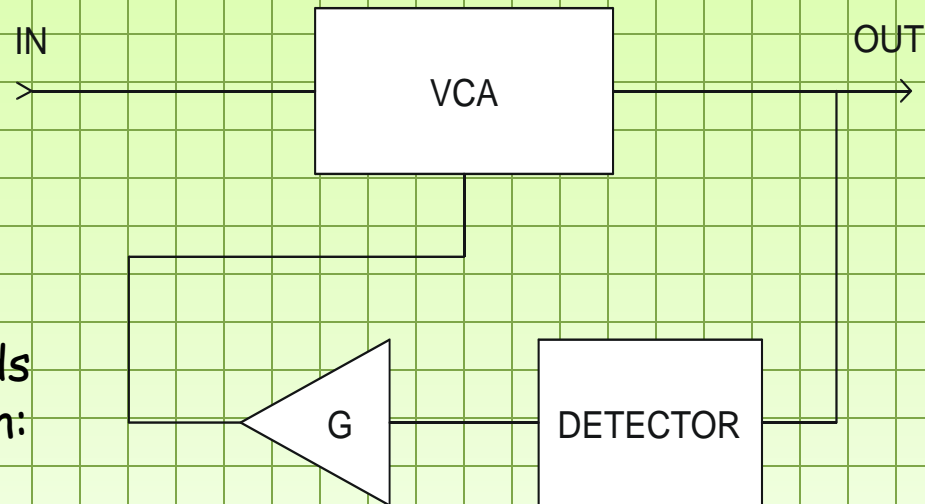
$$\frac{\text{dB}_{IN}}{\text{dB}_{OUT}} = 1 + G$$



- Sign of gain G determines compress vs. expand
- Fewer variations are possible due to stability considerations
 - Infinite compression is unstable!


Adding Thresholds

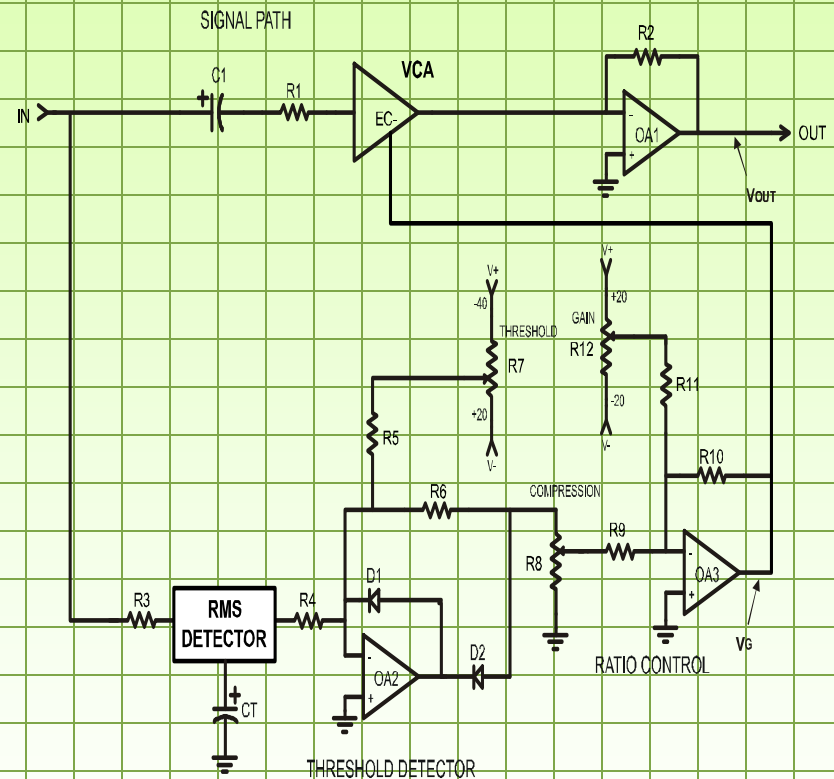- Change G based on detector's output level
 - Half-wave rectifier
 - OA2/D1/D2
- Vary dc offset (R7) before rectifier
 - Changes the "active region" where detector's output passes to the VCA control port
 - Corresponds to a dB threshold



Controlling Ratio and Static Gain

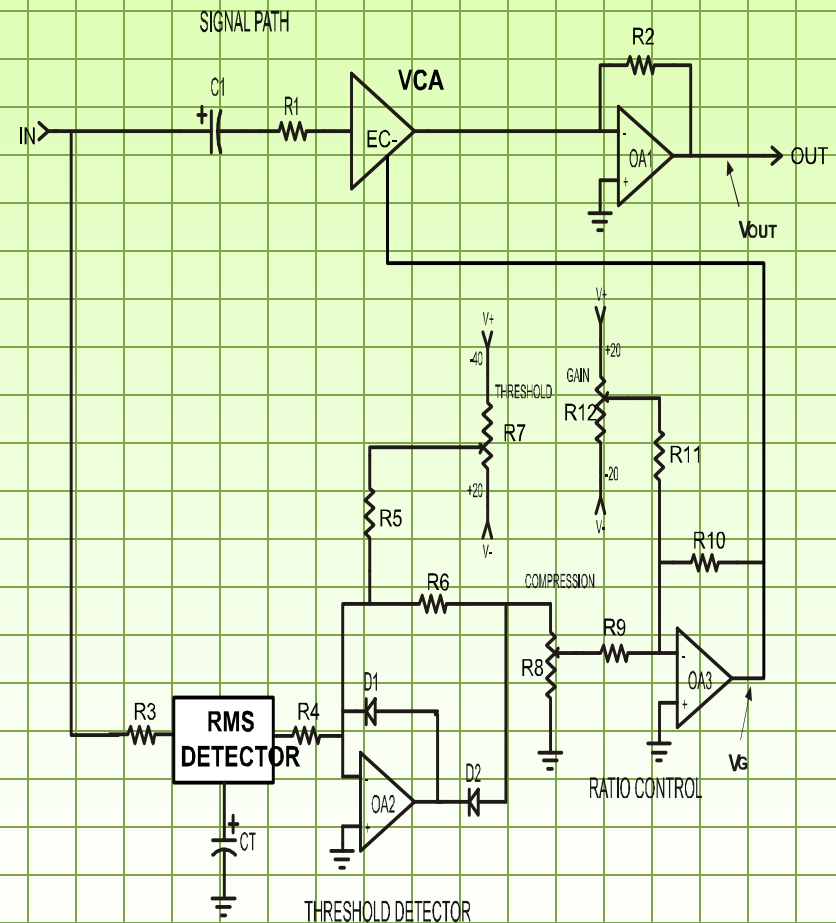- Vary control path gain (R8)
 - Changes G (in the active region)
 - Controls compression/expansion ratio
- Vary dc offset (R12) after clamp circuit
 - Changes static gain



See THAT's app notes for more detail

- AN101a: details about "Log math" involved
- AN100a: side-chain circuit details
 - Compressor application
- Many others for more circuit ideas

THAT Corporation

Department Engineering

Subject **Balanced Outputs**

Name Gary Hebert

Address 123rd AES Convention
New York, October 2007


Balanced Floating Output Drivers

- Imitate some aspects of output transformers
- High common-mode output impedance (several $k\Omega$)
- Low differential output impedance
- Feedback minimizes common-mode output current ($I_{out+} = -I_{out-}$)
- Output appears across two output terminals
 - Whether or not one is grounded

Clipping Behavior



- Traditional designs can lose control over output current if clipped when one output is grounded
 - CM feedback is lost
 - Output current in grounded leg increases to current limit
 - Can lead to distorted crosstalk
- Outsmarts® CM feedback loop maintains control
 - No current limiting
 - Less sensitive PCB layouts

OutSmarts Demo Board - Block Diagram

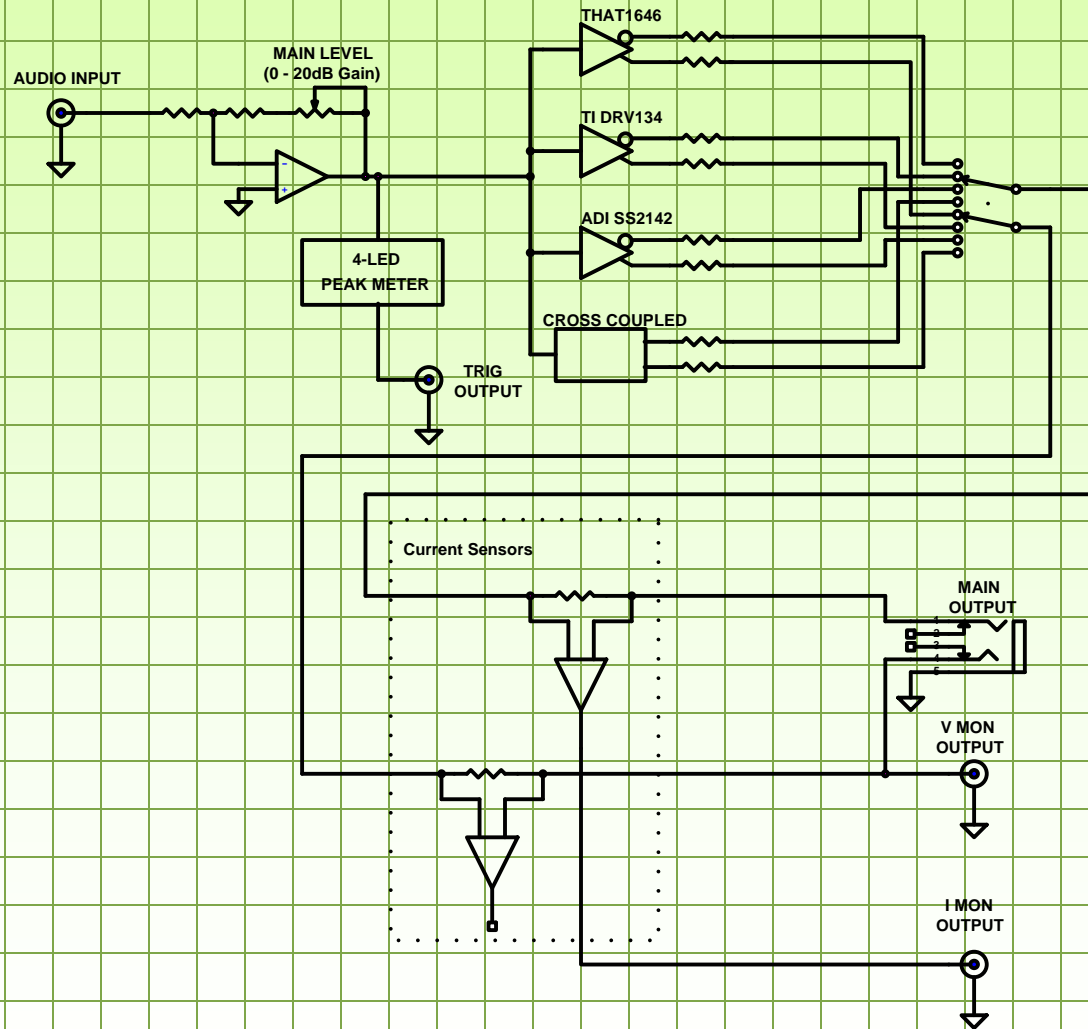

Clipping Into Single-ended Loads



- THAT 1606/1646 Behavior

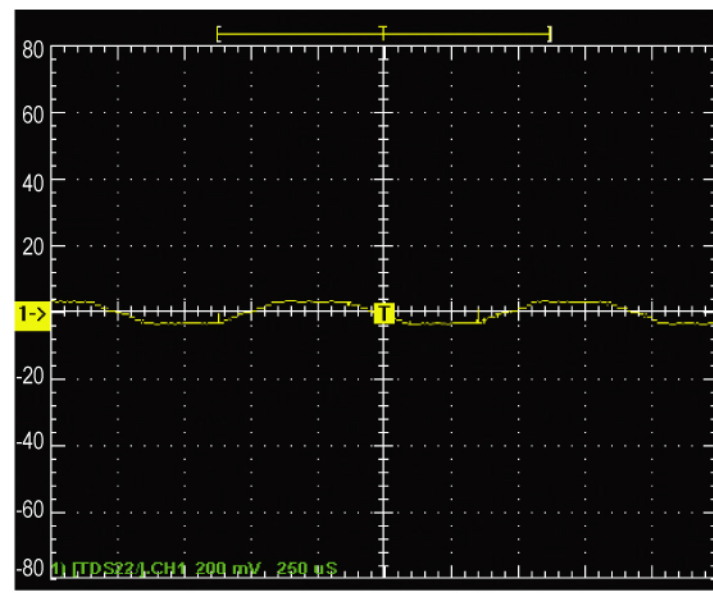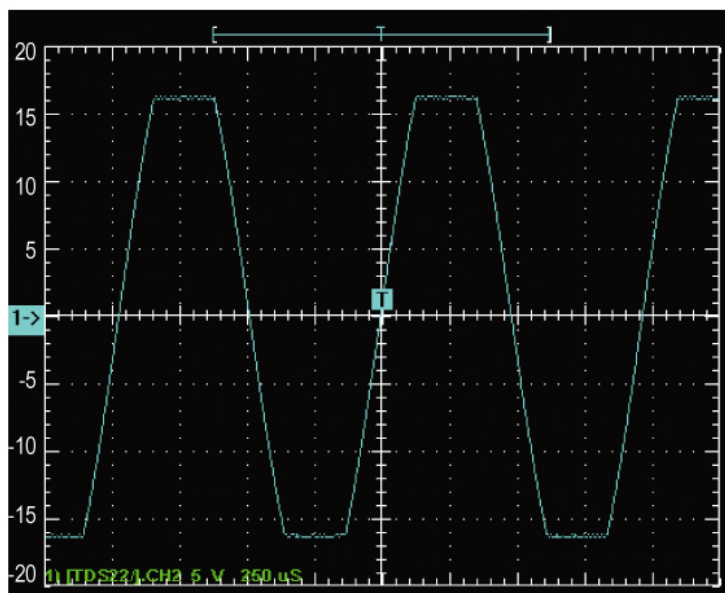

Note: $f_{IN} = 1 \text{ kHz}$, $Z_{LOAD(+)} = 10 \text{ k}\Omega$, $Z_{LOAD(-)} = 0 \Omega$

Clipping Into Single-ended Loads



- SSM2142 Misbehavior

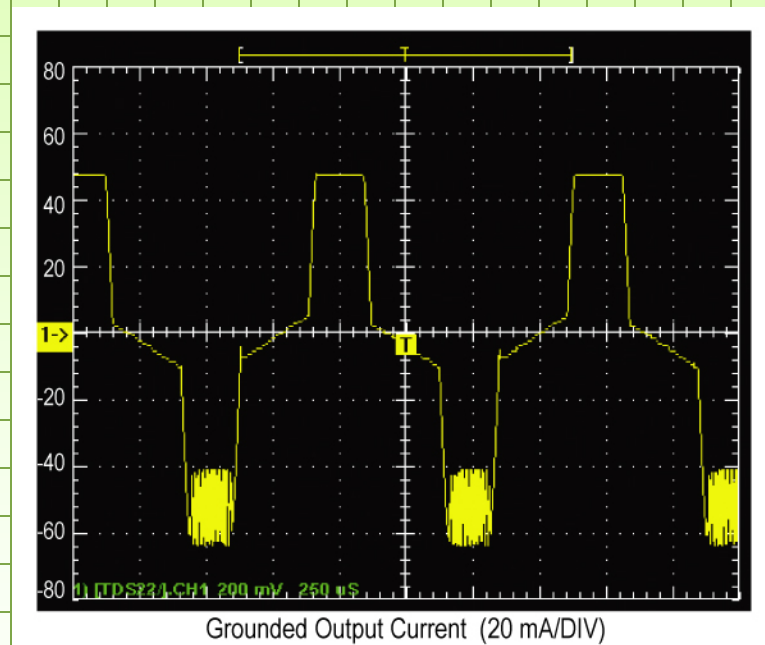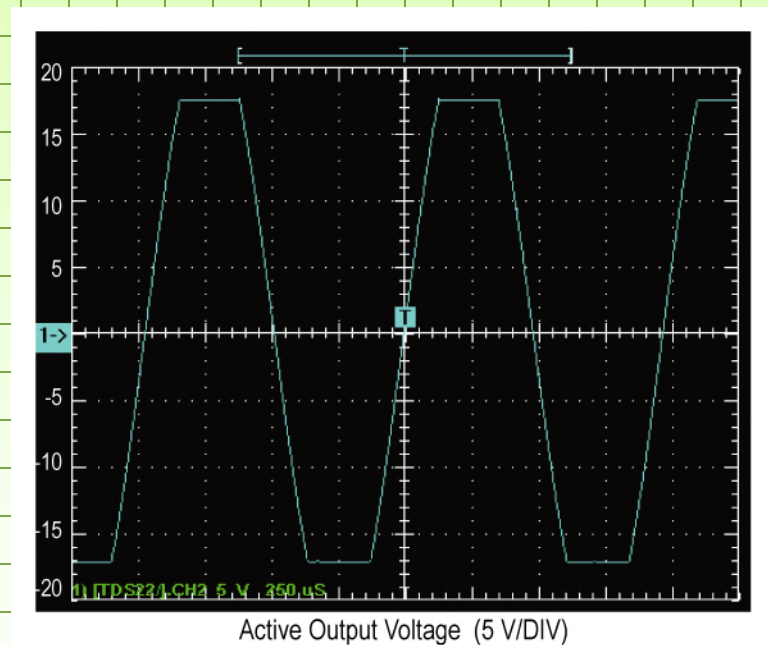

Note: $f_{IN} = 1 \text{ kHz}$, $Z_{LOAD(+)} = 10 \text{ k}\Omega$, $Z_{LOAD(-)} = 0 \Omega$


Clipping Into Single-ended Loads

- DRV134/135 Misbehavior

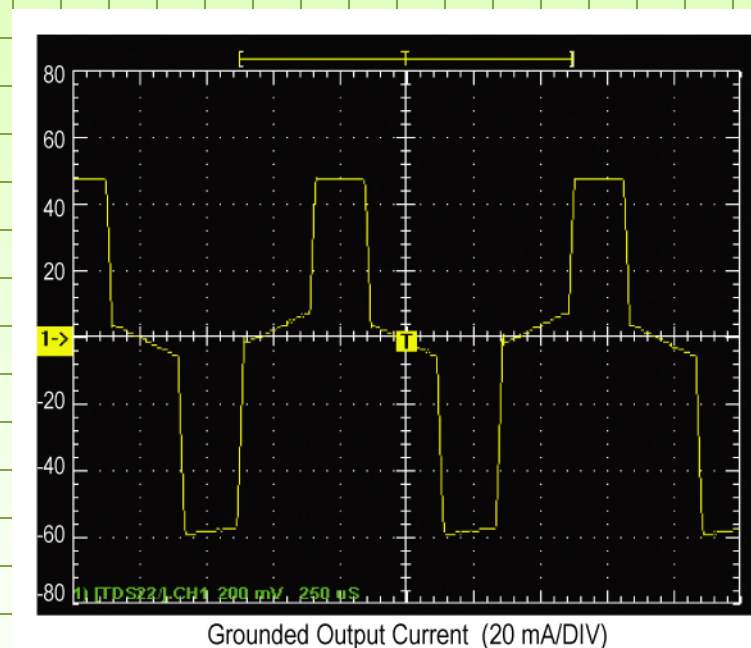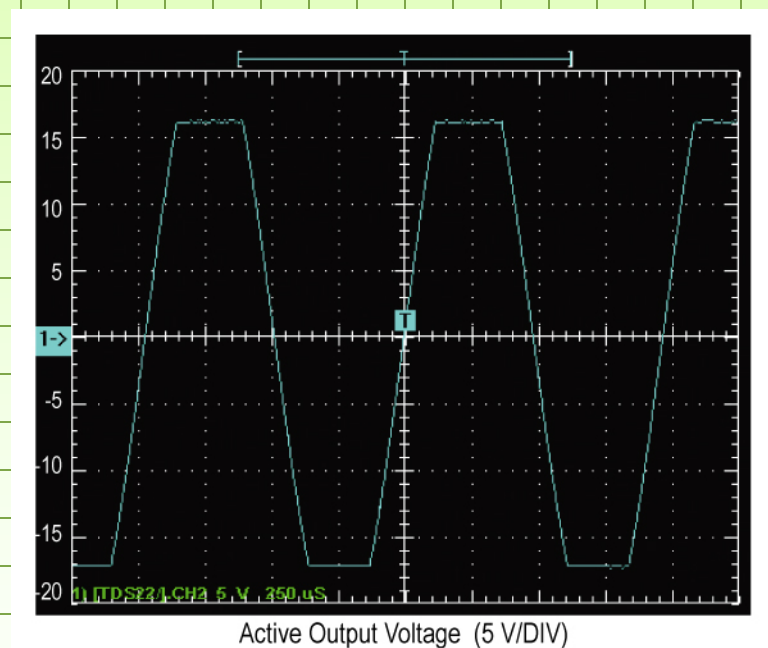

Note: $f_{IN} = 1 \text{ kHz}$, $Z_{LOAD(+)} = 10 \text{ k}\Omega$, $Z_{LOAD(-)} = 0 \Omega$

CMRR Depends on Impedance Ratios

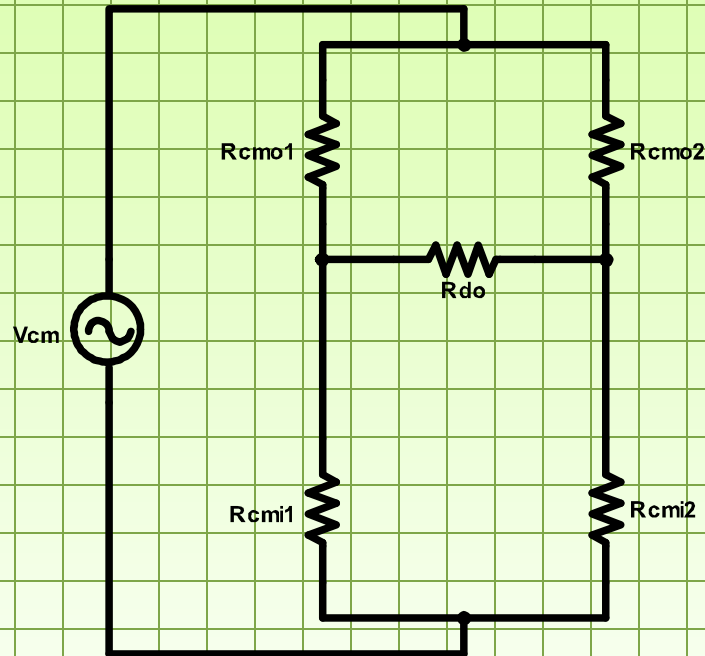


- Wheatstone Bridge
 - Models Balanced Driver/Receiver
- CMRR is high if ratios match
- CMRR degrades if $R_{cmo1}/R_{cmo2} \neq R_{cmi1}/R_{cmi2}$
- CMRR is unaffected by differential signal level

Signal Balance


- Signal Balance measures match of + and - output levels
 - Using a perfectly balanced load
- Signal Balance affects only headroom
- Might affect crosstalk in multipair cables
- Does *not* affect CMRR

Discrete Balanced Floating Output Driver

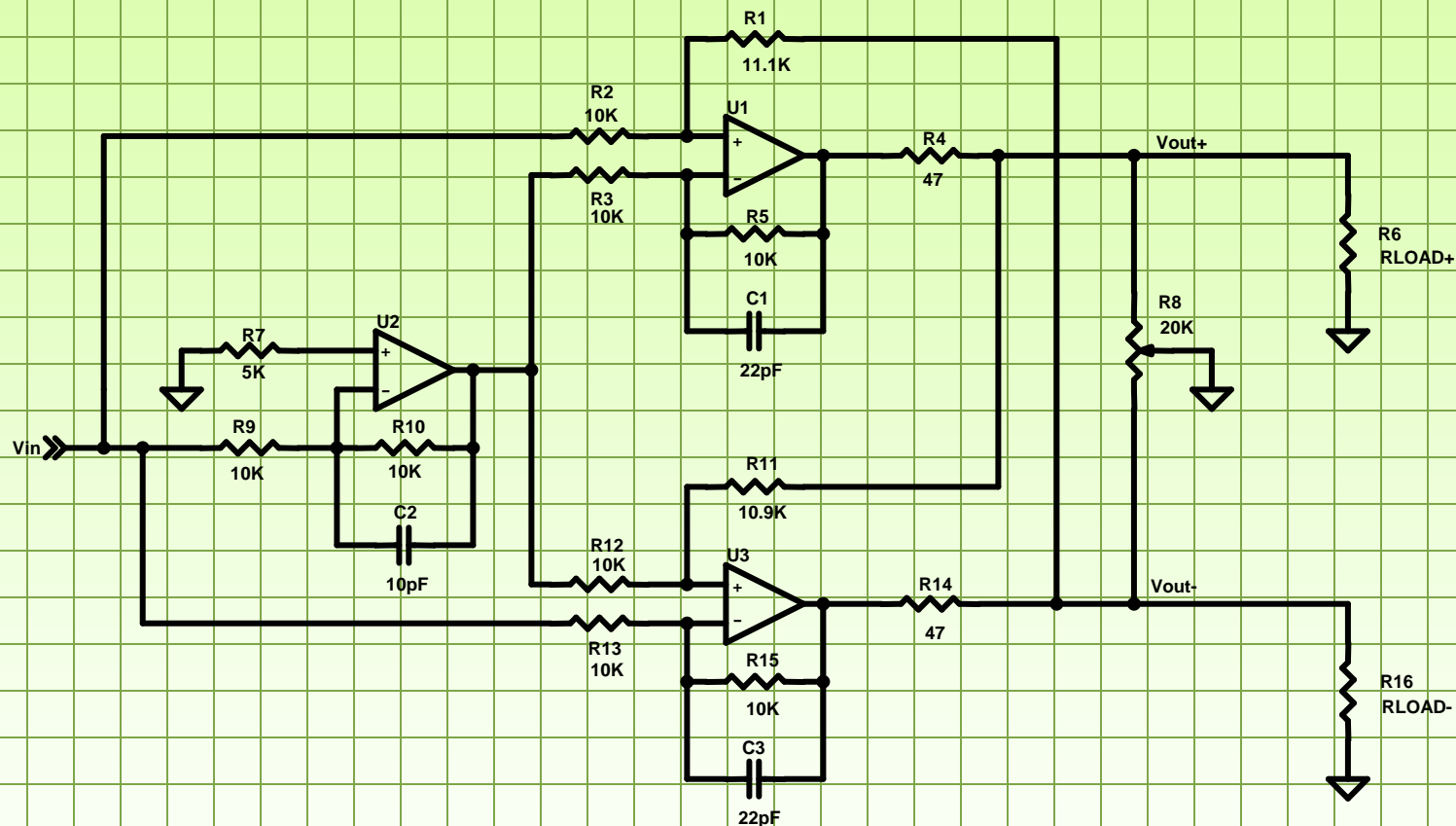


- R1, R11 deliberately increased (nominal 11k Ω)
 - Ensures stability
 - Lowers CM output impedance

Discrete Balanced Floating Output Driver

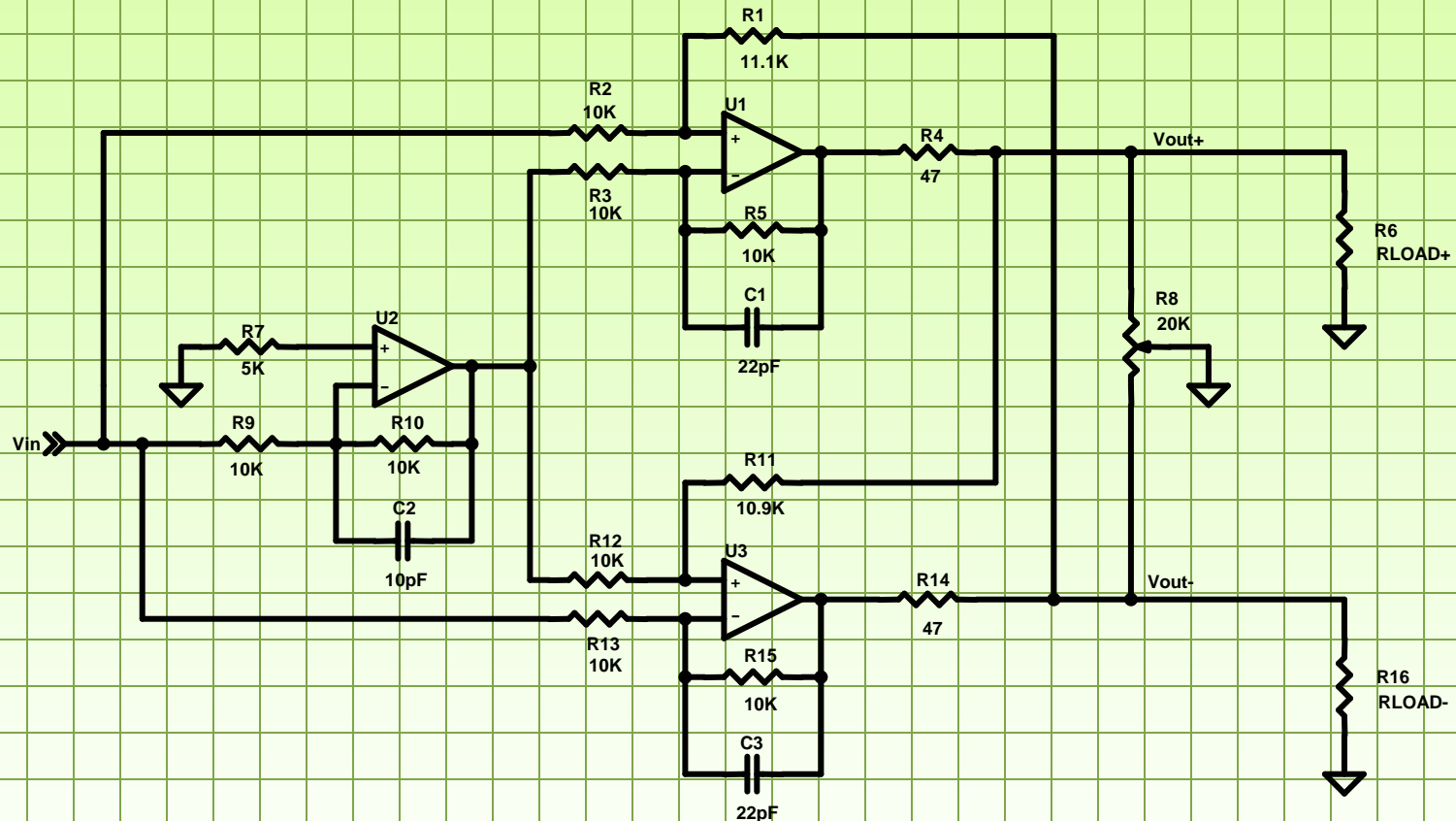


- R8 is typically trimmed for best signal balance
 - Compensates for resistor mismatches (e.g., R1/R11)
 - But this is not the best solution

Signal Balance vs. Pot Rotation

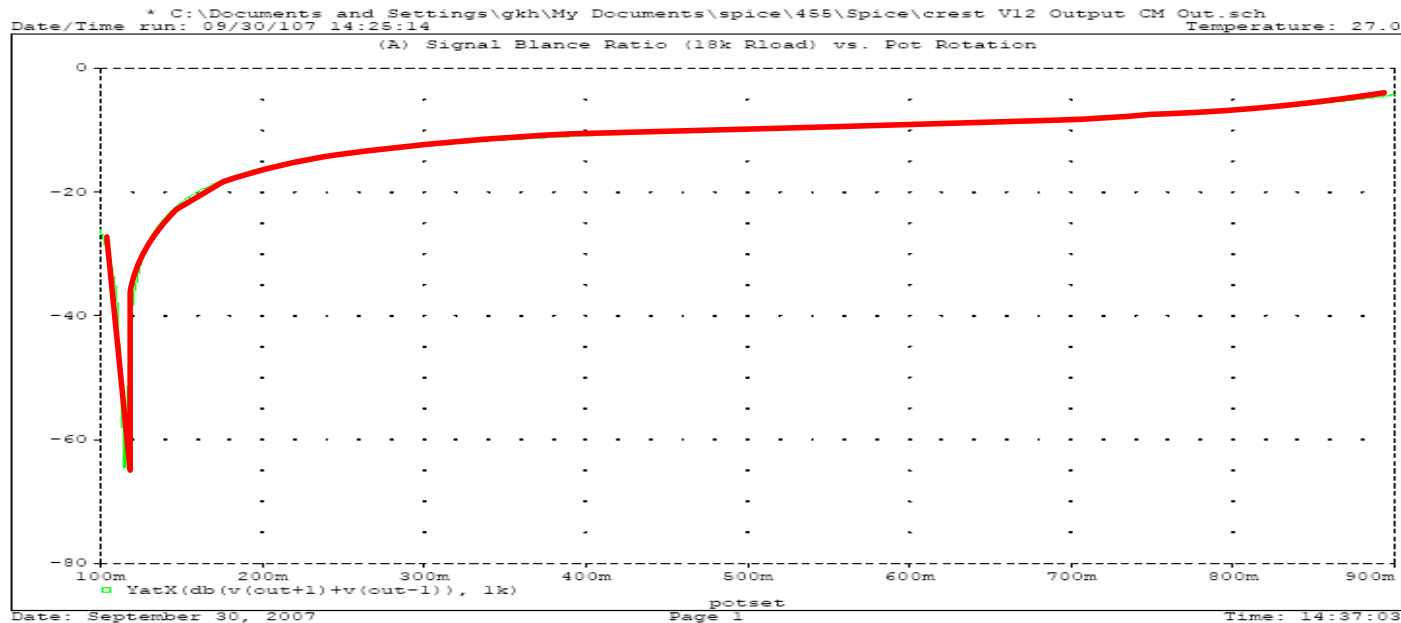


- $SBR = 20\log((V_{o+} + V_{o-})/V_{in})$
- Load is 18 k Ω per output
- Null occurs at about 11.5% pot rotation

CMRR vs. Pot Rotation

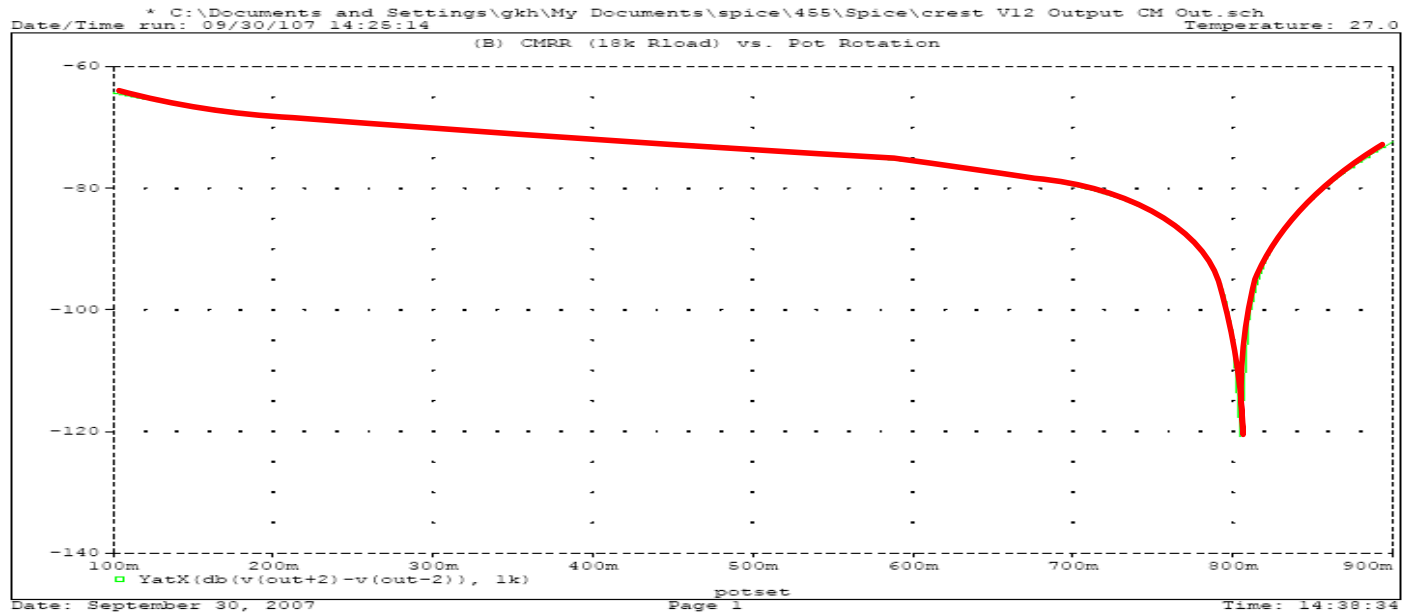


- Same 18 k Ω loads (perfectly matched)
- CMRR null occurs at about 80% pot rotation
- CMRR after trim is 10 dB worse than no trim at all

CMRR vs. Pot Rotation - 10 Meg Ω Zin

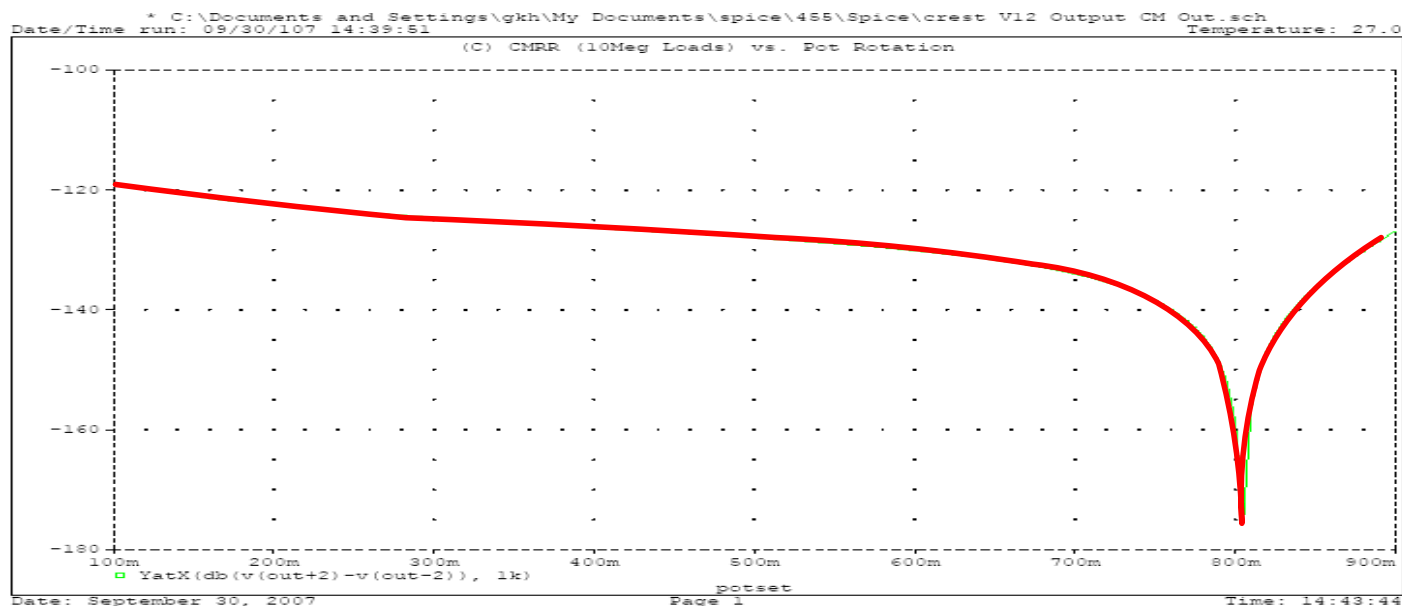


- CMRR vs. Pot Rotation with 10 Meg Ω CM loads
- With InGenius input this isn't an issue

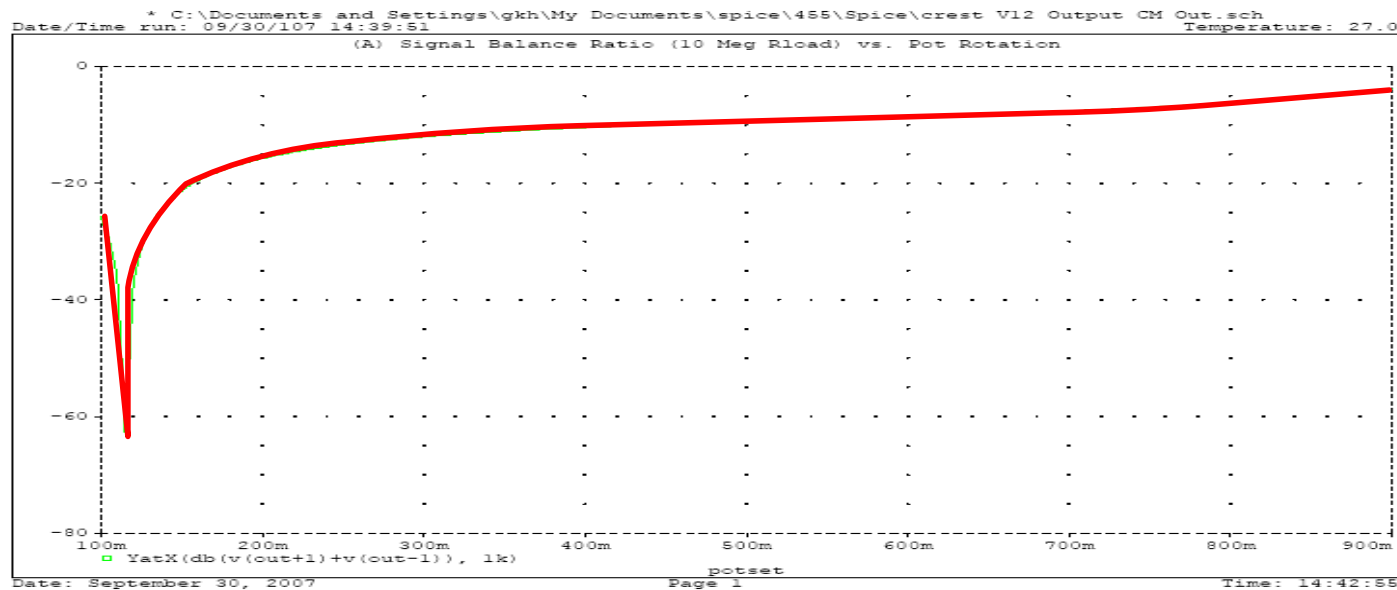Signal Balance vs. Pot Rotation - 10 M Ω Zin



- However, Signal Balance is unchanged with 10 Meg Ω loads

THAT Output Driver ICs

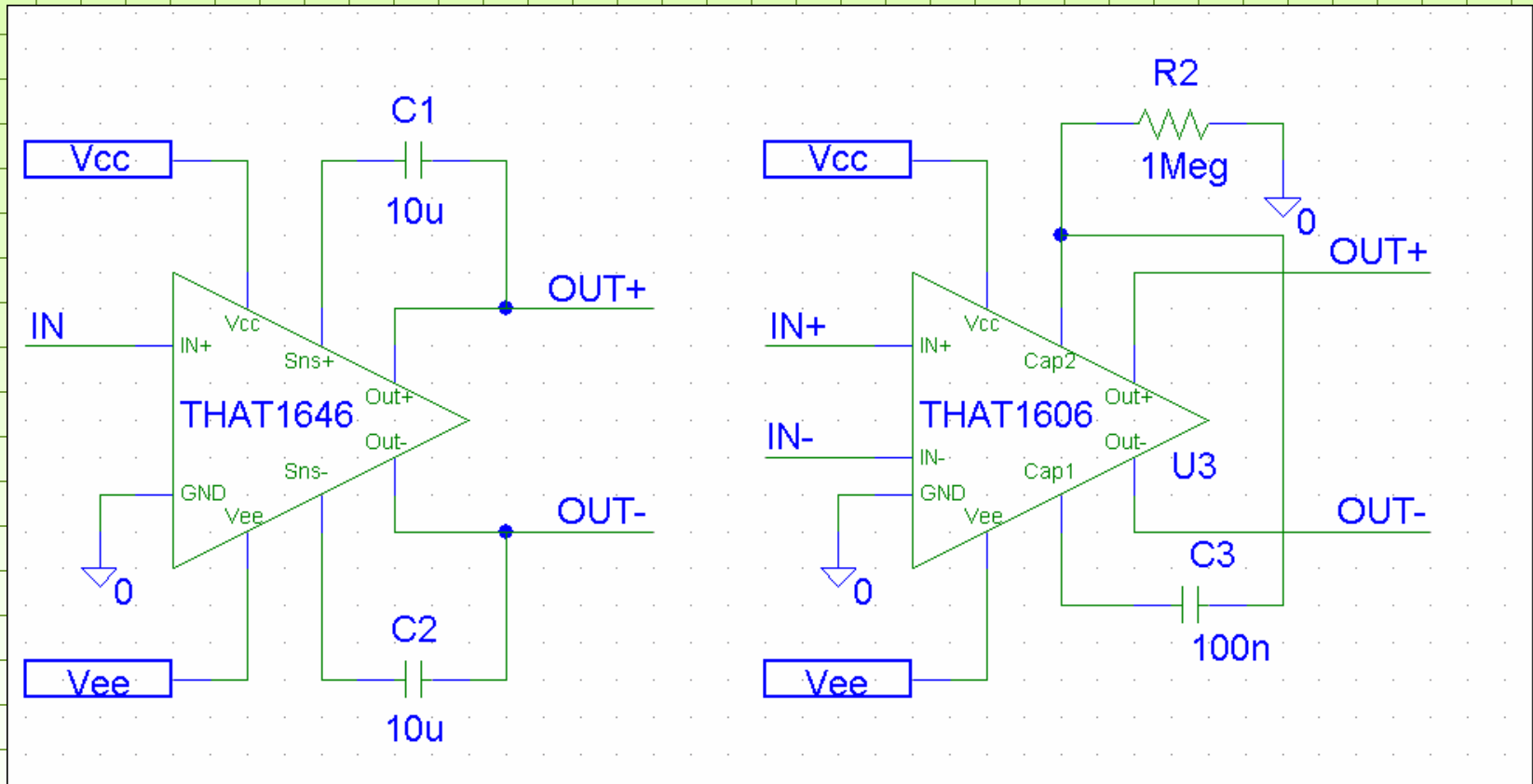

- Trimming is complex - let us do it for you
- 1646/06 include all required trims & adjustments

THAT Corporation

Department Engineering

Chapter *Wrap Up*

Name Bob Moses

Address 123rd AES Convention
New York, October 2007

Conclusions

- Secret #1: new ICs from THAT!
- Secret #2: Mic Preamps need dc stability
 - Use capacitor in series with R_g
 - Output servo is of limited benefit
 - Input servo can work well, but is expensive
- Secret #3: For digital control, put analog switches inside split pairs of R_g
- Secret #4: Match stray loading on R_g pins
- Secret #5: Log math is easy and fun!
- Secret #6: Cross-coupled balanced outputs misbehave in some real world conditions
- Secret #7: OutSmarts® delivers optimal performance under tortuous conditions