

**IN THIS COLUMN, WE TRY TO BRING YOU** news and details of new and interesting semiconductors and related matters without any month-to-month continuity. This month, because of long-time reader interest in volume expanders and audio noise reduction, we are deviating from the established format to show the circuit of the volume expander that complements the volume compressor discussed last month.

The hi-fi expander in Fig. 1 includes de-emphasis and attack and decay times to complement the compressor. Again, an external op-amp is substituted for the one in the Signetics NE570 compandor IC. In this case, the circuit performance demands a slew rate better than the 0.6 volts-per-microsecond provided by the NE570 op-amp. The expander, like the compressor, has a unity-gain level of 0 dBm. Adjustments are provided for harmonic distortion and DC shift.

Make the **THD TRIM** adjustments first using a 10-kHz 0-dBm (774.6 mV) signal. Adjust the **DC SHIFT TRIM** for minimum envelope bounce when tone bursts are fed through the circuit.

Performance is reported to be spectacular when the expander is applied to consumer tape recorders.

