


Paraphase Tone Control

011

Ton Giesberts


As opposed to the widespread Baxandall circuit (dating back to 1952!) a 'paraphrase' tone control supplies a straight frequency response as long as the bass and treble controls are in the same position. This unique property makes the 'paraphrase' configuration of interest if *only* treble or bass needs to be adjusted — it is not possible to adjust both at the same time! Essentially, it's the difference in setting of the tone controls that determines the slope of the frequency response, and the degree of bass/treble correction.

The circuit in **Figure 1** is simplicity itself, based on two networks C1-C2-C3/R9-R10-R11 and C5-C6-C7/R12-R13-R14. The first is for the high frequencies (treble) response, the second, for the low frequencies (bass). The roll-off points have been selected, in combination with C4 and C8, for the sum of the two output signals to re-appear with a 'straight' frequency response again at the output. Roughly equal output levels from the networks are ensured by $R6 = 7.15\text{ k}\Omega$ and $R8 = 6.80\text{ k}\Omega$. However, the operating principle requires the input signals to the two networks to be in anti-phase. For best operation the networks are driven by two buffers providing some extra gain. The gain of IC1.D is slightly

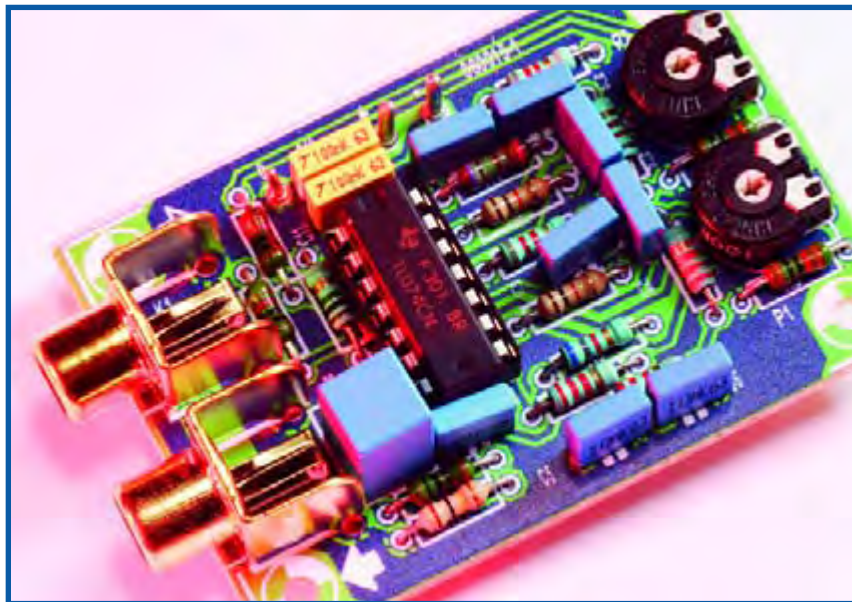

Specification

Current consumption (no signal)	8 mA
Max. input signal	$1 V_{\text{eff}}$ (at max. gain)
Gain at 20 Hz	+13.1 dB max. -6.9 dB min.
Gain at 20 kHz	+12.2 dB max. -7.6 dB min.
Gain (controls at mid position)	2.38 x
Distortion ($1 V_{\text{eff}}$, 1 kHz)	0.002% (B = 22kHz) 0.005% (B = 80 kHz)

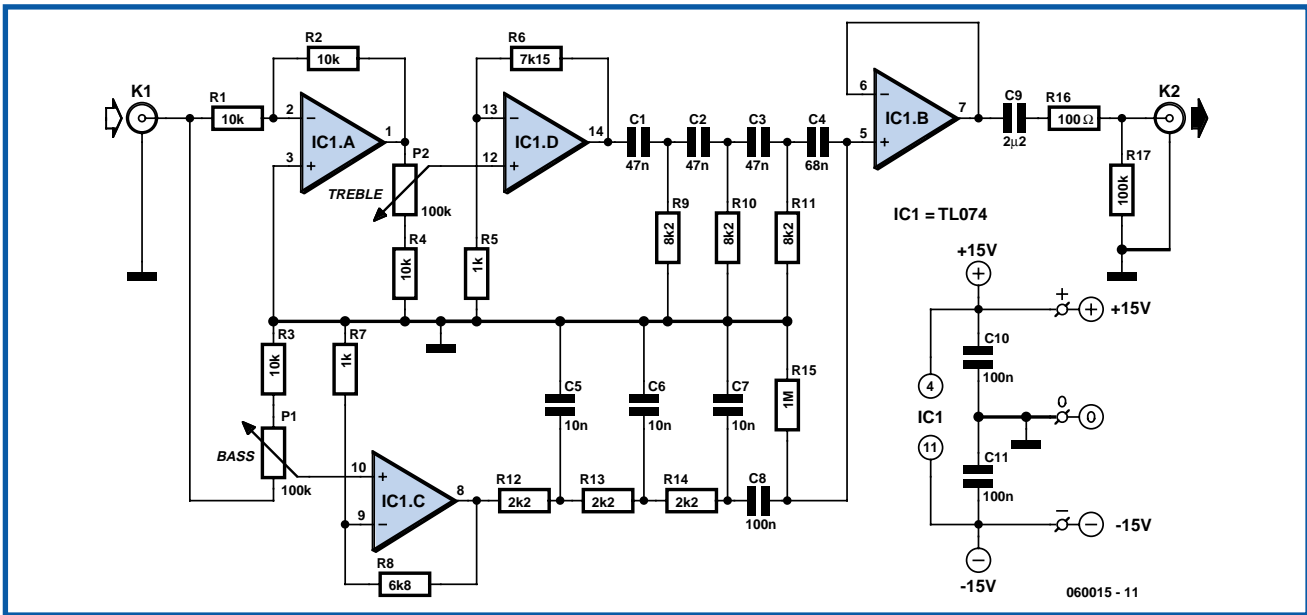

higher than that of IC1.C to ensure the overall response curve remains as flat as possible at equal settings of the tone controls. Because each network introduces a loss of about 1.72 (times), IC1.D and IC1.C first amplify the signal. The gain is set at about 8 (times) allowing input signal levels up to 1 V to pass the circuit at maximum gain and distortion-free. The gain also compensates the attenuation if you prefer to keep the tone controls at the

mid positions for a straight response. To audio fans, the circuit is rewarding to experiment with, especially in respect of the crossover point of the two networks. R3 and R4 determine the control range,

which may be increased (within limits) by using lower resistor values here. The values shown ensure a tone control range of about 20 dB. IC1.B buffers the summed signal across



COMPONENTS LIST

Resistors
 R1-R4 = 10kΩ
 R5,R7 = 1kΩ
 R6 = 7kΩ15
 R8 = 6kΩ80
 R9,R10,R11 = 8kΩ2
 R12,R13,R14 = 2kΩ2
 R15 = 1MΩ
 R16 = 100Ω
 R17 = 100kΩ
 P1,P2 = 100kΩ preset or chassis-mount control potentiometer, linear law

Capacitors
 C1,C2,C3 = 47nF MKT, lead pitch 5mm
 C4 = 68nF MKT, lead pitch 5mm
 C5,C6,C7 = 10nF MKT, lead pitch 5mm
 C8,C10,C11 = 100nF MKT, lead pitch 5mm
 C9 = 2µF2 MKT, lead pitch 5mm or 7.5mm

Semiconductors
 IC1 = TL074

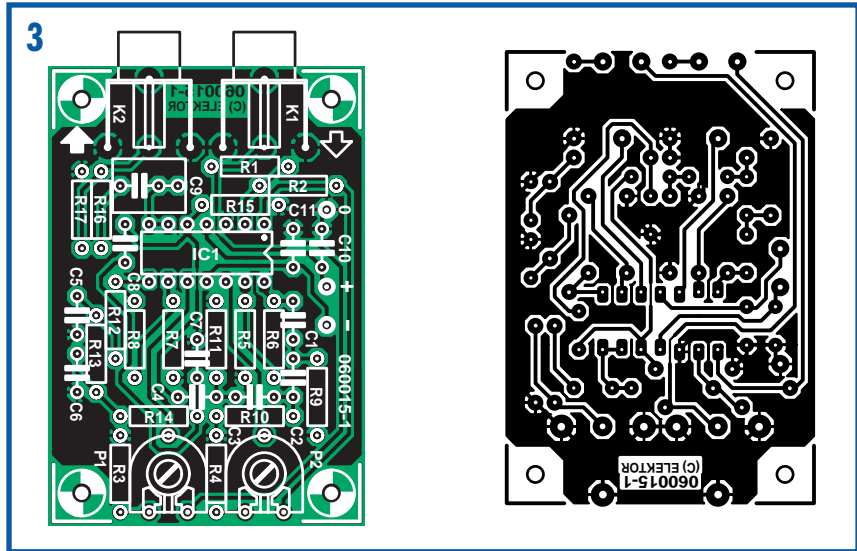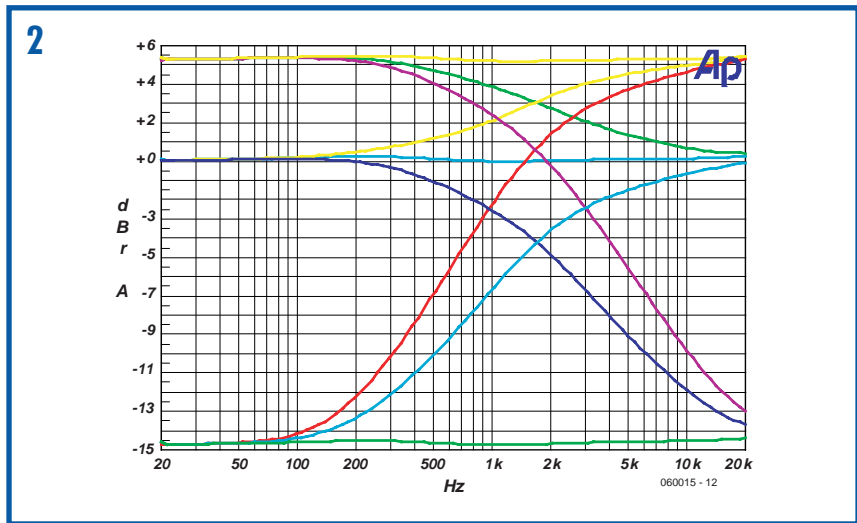Miscellaneous
 K1,K2 = line socket, PCB mount, e.g. T-709G (Monacor/Monarch)
 PCB, ref. 060015-1 from The PCBShop



R15. C9 removes any DC-offset voltage and R16 protects the output buffer from the effects of too high capacitive loads. R17, finally, keeps the output at 0 V. The choice of the quad opamp is relatively uncritical. Here the unassuming TL074 is used but you may even apply rail to rail opamps as long as they are

stable at unity gain. Also, watch the supply voltage range. The graph in **Figure 2** (produced by our Audio Precision analyser) shows nine response curves obtained by setting the two tone controls to minimum, mid position and maximum. Note that 0 dB is relative to the mid position of the pots!

A simple circuit board was designed for the project (**Figure 3**). Linear-law potentiometers may be fitted directly onto the board. Two boards are required for a stereo application. The relevant connections on the boards are then wired to a stereo control potentiometer.