

# Use off-the-shelf linear ICs for sophisticated audio designs


*With a little creativity and a good understanding of common linear circuits, you can produce high-performance audio designs—such as V/F converters, VCAs, preamps and panning circuits—with simple, inexpensive parts.*

**Jim Williams**, National Semiconductor Corp

Op amps can serve in applications other than audio amplifiers; you can apply them and other off-the-shelf linear ICs to create more sophisticated audio and electronic-music circuits. And although these applications present stringent performance demands, don't assume you'll need excessively complicated and expen-

sive designs; the linear circuits described here achieve high performance at low cost.

As an example of the unusual use of conventional components, consider **Fig 1's** exponential V/F converter. Suitable for use in music synthesizers, this circuit provides an output that changes its frequency one octave in response to a 1V control-input variation. Similar to conventional nonlinear converters, it exploits

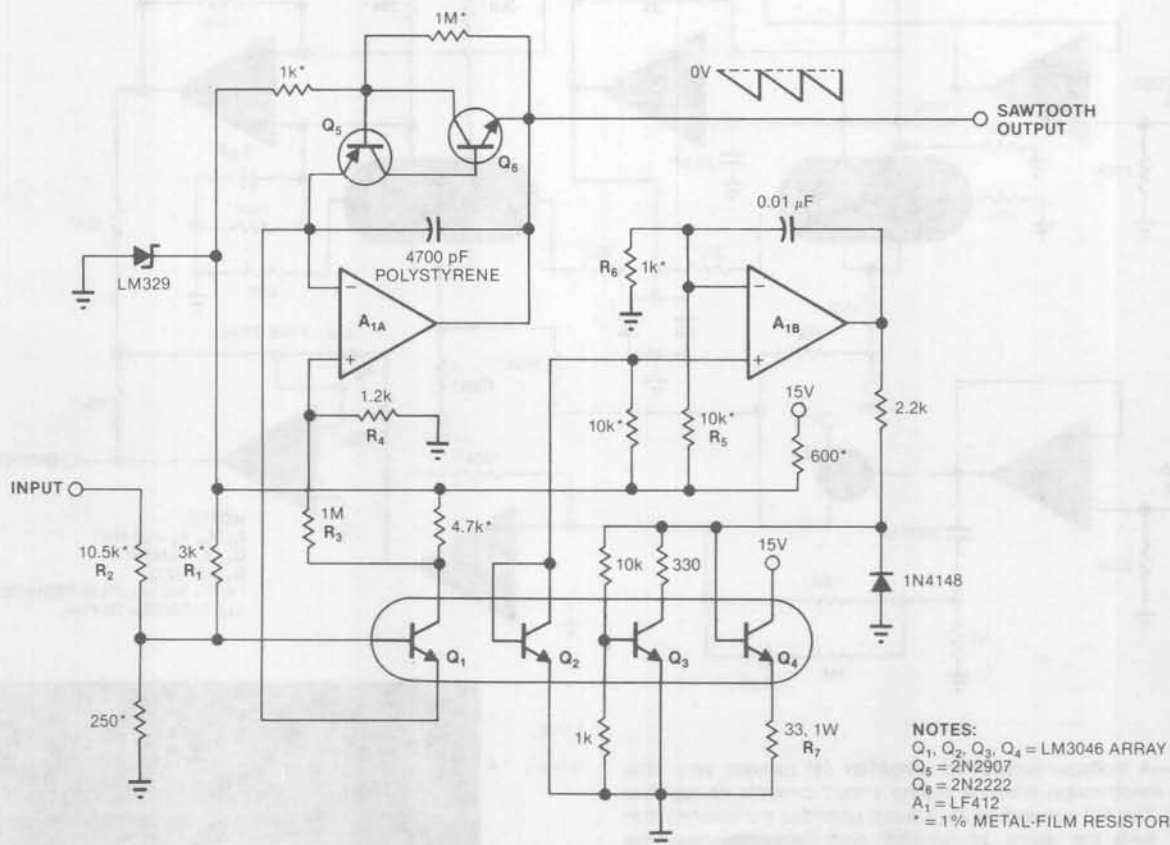

**Fig 1**—A temperature-compensated transistor array stabilizes this exponential voltage-to-frequency converter. Q<sub>2</sub> senses the array's temperature and A<sub>1B</sub> drives chip heater Q<sub>4</sub>, maintaining a stable operating environment for logarithmic converter Q<sub>1</sub>. The circuit's negative-going sawtooth output results from A<sub>1</sub>'s integration of Q<sub>1</sub>'s collector current until it reaches Q<sub>5</sub> and Q<sub>6</sub>'s threshold.

## A servo loop eliminates temperature-dependent drift

the logarithmic relationship between a transistor's base-emitter voltage and collector current. However, a unique thermal servo loop eliminates temperature-dependent transfer-function errors.

Generating the circuit's negative-going sawtooth output, op amp  $A_{1A}$  integrates  $Q_1$ 's collector current until  $Q_5$  and  $Q_6$  turn on. These feedback transistors then discharge the integrating capacitor, the output rises to 0V and the cycle repeats.

$Q_1$  is a vital element in this circuit because its  $V_{BE}/I_C$  characteristics ensure that  $A_{1A}$ 's input current—and thus the output frequency—remain an exponential function of the control voltage. Assisting  $Q_1$ , transistors  $Q_2$ ,  $Q_3$ ,  $Q_4$  and op amp  $A_{1B}$  form a temperature-controlled loop that stabilizes  $Q_1$ 's operating point by thermally compensating the LM3046 transistor array.

To perform this compensation,  $Q_2$ 's base-emitter junction senses array temperature, and  $Q_4$  heats the


chip.  $A_{1B}$  varies this heater transistor's dissipation until  $Q_2$ 's  $V_{BE}$  drop equals the reference level set by  $R_5$  and  $R_6$ . Furthermore,  $Q_3$  and  $R_7$  limit  $Q_4$ 's maximum operating power and ensure proper servo functioning during circuit power-up.

In addition to stabilizing  $Q_1$ 's collector bias, the LM329 6.9V reference also fixes the  $Q_5/Q_6$  firing point. These two transistors exhibit opposing temperature coefficients, so their switching threshold is compensated to approximately 100 ppm/°C. The polystyrene integrating capacitor's -120-ppm/°C TC cancels remaining firing-level uncertainty.


To establish a 20-Hz quiescent output frequency,  $R_1$  biases the circuit's input.  $R_2$  trims the converter's transfer gain. Op-amp input resistors  $R_3$  and  $R_4$  maintain exponential conformity to within 0.5% from 20 Hz to 15 kHz by providing first-order compensation for  $Q_1$ 's bulk emitter resistance.

## Reduce VCA feedthrough


The next circuit, a voltage-controlled amplifier (VCA), also uses a simple error-correction scheme to improve its performance (Fig 2). Commonly employed

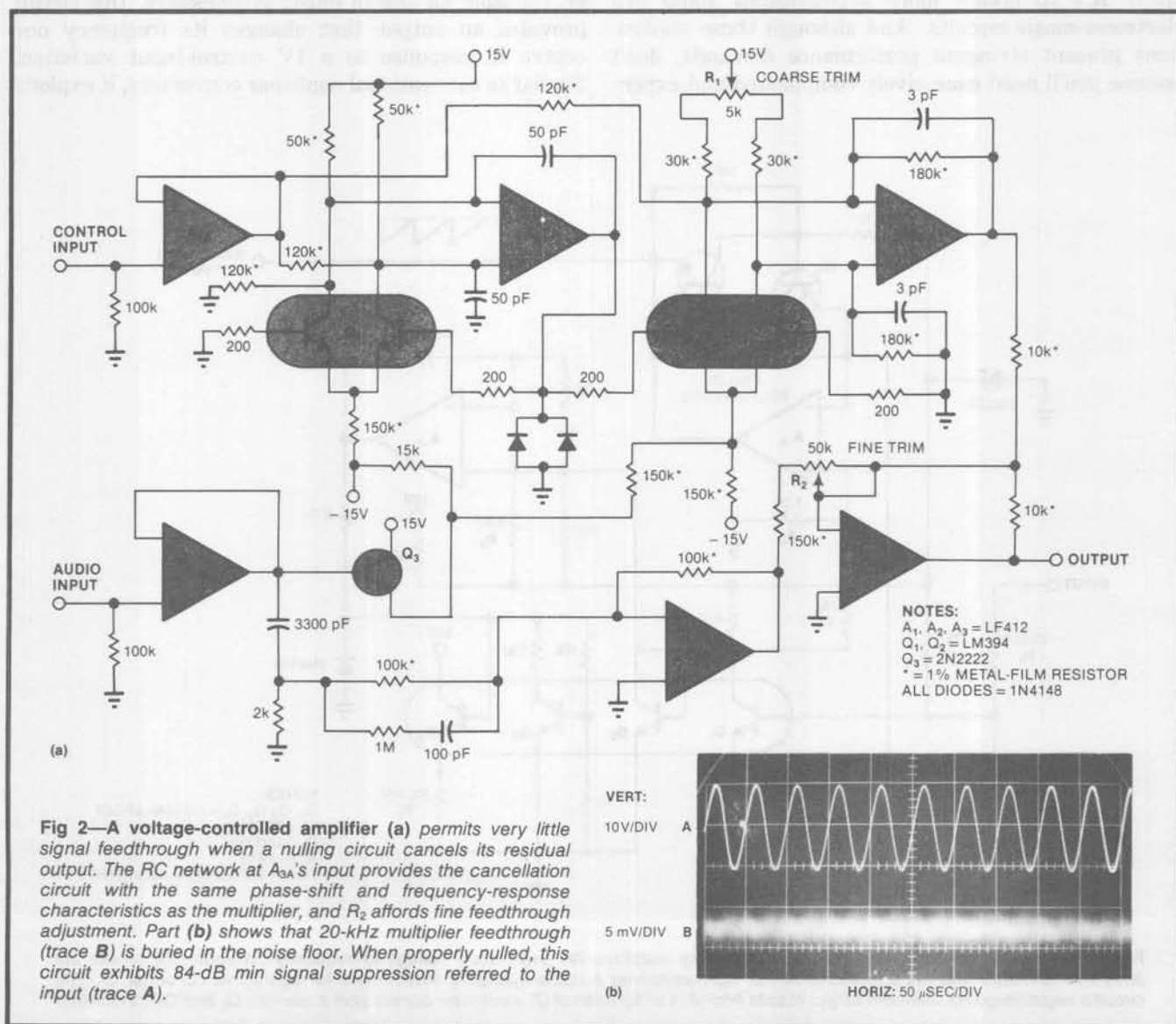

**Fig 2—A voltage-controlled amplifier (a) permits very little signal feedthrough when a nulling circuit cancels its residual output. The RC network at  $A_{3A}$ 's input provides the cancellation circuit with the same phase-shift and frequency-response characteristics as the multiplier, and  $R_2$  affords fine feedthrough adjustment. Part (b) shows that 20-kHz multiplier feedthrough (trace B) is buried in the noise floor. When properly nulled, this circuit exhibits 84-dB min signal suppression referred to the input (trace A).**

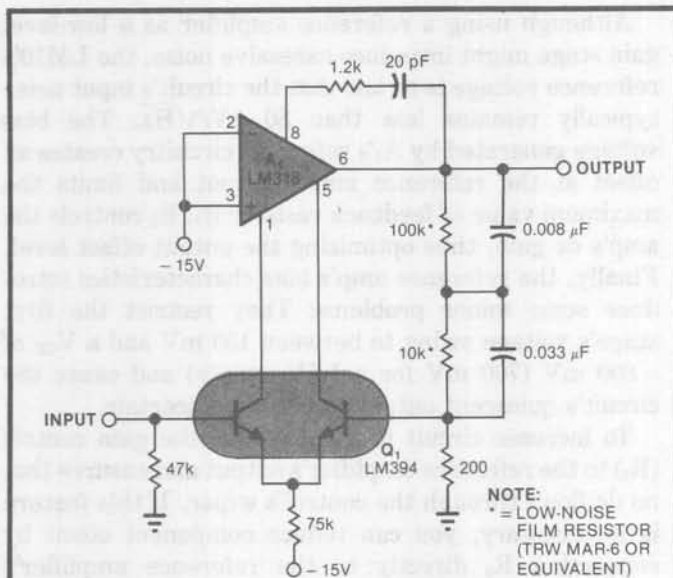

**Fig 3**—Lower input noise results when an external transistor pair replaces the first stage of an op amp. This design avoids the loop-instability problems often caused by adding external stages to an op amp because the additional transistors replace rather than complement the LM318's input devices.

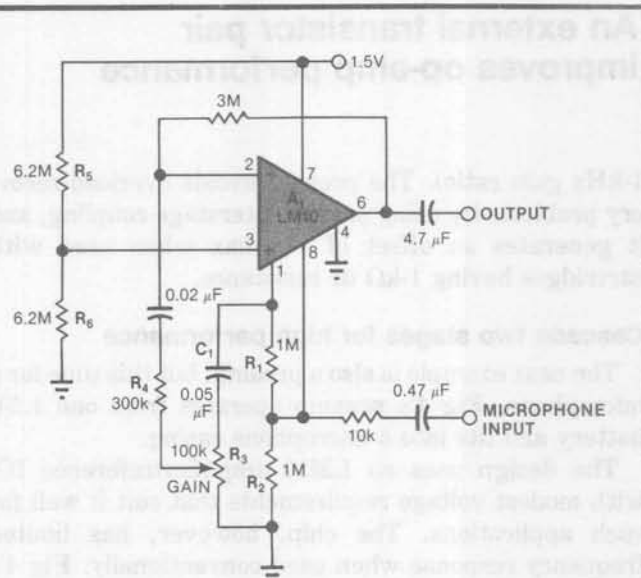

**Fig 4**—This microphone preamp operates from supplies as low as 1.5V. Its LM10 reference amplifier provides a voltage gain of 100 with an input noise level of less than 50 nV/√Hz. The chip's op-amp section amplifies the reference output by an additional 20 dB.

in recording-studio mixing consoles, VCAs must permit minimal signal feedthrough when their control inputs reach 0V. Conventional analog multipliers aren't optimal for this application; although they behave well in high-gain regions, they afford inadequate high-frequency signal suppression with their control channels off.

To reduce the feedthrough levels of its simple VCA, **Fig 2a**'s design uses a nulling technique. Op amps  $A_{1A}$  and  $A_{1B}$  and emitter-follower  $Q_3$  buffer the circuit's control and audio inputs and then feed these signals to a transconductance multiplier composed of  $A_{2A}$ ,  $Q_1$  and  $Q_2$ .  $A_{2B}$  converts  $Q_2$ 's differential collector currents to a single-ended audio output.  $R_1$  allows coarse feedthrough trimming at 10 kHz to approximately -65 dB (relative to the input signal level).

To further reduce feedthrough,  $A_{3A}$  and  $A_{3B}$  null the multiplier's OFF-state output with the audio input. The RC network at inverter  $A_{3A}$ 's input provides phase shift and frequency response similar to the multiplier's feedthrough characteristics—thus, residual signals cancel out when  $A_{3B}$  combines the outputs from  $A_{3A}$  and  $A_{2B}$ . The nulling circuit's gain control,  $R_2$ , allows fine feedthrough trimming to -84 dB at 20 kHz.

To adjust this VCA, apply a 20V p-p, 20-kHz sine wave to the audio input, and with the control input grounded, adjust  $R_1$  for minimum output from  $A_{2B}$ . Then trim  $R_2$  for the lowest level at  $A_6$ 's output. **Fig 2b** illustrates the circuit's typical feedthrough signal (trace **B**) for a 20-kHz input (trace **A**) when properly trimmed. Note that circuit noise almost obscures the waveform.

In addition to its excellent feedthrough suppression, this VCA exhibits only 0.05% total harmonic distortion (THD) throughout its 60-kHz power bandwidth. To obtain best circuit performance, construct it on a rigid

circuit board, enclose it in a well-shielded box and employ proper grounding and noise reduction.

### Replace an op amp's inputs

Instead of correcting a circuit's inherent errors as in the previous designs, you can use your knowledge of an IC's internal workings to eliminate deficiencies before they occur. For example, **Fig 3** illustrates an RIAA-equalized phono preamp with a noise figure less than 2 dB typ; it uses an LM394 ultralow-noise transistor pair at an LM318's compensation inputs instead of the device's internal input transistors.

This technique achieves lower noise than the unaltered op amp without introducing loop instability. Stability criteria become especially critical in RIAA circuits because the equalization function requires 100% feedback at high frequencies. Connecting the op amp's unused inputs to the negative supply shuts off the device's first differential pair and allows the external devices to operate into the LM318's output stages.

The distortion performance of **Fig 3**'s circuit exceeds the measurement capability of most test equipment: THD within the audio band remains less than 0.002% for outputs to 0.1V rms, and 20-kHz distortion rises only to 0.007% at 5V rms. Referred to a 10-mV input, the preamp's noise level equals -90 dB, with absolute values measuring 0.55  $\mu$ V and 70 pA rms over a 20-kHz bandwidth—levels below the noise generated by most phono cartridges.

**Fig 3**'s phono preamp also performs well in transient-intermodulation (TIM) tests. When fed with a 200-mV input—consisting of 10- and 11-kHz sine waves equally mixed—the circuit generates a 1-kHz output of only 80  $\mu$ V. The TIM level, therefore, is 0.004% (or 0.0008% if you include the RIAA function's 14-dB (5:1) 10- to

## An external transistor pair improves op-amp performance

1-kHz gain ratio). The preamp avoids overload-recovery problems by using only dc interstage coupling, and it generates an offset of 1V max when used with cartridges having 1-k $\Omega$  dc resistance.

### Cascade two stages for high performance

The next example is also a preamp, but this time for a microphone. Fig 4's preamp operates from one 1.5V battery and fits into a microphone casing.

The design uses an LM10 amplifier/reference IC, with modest voltage requirements that suit it well for such applications. The chip, however, has limited frequency response when used conventionally. Fig 4's circuit extends the device's operating range by cascading its reference amplifier and op amp to form a high-gain preamp.

Here are the details. The microphone input drives A<sub>1</sub>'s reference amplifier, which has a unity-gain bandwidth of 500 kHz. Feedback around this stage yields an ac voltage gain of 100. The op amp, which operates more slowly than the reference amp, provides an additional 20 dB of voltage amplification, resulting in overall circuit gain of 60 dB. The preamp's bandwidth extends to 10 kHz unloaded and reaches 5 kHz with a 500 $\Omega$  load.

Although using a reference amplifier as a low-level gain stage might introduce excessive noise, the LM10's reference voltage is so low that the circuit's input noise typically remains less than 50 nV/ $\sqrt{\text{Hz}}$ . The bias voltage generated by A<sub>1</sub>'s reference circuitry creates an offset at the reference amp's output and limits the maximum value of feedback resistor R<sub>1</sub>. R<sub>2</sub> controls the amp's dc gain, thus optimizing the output offset level. Finally, the reference amp's bias characteristics introduce some minor problems: They restrict the first stage's voltage swing to between 150 mV and a V<sub>CC</sub> of -800 mV (700 mV for a 1.5V supply) and cause the circuit's quiescent output to become uncertain.

To increase circuit life, C<sub>1</sub> couples the gain control (R<sub>3</sub>) to the reference amplifier's output and ensures that no dc flows through the control's wiper. If this feature is unnecessary, you can reduce component count by connecting R<sub>4</sub> directly to the reference amplifier's output (A<sub>1</sub>, pin 1) and using R<sub>1</sub> as a gain control. However, the 70-nA bias current that normally flows through the feedback resistor might increase noise.

### DAC pans audio signal

Another approach to solving audio-design problems involves multiplying DACs. Fig 5 shows a digitally programmable panning circuit that splits an input between two output channels. The DAC input code (D) determines the relative levels of the two channels, and op amps A<sub>1A</sub> and A<sub>1B</sub> convert the DAC's complementary current outputs into voltages. The relationship of the



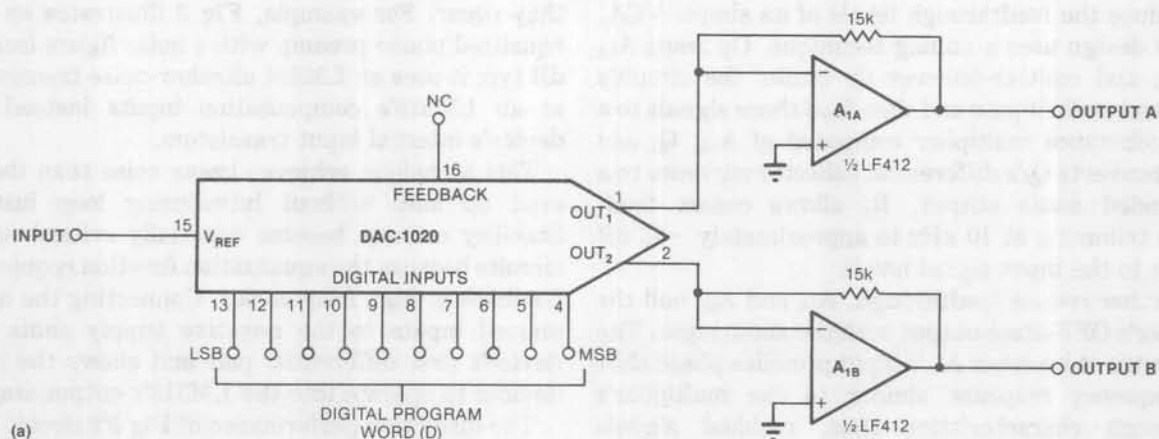


Fig 5—A DAC controls the ratio of two output signals in the pan-pot circuit shown in (a). Op amps A<sub>1A</sub> and A<sub>1B</sub> convert the DAC's complementary output currents to voltage signals. The ratio of the pan pot's outputs (b) changes as a digital ramp drives the DAC input. The sum of the two signals remains constant, regardless of the digital control word.

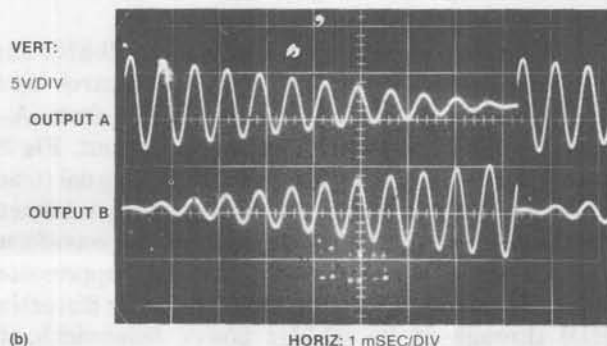

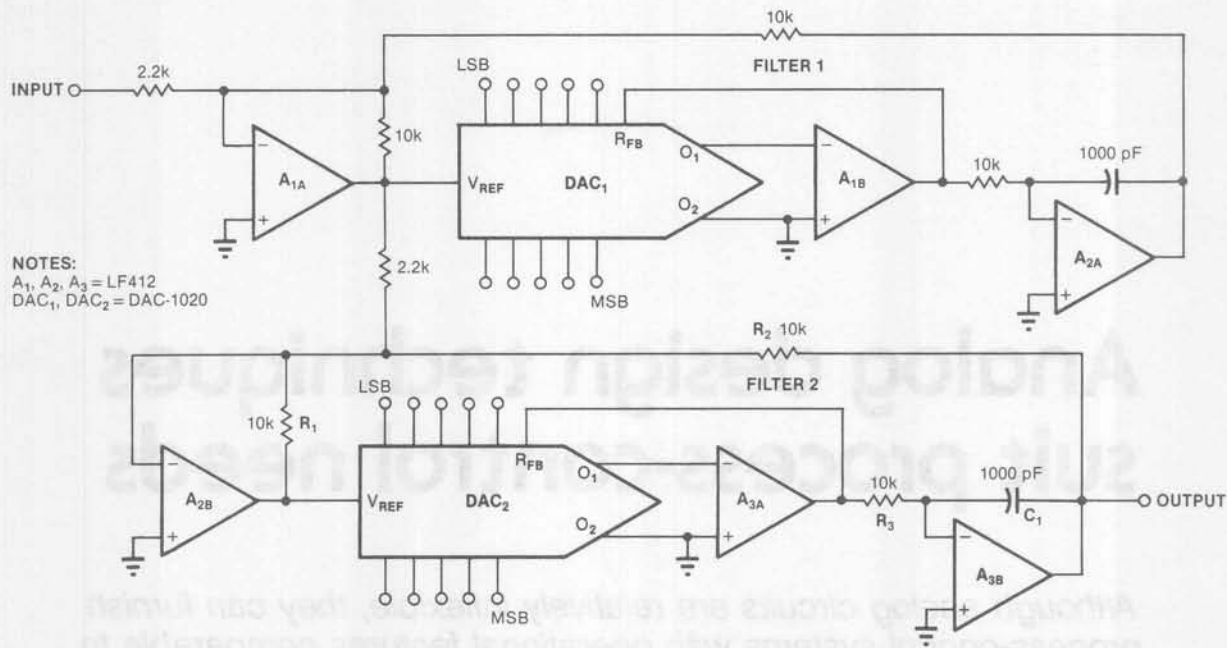

NOTES:  
 A<sub>1</sub>, A<sub>2</sub>, A<sub>3</sub> = LF412  
 DAC<sub>1</sub>, DAC<sub>2</sub> = DAC-1020

Fig 6—Two DACs control the passband of this first-order filter. The input codes determine the gains of integrators A<sub>2A</sub> and A<sub>3B</sub>.

two output signals to the digital input in Fig 5's design is given by:

$$\text{OUTPUT A} = - \left[ \text{INPUT} \times \left( \frac{3D}{2048} \right) \right],$$

$$\text{OUTPUT B} = - \left[ \text{INPUT} \times \frac{3(1024 - D)}{2048} \right]$$

and Fig 5b illustrates the circuit's operation when a digital ramp controls the DAC inputs.

This circuit differs from conventional DAC applications because the converter's internal feedback resistor remains unconnected; the circuit's discrete resistors permit better matching of the output channels. Each op amp exhibits 300-ppm/°C gain drift arising from mismatches between the DAC's ladder resistors and op-amp feedback elements. You can eliminate these small errors, though, by using a separate DAC, with complementary digital inputs, for each channel.

You can also employ DACs in programmable-audio-filter designs. Fig 6's circuit, a first-order bandpass network, utilizes two identical state-variable filters. The DACs control the gains of integrators A<sub>2A</sub> and A<sub>3B</sub> and thus determine the filters' cutoff frequencies.

You achieve a bandpass characteristic by connecting the first filter's high-pass output (taken from the output of A<sub>1A</sub>) to the second filter's input. Filter 2's low-pass output then contains only those signals that lie within the passband established by the DACs' input codes.

You can determine filter 2's low-pass cutoff frequency (f<sub>c</sub>) as a function of DAC<sub>2</sub>'s program input (D) with

$$f_c = \frac{R_1}{R_2} \left[ \frac{D}{2048 \pi R_3 C_1} \right].$$

For Fig 6's components,

$$f_c = \frac{D}{2048 \pi (10k)(1 \times 10^{-9})}.$$

Filter 1's high-pass output function equals the derivative of the low-pass expression (reference). **EDN**

### Reference

Analog Devices Inc, *Application Guide to CMOS Multiplying D/A Converters*, 1978, pg 32.

### Author's biography

**Jim Williams**, applications manager of National Semiconductor's Linear Applications Group (Santa Clara, CA), specializes in instrument development and analog circuit design. Before joining National, he served as a consultant at Arthur D Little Inc and ran the Instrumentation Development Lab at the Massachusetts Institute of Technology. A former student of psychology at Wayne State University, Jim lists spare-time interests that include tennis, art and collecting antique scientific instruments.

