



Audio Time Delay Systems

CONCLUDED

Build a Digital Audio Delay Line

Computer-type RAM memory and both A/D and D/A converters are used in this second approach

BY JOHN NEVES, STEVE KOLUPAEV, AND DEBBIE DELAHANTY

IN the first two parts of this series, we described an audio delay system based on analog techniques using bucket-brigade devices as the principal active elements. This month we will concentrate on the use of digital techniques to achieve the same purpose.

The project described here uses A/D (analog-to-digital) and D/A (digital-to-analog) converters, random access memory (RAM), and a time base that provides the necessary synchronization for the digital system as well as determining the length of the delay.

Overall Operation. As shown in Fig. 1, the audio input is fed to a filter and amplifier combination that attenuates frequencies above 10 kHz (to prevent aliasing problems) and scales the signal level for the A/D converter.

An 8-bit A/D converter performs a companding conversion that increases the digital signal resolution to an equivalent 11 bits plus sign, giving a dynamic

range of approximately 70 dB. The converter operates under the control of synchronization pulses from the clock/controller. Digital information at the output of the A/D converter passes to a 4096 (4K in computer jargon) \times 8-bit RAM as a series of 8-bit "words." Timed by pulses from the clock/controller, the stream of digital words cycles through a desired number of memory locations, up to the maximum of 4096. At any point in the cycle, as an old sample is read from the data latch and passed to the D/A converter, a new sample is written into the memory.

The length of delay is determined by the number of memory locations through which each sample passes and the length of each sampling interval. (The number of locations traversed is set by the manual switches.) For example, if the sampling frequency is 25 kHz, one sampling interval is 1/25,000 second or 40 microseconds. Therefore, if all 4096 memory locations are used, the total de-

lay will be 4096×40 (μ s) or 163.84 milliseconds. A 20-kHz rate would give a delay of 204.8 milliseconds.

Setting the memory address counter to some number between 1 and 4096 by means of the thumbwheel switches allows the delay to be varied while holding the sampling rate constant. Since the sampling rate also determines system bandwidth, changing the delay in this fashion does not affect frequency response. The fact that digital data is not degraded as it passes through the RAM means that the noise and distortion content of the output signal is also independent of the delay.

After the user-selected storage period, the digital data is read out of the memory and temporarily stored in a latch circuit that holds the digital data steady for the following D/A converter. Upon receipt of an appropriate timing pulse, the latch passes the digital data to the D/A converter where it is converted back into analog form. This analog sig-

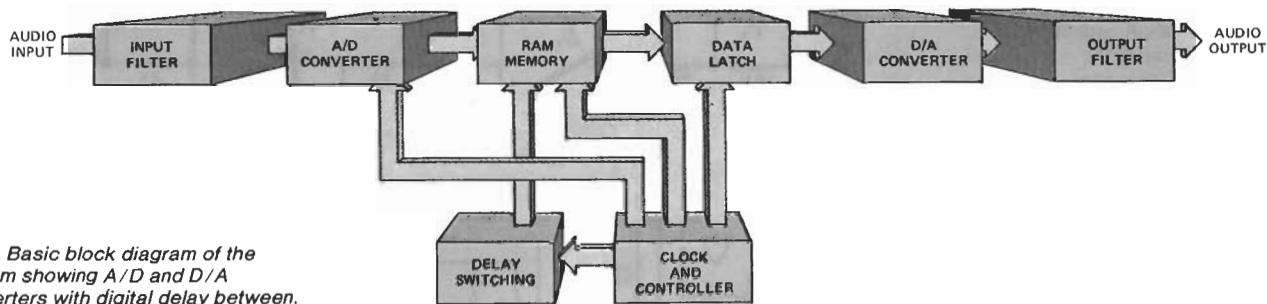


Fig. 1. Basic block diagram of the system showing A/D and D/A converters with digital delay between.

nal, now delayed, is filtered to remove any sampling components above 10 kHz that may be present. After filtering, the audio signal is amplified to bring it up to a level (about 1 volt) that can drive an audio amplifier.

Like the analog unit, the digital delay system is intended to be used with one or two auxiliary power amplifiers and loudspeakers. Ideally, there should be two delay units, one per channel. The signal should be delivered to your listening area at a level about 10 dB below that of the undelayed sound. For reasons detailed in Part 2, less expensive speakers and amplifiers can be used for the delayed sound channels.

To further economize, a single amplifier, speaker, and delay unit can be used. Audio from the two main channels can be resistively mixed and fed to a single delay unit as shown in Fig. 2.

The length of the delay produced by the unit can be adjusted in small increments to tailor it to the acoustics of your listening area. Start with about 20 milliseconds and experiment from there. Provision has been made to feed some of the output signal back to the input to generate reverberation. But if there is too much feedback, oscillation will occur.

Circuit Description. Due to its complexity, the circuit has been broken up into small, functional units. The individual circuits are interconnected by mating "letters-in-a-circle."

Input Filter and A/D Conversion. As shown in Fig. 3, IC1A and IC1B form a low-pass filter that amplifies all signals below 10 kHz. A comparator formed by IC1C monitors the amplified signal and turns on LED1 when the audio reaches the optimum four volts peak-to-peak.

The amplified signal from IC1B (pin 7) is passed to an A/D converter consisting of IC2A, IC18, IC22, IC24 and two of the gates in IC23. Timed by a "start conversion" pulse from the clock/controller, the incoming analog audio is converted into 8-bit binary code that is presented to the RAM for temporary storage. The converter performs a companding action, making the resolution of the digital signal equivalent to an 11-bit

word plus sign. Dynamic range is thus approximately 70 dB.

Memory and Latch. This circuit, shown in Fig. 4, uses eight conventional 4096 (bits) by 1 (bit) static RAMs (IC3 through IC10) arranged to form a 4096 (bits) \times 8 (bits) array. Static RAM is used to avoid the refresh cycles needed by dynamic RAM.

Each RAM element has its own unique address identified by the "An" (*n* stands for a digit) symbol above each RAM address line pin. Each RAM also has one pin (pin 8, R/W) that enables the RAM to accept data when the signal on this pin is in one logic state, and output the data when the pin is in the opposite logic state. Thus, under control of pulses from the clock/controller, the RAM can read in external data, or write out the data contained within its cells. The eight bits of data passed out of the RAM go to a pair of four-input data latches (IC11 and IC12) that hold the data in their internal flip-flops until a properly timed pulse from the clock/

controller causes it to pass to the D/A converter.

D/A Converter and Output Stages. The data from the RAM/latch circuit is applied to IC13, a D/A converter, as shown in Fig. 5. The reconstructed output signal from the D/A converter is almost identical to the filtered analog input, except that it is multiplied by a small scaling factor (due to amplification), contains a small amount of "quantization" noise caused by the D/A conversion, and, of course, is delayed.

After amplification in IC25A brings the signal up to about 1-volt peak-to-peak, the analog signal is passed through an active low-pass filter composed of IC25B and IC25C. The filter cuts off at 10 kHz, and attenuates any sampling frequency components that may remain in the signal. The output of IC25C is then used to drive the external audio amplifier.

Clock and Controller. The system clock, implemented by IC19 in Fig. 6, is the basic timing control for the system. Its main element is a vco (voltage-controlled oscillator) whose frequency is determined by the setting of R21. Varying the clock rate allows the user to experiment with effects such as vibrato, flanging, or frequency modulation. Keep in mind that the vco not only affects delay time but system bandwidth as well.

Counter IC17 accepts the clock signal and is configured to generate the four timed trigger pulses used by the A/D converter, RAM memory, and data latch. The four outputs are buffered by elements of IC20 and IC21 to convert the low-current CMOS outputs of IC17 into signals capable of driving TTL.

As shown in Fig. 6, the four timing pulses are identified as P1, P2, P3, and P4. Pulse P1 commands the start of an A/D conversion in IC18 (Fig. 3), while P2 increments (by 1) the memory address counter of Fig. 7. The resulting memory address points to the oldest stored sample. A new conversion will be completed eight clock pulses after P1.

The RAM is normally in the read mode, which means that the memory

(Figures 3 and 4 are on page 70.
Text continues on page 73.)

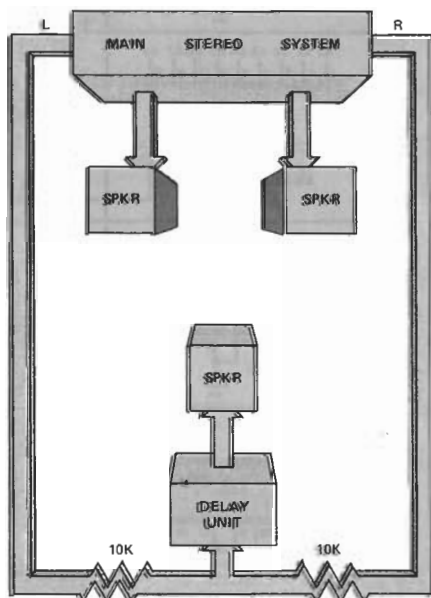


Fig. 2. Audio signals from the two main channels are mixed in resistors and applied to delay unit and a single speaker. Delay is adjusted to suit acoustics.

PARTS LIST

- C1,C4,—0.005- μ F capacitor
- C2—220-pF capacitor
- C13—470-pF capacitor
- C5—10- μ F, 16-V electrolytic
- C6,C7,C19—0.1- μ F ceramic capacitor
- C8 through C11,C16 through C18—1- μ F, Mylar, tantalum, or electrolytic
- C12—0.033- μ F disc capacitor
- C3,C14—0.001- μ F, Mylar or ceramic
- C15—330-pF ceramic capacitor
- C20—47-pF ceramic capacitor
- C21,C22—5000- μ F, 20-V electrolytic
- D1—1N914 diode
- D2 through D5—1N4002 or similar diode
- IC1,IC25—LM324 quad op amp
- IC2—LM311N comparator
- IC3 through IC10—4K \times 1 static RAM, MM5257, T14044, EMM4044, IM7141, MCM2141, 4104, 2613, HM4315, HM4847, or similar
- IC11, IC12—7475, 74LS75, four-bit latch
- IC13,IC22—DAC-76, DAC-88 companding D/A converter (Precision Monolithics or American MicroDevices)
- IC14,IC15,IC16—74193, 74LS193 up-down synchronous 4-bit counter
- IC17—4017 CMOS decade counter
- IC18—DM2502 successive approximation register (National or American MicroDevices)
- IC19—4046 CMOS phase-locked loop
- IC20—4010 CMOS-TTL buffer
- IC21—74LS00 quad two-input NAND gate
- IC23—7486, 74LS86 quad exclusive-OR
- IC24—7474, 74LS74 D flip-flop
- IC26—320T-12, negative 12-volt regulator
- IC27—340T-12, positive 12-volt regulator
- IC28—340T-5, positive 5-volt regulator
- J1,J2—Phono connector
- LED1—Light emitting diode

The following are 1/4-watt, 5% resistors unless otherwise noted:

- R1—47 k Ω
- R2—18 k Ω
- R3—39 k Ω
- R4,R23,R28 through R39,R40,R41—10 k Ω
- R5—680 k Ω
- R6—3.3 k Ω
- R7,R10,R25—22 k Ω
- R8—820 Ω
- R9,R18,R20—4.7 k Ω
- R11,R24—51 k Ω
- R12,R13,R15,R16,R26,R27—2.7 k Ω
- R14—500 Ω potentiometer
- R17,R19—13 k Ω
- R21—10 k Ω potentiometer
- R22—2.2 k Ω
- R42—33 k Ω
- R43,R44,R45—100 k Ω potentiometer
- S1—Spst switch
- T1—24-V CT, 1-A (1.5-A for stereo)
- Misc.—Hex 2-digit thumbwheel switch (2) or 16-pin DIP switches, suitable enclosure (Mod-U-Box MBS 4-10-10 available from Intra Fab, 425 Queens Lane, San Jose, CA 95112 or similar), knobs, press-on type, mounting hardware, etc.

Note: The following are available from Videart, Box 10327, Stanford, CA 94305: etched and drilled pc board at \$18; DM2502 successive approximation register at \$6.80; DAC-88 converter at \$7.50; set of eight memory ICs at \$50. California residents please add 6.5% sales tax.

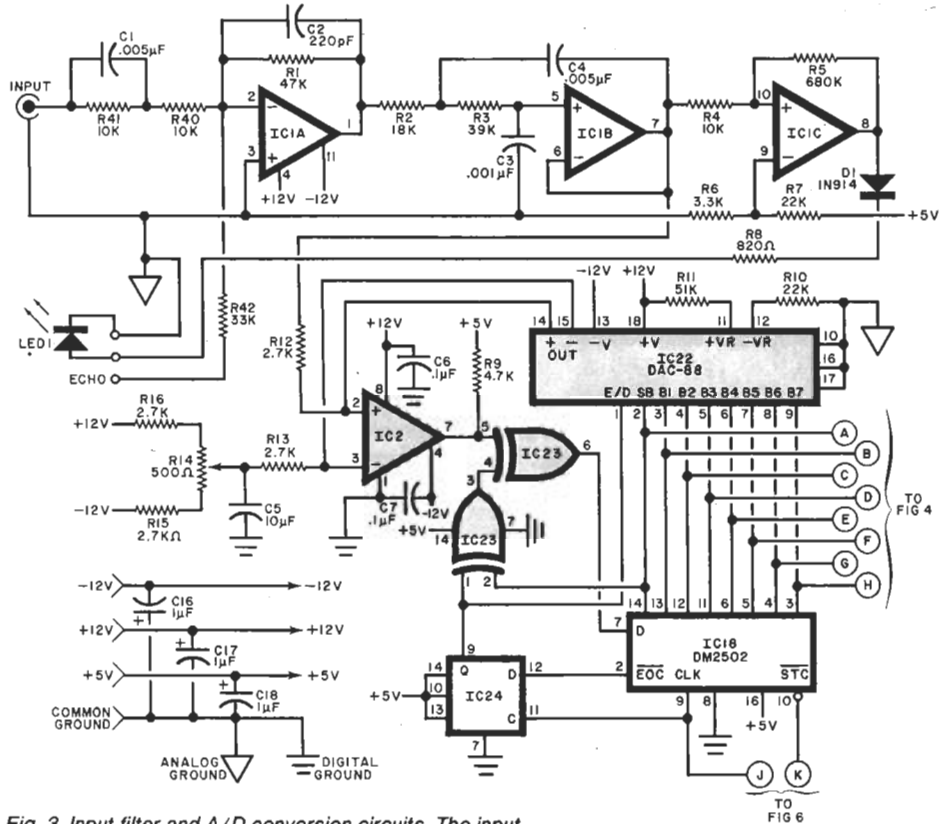


Fig. 3. Input filter and A/D conversion circuits. The input is filtered and amplified first and then converted to 8-bit binary code at the output to Fig. 4. A companding action makes the output equivalent to an 11-bit word plus sign.

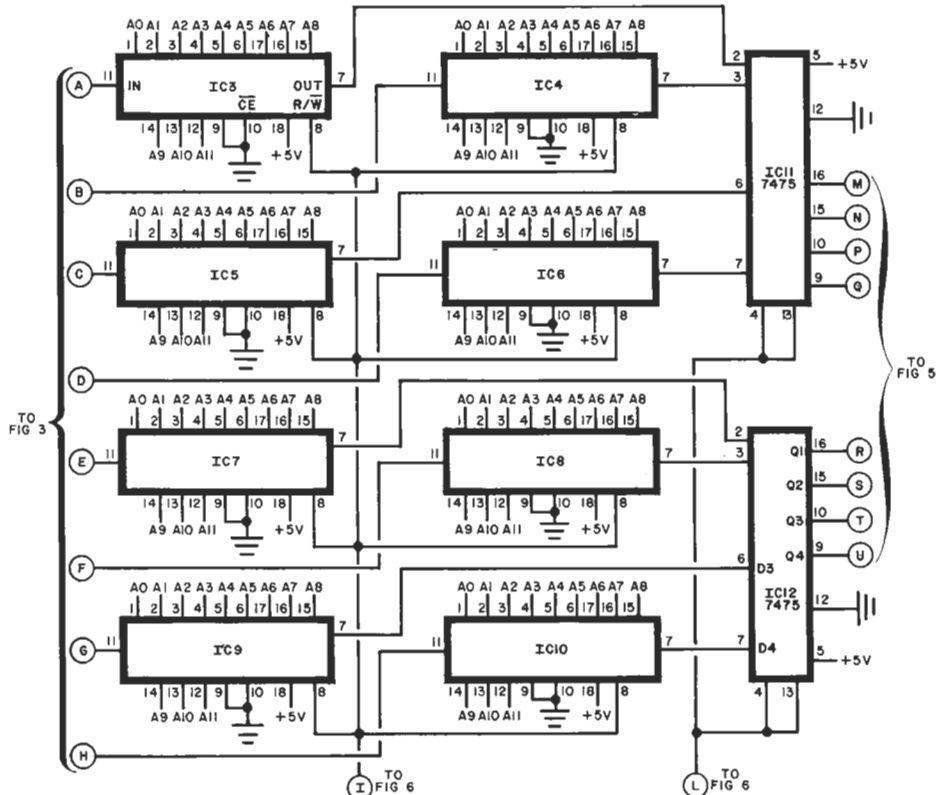


Fig. 4. Memory and latch circuits. Eight static RAM units (IC3 through IC10) are used to form a 4096 by 8 array. Each RAM can read in or write out data as determined by pulses from the clock/controller. Output is held in latches IC11 and IC12.

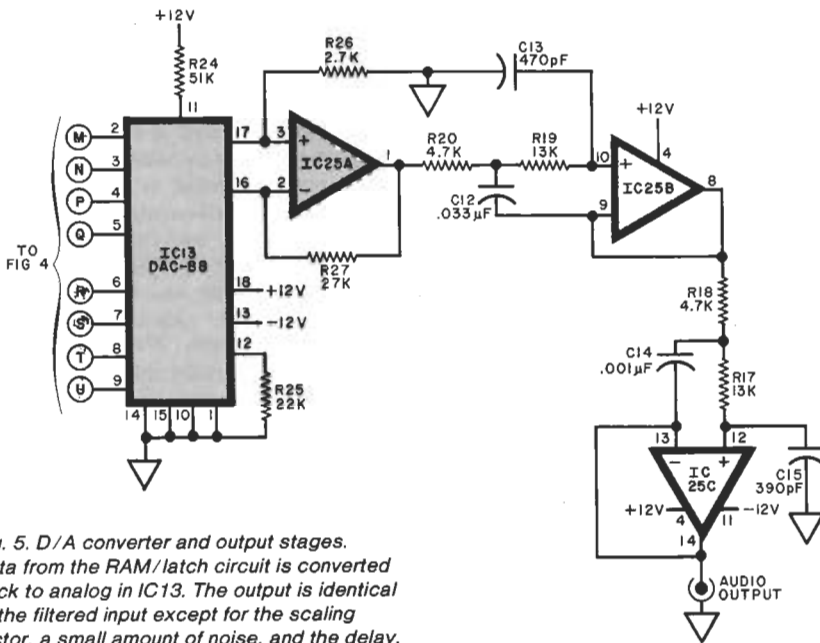


Fig. 5. D/A converter and output stages. Data from the RAM/latch circuit is converted back to analog in IC13. The output is identical to the filtered input except for the scaling factor, a small amount of noise, and the delay.

constantly displays the 8-bit code stored at the address pointed to by the memory address counter at its output. The third pulse, P3, is applied to the data latches (Fig. 4), causing them to load the result of the read operation and hold it stable for D/A conversion by IC13 (Fig. 5), which takes place in less than one microsecond. The last pulse, P4, causes a memory write operation that overwrites the old sample with the 8-bit code currently available at the A/D converter output.

Delay Switching. The delay switching uses three ICs to select the RAM memory addresses dialed in via the user-accessible switches as shown in Fig. 7.

Programmable counters IC14, IC15, and IC16 are cascaded with the clock input presented to IC16. Its "carry" output drives IC15, which in turn drives IC14. These counters can be preset to any desired modulo output by entering the control data on the input pins—in this case, voltage or ground from the user-selectable switches connected to S2 and S3. Thus, the outputs of each IC will agree with the manually preset count, independent of the clock frequency. Since there are 12 address lines, the count can reach a maximum of $2^{11} + 2^{10} + 2^9 \dots + 2^0 = 2^{12} - 1 = 4095$ and the delayed bits can pass through any desired number of memory locations.

Power Supply. The power supply, shown in Fig. 8, uses a full-wave rectifier in conjunction with -12, +12, and +5-volt regulators. The system draws 450 mA at +5 volts, and about 20 mA from each of the 12-volt supplies.

The 5-volt power requirement can be reduced by using "LS" or "C" versions of IC11, IC12, IC14, IC15 and IC16. Do not use "L" devices because these usually have different pinouts. Regulators IC27 and IC28 should be supplied with heat sinks.

Construction. Given the complexity of the circuit, construction is best implemented by using either Wire-Wrap Techniques or a printed circuit board. In the former case, care should be exercised concerning the ground connections. As shown in the schematics, the analog digital grounds should be isolated from each other and merge only at the power supply common point.

Due to their size, etching and drilling guides and component layout for a double-sided pc board for the project are not reproduced here, but can be obtained by sending a self-addressed 9-by-12 envelope with two units of first-class postage to Dept. DDL, Editorial, POPULAR ELECTRONICS, One Park Ave., New York, NY 10016.

Outputs of the address counters (IC14, IC15, and IC16) should be kept as short as possible and as far away as possible from the input and output op amps. The use of IC sockets is recommended, and the proper installation of polarized elements must be observed.

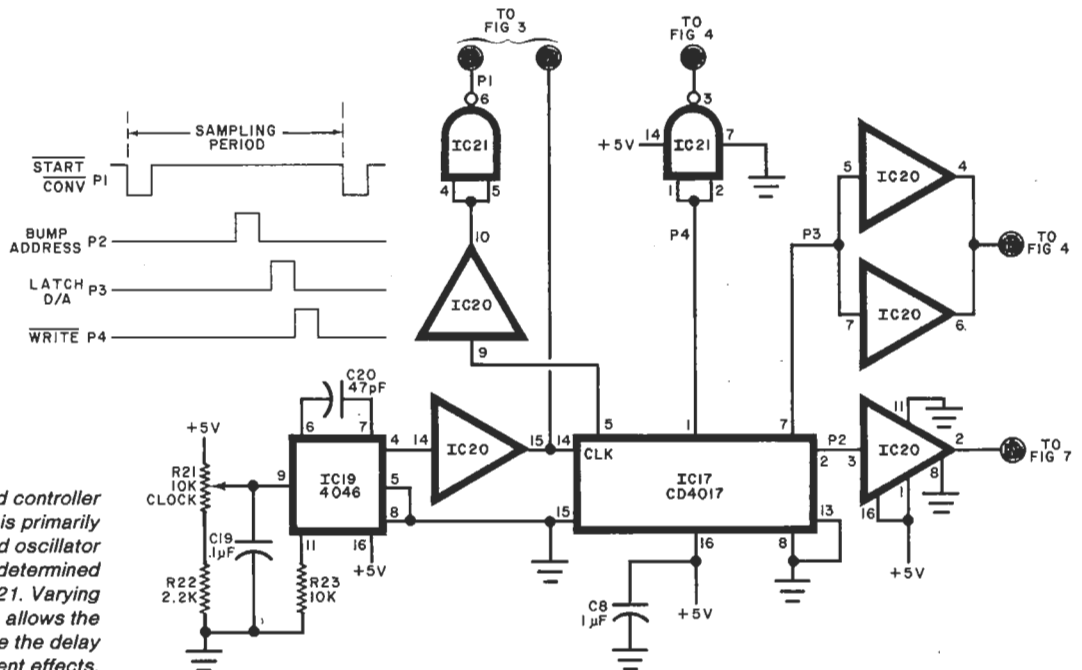


Fig. 6. Clock and controller circuits. This is primarily a voltage-controlled oscillator whose frequency is determined by the setting of R21. Varying the clock rate allows the user to change the delay and get different effects.

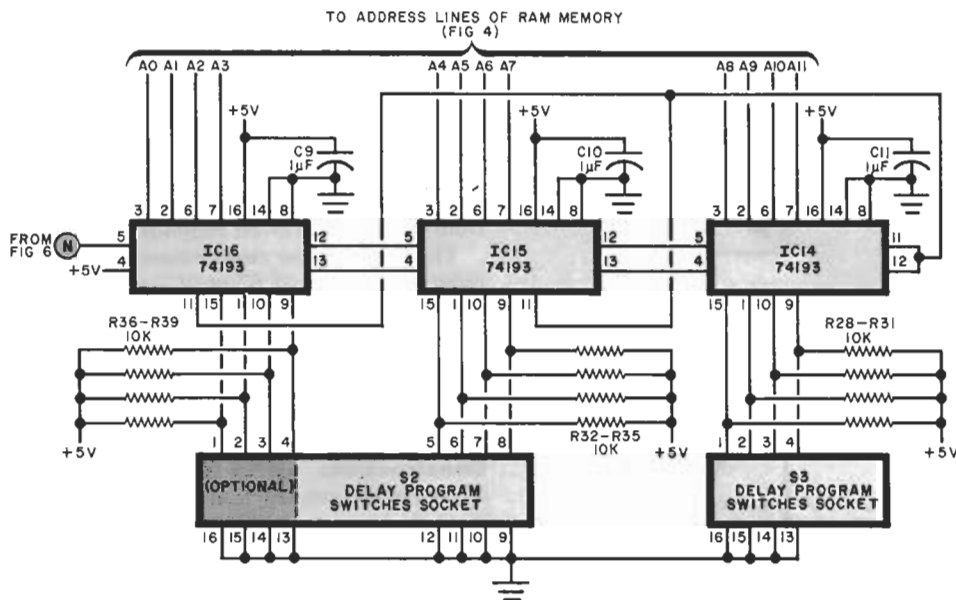


Fig. 7. Delay switching circuits. Three ICs are used to select the RAM memory addresses dialed in by the program switches S2 and S3.

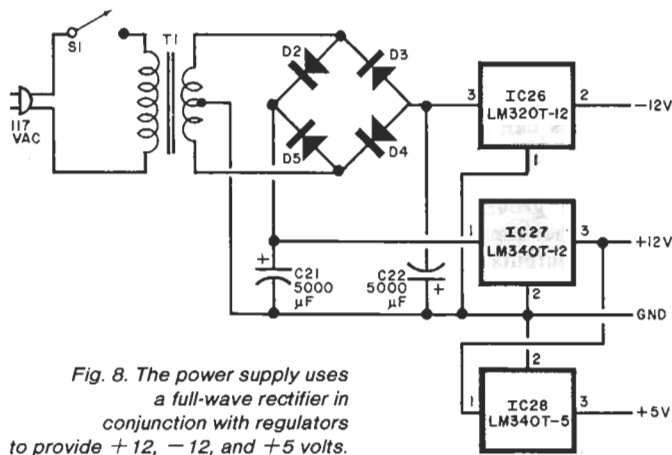


Fig. 8. The power supply uses a full-wave rectifier in conjunction with regulators to provide +12, -12, and +5 volts.

After the board is completed, it can be installed in a suitable metal enclosure and interconnected as shown in Fig. 9. Although this illustration shows a pair of thumbwheel switches used to select the delay, DIP switches, such as those used in computer boards, can be substituted. The input gain control, R43, output gain control, R44, reverb control, R45, audio connectors, J1 and J2, peak indicator, LED1, and the two delay-select switches can be mounted on the front panel. For stereo, dual potentiometers are used for R43 through R45, along with two sets of thumbwheel switches and two peak indicator LEDs.

Adjustment. With the delay unit connected to an audio system as shown in Fig. 2, set R14 and R21 to their center positions. Place the delay switches (S2 and S3) in the minimum configuration (all switches open). Then adjust echo (reverb) potentiometer R45 for its minimum resistance, and the audio input control (R43) to its center rotation position.


Apply a 1-kHz sine-wave signal to the audio input (J1), and an oscilloscope to the J2 audio output connector. With power turned on, adjust output control R44 for a convenient scope display.

Increase the audio input level, either by adjusting R43 or the audio signal generator's level control, until some clipping is noted on the output waveform. Successively adjust the input level and R14 to obtain a symmetrically clipped sine wave. Then reduce the input level to just below clipping, so that a clean sine wave is displayed.

Increase the sine-wave input frequency to 5 kHz and adjust R21 to minimize any serrated edges on the displayed waveform. Besides reducing noise, this adjustment also controls the sampling frequency (and bandwidth).

If an oscilloscope is not available, you can perform these adjustments by ear. Preset switches S2 and S3 for the desired amount of delay. Use a source of actual program material in place of the signal generator and your ears as "distortion monitors." Adjust the potentiometers for best audible performance. The results obtained by this method will, of course, be less accurate, but will be useful if care is taken in performing the adjustments.

 With proper audio input levels, a 4-volt peak-to-peak signal should be seen at pin 7 of IC1B (A/D converter input). If you should require more gain, the value of R1 (feedback resistor for IC1A) can be increased.



Front view of prototype showing input, output, and reverberation adjustments (see Fig. 9 on next page) and thumbwheel switches to determine delay for two channels.


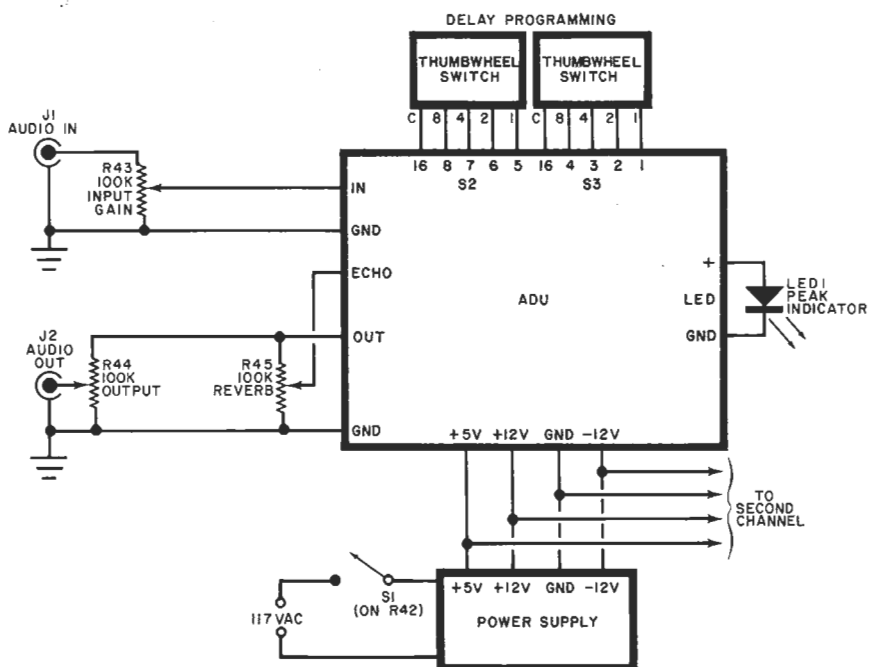


Fig. 9. Schematic of components that are not mounted on the printed circuit board. See photos below and on previous page for ways in which to locate the components.

The memory address counter (IC14, IC15, IC16) can be checked by setting S2 and S3 for maximum delay. This causes each of these IC's to count down by 16. An oscilloscope or frequency counter can then be connected to the A0 through A11 outputs of these ICs to note the decreasing frequencies.

A scope can also be used to follow the

 audio signal through to the A/D converter. The digital outputs of IC18 vary with the applied audio signal. If a dc voltage level from zero to about 1 volt is applied to the input, the bit changes can be observed as the input voltage level is changed. Zero volts will produce all zeroes and 1 volt will create all ones, with 254 binary states between the two. ♦



Internal view of prototype shows arrangement of board and components on front panel.

BUILDING THIS CIRCUIT
IS NOT RECOMMENDED

THE TECHNOLOGY IS TOO
OLD - MUCH BETTER IS
NOW AVAILABLE

THIS CIRCUIT IS PRESENTED
ONLY BECAUSE STUDY OF
IT CAN GIVE A PERSON
BETTER UNDERSTANDING
OF THE THEORY BEHIND
MODERN TECHNOLOGY