

4. CHUG- CHUG

The schematic diagram for this project is shown in Fig. 4. Op-amp IC1, a CA3240 dual MOSFET-input device (equivalent to two CA3140's), is used as a white-noise source. The white noise appears on pin 7 of IC1 as a current rather than a voltage signal. The noise is not converted to a voltage because of the low AC impedance around IC1. That low impedance makes the layout less critical than for other types of noise sources, and eliminates the need for shielding to prevent hum pickup.

Op-amp IC2 is used as a driver stage for the push-pull output stage formed


by Q5 and Q6. Negative feedback is taken from that output stage and brought back to pin 2 of IC2. Resistors R6 and R8 determine the minimum amount of negative feedback, and hence the maximum gain.

Transistors Q2, Q3, and Q4 form a variable-frequency multivibrator; resistor R11 is the SPEED control, and is used to control the multivibrator's frequency. The output from the multivibrator is differentiated by C8, and is then applied to modulator transistor Q1 through D1 and R7. Transistor Q1 modulates the gain of the output-amplifier

stage by changing the impedance to ground seen by R6 and C4. That creates chopped white-noise; there is also residual low-level noise from IC2 when Q1 is not conducting. When the multivibrator's frequency is reduced using R11, C8 discharges slowly, creating a sound similar to escaping steam from a stopped locomotive. As the multivibrator's frequency is increased, the toy generates a sound like an accelerating locomotive.

Construction details

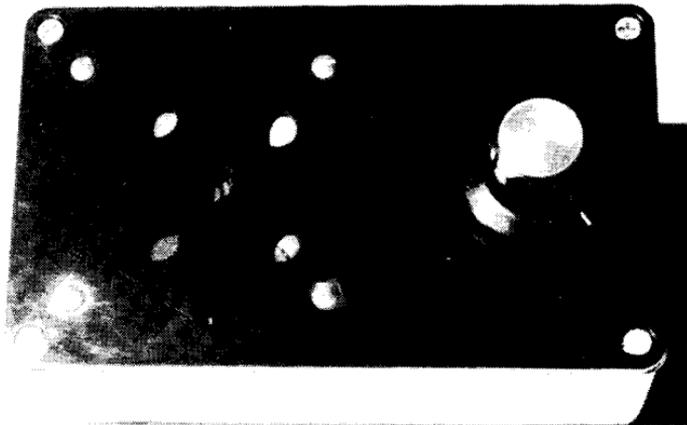The only thing to keep in mind when
continued on page 93



TOYS FOR THE HOLIDAYS

continued from page 54

laying-out the circuit is not to route the output of IC1 near the input to that IC. If possible, use a 100-mA current-limited power-supply in place of battery B2 while adjusting the circuit; doing that will protect transistors Q5 and Q6, and prevent draining the battery.

The first thing you'll need to do is to find the proper value for R3. Start by shorting Q1's collector to ground. Then, increase the value of R3 until the current drain from the power supply is less than 60 milliamperes. When that is done, remove the short from Q1.

To see if the device is operating properly, close switch S1 and reduce the resistance of R11. Wait 10 seconds, then rotate R11 slowly, and you should hear a sound similar to that of a steam locomotive picking up speed.

There you have it—four simple toys that any child would enjoy. We have built several of each and submitted them to some very tough "critics"—several children that we know! The results were very positive!

R-E

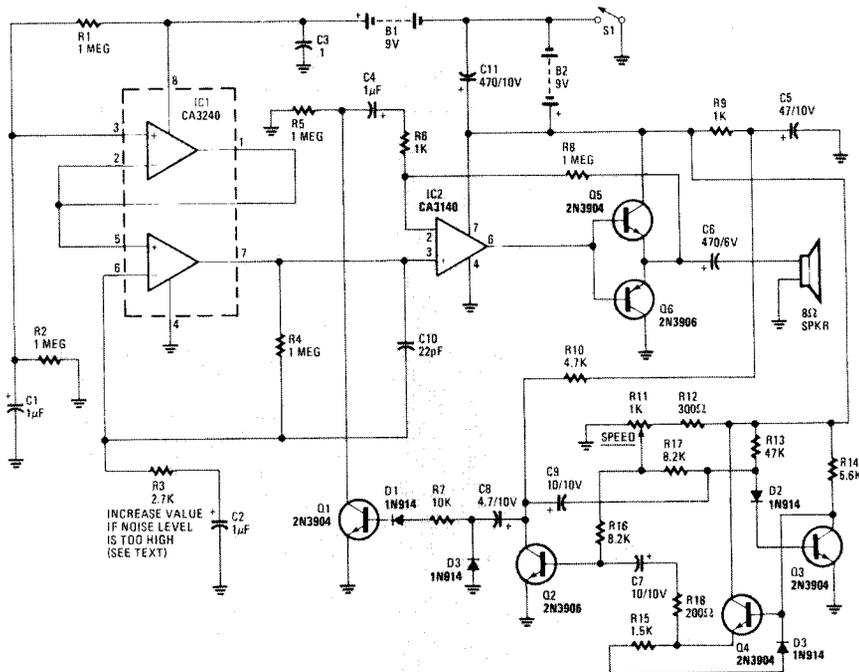


FIG. 4—THE CHUG-CHUG TOY simulates the sound of a steam locomotive. A dual MOSFET-input op-amp, IC1, is used as a white noise generator in this circuit.

PARTS LIST—CHUG-CHUG

Resistors, ¼ watt, 5%, unless otherwise noted

R1, R2, R5, R8—1 megohm
 R3—2700 ohms
 R6, R9—1000 ohms
 R7—10,000 ohms
 R10—4700 ohms
 R11—1000 ohms, potentiometer, linear taper
 R12—300 ohms
 R13—47,000 ohms
 R14—5600 ohms
 R15—1500 ohms

R16, R17—8200 ohms

R18—200 ohms

Capacitors

C1, C2, C4—1 μF, 10 volts or higher, electrolytic
 C3—0.1 μF, Mylar or ceramic disc
 C5—47 μF, 10 volts or higher, electrolytic
 C6—470 μF, 6 volts or higher, electrolytic
 C7, C9—10 μF, 10 volts or higher, electrolytic
 C8—4.7 μF, 10 volts or higher, electrolytic
 C10—22 pF, mica or ceramic disc
 C11—470 μF, 6 volts or higher, electrolytic

Semiconductors

D1—D3—1N914 or equivalent silicon diode
 IC1—CA3240 (RCA) or equivalent dual op-amp
 IC2—CA3140 (RCA) or equivalent op-amp
 Q1—Q5—2N3904, 2N2222, or equivalent NPN transistor
 Q6—2N3906 or equivalent PNP transistor
 B1, B2—9-volt battery, transistor-radio type
 S1—SPST switch
Miscellaneous: Wire, solder, miniature 8-ohm speaker, etc.