

# The Solid-State Bird

WHISTLES AND WARBLES LIKE A CANARY

BY JOHN S. SIMONTON, JR.

**I**F YOU LIKE the sweet, warbling song of a canary but don't dig that cage to be cleaned, try this electronic bird—a real solid-state, battery-operated singer. When turned on, the bird whistles down-scale for a few seconds, breaks into a warble, and, after several seconds, shuts off—only to start again automatically in a few more seconds.

The bird's circuit, shown schematically in Fig. 1, is deceptively simple in appearance. The most immediately obvious feature is an astable multivibrator made up of  $Q1$ ,  $Q2$ , and their associated base timing circuits. Not so obvious is the blocking oscillator whose principal components are  $Q2$ ,  $C2$ , and  $T2$ . The latter produces the warble.

When power is turned on, the bias circuits cause  $Q1$  to be turned on and  $Q2$  off. Capacitor  $C1$  is initially discharged; but, as it begins to charge up through  $R3$ ,

$Q2$  becomes forward biased by the current through  $T1$  and  $R4$ . Eventually, the point is reached where  $Q2$  acts as a blocking oscillator, and  $Q1$  follows it because of coupling through  $C5$ .

During this oscillation,  $C1$  is charged in a negative direction as a result of the half-wave rectification provided by  $Q2$  (which is reverse biased during negative half cycles). Since the charging current is heavy at first and tapers off as  $C1$  charges, the inductance of  $T1$  goes from a low value to a high one because of the decreasing core saturation. The output tone then decreases in pitch.

Capacitor  $C1$  goes rapidly negative with respect to ground, and its effect in the biasing of  $Q2$  is replaced by the action of the oscillator itself during the positive half cycles and the charging current through  $C4$  during the negative half cycles. Eventually,  $C4$  charges to the

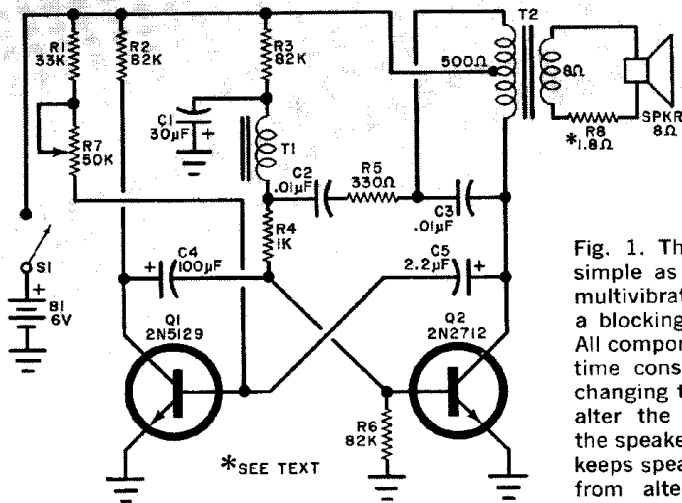


Fig. 1. The circuit is not as simple as it looks. Besides a multivibrator, there is also a blocking oscillator in there. All components are part of one time constant or another, so changing the value of one will alter the final sounds. Note the speaker damping (R8) that keeps speaker acoustic loading from altering the oscillator.


### PARTS LIST

B1—6-volt battery (4 AA cells in series)  
 C1—30- $\mu$ F, 6-volt electrolytic capacitor  
 C2, C3—0.01- $\mu$ F disc capacitor  
 C4—100- $\mu$ F, 6-volt electrolytic capacitor  
 C5—2.2- $\mu$ F, 6-volt electrolytic capacitor  
 Q1—2N5129 transistor  
 Q2—2N2712 transistor  
 R1—33,000-ohm,  $\frac{1}{2}$ -watt resistor  
 R2, R3, R6—82,000-ohm,  $\frac{1}{2}$ -watt resistor  
 R4—1000-ohm,  $\frac{1}{2}$ -watt resistor  
 R5—330-ohm,  $\frac{1}{2}$ -watt resistor  
 R7—50,000-ohm trimmer PC potentiometer

R8—1.8-ohm,  $\frac{1}{2}$ -watt resistor  
 S1—Spst slide or toggle switch  
 T1—10K:2K driver transformer (Lafayette TR-98, 99F61269 or similar)  
 T2—500-ohm CT:8-ohm output transformer (Lafayette TR-116, 99F61293 or similar)  
 Misc.—8-ohm speaker, plastic case, battery clips, wire solder, etc.  
 Note—The following are available from PAIA Electronics, PO Box 14359, Oklahoma City, OK 73114: etched and drilled PC board, \$1.25; complete kit less batteries and case, \$5.95; both postpaid in USA.

point where its contribution to the Q2 biasing is small and the base/emitter junction of Q2 is reverse biased during a larger portion of each succeeding cycle. At some point, the blocking oscillator starts to "squegg." That is, the charge ac-

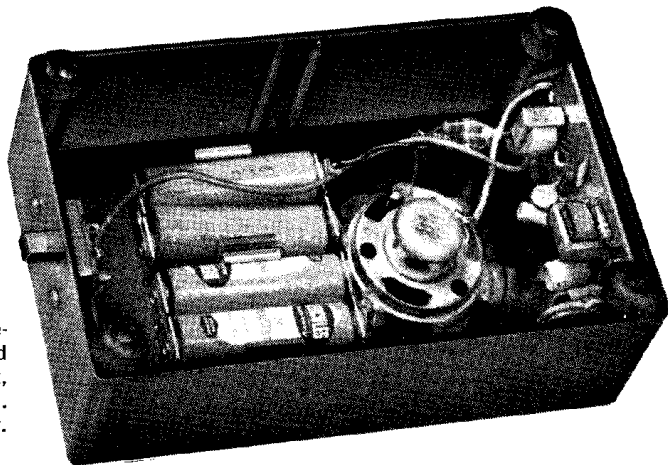cumulated on C2 during negative half cycles is large enough that Q2 is turned off completely until the charge leaks off. Once the charge has leaked off, Q2 can oscillate once more. This charge-discharge cycle happens so rapidly that the audio



In prototype mounting arrangement, the speaker is mounted at the "bottom" of the box, while the "top" is left open. The rubber feet fit in cover.


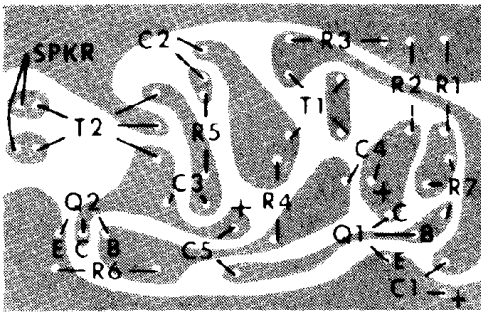


Fig. 2. Actual size foil pattern (right) and component installation (above). Note that miniature transformers must be used on this small PC board. It has been laid out so that it just fits in 6" x 3" x 2" plastic utility box.

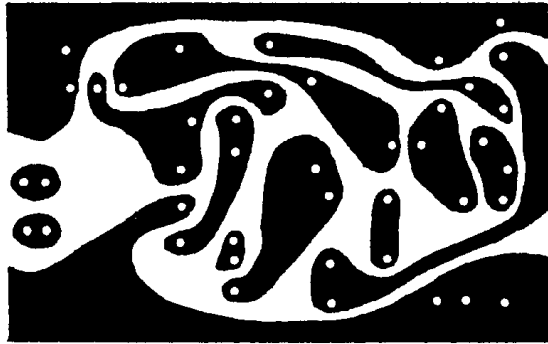

tone generated sounds like a warbling bird. Finally, C4 discharges to the point where it makes no contribution to the biasing of Q2 and the latter turns off. With Q2 off, Q1 turns on and the cycle repeats.

**Construction.** Layout of the bird is not critical and any method of construction may be used. If you want to use a printed circuit board, the foil pattern and layout in Fig. 2 can be used. During assembly, be sure to observe the polarities of capacitors and semiconductors and do not overheat the components when soldering.

Component values are important. The circuit will work with the normal 10% tolerance of resistors and 20% tolerance of capacitors, but variations of any larger degree will throw it off. Every component determines some type of time constant, so if you change the value of one component, be prepared to change the rest.

Install leads on the board for the speaker and battery, making them long enough to reach when the board is located in the selected cabinet.

Since the output stage [Q2] works di-

rectly into the speaker without any buffering, any change in the speaker loading will be reflected back into the oscillator circuit, resulting in a change in the sound. This means that the selected enclosure (for board, batteries, and speaker) must have no resonant or antiresonant peaks. Resistor R8 is included as an option to isolate (partially) the speaker from the circuit.

The prototype was built in a conventional 6" X 3½" X 2" plastic case with the front cover not used. In the bottom of the case a hole was cut for the speaker. Make the hole slightly smaller than the diameter of the speaker and cement the speaker to the case behind the hole. Four rubber feet were attached to the holes on the opposite side (where the front panel was). The battery clips were mounted on the same side as the speaker with the PC board cemented to one wall and the power switch on the other wall.

The plastic case should be dressed up with a toy bird to complete the illusion. There are many garden supply houses that stock colorful stuffed birds—some even have small wood or metal cages to enclose the bird. ♦