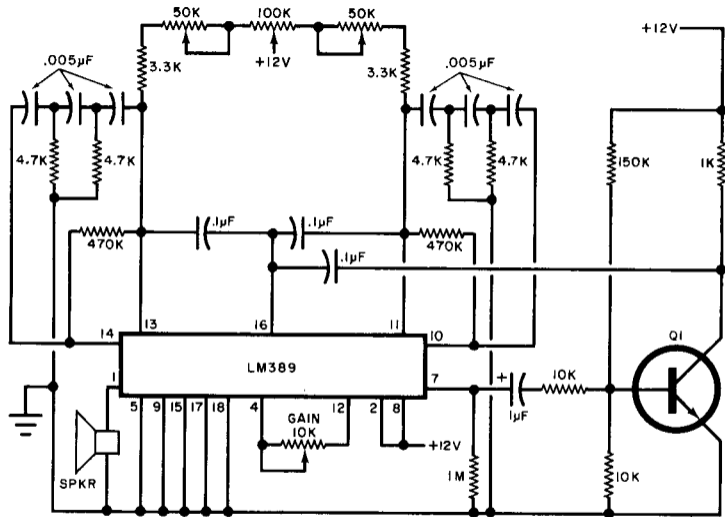


**Reader's Circuit.** You may have been intrigued by Harold Wright's *Model Railroad Sound Synthesizer* in last December's issue but would rather tackle something a little simpler for a start. If so, you might like to try the inexpensive model train steam whistle circuit shown in Fig. 3. Submitted by reader Ralph O. Bentley (606 Lake View, South Milwaukee, WI 53172), the circuit requires only two active devices, an LM389 IC and a small general-purpose npn transistor, *Q1*. Designed for operation on a standard 12-volt dc source, the circuit can be assembled on perf board. The LM389 was described in our September, 1976 "Solid State" column. Manufactured by the National Semiconductor Corporation (2900 Semiconductor Drive, Santa Clara, CA 95051), the device comprises three uncommitted general-purpose transistors and a ten-transistor low-power audio amplifier in an 18-pin DIP.

Ralph has used two of the IC's uncommitted transistors as RC phase-shift audio oscillators, coupling their outputs to the input of the audio amplifier section at pin 16. The remaining transistor is diode-connected and used as a white-noise generator, with its output applied to external transistor *Q1*, where the noise signal is amplified and applied back to the audio amplifier section through another capacitor. Each phase-shift oscillator can be individually "tuned" with a 50k potentiometer, with a common 100k potentiometer serving to establish tonal balance. The amplifier's gain is controlled by a potentiometer connected between pins 4 and 12. Capable of delivering up to 500 nW to a 16-ohm PM loudspeaker, the amplifier provides ample output for most uses.

Standard components are used in the design. Except for the potentiometers, all resistors can be either one-quarter or one-half watt types, at the builder's option. The electrolytic, which



*Fig. 3. Inexpensive circuit for a model train steam whistle sent in by a reader.*