
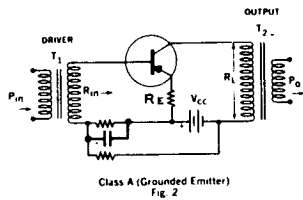


Example Calculations For Transistorized Amplifiers.

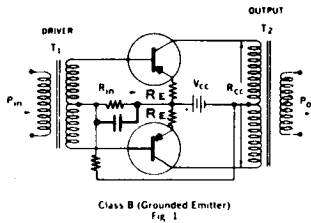

PROBLEM 1:

To determine required primary impedance of Output Transformer T_2 and Transistor Dissipation.

Example 1

GIVEN:

$V_{CE} = 12$ volts $\approx V_{CC}$ (Supply Voltage)
 $P_o = 5$ watts to Speaker Load

SOLUTION:

Assume Transformer Efficiency of 80%. Then Transistor Output power required $= \frac{5}{.8} = 6$ watts.

- Using nomograph, draw straight line from Output Power of 6 watts on Scale B through Collector Volts V_{CE} of 12 on Scale D. Extend line and read Primary Impedance R_{cc} of 48 ohms C.T. for Class B operation on Scale E, or R_L of 12 ohms for Class A on Scale F.
- Read Transistor Dissipation of 1.5 watts each for Class B operation on Scale A, or 12 watts for Class A on Scale C. Verify that Transistor Dissipation ratings are not exceeded.
- Suitable Class B Output Transformer would be Elcom TO648C which has a rating of 48 ohms C.T. to 4/8/16 at 10 watts.

PROBLEM 2:

To determine primary and secondary Impedances of Driver Transformer (T_1) to match transistor Input Impedance (R_{in}). Also to determine required Driving Power (P_{in}).

For Class B Output Stage

(See Fig. 1 and footnotes)

$$R_{in} \approx 4 h_{ie} \text{ (assuming } R_E \text{ is negligible)}$$

$$P_{in} \approx \frac{4 h_{ie} P_{opp}}{(h_{ie})^2 R_{cc}}$$

For Class A Output Stage

(See Fig. 2 and footnotes)

$$R_{in} \approx h_{ie} \text{ (assuming } R_E \text{ is negligible)}$$

$$P_{in} \approx \frac{h_{ie} P_{oA}}{(h_{ie})^2 R_L}$$

Example 2

GIVEN:

Assume G.E. 2N656A's or RCA 2N1481's in Class B Output Stage of Example 1, Fig. 1.
Transistor Output Power $P_{opp} = 6$ watts. $V_{CE} = 12$ Volts.
Primary Impedance R_{cc} of $T_2 = 48\Omega$ C.T.

SOLUTION:

- Transistor handbook ratings of 2N656 are: $h_{ie} \approx 40$ and $h_{ie} \approx 200$.
- $R_{in} \approx 4 h_{ie} = 4 \times 200 = 800\Omega$ C.T. Secondary Impedance of T_1 .
- $P_{in} \approx \frac{4 h_{ie} P_{opp}}{(h_{ie})^2 R_{cc}} = \frac{4 \times 200 \times 6}{(40)^2 \times 48} = 62.5\text{mw}$.

Allowing for typical transformer efficiency of 75%, Input Power to T_1 should be $\frac{62.5}{.75} = 83.3\text{mw}$.

d. Use nomograph to determine primary impedance of Driver Transformer T_1 by drawing line from 83.3mw. on Scale B through 12 volts D.C. on Scale D. Read Class A primary impedance of 850Ω on Scale F. (Assuming Driver is Class A)

e. Suitable Driver Transformer would be Elcom TI26. This transformer has a 1:1 impedance ratio whose impedance values and power handling capacity is close enough to required circuit values for proper performance.

REFERENCE INFORMATION

CLASS B FORMULAS (Assumes > 50mw. power level)

$$\text{Transistor Power Output, } P_{opp} = \frac{2V_{ce}^2}{R_{cc}}$$

$$\text{Power Gain, } G_B = \frac{(h_{ie})^2 R}{4 h_{ie}}$$

$$\text{Power In, } P_{in} = \frac{P_{opp}}{G_B} = \frac{4 h_{ie} P_{opp}}{(h_{ie})^2 R}$$

$$R_{in} = 4(h_{ie} + h_{ie} R_E) \text{ (When } R_E \text{ is not negligible)}$$

CLASS A FORMULAS (Assumes > 10mw. power level)

$$\text{Transistor Power Output, } P_{oA} = \frac{V_{CE}^2}{2R_L}$$

$$\text{Power Gain, } G_A \approx \frac{(h_{ie})^2 R_L}{h_{ie}}$$


$$\text{Power In, } P_{in} = \frac{P_{oA}}{G_A} = \frac{h_{ie} P_{oA}}{(h_{ie})^2 R_L}$$

$$R_{in} = h_{ie} + h_{ie} R_E \text{ (when } R_E \text{ is not negligible)}$$

REFERENCES: Motorola 1960 Power Transistor Handbook pgs. 64-81.
G.E. Transistor Manual 5th Edition pgs. 44-47.


TRANSISTOR LOAD IMPEDANCE AND DISSIPATION NOMOGRAPH

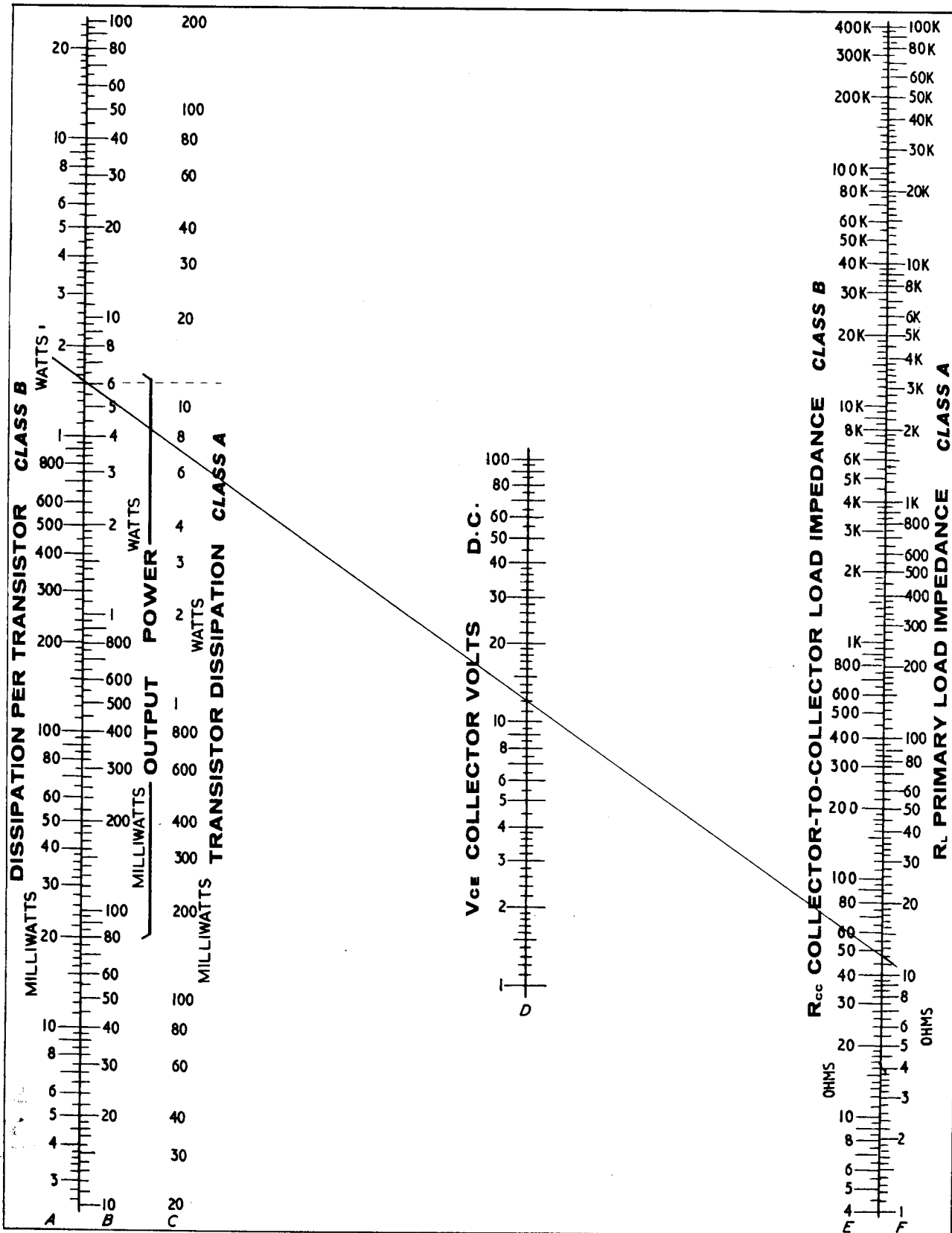FOR CLASS A AND B TRANSFORMER COUPLED TRANSISTOR AUDIO AND SERVO AMPLIFIER



TRANSISTOR LOAD IMPEDANCE NOMOGRAPH TRANSISTOR AUDIO AND SERVO AMPLIFIERS

FOR CLASS B TRANSFORMER - COUPLED

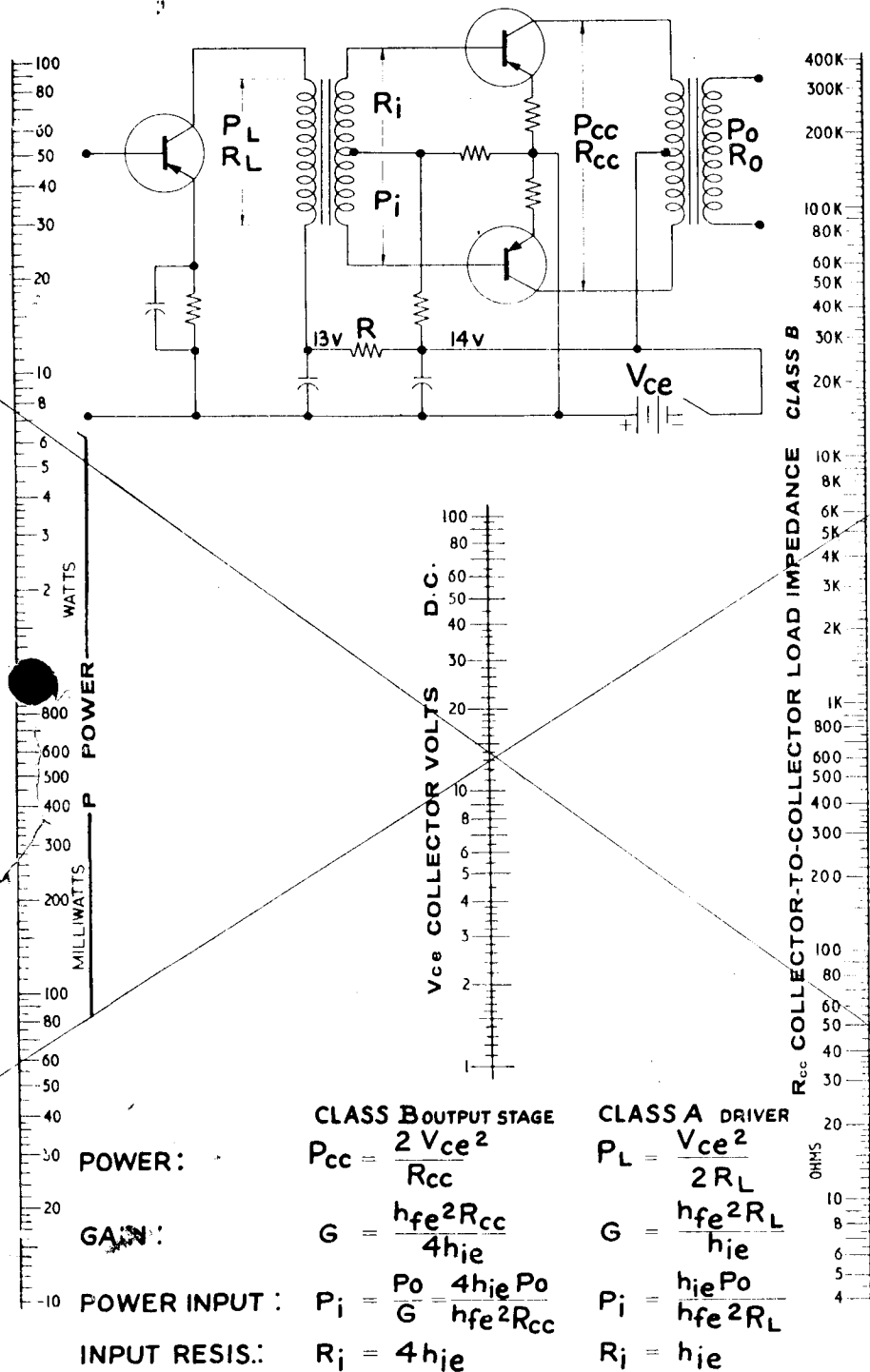

NOTES

- When reading the R_{cc} scale, divide R_{cc} by 4 to get R_L ; when entering the R_{cc} scale with R_L , multiply R_L by 4.
- Pri. load impedance of single-ended stage is $R_L = \frac{R_{cc}}{4}$.
- These formulae are approximations for convenience. For more exact relations reference should be made to suitable texts, particularly in regard to the transistor parameters, h_{ie} and h_{fe} .

Example: To determine the correct driver and output transformers in the above typical circuit —

$V_{ce} = 14V$ DC amplifier supply
 $P_o = 6$ watts power output
 $R_o = 8$ ohms output impedance

- Assume the output transformer efficiency to be 80%, then

$$P_{cc} = \frac{6}{0.8} = 7.5 \text{ watts.}$$

- On the nomograph draw a line from 7.5 watts on **P** scale through 14 Volts on the V_{ce} scale to read 50 ohms on the R_{cc} scale. The nearest Hammond transformer would be the 147R which has a rating of 48 ohms ct to 4/8/16 ohms at 10 watts.

- The driving power required for a pair of transistors having $h_{fe} = 40$, $h_{ie} = 100$ is $P_i = \frac{4(100)(7.5)}{40^2(48)} = 39$ mw.

Allowing for 67% efficiency, a driving power P_L of 59 mw should be available.

- The secondary impedance of the driver transformer is equal to the input resistance (R_i) of the output transistors.

R_i is usually specified for Class B power transistors, but where h_{ie} is given, R_i may be found approximately from the relation $R_i = 4 h_{ie}$. Where $h_{ie} = 100$, $R_i = 400$ ct.

- The primary impedance can be taken from the nomograph by drawing a line through 59 mw on the **P** scale and 13 volts on the V_{ce} scale. Being single-ended the primary impedance is

$$\frac{5600}{4} = 1400 \text{ ohms.}$$

The transformer is therefore 1400/400 ohms ct at 59 mw rating, and the Hammond type 148F would be about right. (1500/500 ohms ct)