

Class D Audio Amplifier Using PIC24FV16KM202

*Author: Justin O'Shea
Steve Bowling
Frank Aloe
Microchip Technology Inc.*

This application note provides a method to implement a class D amplifier using only the analog features of the PIC24FV16KM202 and minimal external components. This leaves the processor completely available for other application processes. The design presented is a single channel, full bridge (push-pull) Class D amplifier.

INTRODUCTION


Class D amplifiers have become a popular audio amplifier topology due to their high efficiency and subsequent low cost. The high current output stage is implemented using binary switches, resulting in minimal heat generation and power loss. This allows for the power supply, heat sink and overall physical size of the amplifier to be minimized. Typical efficiency of a class D amplifier is over 90%, as opposed to 50% for a typical class AB amplifier. In an AB design, most of the inefficiency is a result of the output stage devices being required to operate in the linear region. As current flows through the devices, it is converted to heat instead of being delivered to the load.

CLASS D TOPOLOGY OVERVIEW

A Class D audio amplifier is essentially a PWM amplifier. The input audio signal is used as the modulation reference for a PWM carrier. The resulting PWM signal is used to drive a higher power output stage, and filtered to recover the amplified audio. A class D amplifier is composed of 4 main functions as shown in Figure 1. These functions are:

- Triangle wave generator
- Audio modulation comparator
- Switch controller and output stage
- Low pass filter


FIGURE 1: CLASS D AMPLIFIER BLOCK DIAGRAM

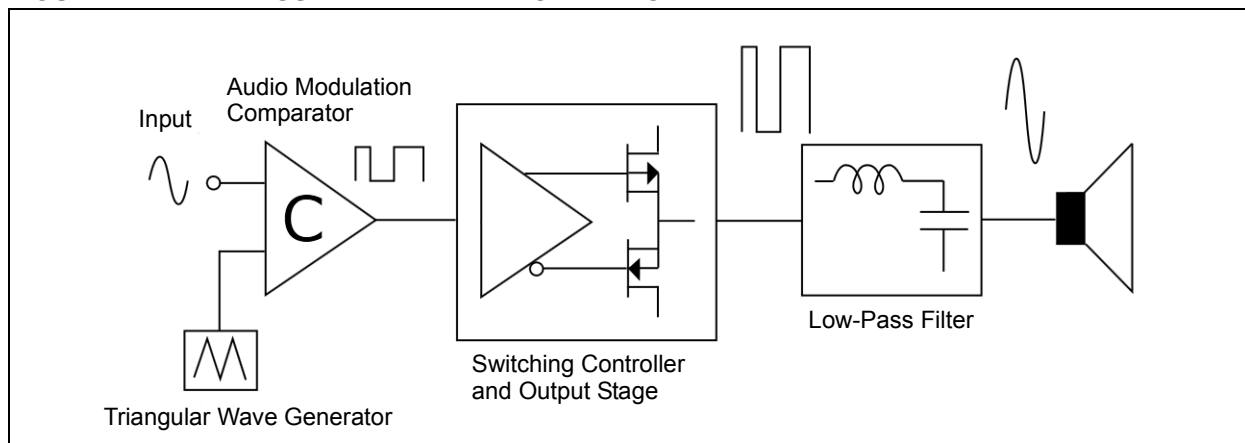

The analog audio signal is first compared to a high frequency triangle wave, using a comparator, to create a pulse waveform that is directly proportional to the instantaneous values of the audio signal. This results in a digital representation of the analog signal that can now be used to drive the output devices only in 'on' and 'off' states, as shown in Figure 2. Additional logic is used to produce the inverse of the digital signal to drive the complementary switch pair. Next, a switch controller provides signal timing and gate drive voltages for the output devices. The output switches pro-

vide voltage gain proportional to the supply voltage, and high current capability to drive the speaker coil. Finally, a low pass filter is used to remove the carrier frequency and recreate the analog audio signal.

FIGURE 2: CLASS D ANALOG AND DIGITAL WAVEFORMS

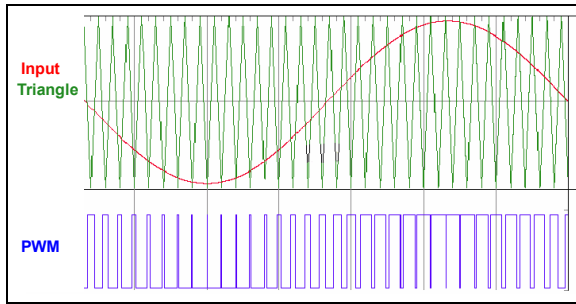

ANALOG INPUT STAGE

The incoming audio signal needs to be conditioned and filtered before it is compared to the triangle wave. A low pass filter should be used to prevent aliasing, and the level should be limited to below that of the triangle wave. The amplitude of the audio signal may need to be attenuated or amplified to match that of the comparator supplies and triangle wave amplitude. To improve signal-to-noise ratio, the peak level audio input should be as close to system full scale as possible. Depending on the application and loudspeaker to be driven, it may be beneficial to band limit the input signal. For example, if a small speaker is used that cannot produce tones below 100 Hz, the input should be high pass filtered to reduce wasted energy and possible speaker damage.


AMPLIFIER POWER SUPPLY CONSIDERATIONS

A stable DC power supply is important for a class D design. The power supply plays a critical role in the performance of the amplifier including gain, THD and noise. Class D amplifiers have little to no power supply noise rejection; any noise or voltage drops from loading will be passed on to the output. Due to the digital nature of the class D design, the power supply has to deliver large current transients each time the output devices switch. The power supply can also be affected from the energy storage elements in the low pass filter and loud speaker coil.

OUTPUT STAGE DESIGN

Using a full bridge output stage reduces the power supply's effect on performance degradation, and can be implemented with a single rail design. Some amount of 'dead time' is needed to prevent damaging current flow through the switches. Dead time is a delay in driving a switch high due to the capacitive settling effects of the output switch. This prevents both switches from being closed at the same time, effectively shorting V+ to GND. The amount of dead-time is dependent on the switches on/off delay, and will affect THD. A full bridge topology has reduced offset and THD compared to a half bridge, and can be implemented without a feedback circuit. When idle, the PWM duty cycle is 50% and the average voltage on both ends of the speaker coil is $V+/2$. Figure 3 shows a full bridge output design.

FIGURE 3: FULL BRIDGE OUTPUT CIRCUIT DIAGRAM

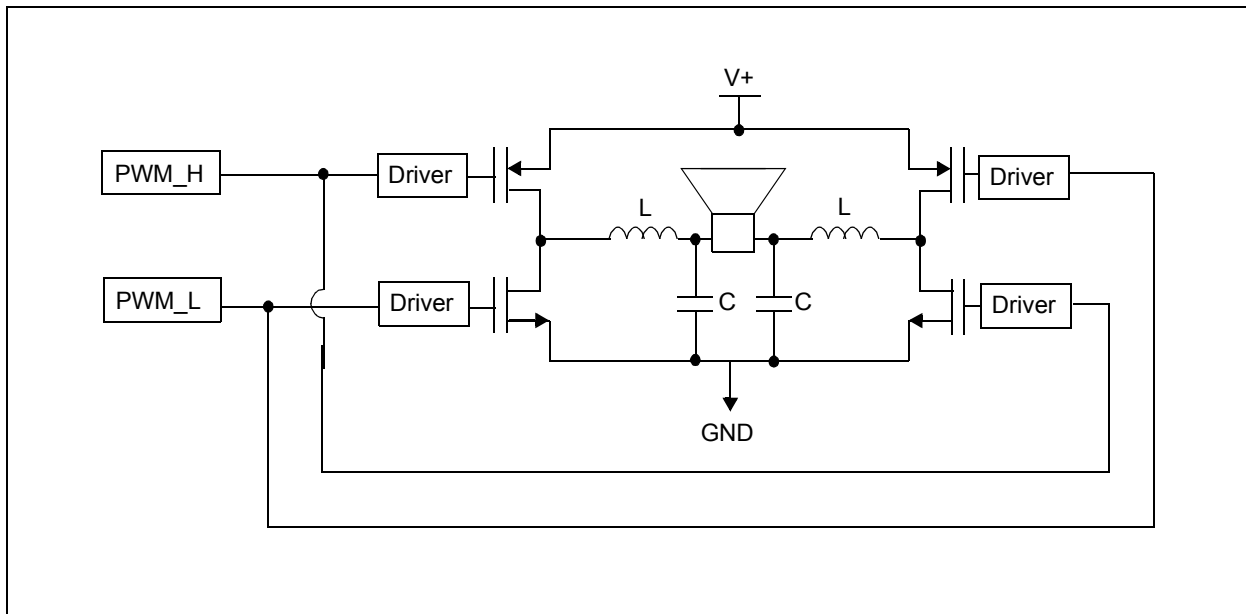


OUTPUT FILTER DESIGN

A typical class D output filter is a 2nd order L-C low pass filter with no resistive components to waste power. The filter cut off frequency should be at least four times lower than the switching frequency of the triangle generator. The application's speaker nominal impedance will guide the initial values of the inductors and capacitors. However, the speaker coil's own inductance and capacitance also interact with the filter elements and should be considered in the design. The power level of the amplifier and resulting current delivered through the filter guides the power rating of the filter elements. Lastly, some designs may have restrictions on radiated emissions (EMI). The filter design, physical location and trace routing need to be considered for best performance.

IMPLEMENTING A CLASS D AMPLIFIER USING THE PIC24FV16KM202

The PIC24FV16KM202 has a wide range of analog and digital peripherals that can be used to create an analog class D amplifier. The KM device also has configurable internal connections between the peripherals that reduce external PCB routing and free up I/O pins for other uses. The 'FV' variant of the KM family was chosen for its 5V operation, improving the signal-to-noise ratio of the system. The peripherals and connections used for the amplifier are shown in [Figure 4](#).

FIGURE 4: PIC24FV16KM202 PERIPHERAL CONNECTIONS

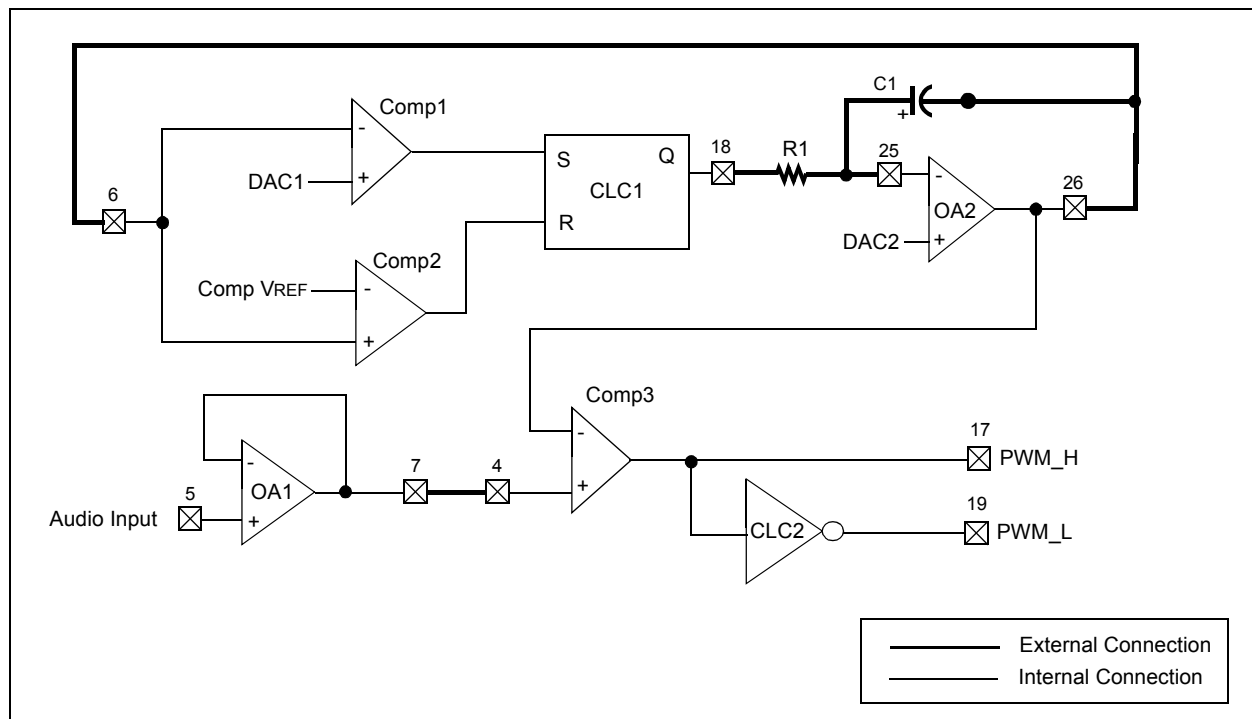

Op amp OA1 is used as a buffer for the incoming audio signal. The triangle generator is implemented using a pair of comparators, a CLC module setup as an SR latch and an op amp configured as an integrator. The comparators are wired as a windowed comparator, with thresholds set by DAC1 and the comparator voltage reference. The windowed comparator's output is then converted to a square wave using the SR latch, and finally a triangle wave via the integration function of opamp1. The triangle wave is fed back to the window comparator completing the self resonator circuit. Comparator Comp3 creates the pulse waveform by comparing the triangle waveform to the audio input. CLC2 configured as an inverter provides the complement signal for the full bridge topology.

Comparators

Three comparators are used in the design. Comparator Comp1 and Comp2 function as a windowed comparator using the comparator voltage reference and DAC1 to set the voltage threshold levels. Comparator inputs C1INB and C2IND are chosen as they are on the same pin and do not need an external traces.

Comparator Comp3 is used to compare the audio signal to the triangle wave to create the digital PWM signal shown in [Figure 2](#). Comparator input C3INA is chosen as it is on the same pin and op amp OA2's output.

Operational amplifiers

Op amp OA1 is utilized as a buffer for the incoming analog audio signal. It is set up as a voltage follower utilizing the selectable internal connection from the output to the inverting input. Optionally, op amp OA1 can be setup as a filter with or without gain. Op amp OA2 is used in the triangle generator as an integrator, with its output fed back to the window comparator to create an oscillator.

DACs

The Digital to Analog Converters (DACs) are used in a static state to provide a programmable DC voltage level for the triangle generator. DAC1 is internally connected to comparator 1's non-inverting input as the upper voltage threshold of the window comparator. DAC2 is internally connected to op amp OA2's non-inverting input and used to set the DC bias level, at $2.5V (V+/2)$.

Configurable logic Cells (CLCs)

The CLCs provide digital logic for the triangle wave generator and digital output. CLC1 is configured as an RS flip flop to create a single square wave from the window comparator's outputs. CLC1's inputs are internally connected to the comparator outputs. CLC2 is set up as an inverter to create a complementary PWM signal for the low side switches.

OTHER USES OF THE MICROCONTROLLER IN CLASS D AMPLIFIER DESIGN

The use of only the analog peripherals allows the microcontroller's processor and other peripherals to be available for use. Below are some examples of additional features that are specific to audio amplifiers.

Switch Mode Power Supply Control

The PIC24FV16KM202's Capture/Compare/PWM (MCCP and SCCP) and ADC peripherals are capable of controlling a switch mode power supply. The power supply can be used to boost DC voltages for higher amplifier output, or to convert line AC power to DC.

Thermal Overload and Over Current Protection

The PIC24FV16KM202's ADC or digital I/O can be used to sense the operational conditions of the amplifier and take action if needed. A temperature sensor can be used to measure amplifier output switch temperature and shut down the amplifier if a threshold is exceeded. If the speaker leads are accidentally shorted, the system can sense excessive current and shut down the amplifier. Indication of either of these conditions can be accomplished with I/O pins directly driving LEDs.

Automatic On/Off Sense

Some applications benefit from the ability to sense whether an audio input signal is present, and enable/disable the amplifier. This can be especially useful when there is no other way for the amplifier to communicate with the rest of the audio system. For low-power applications, the PIC24FV16KM202 can shut down the amplifier and put itself to sleep to conserve energy until it is needed again.

Remote Gain Control

User control of volume level is desired in some amplifier applications. The location of this remote control can be a long distance away and in a noisy environment where routing the audio signal there and back is not desired. One of the PIC24FV16KM202's several digital communication peripherals can be used to communicate to the remote control.

Audio Tone Generation

If the application has buttons or user inputs, it may be useful to use audio tones as confirmations. The PIC24FV16KM202's CCP peripheral can be used as a tone generator, and the output can be mixed into the audio signal with one of the op amps.

DESIGN DETAILS AND PERFORMANCE RESULTS

The design presented in [Figure :A](#) was built and its performance was evaluated. For ideal symmetry of the triangle wave, a frequency of 32 kHz was selected. To determine the R1 and C1 values for the integrator, the desired frequency and voltage amplitude are used as shown in [Equation 1](#). For a nominal frequency of 32 kHz, 560 Ohms and 10 nf values were chosen. The triangle wave minimum and maximum voltage of 1V (VREF) and 3.75V (DAC1) were chosen to sample an audio input amplitude of 2.5V, with a DC offset of 2.5V.

EQUATION 1: TRIANGLE GENERATOR INTEGRATOR FREQUENCY

$$F = \frac{1}{2 \cdot R1 \cdot C1 \cdot Vpk - pk}$$

where $Vpk - pk = VDAC1 - VREF$

The system's upper frequency limit is set 2 octaves below the PWM frequency, at 8 kHz. The input band-pass filter is designed with corner frequencies of 60 Hz and 8.25 kHz. The output low pass LC filter is also designed with a corner frequency of 8 Khz, using the equations for a full bridge output show in [Equation 2](#).

EQUATION 2: FULL BRIDGE LC OUTPUT FILTER EQUATIONS FREQUENCY

$$F = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$

For a critically damped alignment with Q of 0.707, L and C are:

$$C = \frac{1}{\pi \cdot f \cdot \sqrt{2}}$$

$$L = \frac{R \cdot \sqrt{2}}{4 \cdot \pi \cdot f}$$

Where R is speaker impedance

For an 8 Ohm speaker, standard C and L values of 3.3 μ F and 100 μ H results in a corner frequency of 8.7 kHz and a Q of 0.73.

With a 12 VDC power supply, the amplifier delivered 9 Watts into 8 Ohms with less than 1% THD. The resulting bandwidth is sufficient for most applications using a single, small to medium sized speaker. Alternatively, this Class D design can also be used for a subwoofer amplifier application.

For additional information on Microchip power supply products and solutions, see:


<http://www.microchip.com/intelligentpower/>

CONCLUSION

The PIC24FV16KM202's wide range of analog and digital peripherals allows it to be used to create complete solutions including a class D amplifier. The internal connections between peripherals reduce the pin count needed for implementation, leaving the I/O pins available for other uses. Using the PIC24FV16KM202's peripherals instead of discrete components to realize a Class D design minimizes PCB area and overall cost.

APPENDIX A: SCHEMATICS

FIGURE A: PIC24FV16KM202 CLASS D AMPLIFIER

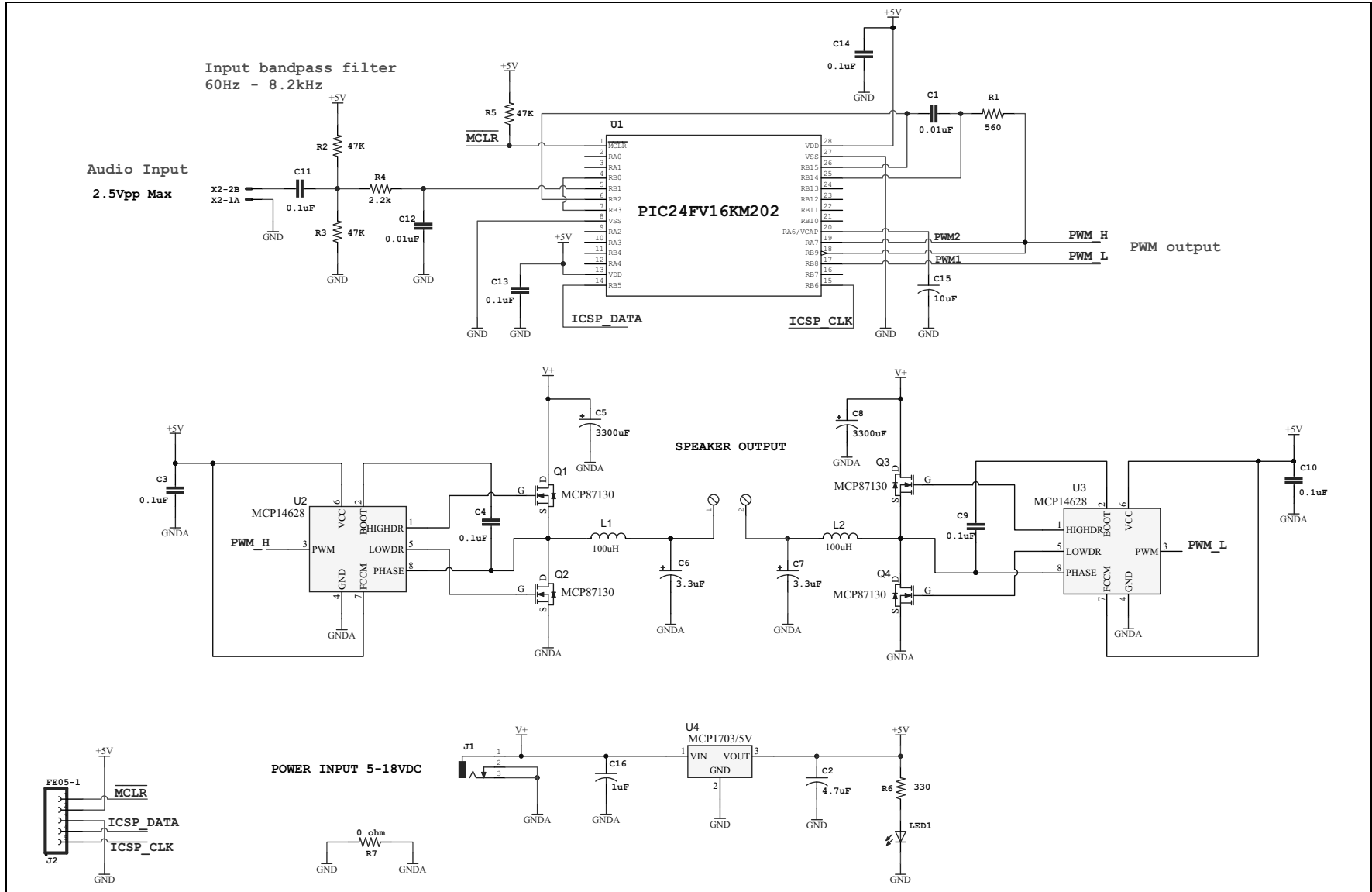

APPENDIX B: APPLICATION CODE

EXAMPLE 1: INITIALIZATION CODE

```

// Port setup for OpAmps
_TRISB1 = 1;           // OpAmp1 non-inverting input, Analog input, Pin 5
_ANSB1 = 1;
_TRISB3 = 1;           // OpAmp1 output, Analog input (see Errata), Pin 7
_ANSB3 = 1;

_TRISB15 = 1;          // OpAmp2 output, Analog input (see Errata)
_ANSB15 = 1;
_TRISB14 = 1;          // OpAmp2 inverting input, Analog input, Pin 25
_ANSB14 = 1;

// Port setup for Comparators
_TRISB2 = 1;           // Comparator 1 inverting input B, Analog input, Pin 6
_ANSB2 = 1;

_TRISB2 = 1;           // Comparator 2 inverting input D, Analog input, Pin 6
_ANSB2 = 1;

_TRISB0 = 1;           // Comparator 3 inverting input D, Analog input, Pin 4
_ANSB0 = 1;
_TRISB15 = 1;          // Comparator 3 non-inverting input A, Analog input, Pin 26
_ANSB15 = 1;
_TRISB8 = 0;           // Comparator 3 output, Analog output, Pin 17
_ANSB8 = 0;

// Port setup for CLCs
_TRISB9 = 0;           // CLC1, Digital output, Pin 18
_ANSB9 = 0;

_TRISB7 = 0;           // CLC2, Digital output, Pin 19
_ANSB7 = 0;

// Port setup for DACs
_TRISB12 = 0;          // DAC1 Output, Analog output, Pin 23
_ANSB12 = 1;

// Comparator Reference initialization
CVRCONbits.CVRSS = 0;  // Use AVdd and AVss as reference source
CVRCONbits.CVR = 0x07; // Comp Vref value select, 7 / 32 * 5V = 1.09V
CVRCONbits.CVREN = 1;  // Enable comparator voltage reference

// DAC1 initialization
DAC1CONbits.DACREF = 2; // DAC Vref = AVdd
DAC1DAT = 192;          // Vout = 192 / 256 * 5V = 3.75 V
DAC1CONbits.DACOE = 0;  // Output disabled, use internal connection to comp2
DAC1CONbits.DACEN = 1;  // Enable DAC1

```

EXAMPLE 1: INITIALIZATION CODE (CONTINUED)

```
// DAC2 initialization
DAC2CONbits.DACREF = 2;    // DAC Vref = Avdd
DAC2CONbits.DACOE = 0;    // Output disabled, use internal connection to OA2
DAC2DAT = 128;           // Vout = 128 / 256 * 5V = 2.5V
DAC2CONbits.DACEN = 1;    // Enable DAC2

// Comparator initialization
CM1CONbits.CREF = 2;      // Connect non-inverting input to DAC1 output
CM1CONbits.CCH = 0;      // Connect inverting input to C1INB (pin 6)
CM1CONbits.CPOL = 1;     // Invert output
CM1CONbits.COE = 0;      // Output disabled, use internal connection to CLC1
CM1CONbits.CON = 1;      // Enable Comparator 1

CM2CONbits.CREF = 1;      // Connect non-inverting input to comparator reference
CM2CONbits.CCH = 2;      // Connect inverting input to C2IND (pin 6)
CM2CONbits.COE = 1;      // Output disabled, use internal connection to CLC1
CM2CONbits.CON = 1;      // Enable Comparator 2

CM3CONbits.CREF = 0;      // Connect non-inverting input to C3INA (pin 26)
CM3CONbits.CCH = 2;      // Connect inverting input to C3IND (pin 4)
CM3CONbits.CPOL = 1;     // Invert output
CM3CONbits.COE = 1;      // Output enabled
CM3CONbits.CON = 1;      // Enable Comparator 3

// CLC1 initialization (SR Latch)
CLC1CONL = 0x8083;        // CLC enabled, Output enabled, Mode = 3 (SR latch)
CLC1CONH = 0x0000;        // No Gate inversions
CLC1SELL = 0x0220;        // MUX 3 = Comp 2 output, MUX 2 = Comp 1 output
CLC1GLSL = 0x0008;        // Gate 1 = Data 2 (Comp 1)
CLC1GLSH = 0x0020;        // Gate 3 = Data 3 (Comp 2)

// CLC2 initialization (inverter)
CLC2CONL = 0x8081;        // CLC enabled, Output enabled, Mode = 1 (OR-XOR)
CLC2CONH = 0x0000;        // No Gate inversions
CLC2SELL = 0x2005;        // Data 4 = Comp 3 output, Data 1 = Logic 0
CLC2GLSL = 0x0040;        // Gate 1 = Data 4 (Comp 3, inverted)
CLC2GLSH = 0x0200;        // Gate 4 = Data 1 (logic 0).

// OpAmp 1 initialization (Audio buffer)
AMP1CONbits.SPDSEL = 1;    // High speed mode
AMP1CONbits.NINSEL = 5;    // OpAmp 1 negative input connected internally as voltage follower
AMP1CONbits.PINSEL = 1;    // OpAmp 1 positive input connected to OA1INA (pin 5)
AMP1CONbits.AMPEN = 1;    // Enable OpAmp

// OpAmp 2 initialization (Intergrator for triangle wave generator)
AMP2CONbits.SPDSEL = 1;    // High speed mode
AMP2CONbits.NINSEL = 2;    // OpAmp 1 negative input connected to OP2IND (pin 25)
AMP2CONbits.PINSEL = 5;    // OpAmp 1 positive input connected to DAC2 output
AMP2CONbits.AMPEN = 1;    // Enable OpAmp
```

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable.”

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, FlashFlex, flexPWR, JukeBlox, KEELOQ, KEELOQ logo, Klear, LANCheck, MediaLB, MOST, MOST logo, MPLAB, OptoLyzer, PIC, PICSTART, PIC³² logo, RightTouch, SpyNIC, SST, SST Logo, SuperFlash and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

The Embedded Control Solutions Company and mTouch are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, BodyCom, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, ECAN, In-Circuit Serial Programming, ICSP, Inter-Chip Connectivity, KlearNet, KlearNet logo, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, RightTouch logo, REAL ICE, SQI, Serial Quad I/O, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

GestIC is a registered trademarks of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2014, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-63276-872-8

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949 ==

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



MICROCHIP

Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX
Tel: 512-257-3370

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland
Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Novi, MI
Tel: 248-848-4000

Houston, TX
Tel: 281-894-5983

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

New York, NY
Tel: 631-435-6000

San Jose, CA
Tel: 408-735-9110

Canada - Toronto
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office
Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2943-5100
Fax: 852-2401-3431

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8569-7000
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Chongqing
Tel: 86-23-8980-9588
Fax: 86-23-8980-9500

China - Hangzhou
Tel: 86-571-8792-8115
Fax: 86-571-8792-8116

China - Hong Kong SAR
Tel: 852-2943-5100
Fax: 852-2401-3431

China - Nanjing
Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8864-2200
Fax: 86-755-8203-1760

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

China - Xiamen
Tel: 86-592-2388138
Fax: 86-592-2388130

China - Zhuhai
Tel: 86-756-3210040
Fax: 86-756-3210049

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-3090-4444
Fax: 91-80-3090-4123

India - New Delhi
Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune
Tel: 91-20-3019-1500

Japan - Osaka
Tel: 81-6-6152-7160
Fax: 81-6-6152-9310

Japan - Tokyo
Tel: 81-3-6880-3770
Fax: 81-3-6880-3771

Korea - Daegu
Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur
Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang
Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-5778-366
Fax: 886-3-5770-955

Taiwan - Kaohsiung
Tel: 886-7-213-7830

Taiwan - Taipei
Tel: 886-2-2508-8600
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Dusseldorf
Tel: 49-2129-3766400

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Germany - Pforzheim
Tel: 49-7231-424750

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Venice
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Poland - Warsaw
Tel: 48-22-3325737

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820

03/25/14