



The LT1056 is there as an impedance buffer

The MAX913 can be substituted with a MXL1016 or LT1016.

The first inverter, with the filter on its input, is used to introduce a suitable delay (=keep switch frequency down)

This part is here still somewhat tentative - although it does reflect the current working assumption. Different alternative (old) ideas for this level-shifting and MOSFET driver part are kept in subfiles; amp30pow\_a, amp30pow\_b and so on...

Copyright (c) 2001-2002 Johan Sørensen.  
 Permission is granted to copy, distribute and/or modify this document under the terms of the GNU Free Documentation License, Version 1.1 or any later version published by the Free Software Foundation with the Invariant Sections being this copyright & license notice, with no Front-Cover Texts, and with no Back-Cover Texts.