
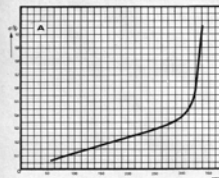


measurement results

- Input impedance: 60 ... 160 k Ω , depending on
 Input sensitivity: 70 ... 170 mV (adjustable)
 Output impedance: 1k Ω or up to 4k7, depending on
 Maximum output level: 180 mV (or up to 850 mV)
 S/N ratio: better than 60 dB
 Input selector: suppression of unwanted inputs: better than 60 dB
 Crosstalk: adjustable;
 in stereo position: -40 ... -50 dB,
 100 Hz ... 10 kHz
 Current consumption: approx. 200 mA (10 V)
 Distortion, as a function of the output voltage from the input selector stage: see graph A

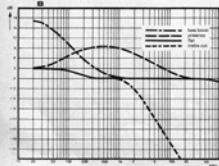

Tone control characteristics: see graph B



part 2

tap preamp

The first part of this article discussed an audio pre-amplifier and control unit operated entirely

by TAP's and dealt with the design of the TAP and the electronic switching controlled by the TAP. This month's article deals with the application of these circuits to a complete touch-controlled preamp with the facilities already described.

A block diagram of the preamp and control unit is given in figure 1. The input selector, with inputs for four signal sources, is followed by a tone control that provides bass lift, presence (middle lift), treble cut, or a flat response. (It should be noted that the touch control panel shows a symbol which could be interpreted as 'treble lift' in the fourth position.) The signal is then fed into a circuit that controls the image width from mono to 'enhanced stereo' by introducing crosstalk between the channels. The signal is fed finally to a volume control that provides four preset gains.


The disc input must be preceded by a suitable RIAA-equalised preamplifier, which may be mounted in the control unit, but preferably in the record deck

as this will give better hum figures and (provided the disc preamp has a low output impedance) the frequency response will be unaffected by cable capacitance.


The TAP, which controls all the functions, is shown in figure 2. Its operation was described in detail in last month's article, but basically, touching any one of the inputs causes the corresponding Q output to become '1' and all the other outputs to become '0'. Only one Q output can be '1' at any time. The Q outputs of the TAP are connected to the corresponding Q inputs of the input selector, tone, width and volume controls.

The Input Selector

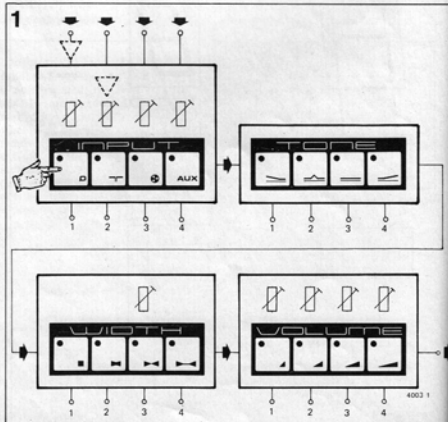The input selector of figure 3 makes use of the electronic 'break contact' de-



2

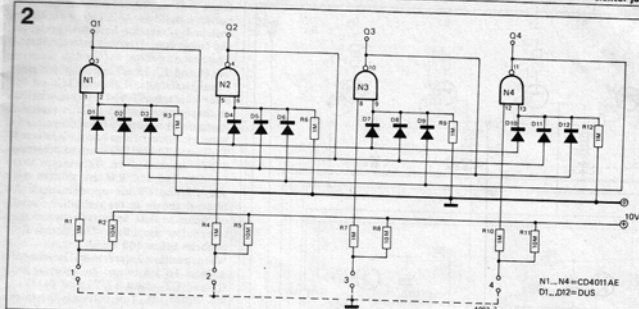

scribed in last month's article to short out the unwanted signals. When one of the inputs 1-4 is selected the corresponding transistor (T1-T4) is turned on. The corresponding pair of transistors for left- and right-hand channels (T5/T6-T11/T12) are turned off so that the desired signal can reach the base of T15 and T16. All the other pairs of transistors are turned on and short the unwanted signals to ground.

The presets on each input allow adjustment of input sensitivity and channel balance to correct channel imbalance in the signal sources. The channel balance of the preamplifier itself may be adjusted by presets in the volume control stage.

The Tone Control

The tone control circuit is shown in

3

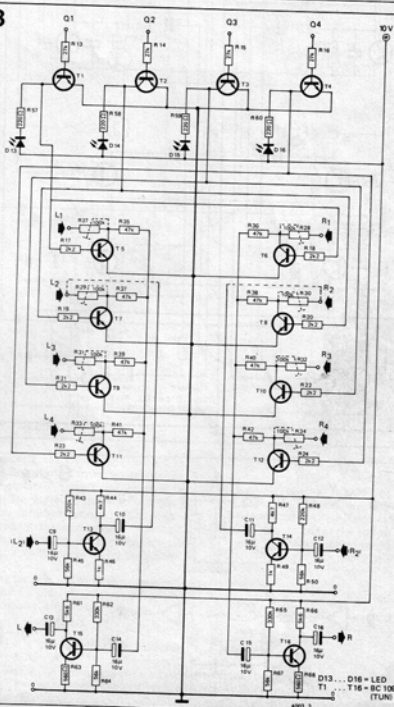


Figure 1. Block diagram of the complete touch-controlled preamplifier consisting of input selector, tone, stereo image width and volume controls. The four units each have a nominal gain of one, so any unit or units may be omitted without affecting the sensitivity.

Figure 2. Circuit of the four-position TAP. Touching one of the inputs causes the appropriate output to become '1'. The Q outputs are used to control the preamplifier functions.

Figure 3. Circuit of the input selector. T13 and T14 provide additional amplification for low-output tuners and can be dispensed with if not required. Presets R27-R34 are used to adjust for the same nominal output for all signal sources. For high-level inputs the value of these presets can be increased to 1 M Ω .

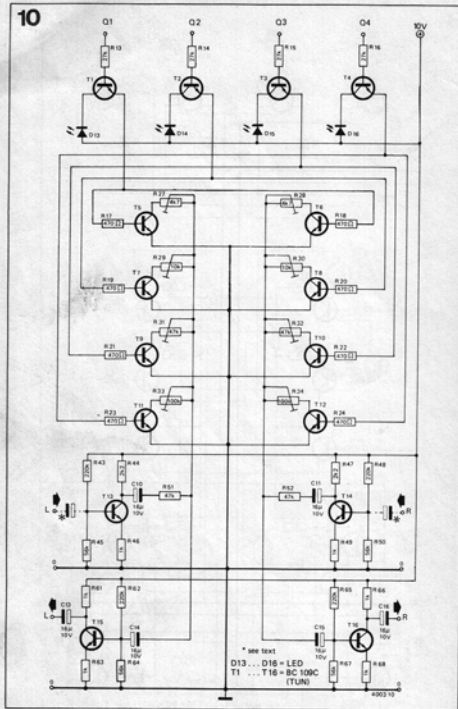


Figure 10. The four-level volume control, which may be preset to the desired listening levels and may be used to adjust channel balance.

Figure 11. Pattern of the universal p.c. board used for each of the four units of the pre-amplifier.

Therefore

$$L_0 = L - k_1 R + k_2 R - k_1 k_2 L \\ = L(1 - k_1 k_2) + (k_2 - k_1) R$$

k_1 was chosen subjectively and it was found that a value of 6 dB ($\times 1/2$) of anti-phase crosstalk gave the best results. This immediately gives some of the values for k_2 .

For a mono signal the proportions of L and R in the output must be equal i.e.

$$1 - k_1 k_2 = k_2 - k_1$$

which means that $k_2 = 1$.

For a normal stereo signal the crosstalk must be zero i.e.


$$k_2 - k_1 = 0$$

which means that $k_2 = 1/2$.

For enhanced stereo there must be only antiphase crosstalk i.e.

$$k_2 = 0.$$

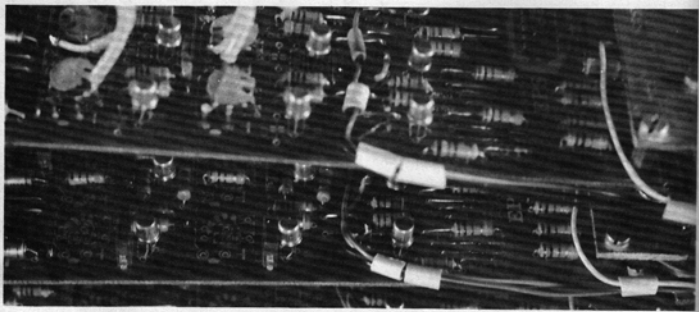The value of k_2 for a reduced width stereo signal (position 2) is purely a mat-



ter of personal taste depending on the image width required and may be adjusted by changing R39 and R40 in figure 9.

Volume Control

This was discussed briefly in last month's article and the complete circuit is given in figure 10. Selecting one of the positions turns on the corresponding pair of transistors T5/T6-T11/T12, grounding the potentiometers connected to each collector. These form attenuators with R51 and R52 which control the levels of the signals fed into the bases of T15 and T16 respectively. The degree of attenuation produced in each position may be altered by the potentiometers to suit personal taste and to adjust the channel balance.

Construction and Adjustment

The four units described are each constructed on a universal printed circuit board, the pattern for which is given in figure 11. The component layouts for the different units are detailed in figures 12-15 and the parts lists are given in the tables 1 and 2. The components common to every board are given in table 1 and those particular to one unit are given in table 2. The capacitors marked * in figures 4, 9, and 10 may be omitted if all 4 boards are used together but should be included if any board is used on its own.

Setting up of the units is a simple matter. The input potentiometers of the input selector stage are adjusted so that the output of this stage is about 100 mV when fed with the nominal signal level of each source. Thus, if the system is to be used with a tuner of nominally 100 mV output the tuner input should be adjusted with 100 mV input signal from an oscillator. If no test equipment is available the circuit may be adjusted using the actual signal sources (disc, radio, tape etc.) and listening on headphones each input potentiometer may be adjusted to give approximately the same volume level. Balance between channels should also be adjusted to compensate for im-


Table 1

	Figures 3, 12	Figures 4, 13	Figures 9, 14	Figures 10, 15
Resistors:				
R17, R18	2k2	2k2	X	470Ω
R19, R20	2k2	2k2	470Ω	470Ω
R21, R22	2k2	X	470Ω	470Ω
R23, R24	2k2	470Ω	470Ω	470Ω
R27, R28	100 k preset	X	X	4k7 preset
R29, R30	100 k preset	10k	X	10k preset
R31, R32	100 k preset	X	X	47k preset
R33, R34	100 k preset	X	X	100k preset
R35, R36	47k	4k7	X	X
R37, R38	47k	18k	47k	X
R39, R40	47k	X	15k	X
R41, R42	47k	X (C7,8)	—	X
R43, R48	220k	220k	39k	220k
R44, R47	4k7	4k7	82Ω	2k2
R45, R50	56k	56k	10k	56k
R46, R49	1k	1k	100Ω	1k
R51, R52	X	47k	15k	47k
R53, R54	—	12k	X	—
R55, R56	X	4k7	X	X
R57	220Ω	220Ω	220Ω	—
R58, R59	220Ω	220Ω	—	—
R60	220Ω	—	—	—
R61, R66	5k6	5k6	2k2	1k
R62, R65	330k	220k	220k	220k
R63, R68	560Ω	1k	1k	1k
R64, R67	56k	56k	56k	56k
R69, R70	X	X	33k	X
R71, R72	X	X	47k	X
R73	X	X	47Ω	X
Capacitors:				
C1, C2	X	82n	X	X
C3, C4	X	68n	X	X
C5, C6	X	15n	X	X
C7, C8	(R41, R42)	15n	—	(R41, R42)
C9, C12	16μ/10 V	—	—	—

(X = omitted; — = wire link)

Table 2

Resistors:		Capacitors:		Semiconductors:
R1, R4, R7, R10 = 1 M		C10, C11, C13, C14, C15, C16 =		D1 ... D12 = DUS
R2, R5, R8, R11 = 10 M		16μ/10 ... 16 volt		D13 ... D16 = LED
R3, R6, R9, R12 = 1 M				T1 ... T16 = BC109C or equ.
R13, R14, R15, R16 = 27k				IC1 = CD4011AE

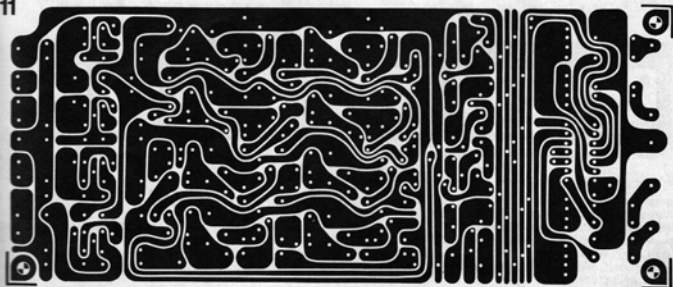

12

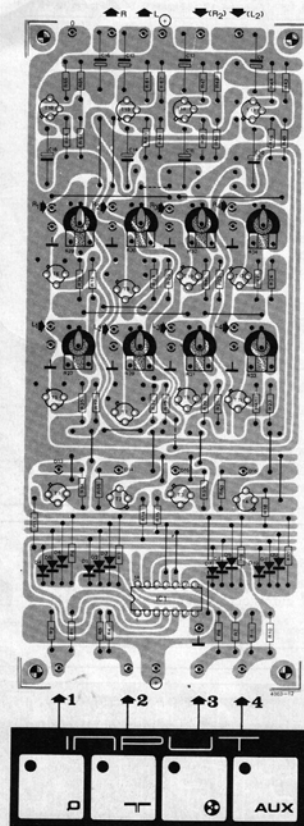


Figure 12. Component layout for the input selector (figure 3).

balance in the signal sources. The volume control settings are next adjusted to give the desired listening levels. Channel balance may also be adjusted to compensate for any imbalance in the preamplifier itself or in the power amplifier and loudspeakers. The unit is now ready for use.

The output level is 200 mV; if this is insufficient for full drive of the power amplifier, R61 and R66 (figures 10 and 15) can be increased to 4k7. The output level then becomes 1000 mV.

13

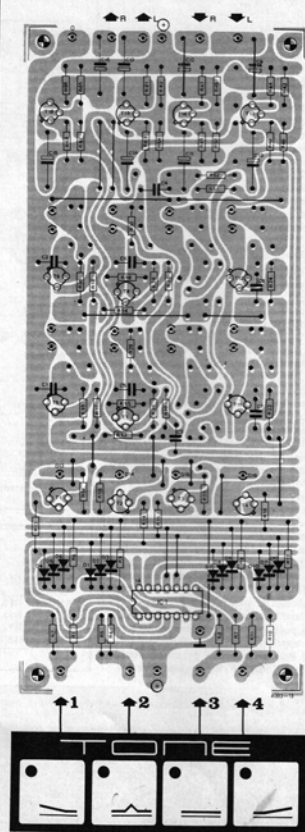


Figure 13. Component layout for the tone control stage (figure 4).

Conclusion

All the units in the touch-controlled preamplifier have a nominal gain of unity and so may be used in any combination without affecting the performance, or they may be used in conjunction with other equipment. It is

14

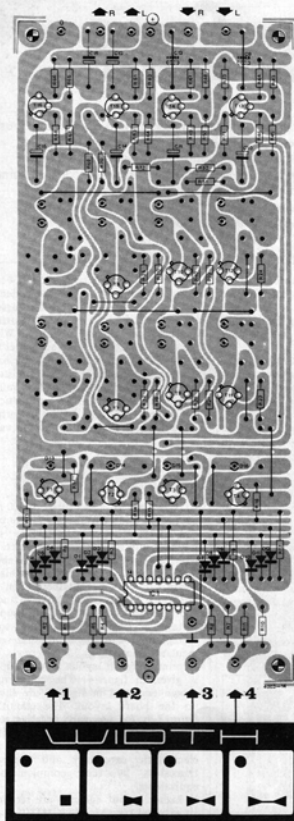


Figure 14. Component layout for the stereo width control (figure 9).

15

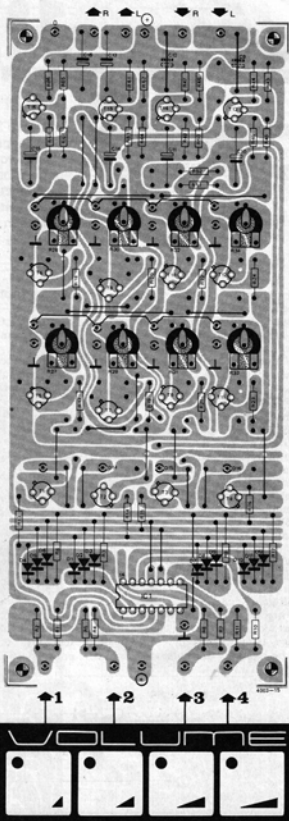


Figure 15. Component layout for the volume control (figure 10).

hoped in a later article to publish details of a touch station selector for radio and other additions to the system.

Design Modification

A small modification has been made to the portions of the circuit using the

'break contact'. Referring to figure 6 of last month's article, when T1 is turned off there is still a residual current of about 6 mA flowing through the LED via R3, R4 and the base-emitter junctions of T3 and T4. With certain types of LED, notably those with a clear plastic encapsulation, this may give rise to a

noticeable glow. This can be eliminated by connecting a 220 Ω resistor across the LED. Current will flow through this resistor but the voltage drop across it will be less than the turn-on voltage of the LED. This modification applies to the following: figure 3, D13-D16; figure 4, D13 and D14.