



COPYRIGHT

This Reference Guide and Video are protected by United States copyright law (Title 17, United States code). Any reproduction without written consent of Michael J. Breault is prohibited.

First printing, December 1993

© Michael J. Breault, All Worldwide Rights Reserved.

Passive Crossovers Theories & Practice Reference Guide was written by Paul D. Vogt

IMPORTANT EQUATIONS

EQUATION FOR CAPACITIVE REACTANCE

$$X_c = \frac{1}{2\pi F_c R} \times 1,000,000$$

X_c = The value of capacitor required
 $\pi \approx 3.14$
 F_c = Your chosen crossover frequency
 R = The impedance of the speaker


EQUATION FOR INDUCTIVE REACTANCE

$$X_L = \frac{R}{(2\pi F_c)} \times 1,000$$

X_L = The value of inductor required
 $\pi \approx 3.14$
 F_c = Your chosen crossover frequency
 R = The impedance of the speaker

SCHEMATICS


First order 2-way schematic

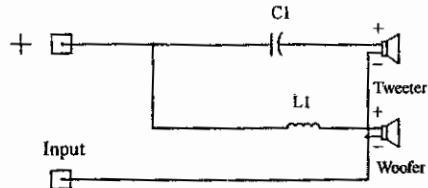

C1 = Capacitor $X_c = \frac{1}{2\pi Fc R} \times 1,000,000$

L1 = coil, $X_L = \frac{R}{(2\pi Fc)} \times 1,000$

First order 3-way schematic

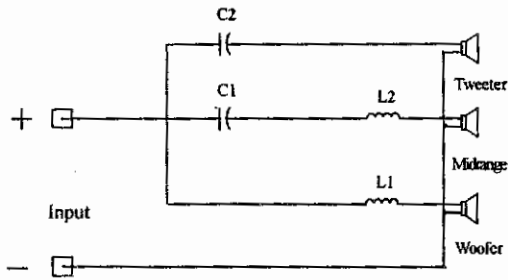


$L_1 = \frac{R}{(2\pi Fc)} \times 1,000$

$C_1 = \frac{1}{2\pi Fc R} \times 1,000,000$ at the same frequency as L1

$C_2 = \frac{1}{2\pi Fc R} \times 1,000,000$

$L_2 = \frac{R}{(2\pi Fc)} \times 1,000$ at the same frequency as C2

Second Order 2-way schematic

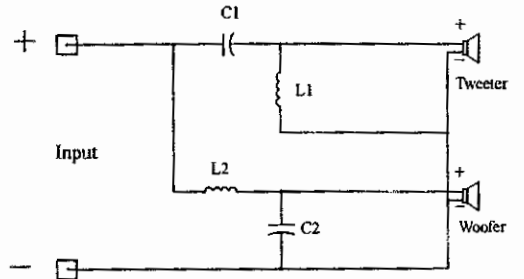


$C_1 = \frac{.1125}{R(F \times 1.3)} \times 1,000,000$ $L_1 = \frac{.2251 \times R}{(F \times 1.3)} \times 1,000$

$C_2 = \frac{.1125}{R(F / 1.3)} \times 1,000,000$ $L_2 = \frac{.2251 \times R}{R(F / 1.3)} \times 1,000$

C = capacitor, L = coil, R = impedance of speaker
F = chosen crossover frequency

Second order 3-way schematic

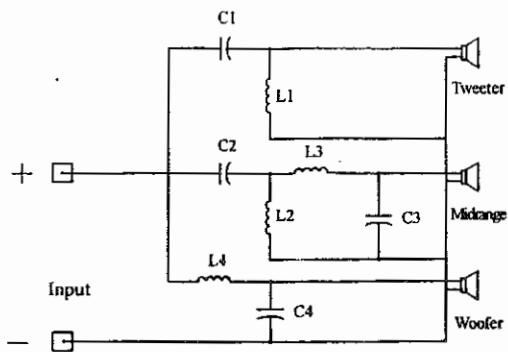

$$C_1 = \frac{.0791}{R_H \times F_H} \times 1,000,000 \quad L_1 = \frac{.3202 \times R_H}{F_H} \times 1,000$$


$$C_2 = \frac{.3236}{R_M \times F_M} \times 1,000,000 \quad L_2 = \frac{1.0291 \times R_M}{F_M} \times 1,000$$

$$C_3 = \frac{.0227}{R_M \times F_M} \times 1,000,000 \quad L_3 = \frac{.0837 \times R}{F_M} \times 1,000$$

$$C_4 = \frac{.0791}{R_L \times F_L} \times 1,000,000 \quad L_4 = \frac{.3202 \times R}{F_L} \times 1,000$$

C = capacitor, L = coil
 R_H = tweeter impedance
 R_M = midrange impedance
 R_L = woofer impedance,
 F_H = the upper crossover frequency
 F_L = the lower crossover frequency
 F_M = square root of (F_H x F_L)

Third order 2-way schematic

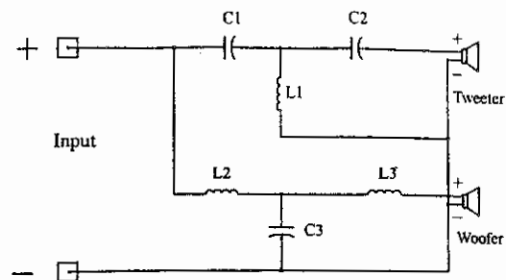

$$C_1 = \frac{.1061}{R_H \times F} \times 1,000,000 \quad L_1 = \frac{.1194 \times R_H}{F} \times 1,000$$


$$\frac{.3183}{R_H \times F} \quad \frac{.2387 \times R_L}{F}$$

$$C_2 = \frac{.2122}{R_L \times F} \times 1,000,000 \quad L_2 = \frac{.0796 \times R_L}{F_M} \times 1,000$$

$$C_3 = \quad \times 1,000,000 \quad L_3 = \quad \times 1,000$$

C = capacitor
 L = coil
 R_H = tweeter impedance
 R_L = woofer impedance,
 F = your chosen crossover frequency

Third order 3-way schematic

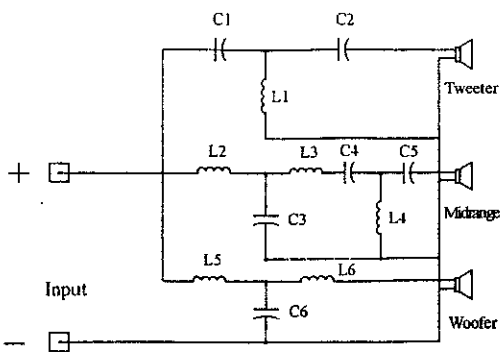

$$C1 = \frac{.1158}{R_H \times F_H} \times 1,000,000 \quad L1 = \frac{.1189 \times R}{F_H} \times 1,000$$

$$C2 = \frac{.2927}{R_H \times F_H} \times 1,000,000 \quad L2 = \frac{.0634 \times R}{F_M} \times 1,000$$

$$C3 = \frac{.0884}{R_M \times F_M} \times 1,000,000 \quad L3 = \frac{.0284 \times R}{F_M} \times 1,000$$

$$C4 = \frac{.3112}{R_M \times F_M} \times 1,000,000 \quad L4 = \frac{.3395 \times R}{F_M} \times 1,000$$


$$C5 = \frac{.9667}{R_M \times F_M} \times 1,000,000 \quad L5 = \frac{.2187 \times R}{F_L} \times 1,000$$

$$C6 = \frac{.2130}{R_L \times F_L} \times 1,000,000 \quad L6 = \frac{.0866 \times R}{F_L} \times 1,000$$

C = capacitor, L = coil, R_H = tweeter impedance,
R_M = midrange impedance, R_L = woofer impedance,

F_H = the upper crossover frequency, F_L = the lower crossover frequency, F_M = square root of (F_H x F_L)

Fourth order 2-way schematic

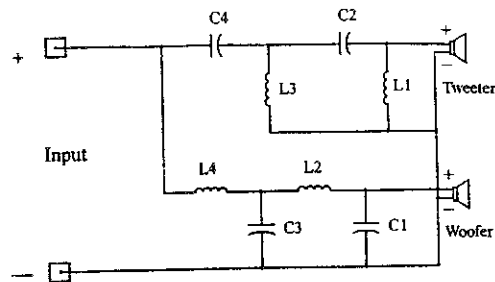

$$C1 = \frac{.1040}{R_H(F \times 1.13)} \times 1,000,000 \quad L1 = \frac{.1009 \times R_H}{F \times 1.13} \times 1,000$$


$$C2 = \frac{.1470}{R_H(F \times 1.13)} \times 1,000,000 \quad L2 = \frac{.4159 \times R_H}{F \times 1.13} \times 1,000$$

$$C3 = \frac{.2509}{R_L(F/1.13)} \times 1,000,000 \quad L3 = \frac{.2437 \times R_L}{F/1.13} \times 1,000$$

$$C4 = \frac{.0609}{R_L(F/1.13)} \times 1,000,000 \quad L4 = \frac{.1723 \times R_L}{F/1.13} \times 1,000$$

C = capacitor, L = coil
R_H = tweeter impedance
R_L = woofer impedance
F = your chosen crossover frequency

Fourth order 3-way schematic

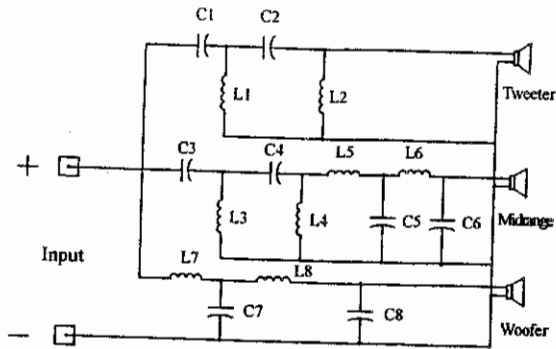

$$C1 = \frac{.0848}{R_H \times F_H} \times 1,000,000 \quad L1 = \frac{.1004 \times R_H}{F_H} \times 1,000$$

$$C2 = \frac{.1686}{R_H \times F_H} \times 1,000,000 \quad L2 = \frac{.4469 \times R_H}{F_H} \times 1,000$$

$$C3 = \frac{.3843}{R_M \times F_M} \times 1,000,000 \quad L3 = \frac{.2617 \times R_M}{F_M} \times 1,000$$

$$C4 = \frac{.5834}{R_M \times F_M} \times 1,000,000 \quad L4 = \frac{1.423 \times R_M}{F_M} \times 1,000$$

$$C5 = \frac{.0728}{R_M \times F_M} \times 1,000,000 \quad L5 = \frac{.0939 \times R_M}{F_M} \times 1,000$$

$$C6 = \frac{.0162}{R_M \times F_M} \times 1,000,000 \quad L6 = \frac{.0445 \times R_M}{F_M} \times 1,000$$

$$C7 = \frac{.2523}{R_L \times F_L} \times 1,000,000 \quad L7 = \frac{.2987 \times R_L}{F_L} \times 1,000$$

$$C8 = \frac{.0567}{R_L \times F_L} \times 1,000,000 \quad L8 = \frac{.1502 \times R_L}{F_L} \times 1,000$$

C = capacitor, L = coil, R_H = tweeter impedance,
 R_M = midrange impedance, R_L = woofer impedance,
 F_H = upper crossover frequency, F_L = lower crossover
frequency, F_M = square root ($F_H \times F_L$)