



FIG. 1—STEREO HEADPHONE ADAPTER has meter and control for balancing the amplifiers' output and the signal to the phones. A mixing circuit can be used to "fill the hole in the middle."

