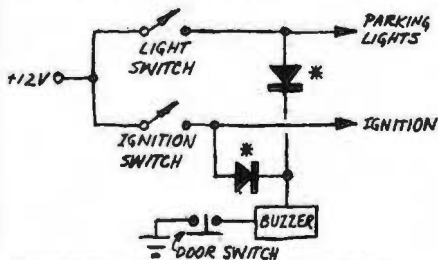


## NO-KEY IGNITION TURN-ON

Anyone who incorporates Mr. Reckling's "Auto Lights Warning Buzzer" (Tips & Techniques, March 1975) in his vehicle will be in for a real surprise when he tries to switch off the engine with the lights on. Examination of the circuit indicates that, with the diode connected as shown, the ignition switch will be bypassed by the light switch through the added diode. This circuit will allow the engine to be started without using an ignition key.

The way to obtain a properly operating



\*FOR POSITIVE-GROUND, REVERSE DIODES.

circuit is to use two diodes in an OR-gate arrangement as shown in my schematic.

DUBY D. TODD  
Grissom AFB, IN