

Although transistor ignition has been available for many years now, there are still millions of cars that have not been provided with the advantages of a complete solid-state ignition system. The solid-state ignition described in this article will give long and reliable service and will also extend the useful life of your spark plugs appreciably.

SOLID-STATE IGNITION

by
Hans Steeman

A full solid-state ignition system has many advantages over conventional systems. It will, for instance:

- enable the engine to be started readily, whether this is cold, wet, or hot — provided your battery is in good condition, of course;
- ensure that even a cold or damp engine continues to run once it has been started;
- ensure that the spark energy is constant and independent of the engine speed;
- considerably reduce carbon deposit on the spark-plug electrodes, thus allowing longer intervals between cleaning and replacement of the plugs.


A comparison

Fig. 1 shows a conventional coil ignition system as used in most petrol engines. The contact breaker points are controlled by the distributor cam: when they open, the current flowing through the primary winding of the coil is interrupted, which causes a high potential to be induced across the secondary winding. This voltage is high enough (10 to 15 kV) to ignite the compressed charge of air and petrol vapour in the


engine cylinder via the spark-plug. The distributor ensures that the high tension is applied to only one cylinder at a time. The distributor is driven by the engine at half engine speed.

In the solid-state ignition system the function of the contact breaker points is transferred to a transistor switch: the points merely serve to trigger the transistor. Because of the consequent appreciable reduction

in current flowing across the points, these become virtually free of wear. The timing diagrams in Fig. 2 show the differences between the ignition pulses generated in the two systems. When the points in the coil ignition system are closed, no current flows through the primary of the coil. Note the overshoot and ringing occurring at the secondary immediately after the points have closed. These phenomena are caused by stray

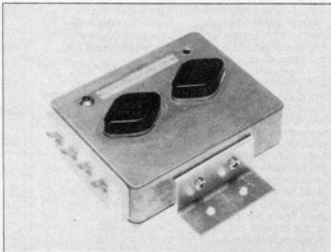

1a

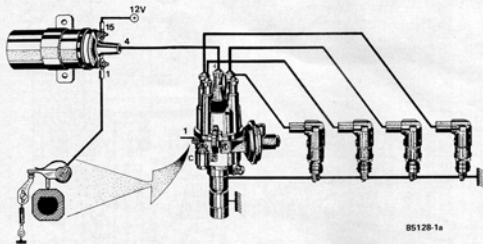

1b


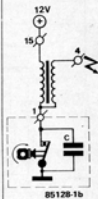


Fig. 1. Conventional coil-ignition system for petrol engines.

Fig. 2. Timing diagrams of coil ignition (left) and solid state ignition (right).

2

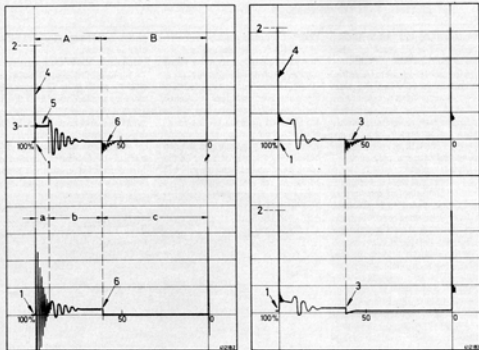

- 1 points open
- 2 ignition voltage
- 3 firing voltage
- 4 peak secondary voltage
- 5 firing voltage level
- 6 points close

- A points open period
- B points closed period
- a spark duration
- b points open period
- c points closed period

- 1 ignition period starts; transistor switched off
- 2 sparking voltage; zener voltage
- 3 transistor switches on
- 4 peak secondary voltage

85128-2

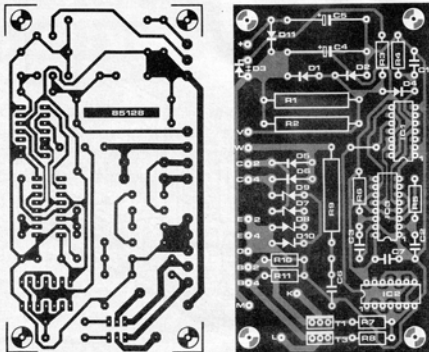


Fig. 4. The printed-circuit board for the solid-state ignition system.

Parts list

Resistors:

- $R_1, R_2 = 100 \text{ } \Omega$, 5 W
 $R_3 = 680 \text{ } \Omega$
 $R_4 = 47 \text{ k}$
 $R_5 = 56 \text{ k}$
 $R_6 = 1 \text{ M}$
 $R_7, R_8 = 220 \text{ } \Omega$
 $R_9 = 1 \text{ } \Omega$, 5 W
 $R_{10}, R_{11} = 8.2 \text{ } \Omega$
 $R_{12}, R_{13} = 47 \text{ } \Omega$, 5 W

Capacitors:

- $C_1 = 10 \text{ n}$
 $C_2 = 33 \text{ n}$
 $C_3 = 470 \text{ n}$
 $C_4 = 220 \mu\text{F}$, 16 V
 $C_5 = 220 \mu\text{F}$, 25 V
 $C_6 = 4.7 \text{ n}$, 630 V
 $C_7 = 100 \text{ n}$

Semiconductors:

- $D_1, D_2, D_4, D_{11} = 1\text{N}4001$
 $D_3 = \text{LED}$; red
 $D_5, D_6 = 1\text{N}5406$
 D_7 to $D_{10} = \text{zener diode } 200 \text{ V}, 1 \text{ W}$
 $T_1, T_3 = \text{BD}437$
 $T_2, T_4 = \text{BUX}20$
 $IC_1 = 4093$
 $IC_2 = 4069$
 $IC_3 = 4538$

Miscellaneous:

- Heat sinks for two TO-3 transistors; not required if a die-cast aluminium box is used
 Insulating plates — preferably Teflon — for mounting the power transistors
 2.5 mm² stranded wire as required
 4 car-type male terminals and mating receptacles for fitting with M3 size self-tapping screws
 four insulating bushes for use with M3 size screws
 metal — preferably die-cast — case 120 x 95 x 30 mm; if a die-cast case cannot be obtained, use thick aluminium sheet
 PCB 8512B

text the power stages from negative pulses and over-voltages.

Monostable MMV₂ is triggered by the output pulses of MMV₁ and generates for each of these a pulse of about 0.5 s at its Q output (pin 10). The duration of this pulse is determined by the time constant R_6C_4 . The pulse ensures that gate N₂ remains open to accept control pulses. When the engine stops, the contact breaker no longer provides control pulses, and the gate closes after

0.5 s. This ensures that the ignition coil cannot burn out when the engine is not running. In that condition, parallel-connected resistors R₁ and R₂ allow a current of about 250 mA to prevent the contact breaker points from corroding.

Construction

When the printed-circuit board — see Fig. 4 — which is available

through our Readers' services, is used, no construction problems are envisaged.


Collector resistors R₁₀ and R₁₃ get quite hot and must, therefore, be glued onto the inside of the lid of the metal case.

The remainder of the construction should broadly follow the lines suggested in Fig. 5. If you cannot get a cast enclosure, fit the power transistors on suitable heat sinks. Do not skimp on the heat conducting paste! Before the ignition is fitted into the vehicle, it should be checked with an ohmmeter to make absolutely certain that it is free of short-circuits.

As shown in Fig. 5, one of the sides of the enclosure should be provided with four insulated car-type male terminals onto which the interconnecting cables are push-fitted by means of mating receptacles. These male and female connectors are available from most motorists' shops. It is advisable to fit the receptacles with insulating sleeves.

The case should be fitted under the bonnet in a position where it is reasonably well protected from water ingress.

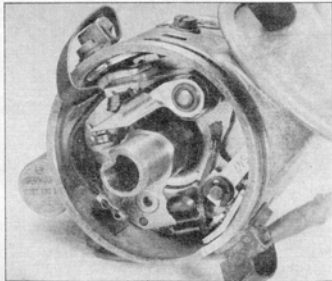It should normally not be necessary to alter the ignition timing. This timing can be checked roughly with the aid of diode D₁, which should light when the points are closed. However, if in any doubt, the timing



5


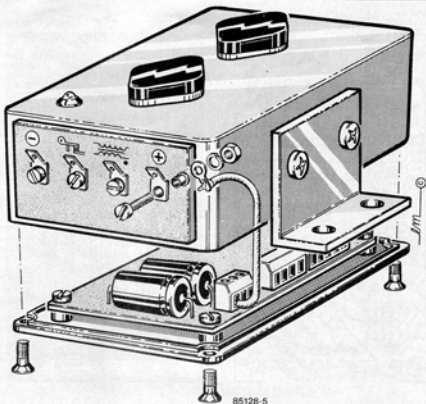
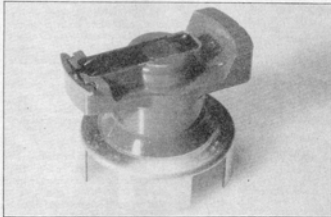


Fig. 5. Artist's impression of how the solid-state ignition system may be constructed and housed.

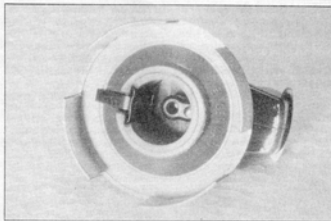

should be checked properly with a stroboscope with the engine turning over at constant speed.

In some cars, a resistor is connected in series with the ignition coil. This resistor, which is shorted out when the engine is started, must not be removed. Apart from the connection to terminal 1 of the coil, i.e. that to the contact breaker, all wiring in the car remains as before. If the car is fitted with a revolution counter, this should remain connected to terminal 1 of the ignition coil. **M**

FINALLY A WARNING: WHEN THE ENGINE IS RUNNING DO NOT UNDER ANY CIRCUMSTANCES TOUCH THE TERMINALS OR COMPONENTS OF THE IGNITION SYSTEM, BECAUSE THE HIGH TENSION PRESENT AT VARIOUS PLACES MAY BE FATAL.