

# Choose the right f.e.t.

Blind use of any old f.e.t. can result in disastrous circuit performance and possibly catastrophic failure of a device. These notes should help you select an appropriate device for the six applications illustrated.

by T. Jones

Siliconix Ltd

## Constant current source

In one of the lesser-used applications, the f.e.t. approaches the ideal current source. Operation in the pinch-off (see Fig. 1) region results in virtually-constant  $I_D$  for large variations in  $V_{DS}$  and constant  $V_{GS}$ . This is due to the low output conductance ( $g_{OSS}$ ) of the f.e.t. defined by  $\Delta I_D / \Delta V_{DS}$ . It is related to the more commonly used term "dynamic impedance" ( $Z_D$ ) of a current source by  $Z_D = 1/g_{OSS}$ . For good regulation  $g_{OSS}$  should be as low as possible.

Fig. 2 shows a basic current source. Resistor  $R_S$  is used to set the value of  $V_{GS}$  and thus the value of constant  $I_D$ . For a given  $I_D$ , the required value of  $V_{GS}$  is

$$V_{GS} \approx V_p \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

which enables  $R_S$  to be calculated from  $R_S = V_{GS} / I_D$ .

If  $R_S$  is made variable, a wide range of  $V_p$  and  $I_{DSS}$  values can be accommodated provided  $I_{DSS} < I_D$ . However, if a nominal  $I_D$  is required and trimming of  $R_S$  is not practical, choose an f.e.t. with small "data sheet" spreads of  $V_p$  and  $I_{DSS}$ .

The resultant dynamic impedance of Fig. 2 is

$$Z_D = \frac{1 + R_S g_{fs}}{g_{OSS}}$$

and therefore high  $g_{OSS}$  devices are desirable.

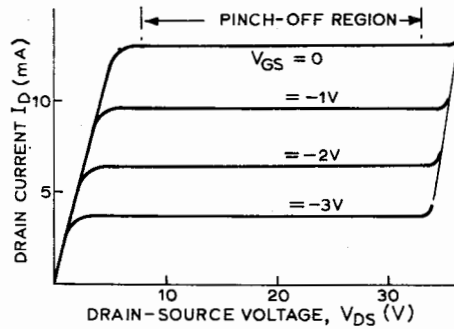


Figure 1

Another requirement for good regulation is that the drain-to-source voltage  $V_{DS}$  is maintained above the pinch-off voltage, otherwise  $g_{OSS}$  will be greatly increased (and dynamic impedance reduced). Ideally  $V_{DS}$  should be at least twice the value of  $V_p$ . Therefore, for correct operation the total voltage across the f.e.t. and  $R_S$  should be a minimum of  $2V_p + V_{GS}$ .

In certain circumstances the permitted voltage drop across the current source may be limited. If so, choose an f.e.t. with a low  $V_p$ .

 


Figure 2

 


Figure 3

Fig. 3 shows an improved current source using two cascaded f.e.t.s. The resulting dynamic impedance is

$$Z_D = \frac{g_{fs1}(1 + R_S g_{fs2})}{g_{OSS1} g_{OSS2}}$$

## Analogue switch

Figure shows an n-channel junction f.e.t. in a basic analogue switch configuration. The on-resistance  $r_{DS}$  should be as low as possible if a significant error in the sampled voltage is to be avoided. The error due to  $r_{DS}$  (at low frequency) is

$$e_{in} \frac{R_S + r_{DS}}{R_S + R_L + r_{DS}}$$

where  $R_S$  is the signal source impedance and  $R_L$  the load impedance.

In the off condition, the f.e.t. exhibits a certain amount of drain-to-source leakage

current ( $I_{Doff}$ ) which gives rise to an error voltage developed across  $R_L$ . The error due to  $I_{Doff}$  at low frequency is  $I_{Doff} \cdot R_L$ . For this reason,  $I_{Doff}$  must be correctly specified.

 


Figure 4

To turn the f.e.t. off, the gate must be driven negative with respect to the source by at least the value of  $V_p$ . Thus the required drive voltage is

$$V_{G(min)} = V_p + V_{analogue(pk)}$$

If the available drive voltage is limited, use low  $V_p$  devices.

### Voltage-controlled resistor

Where operated with very low values of  $V_{DS}$ , f.e.t.s exhibit predictable changes in  $R_{DS}$  for given changes in  $V_{GS}$ . Under such conditions, f.e.t.s can be considered as a resistor whose value is determined by the value of the applied  $V_{GS}$ . Hence the term voltage-controlled resistor.

This characteristic makes the f.e.t. an ideal candidate for potential divider, attenuator and a.g.c. applications. Circuit shows an n-channel junction device used in a basic potential divider. Here, the  $R_{DS}$  should be significantly lower than  $R_L$ . The  $R_{DS}$  can be defined as  $R_{DS0}/(1 - V_{GS}/V_p)$ , where  $R_{DS0} = R_{DS}$  at  $V_{GS} = 0$ .

As can be seen in the graph, the output characteristics are extremely linear in the

 


Figure 5

region  $|V_{DS}| \ll |V_p|$ . This bilateral characteristic can be used to advantage for the a.g.c. of low-level a.c. signals. If, however,  $V_{DS}$  exceeds  $0.1V_p$ , the output characteristics become markedly non-linear.

 


Figure 6

### Low frequency amplifier

Under normal amplifier operation, the gate/source junction is a reverse-biased diode which presents a high impedance to the input signal. It is this high input impedance which makes the f.e.t. superior to its bipolar counterpart if loading of the input signal is to be avoided. The input impedance can be characterized by the gate current  $I_G$  which should be specified at the  $V_{DG}$  and  $I_D$  required for normal operation.

Circuit shows the basic common-source amplifier. The gain is

$$\frac{g_{fs} \cdot R_L}{1 + g_{fs} \cdot R_S}$$

and if  $R_S$  is decoupled at the frequencies in question by a suitable capacitor, it becomes  $\approx g_{fs} R_L$ .

Graph shows a typical transfer characteristic. As  $g_{fs}$  is the slope of the characteristic at any given point,  $g_{fs}$  is a maximum when  $V_{GS} = 0$ . The  $g_{fs}$  at any other point on the curve can be found from  $g_{fs} = g_{fs0}(1 - V_{gs}/V_p)$  or  $g_{fs0}/\sqrt{I_{DSS}/I_D}$ , where  $g_{fs0} = g_{fs}$  at  $V_{gs} = 0$  and  $I_{DSS} = I_D$  at  $V_{gs} = 0$ .

Drain current decreases with increasing temperature by approximately 0.7% degC. This phenomenon can result in undesirable

 


Figure 7

variations in stage gain. Fortunately, this drift can be minimized by another effect which causes the effective  $V_{GS}$  to decrease by approximately 2.2mV/degC. This latter phenomenon causes  $I_D$  to increase with increasing temperature. Minimal d.c. drift will occur at the point where the two effects cancel each other. This point can be defined as  $I_{DZ} = I_{DSS}(0.63/V_p)^2$ , where  $I_{DZ} = I_D$  for zero d.c. drift. High- $V_p$  devices must be biased to low values of  $I_D$ , with a resultant drop in  $g_{fs}$ .

For low-noise applications, care should be taken in specifying the noise performance of the device. The major contribution of noise is from  $1/f$  noise. This is normally characterized by manufacturers as "en" (short-circuit equivalent noise voltage in  $nV/\sqrt{Hz}$ ) at various spot frequencies. However, for high signal-source impedances, the effect of noise current ( $i_n$ ) becomes significant; since, at low frequencies,  $i_n$  is a function of gate leakage current, low  $I_G$  is desirable. Both  $i_n$  and  $I_G$  should be specified at the operating values of  $V_{DS} + I_D$ .

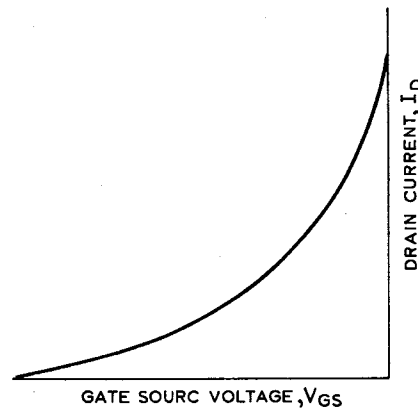


Figure 8

### Electrometer circuit

The high input impedance of the f.e.t. makes it the ideal choice for electrometer applications. The basic electrometer circuit shown uses two and an inexpensive operational amplifier. Transistor  $Tr_1$  is a source follower with  $Tr_2$  acting as a dynamic source impedance. Resistor  $R_f$  sets the measuring range and  $R_1$  through  $R_3$  provide intermediate scaling. Choose  $Tr_1$  to have low  $I_{GSS}$ , and the  $I_{DSS}$  of  $Tr_1$  and  $Tr_2$  to be matched as closely as possible; although  $R_4$  will null some mismatch in addition to nulling the offset of the op-amp. Typically,  $Tr_1$  and  $Tr_2$  would be a dual f.e.t.

The value of the feedback resistor ( $R_f$ ) is the reciprocal of the measuring range, with a scaling factor of unity.

 


Figure 9

## Differential amplifier

The circuit below uses three junction devices in a differential amplifier configuration. The  $I_{DSS}$ ,  $g_{fs}$  and  $V_{GS}$  of  $Tr_1$  and  $Tr_2$  should be matched as closely as possible; the  $V_{GS}$  match should be specified at the operating value of  $I_D$ . If good matching is ensured, the gain is

$$\frac{g_{fs}R_L}{1 + g_{os}R_L}$$

Using low  $g_{os}$  devices, this approximates to  $g_{fs}R_L$ .

In practice,  $Tr_1$  and  $Tr_2$  may be either a matched pair of discrete devices or a dual f.e.t. Dual f.e.t.s tend to be cheaper than their matched-pair equivalent and, with the increasing use of monolithic duals, are inherently more reliable. Also, with the two semiconductor elements in close proximity in the same package, either two-chip or monolithic, thermal behaviour is more predictable.

 


Figure 10

The common-mode gain of the differential stage is approximately

$$\frac{g_{fs}R_L}{1 + 2Z_Sg_{fs}}$$

assuming perfect matching of the f.e.t.s and load resistors, and where  $Z_S$  is the source impedance.

Therefore inclusion of  $Tr_3$  as a current source presenting a high dynamic source impedance greatly reduces the common-mode gain. The minimum  $I_{DSS}$  of  $Tr_3$  must be the sum of  $Tr_1$  and  $Tr_2$  bias currents.

### Further reading

Siliconix application notes Field Effect Transistor Current Source, by J. S. Sherwin  
FETs As Analogue Switches, by Shelby Givens  
Biasing FETs For Zero D.C. Drift, by Lee L. Evans