

FET

PRINCIPLES AND CIRCUITS

Field-Effect Transistors

by Ray Marston

Part 1

Ray Marston explains FET (Field-Effect Transistor) basics in this opening episode of this new four-part series.

Field-Effect Transistors (FETs) are unipolar devices, and have two big advantages over bipolar transistors: one is that they have a near-infinite input resistance and thus offer near-infinite current and power gain; the other is that their switching action is not marred

by charge-storage problems, and they thus outperform most bipolars in terms of digital switching speeds.

Several different basic types of FETs are available, and this opening episode looks at their basic operating principles. Parts 2 to 4 of the series will show practical ways

of using FETs.

FET BASICS

An FET is a three-terminal amplifying device. Its terminals are known as the source, gate, and drain, and correspond respectively to the emitter, base, and collector of a normal

transistor. Two distinct families of FETs are in general use. The first of these is known as 'junction-gate' types of FETs; this term generally being abbreviated to either JUGFET or (more usually) JFET.

The second family is known as either 'insulated-gate' FETs or Metal Oxide Semiconductor FETs, and these terms are generally abbreviated to IGFET or MOSFET, respectively. 'N-channel' and 'p-channel' versions of both types of FET are available, just as normal transistors are available in npn and pnp versions. Figure 1 shows the symbols and supply polarities of both types of bipolar transistor, and compares them with both JFET versions.

Figure 2 illustrates the basic construction and operating principles of a simple n-channel JFET. It consists of a bar of n-type semiconductor material with a drain terminal at one end and a source terminal at the other. A p-type control electrode or gate surrounds (and is joined to the surface of) the middle section of the n-type bar, thus forming a p-n junction.

In normal use, the drain terminal is connected to a positive supply and the gate is biased at a value that is negative (or equal) to the source voltage, thus reverse-biasing the JFET's internal p-n junction, and accounting for its very high input impedance.

With zero gate bias applied, a current flow from drain to source via a conductive 'channel' in the n-type bar is formed. When negative gate bias is applied, a high resistance region is formed within the junction, and reduces the width of the n-type conduction channel and thus reduces the magnitude of the drain-to-source current. As the gate bias is increased, the 'depletion' region spreads deeper into the n-type channel, until eventually, at some 'pinch-off' voltage value, the depletion layer becomes so deep that conduction ceases.

Thus, the basic JFET of Figure 2 passes maximum current when its gate bias is zero, and its current is reduced or 'depleted' when the gate bias is increased. It is thus known as a 'depletion-type' n-channel JFET. A p-channel version of the device can (in principle) be made by simply transposing the p and n materials.

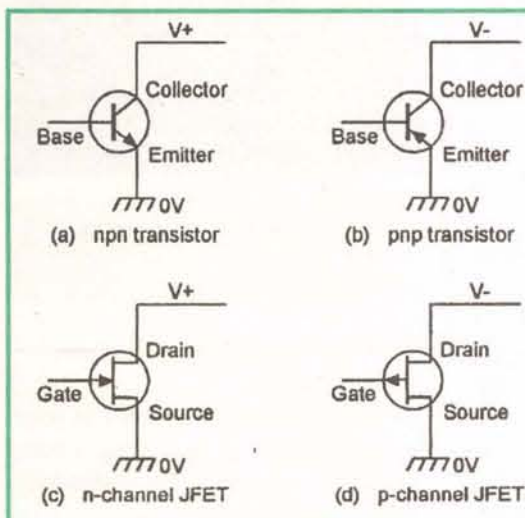


Figure 1. Comparison of transistor and JFET symbols, notations, and supply polarities.


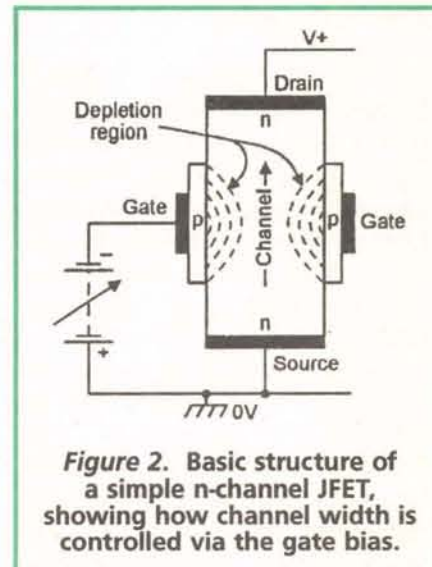


Figure 2. Basic structure of a simple n-channel JFET, showing how channel width is controlled via the gate bias.

EASILY ADD TEXT TO VIDEO WITH BOB-II

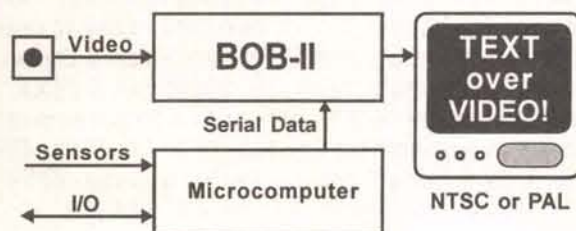- Auto-switching genlock overlay module
- Generates complete video signal on-board
- Up to 308 characters in 11 rows, 28 cols
- Fast 'RS-232' serial control (2400-19.2kbps)
- Small footprint; only 3.50" by 1.05"
- Developer board now available (BNAB)
- Compatible with Parallax™ BASIC Stamp™



Only \$79.95 ea. (NTSC qty. 1-9)



DECADE ENGINEERING
Tel: 503.743.3194 ~ Fax: 503.743.2095
www.decadenet.com

PRINTED CIRCUIT BOARDS

Since 1969

Prototype to Production
Quick • Quality • Service • Price

- Single Sided
- Double Sided
- Multi-Layer
- Surface Mount
- Punch Press Capability
- LPI

QUICK TURN AROUND
COMPLETE IN-HOUSE CAPABILITY

CIRCUIT ETCHING TECHNICS

Since 1969

700 Lee Street
Elk Grove Village
Illinois 60007

Phone: 847-228-1722
Fax: 847-228-1816
Modem: 847-228-6549
Toll Free: 888-657-3827

E-MAIL — CET@MET-NET.COM
WEB ADDRESS —
WWW.MET-NET.COM/USERS/CET

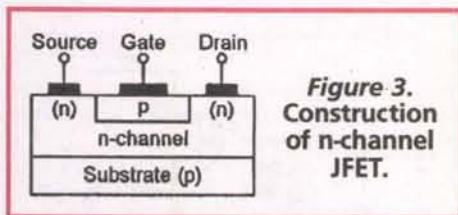


Figure 3.
Construction
of n-channel
JFET.

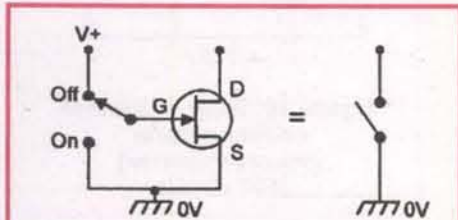


Figure 6. An n-channel
JFET can be used as a
voltage-controlled switch.

JFET DETAILS

Figure 3 shows the basic form of construction of a practical n-channel JFET; a p-channel JFET can be made by transposing the p and n materials. All JFETs operate in the depletion mode, as already described. Figure 4 shows the typical transfer characteristics of a low-power n-channel JFET, and illustrates some important features of this type of device. The most important characteristics of the JFET are as follows:

(1). When a JFET is connected to a supply with the polarity shown in Figure 1 (drain +ve for an n-channel FET, -ve for a p-channel FET), a drain current (I_D) flows and can be controlled via a gate-to-source bias voltage V_{GS} .

(2). I_D is greatest when $V_{GS} = 0$, and is reduced by applying a reverse bias to the gate (negative bias in an n-channel device, positive bias in a p-type). The magnitude of V_{GS} needed to reduce I_D to zero is called the 'pinch-off' voltage, V_p , and typically has a value between 2 and 10 volts. The magnitude of I_D when $V_{GS} = 0$ is denoted I_{DSS} , and typically has a value in the range 2 to 20mA.

(3). The JFET's gate-to-source junction has the characteristics of a silicon diode. When reverse-biased, gate leakage currents (I_{GSS}) are only a couple of nA ($1\text{nA} = .001\mu\text{A}$) at room temperature. Actual gate signal currents are only a fraction of an nA, and the input impedance of the gate is typically thousands of megohms at low frequencies. The gate junction is shunted by a few pF, so the input impedance falls as frequency rises.

If the JFET's gate-to-source junction is forward-biased, it conducts like a normal silicon diode. If it is excessively reverse-biased, it avalanches like a zener diode. In either case, the JFET suffers no damage if gate currents are limited to a few mA.

(4). Note in Figure 4 that, for each V_{GS} value, drain current I_D rises linearly from zero as the drain-to-source voltage (V_{DS}) is increased from zero up to some value at which

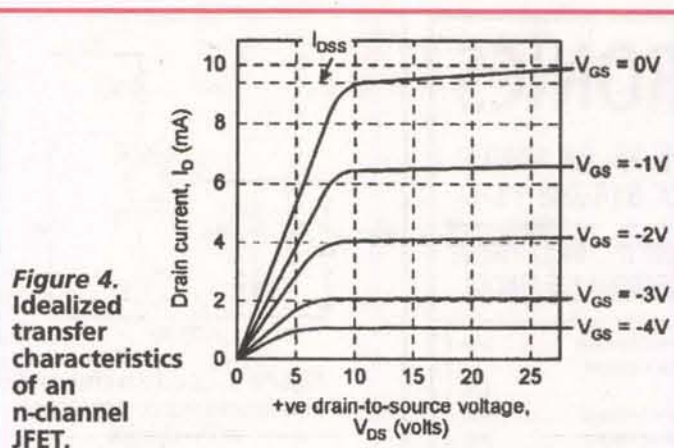


Figure 4.
Idealized
transfer
characteristics
of an
n-channel
JFET.

a 'knee' occurs on each curve, and that I_D then remains virtually constant as V_{DS} is increased beyond the knee value. Thus, when V_{DS} is below the JFET's knee value, the drain-to-source terminals act as a resistor, R_{DS} , with a value dictated by V_{GS} , and can thus be used as a voltage-variable resistor, as in Figure 5.

Typically, R_{DS} can be varied from a few hundred ohms (at $V_{GS} = 0$) to thousands of megohms (at $V_{GS} = V_p$), enabling the JFET to be used as a voltage-controlled switch (Figure 6) or as an efficient 'chopper' (Figure 7) that does not suffer from offset-voltage or saturation-voltage problems.

Also note in Figure 4 that when V_{DS} is above the knee value, the I_D value is controlled by the V_{GS} value and is almost independent of V_{DS} , i.e., the JFET acts as a voltage-controlled current generator. The JFET can be used as a fixed-value current generator by either tying the gate to the source as in Figure 8(a), or by applying a fixed negative bias to the gate as in Figure 8(b). Alternatively, it can (when suitably biased) be used as a voltage-to-current signal amplifier.

(5). FET 'gain' is specified as

transconductance, g_m , and denotes the magnitude of change of drain current with gate voltage, i.e., a g_m of 5mA/V signifies that a V_{GS} variation of one volt produces a 5mA change in I_D . Note that the form I/V is the inverse of the ohms formula, so g_m measurements are often expressed in 'mho' units. Usually, g_m is specified in FET data sheets in terms of mmhos (milli-mhos) or μmhos (micro-mhos). Thus, a g_m of 5mA/V = 5-mmho or 5000- μmho .

In most practical applications, the JFET is biased into the linear region and used as a voltage amplifier. Looking at the n-channel JFET, it

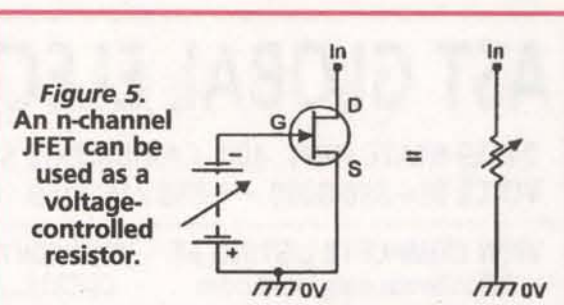


Figure 5.
An n-channel
JFET can be
used as a
voltage-
controlled
resistor.


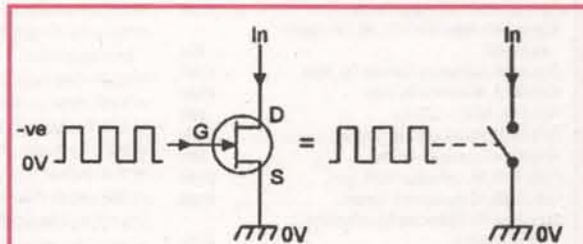


Figure 7. An n-channel JFET can be used as an electronic chopper.

can be used as a common source amplifier (corresponding to the bipolar npn common emitter amplifier) by using the basic connections in Figure 9.

Alternatively, the common drain or source follower (similar to the bipolar emitter follower) configuration can be obtained by using the connections in Figure 10, or the common gate (similar to common base) configuration can be obtained by using the basic Figure 11 circuit. In

Figure 8. An
n-channel JFET
can be used as a
constant-current
generator.

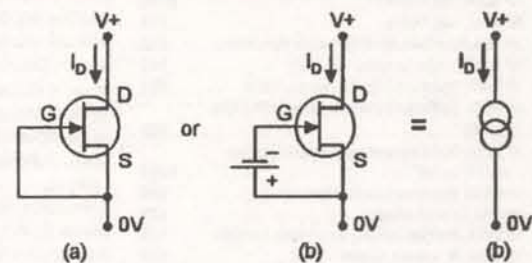

BIG POWER LOW COST



Dominos are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominos are true plug-and-go control.

Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware dock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**

Micromint, Inc

740 Florida Central Pkwy., Longwood, FL 32750
(407) 262-0066

plug-ins
test sets
counters
generators
oscilloscopes
power supplies
spectrum analyzers
& much more!

www.levylatham.com
PRIVATE MARKETERS OF U.S. GOVERNMENT MILITARY SURPLUS ASSETS

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
 VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
 QUICKLY ... AT REASONABLE PRICES.

Advantest RS372P, Microwave Power Meter	\$1,700	HP 6299A, Power Supply, 0-40V @ 1.5A (metered)	\$175
Boonton 4200, Power Meter w/6E, /4E-S/21, Sensor and Manual	\$750	HP 6294A, Power Supply, 0-60V @ 1A (metered)	\$275
Fluke 5100B, Multifunction Calibrator, Opt. 03/05	\$2,800	New in box w/manual	\$275
Fluke 5100B, Multifunction Calibrator	\$2,400	HP 6299A, Power Supply, 0-100V @ 75A Metered	\$225
Fluke 515A, Portable Calibrator	\$750	HP 6428B, Power Supply, 0-20V @ 0-45A Metered	\$550
Fluke 5200A, Programmable AC Calibrator	\$1,000	HP 651B, Test Oscillator, 10Hz-10MHz	\$125
Fluke 5215A, Precision Power Amp	\$800	HP 652B, Test Oscillator, 10Hz-10MHz	\$125
Fluke 5440B, DC Calibrator, 0-1100V, 3ppm	\$2,900	HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator	\$225
Fluke 5790A, AC Measurement Standard	\$9,500	HP 6626A, Bipolar Power Supply/Amp $\pm 50V @ \pm 1A$	\$475
Fluke 6060A/AN, Synthesized Signal Generator, 100KHz-1050MHz	\$1,750	HP 8116A, Programmable Pulse/Function Generator, 50MHz	\$2,400
Fluke 6070A, Synthesized RF Signal Generator, 200KHz-520MHz	\$1,400	HP 8165A, Programmable Sig Source, 1mHz-50MHz	\$950
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack	\$145	HP 8165A, Programmable Pulse Generator, 50MHz, Opt. 002	\$1,100
Fluke 8050A, DMM 4-1/2 Digit w/o Battery Pack	\$145	HP 8350A, Spectrum Analyzer Mainframe	\$800
Fluke 8840A, DMM 5-1/2 Digit w/GPIB	\$375	HP 8350B, Spectrum Analyzer Mainframe	\$1,100
Gigatronics 600, Frequency Synthesizer, 6-12GHz	\$950	HP 853A, Spectrum Analyzer Mainframe	\$750
Gigatronics 600, Frequency Synthesizer, 10-18GHz	\$950	HP 853A, Spectrum Analyzer, w/8558B, 1-1500MHz	\$1,800
Gigatronics 6061A, Synthesized Signal Generator, 10KHz-1050MHz	\$2,200	HP 853A, Spectrum Analyzer, w/8559A, 0.1-21GHz	\$2,200
Gigatronics 8541, Power Meter	\$1,400	HP 86222A, RF Plug-In, 0.1-2.4GHz, NICE1	\$850
HP 105B, Quartz Oscillator	\$525	HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003	\$1,800
HP 141T, Spectrum Analyzer Mainframe	\$375	HP 8640B, Signal Generator, 5-512MHz, Opt. 001 or 003	\$700
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz	\$1,100	HP 8656A, Synthesized Signal Generator, 100KHz-990MHz	\$1,400
		HP 8657A, Synthesized Signal Generator, Opt. 002, 100KHz-1040MHz, Readout	\$2,500
		HP 8672A, Frequency Synthesizer, 2-18GHz	\$3,500
		HP 8730A, Opt. IC2, IF7, 8ZE, Tuner Analyzer, 300KHz-1300MHz w/87030A 10MHz-100MHz Tuner Test Set	\$3,400
		HP 8901A, Modulation Analyzer, Opt. 004	SPECIAL \$650
		HP 8901A, Modulation Analyzer, Opt. 001/003/010	\$850
		HP 8901A, Modulation Analyzer, Opt. 001/002/003/010	\$950
		HP 8901B, Modulation Analyzer, 150KHz-1300MHz, Opt. 004	\$1,800
		Kikusui COS6100m, (100MHz) 5 Channel 12 Trace Scope	\$299
		Lambda LLS9040, Digital Power Supply, 0-40V @ 20A	\$725
		Marconi 218, Signal Generator, 80KHz-520MHz NICE1	\$850
		Racal Dana 1991, Counter/Timer, 2 Channel	\$275
		Racal Dana 1992, Counter/Timer, 1GHz	\$375
		Sencore CM2000, Computer Analyzer	SPECIAL \$1,400
		Sencore LC102, Capacitor/Inductor Analyzer	\$950
		Sorenson DCR10-120B, Power Supply, 0-10V @ 120A	SPECIAL \$650
		Sorenson DCR40-125A, Power Supply, 0-40V @ 125A	SPECIAL \$950
		Sorenson DCR-80-5A, Power Supply, 80V @ 5A (metered)	\$375
		Sorenson SRL10-100, Power Supply, 0-10V @ 100A	SPECIAL \$500
		Sorenson SRL20-40, Power Supply, 0-20V @ 40A	SPECIAL \$500
		Tegam M1011A-11, Ratio Standard, UNUSED	\$375
		Tek TM504, Power Module, 4 Slot	\$150
		Tek TM506, Power Module, 6 Slot	\$200
		Tek TR503, Plug-In Tracking Generator, 100KHz-1.8GHz	\$575
		Tek 11201A, Digitizing Touch Screen Scope (400MHz) w/Tek LC 100 Printer	\$1,299
		Tek 2235, Scope (100MHz) Dual Trace	\$650
		Tek 2236, Scope (100MHz) w/Counter/Timer/DMM	\$850
		Tek 2246, Scope (100MHz) 4-Channel Cursor RO	SPECIAL \$1,200
		Tek 2247A, Scope (100MHz) Dual Trace w/Counter/Timer/Voltmeter	SPECIAL \$1,400
		Tek 2336, Scope (100MHz) Dual Trace	SPECIAL \$525
		Tek 2430A, Digital Scope (150MHz) w/manuals & probe, NICE1	\$2,200
		Tek 2445, Scope (150MHz), 4-Channel Cursor Readout	\$1,100
		Tek 2445A, Scope (150MHz), 4-Channel Cursor Readout	\$1,400
		Tek 2465, Scope (300MHz), 4-Channel Cursor Readout	\$1,400
		Tek 453, Scope (60MHz), Dual Trace	\$175
		Tek 465, Scope (100MHz), Dual Trace	\$425
		Tek 465B, Scope (100MHz), Dual Trace	\$475
		Tek 466, Scope (100MHz storage), Dual Trace	\$575
		Tek 475, Scope (200MHz), Dual Trace	\$475
		Tek 475A, Scope (250MHz), Dual Trace	\$625
		Tek 485, Scope (350MHz), Dual Trace	\$700
		Tek 492, Spectrum Analyzer, 50KHz-21GHz, Opt. 1,2,3	\$4,500
		Tek 520A, NTSC Vectorscope	\$400
		Tek 576, Curve Tracer	SPECIAL \$1,400
		Tek 7104, Scope (1GHz), Dual Trace	\$1,200
		Tek 7104, Scope (1GHz) w/7A29, 7A29, 7B10 & 7B15	\$2,200
		Tek 7844, Scope (dual beam) w/7A24, 7A26, 7B80 & 7B87	\$750
		Unifron CRO54-3, Power Frequency Converter, 50/60Hz-400Hz, 5KV, LESS THAN 100 HOURS, LIKE NEW	\$1,200
		Wavetek 145, Pulse/Function Generator, .0001-20MHz	\$300
		Wavetek 270, Function Generator, .01Hz-12MHz	\$675
		Wavetek 288, Synthesized Function Generator, 20Hz-20MHz (unused)	\$800
		Wavetek 442, Dual HiLo Filter, 1Hz-10KHz	\$400
		Wiltron 54107A, Scaler Measurement System, 1MHz-1500MHz	\$3,500
		Wiltron 6637A, Programmable Sweep Generator, 2-18.6GHz	\$1,900

**TURN IDLE TEST EQUIPMENT
 — INTO CASH —
 CALL OR FAX FOR QUOTATION**

HP 141T, Spectrum Analyzer w/8552B/8556A, 20Hz-300KHz	\$1,000
HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz	\$1,600
HP 141T, Spectrum Analyzer w/8552B/8555A, 10MHz-18GHz	\$1,800
HP 1630G, Logic Analyzer w/pods	\$575
HP 1633A, Logic Analyzer	\$2,000
HP 1651A, Logic Analyzer	\$875
HP 214B, Pulse Generator, 200W Pulse/50 ohms, 10MHz	\$625
HP 3312A, Function Generator, 1Hz-13MHz	\$425
HP 3325A, Synthesized Function Generator, 21MHz	\$650
HP 3325A, Synthesized Function Generator, HP1B, 21MHz, Opt. 002	\$825
HP 3326A, DC-13MHz Synthesized Function Generator 40V P-P, Opt. 002	\$3,400
HP 3336C, Synthesizer Level Generator	\$950
HP 334A, Distortion Analyzer	\$275
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V	\$125
HP 3406A, RF Voltmeter, 50uV-3V, 1.2GHz	\$200
HP 3455A, DMM 5-1/2 Digit	\$250
HP 3456A, DMM 6-1/2 Digit	\$475
HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function	\$175
HP 3488A, Switch Control	\$325
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz	\$500
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout	\$650
HP 3730B, Down Converter Mainframe	\$625
HP 400EL, AC Voltmeter, 10Hz-10MHz	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V	\$175
HP 415E, SWR Meter	\$100
HP 432A, Power Meter w/Cable/847B, .01-18GHz Sensor	\$350
HP 436A, Power Meter w/Opt. 022 HP1B	\$650
HP 436A, Power Meter	\$450
HP 4972A, LAN Protocol Analyzer	\$750
HP 4972A, LAN Protocol Analyzer w/software, Opt. 002/005	\$750
HP 5315B, Counter, 100MHz, Opt. 001, w/Manual, NICE1	\$275
HP 5315B, Counter, 1GHz, Opt. 001/003, w/Manual	\$425
HP 5316A, Counter, 100MHz, HP1B	\$350
HP 5328A, Counter, 100MHz w/DVM/Opt. 021	\$200
HP 5328A, Counter, 500MHz	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven	\$500
HP 5345A, Counter, 500MHz	\$450
HP 5345A, Counter, 500MHz, HP1B	\$650
HP 59303A, D/A Converter	\$125
HP 6002A, Power Supply, 0-50V @ 0-10A Metered	\$450
HP 6034A, System Power Supply, 0-60V @ 10A-200W	\$525
HP 6101A, Power Supply, 0-20V @ 1A	\$125
HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A	\$150
HP 6112A, Power Supply, 40V @ .5A (metered)	\$150
HP 6177C, DC Current Source to 100V @ 500mA	\$275
HP 6202B, Power Supply, 40V @ .75A (metered)	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered)	\$150
HP 6205B, Power Supply (dual), 0-40V @ .3A, 0-20V @ .8A (metered)	\$175
HP 6206B, Power Supply, 0-60V @ 1A (metered)	\$200
HP 6227B, Dual Tracking PS 0-25V @ 2A	\$375
HP 6264B, Power Supply, 0-20V @ 20A	\$225
HP 6265B, Power Supply, 40V @ 3A (metered)	\$200
HP 6266A, Power Supply, 40V @ 6A (metered)	\$200
HP 6266B, Power Supply, 0-40V @ 5A	\$275
HP 6269, Power Supply, 0-40V @ 0-50A Metered	\$750

• 60-DAY WARRANTY
 • 10-DAY RIGHT OF RETURN
 • SATISFACTION GUARANTEED

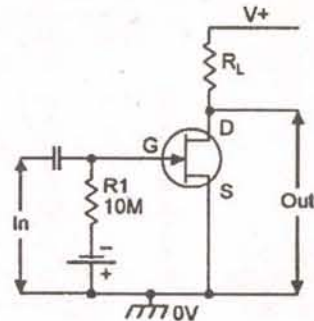


Figure 9. Basic n-channel common-source amplifier JFET circuit.

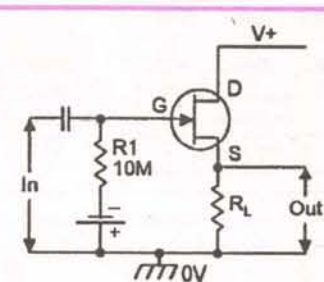


Figure 10. Basic n-channel common-drain (source-follower) JFET circuit.

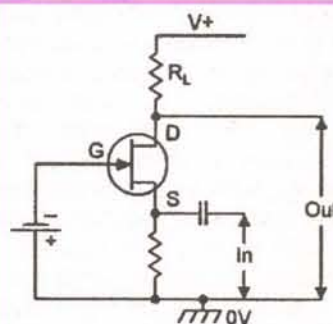


Figure 11. Basic n-channel common-gate JFET circuit.

practice, fairly accurate biasing techniques (discussed in Part 2 of this series) must be used in these circuits.

THE IGFET/MOSFET

The second (and most important) family of FETs are those known under the general title of IGFET or MOSFET. In these FETs, the gate terminal is insulated from the semiconductor body by a very thin layer of silicon dioxide, hence the title 'Insulated Gate Field Effect Transistor,' or IGFET. Also, the devices generally use a 'Metal-Oxide Silicon' semiconductor material in their construction, hence the alternative title of MOSFET.

Figure 12 shows the basic construction and the standard symbol of the n-channel depletion-mode FET. It resembles the JFET, except that its gate is fully insulated from the body of the FET (as indicated by the Figure 12(b) symbol) but, in fact, operates on a slightly different principle to the JFET.

It has a normally-open n-type channel between drain and source, but the channel width is controlled by the electrostatic field of the gate bias. The channel can be closed by applying

suitable negative bias, or can be increased by applying positive bias.

In practice, the FET substrate may be externally available, making a four-terminal device, or may be internally connected to the source, making a three-terminal device.

An important point about the IGFET/MOSFET is that it is also available as an enhancement-mode device, in which its conduction channel is normally closed but can be opened by applying forward bias to its gate.

Figure 13 shows the basic construction and the symbol of the n-channel depletion-mode IGFET/MOSFET. Here, no n-channel drain-to-source conduction path exists through the p-type substrate, so with zero gate bias there is no conduction between drain and source; this feature is indicated in the symbol of Figure 13(b) by the gaps between source and drain.

To turn the device on, significant positive gate bias is needed, and when this is of sufficient magnitude, it starts to convert the p-type substrate material under the gate into an n-channel, enabling conduction to take place.

Figure 14 shows the typical transfer characteristics of an n-channel enhancement-mode IGFET/MOSFET,

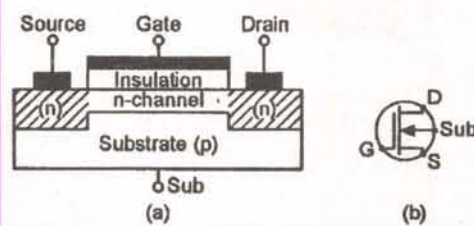


Figure 12. Construction (a) and symbol (b) of n-channel depletion-mode IGFET/MOSFET.

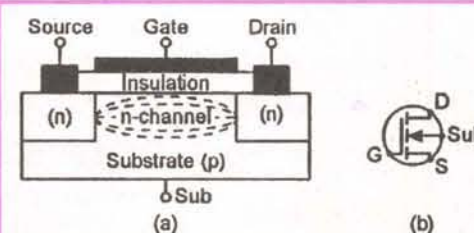


Figure 13. Construction (a) and symbol (b) of n-channel enhancement-mode IGFET/MOSFET.

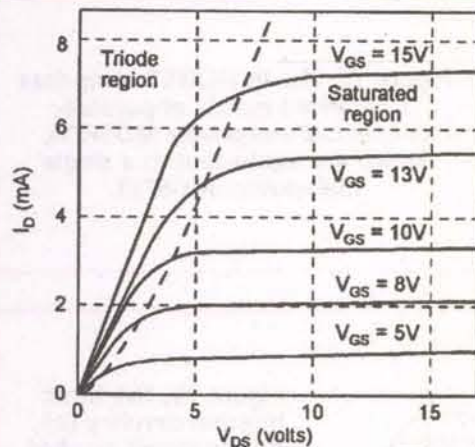


Figure 14.
Typical transfer characteristics of n-channel enhancement-mode IGFET/MOSFET.

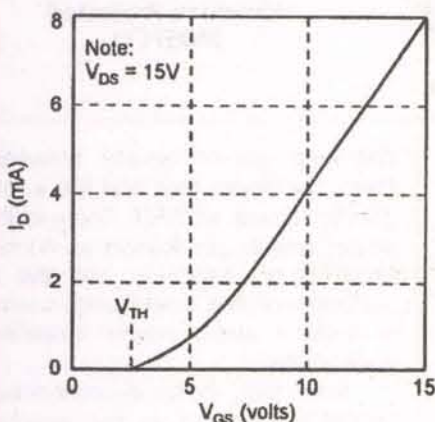


Figure 15.
Typical V_{GS}/I_D characteristics of n-channel enhancement-mode IGFET/MOSFET

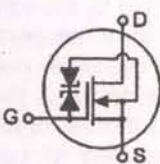


Figure 16.
Internally-protected n-channel depletion-mode IGFET/MOSFET.

impedance of MOSFET devices makes them liable to damage from electrostatic discharges and, for this reason, they are often provided with internal protection via integral diodes or zeners, as shown in the example in Figure 16.

VFET DEVICES

In a normal small-signal JFET or MOSFET, the main signal current flows 'laterally' (see Figures 3, 12, and 13) through the device's conductive channel. This channel is very thin, and maximum operating currents are consequently very limited (typically to maximum values in the range 2 to 40mA).

In post-1970 times, many manufacturers have tried to produce viable high-power/high-current versions of the FET, and the most successful of these have relied on the use of a 'vertical' (rather than lateral) flow of current through the conductive channel of the device. One of the best known of these devices is the 'VFET,' an enhancement-mode power MOSFET which was first introduced by Siliconix way back in 1976.

Figure 17 shows the basic structure of the original Siliconix VFET. It has an essentially four-layer structure, with an n-type source layer at the top, followed by a p-type 'body' layer, an epitaxial n-type layer, and (at the bottom) an n-type drain layer. Note that a 'V' groove (hence the 'VFET' title) passes through the first two layers and into the third layer of the device, and is electrostatically connected (via an insulating silicon dioxide film) to the gate terminal.

If the gate is shorted to the source, and the drain is made posi-

and Figure 15 shows the V_{GS}/I_D curves of the same device when powered from a 15V supply. Note that no I_D current flows until the gate voltage reaches a 'threshold' (V_{TH}) value of a few volts, but that beyond this value, the drain current rises in a non-linear fashion.

Also note that the transfer graph is divided into two characteristic regions, as indicated (in Figure 14) by the dotted line, these being the 'triode' region and the 'saturated' region. In the triode region, the device acts like a voltage-controlled resistor; in the saturated region, it acts like a voltage-controlled constant-current generator.

The basic n-channel MOSFETs of Figures 12 and 13 can — in principle — be converted to p-channel devices by simply transposing their p and n materials, in which case their symbols must be changed by reversing the directions of their substrate arrows.


A number of sub-variants of the MOSFET are in common use. The type known as 'DMOS' uses a double-diffused manufacturing technique to provide it with a very short conduction channel and a consequent ability to operate at very high switching speeds. Several other MOSFET variants are described in the remainder of this opening episode.

Note that the very high gate

FREE to all Electronics Addicts

\$199 To All Others!

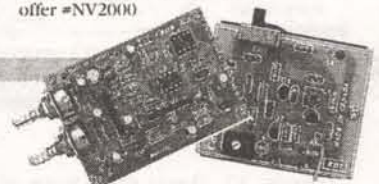when you mention this special offer #NV2000



For the first time ever we've decided to offer a proprietary software package titled, "Basic Electronics Concepts" to the general public. (Until now, the software hasn't been available to the public, at any price!)

Over 1500 Electronics teachers nationwide use this exact software package to teach Junior High through Graduate Students the basics of electronics, teaching them step by step. The total course of instruction is over 10 full hours and teaches all about resistors, potentiometers, photocells, capacitors, speakers, silicon diodes, SCRs, NPN transistors, PNP transistors, transistor oscillators, and IC timers!

We sell this package day in and day out for \$199 to teachers, parents, and hobbyists that want a detailed, complete method of teaching electronics to themselves, friends or children.

Here's our offer: As part of our "Grand Opening", for a limited time every first time order on the web will receive a copy of this incredible software absolutely free!

We have a limited quantity of the software program in stock, at last check, approximately 1136 units, so place your order today!

Here's a few of the 117 different kits that you can build that we offer ONLINE:

*Color Organs • FM Transmitter Kits
Amplifier Kits • Strobe Light Kits
Alarm Kits • Radios Kits • Meter Kits
Keypad Lock Kits • Infrared Kits
and more!*

We carry national brands and guarantee that your order will arrive promptly and be exactly what you expected! **ORDER NOW!**

Build a kit today!


24 Hour Ordering on the web:
www.HobbyTron.com

PHONE: 877-606-8766 FAX: 800-470-1606
TRON



Write In 128 on Reader Service Card.


RF Data Modules

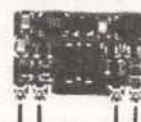

AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10

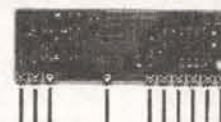

AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95



FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair. (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

Transceiver..... RTcom-4xx..... \$247.90
Transmitter..... RTcomTx-4xx..... \$ 87.15
Receiver..... RTcomRx-4xx..... \$105.52



Tel: (416)236-3858
Fax: (416)236-8866
www.abacom-tech.com
abacomtech@compuserve.com

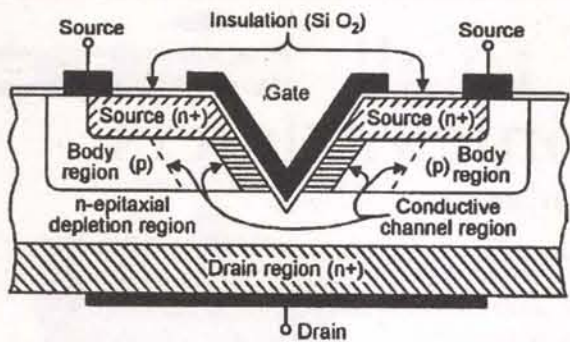


Figure 17. Basic structure of the VFET power device.

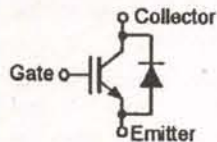


Figure 20. Normal circuit symbol of the IGBT (Insulated Gate Bipolar Transistor).

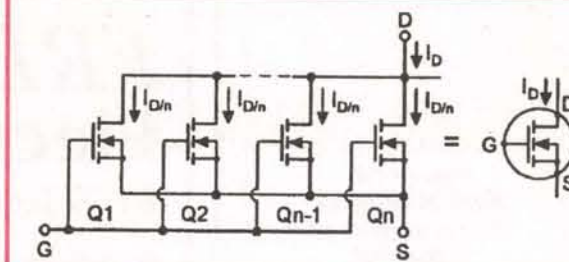


Figure 18. The IR HEXFET comprises a balanced matrix of parallel-connected low-power MOSFETs, which are equivalent to a single high-power MOSFET.

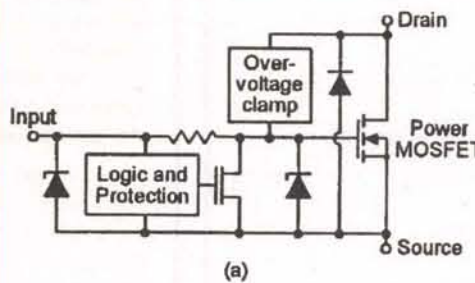


Figure 19. The basic internal circuitry (a) and the circuit symbol (b) of the TOPFET (Temperature and Overload Protected MOSFET).

tive, no drain-to-source current flows, because the diode formed by the p and n materials is reverse-biased. But if the gate is made positive to the source, the resulting electrostatic field converts the area of p-type material adjacent to the gate into n-type material, thus creating a conduction channel in the position shown in Figure 17 and enabling current to flow vertically from the drain to the source.

As the gate becomes more positive, the channel width increases, enabling the drain-to-source current to increase as the drain-to-source resistance decreases. This basic VFET can thus pass reasonably high currents (typically up to 2A) without creating excessive current density within the channel regions.

The original Siliconix VFET design of Figure 17 was successful, but imperfect. The sharp bottom of its V-groove caused an excessive electric field at this point and restricted the device's operating voltage. Subsequent to the original VFET introduction, Intersil introduced their own

version of the 'VMOS' technique, with a U-shaped groove (plus other modifications) that improved device reliability and gave higher maximum operating currents and voltages. In 1980, Siliconix added these and other modifications to their own VFET devices, resulting in further improvements in performance.

OTHER POWER FETs

Several manufacturers have produced viable power FETs without using 'V'- or 'U'-groove techniques, but still relying on the vertical flow of current between drain and source. In the 1980s, Hitachi produced both p-channel and n-channel power MOSFET devices with ratings up to 8A and 200V; these devices were intended for use mainly in audio and low-RF applications.

Supertex of California and Farranti of England pioneered the development of a range of power MOSFETs with the general title of 'vertical DMOS.' These featured high operating voltages (up to 650V), high

current rating (up to 16A), low on resistance (down to 50 milliohms), and very fast operating speeds (up to 2GHz at 1A, 500MHz at 10A).

Siemens of West Germany used a modified version of DMOS, known as SIPMOS, to produce a range of n-channel devices with voltage ratings as high as 1kV and with current ratings as high as 30A.

One International Rectifier solution to the power MOSFET problem is a device which, in effect, houses a vast array of parallel-connected low-power vertical MOSFETs or 'cells' which share the total current equally between them, and thus act like a single high-power MOSFET, as indicated in Figure 18. These devices are named HEXFET, after the hexagonal structure of these cells, which have a density of about 100,000 per square centimeter of semiconductor material.


Several manufacturers produce power MOSFETs that each comprise a large array of parallel-connected low-power lateral (rather than horizontal) MOSFET cells that share the total

operating current equally between them; the device thus acts like a single high-power MOSFET. These high-power devices are known as lateral MOSFETs or L-MOSFETs, and give a performance that is particularly useful in super-fi audio power amplifier applications.

Note that, in parallel-connected MOSFETs (as used in the internal structure of the HEXFET and L-MOSFET devices described above), equal current sharing is ensured by the conduction channel's positive temperature coefficient; if the current in one MOSFET becomes excessive, the resultant heating of its channel raises its resistance, thus reducing its current flow and tending to equalize it with that of other parallel-connected MOSFETs. This feature makes such power MOSFETs almost immune to thermal runaway problems.

Today, a vast range of power MOSFET types are manufactured. 'Low voltage' n-channel types are readily available with voltage/current ratings as high as 100V/75A, and 'high voltage' ones with ratings as

Any waveform you want!

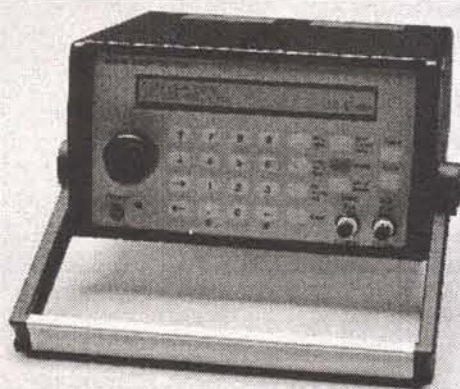


Telulex Inc. model SG-100A


- New Features:**
- ✓ 21.5 MHz
 - ✓ .01 Hz steps
 - ✓ multi-unit phaselock

- **Synthesized Signal Generator**
Clean sinewaves DC-21.5 MHz with .001% accuracy!
.01 Hz steps. DC Offset. RS232 remote control.
- **Arbitrary Waveform Generator**
40 Megasamples/Second. 32,768 points. 12 bit DAC

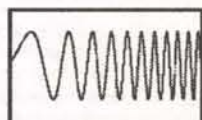
- **Function Generator**
Ramps, Triangles, Exponentials, Noise & more.
0 to 2 MHz in 1 Hz steps. Continuous or Triggered.
- **Pulse Generator**
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

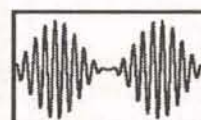


Int/Ext AM, SSB, Dualtone Gen.

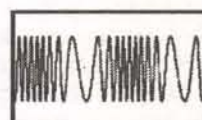


Int/Ext FM, PM, BPSK, Burst

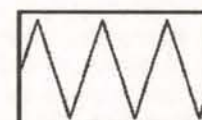


Ramps, Triangles,

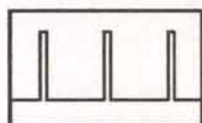


Pulse Generator

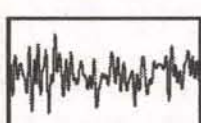

Noise

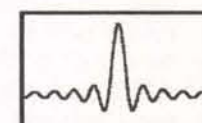

Arbitrary Waveforms

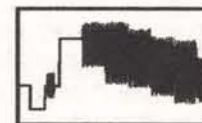

Unlimited Possibilities!

Telulex Inc.

2455 Old Middlefield Way S
Mountain View, CA 94043

Tel (650) 938-0240
Fax (650) 938-0241

<http://www.Telulex.com>
Email: sales@Telulex.com

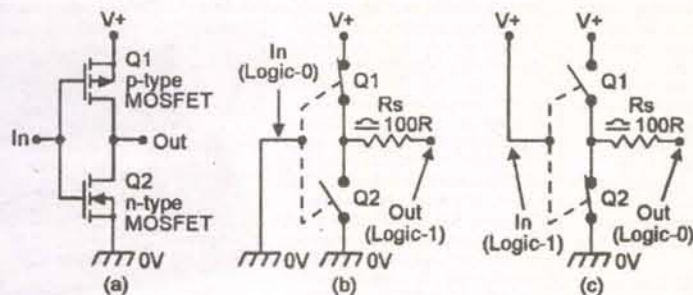


Figure 21. Basic CMOS circuit (a), and its equivalent with (b) a logic-0 input and (c) a logic-1 input.

high as 500V/25A.

One of the most important recent developments in the power-MOSFET field has been the introduction of a variety of so-called 'intelligent' or 'smart' MOSFETs with built-in overload protection circuitry; these MOSFETs usually carry a distinctive registered trade name. Philips devices of this type are known as TOPFETs (Temperature and Overload Protected MOSFETs); Figure 19 shows (in simplified form) the basic internal circuitry and the circuit symbol of the TOPFET.

The Siemens version of the smart MOSFET is known as the PROFET. PROFET devices incorporate protection against damage from short circuits, over temperature, overload, and electrostatic discharge (ESD). International Rectifier produce a range of smart n-channel MOSFET known as SMARTFETs; these incorporate protection against damage from short circuits, over temperature, overvoltage, and ESD.

Finally, yet another recent and important development in the n-channel power MOSFET field, has been the production — by various manufacturers — of a range of high power devices known as IGBTs (Insulated Gate Bipolar Transistors), which have a MOSFET-type input and an internally protected high-voltage high-current bipolar transistor output. Figure 20 shows the normal circuit symbol of the IGBT. Devices of this type usually have voltage/current/power ratings ranging from as low as 600V/6A/33W (in the device known as the HGTD3N603), to as

high as 1200V/520A/3000W (in the device known as the MG400Q1US51).

CMOS BASICS

One major FET application is in digital ICs. The best known range of such devices use the technology known as CMOS, and rely on the use of complementary pairs of MOSFETs. Figure 21 illustrates basic CMOS principles. The basic CMOS device comprises a p-type and n-type pair of enhancement-mode MOSFETs, wired in series, with their gates shorted together at the input, as shown in Figure 21(a). The pair are meant to use logic-0 or logic-1 digital input signals, and Figures 21(b) and 21(c), respectively, show the device's equivalent circuit under these conditions.

When the input is at logic-0, the upper (p-type) MOSFET is biased fully on and acts like a closed switch, and the lower (n-type) MOSFET is biased off and acts like an open switch; the output is thus effectively connected to the positive supply line (logic-1) via a series resistance of about 100R.

When the input is at logic-1, the MOSFET states are reversed, with Q1 acting like an open switch and Q2 acting like a closed switch, so the output is effectively connected to ground (logic-0) via 100R. Note in both cases that the entire signal current is fed to the load, and none is shunted off by the CMOS circuitry; this is a major feature of CMOS technology. **NV**

M.E.M. ELECTRONICS CO.

DISTRIBUTOR FOR THE NEW

SIMS SVR-S825 8 HOUR DIGITAL VOICE RECORDER

- 8 HOUR RECORDING/PLAYBACK or 396 MESSAGES ON FLASH EPROM
- MINIATURE SIZE AND LIGHTWEIGHT, VOX, BACKLIT LCD DISPLAY
- GREAT-4- JOURNALISTS, DOCTORS, LAWYERS, ENGINEERS, STUDENTS
- DOWNLOADING WIN '95 & '98 SOFTWARE ON CD INCLUDED ALSO EXT. MIC., EARPHONE, "AAA" BATTERIES, DUBBING CORD INCLUDED



****GREAT FOR SSTV IMAGE STORAGE****
THE SVR-S825 WILL HOLD OVER 800, COLOR IMAGES AND THEN DOWNLOAD TO ANY SSTV, PC SOFTWARE!

NEW — LOW COST, 2.5", 4" AND 6.8" COLOR TFT-LCD VIDEO MODULES WITH NTSC DRIVER CARDS *** CALL 4 INFO!
FOR PRICING AND LITERATURE ON THESE AND OTHER GREAT PRODUCTS
CALL: 215 - 657 - 3119 E-MAIL: mocenter@erols.com
<http://www.memelectronics.com>


Write in 129 on Reader Service Card.

Digital Storage Oscilloscopes

From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

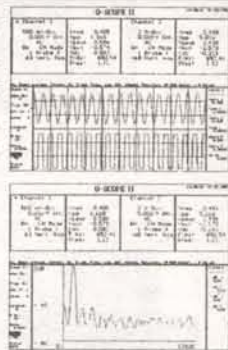O-Scope Ip \$189.
O-Scope II \$349.
Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit.

Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With **NEW** gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from **DFA5** 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems ???
Check out Serial !! Our lowcost serial channel analyzer only \$99.00.

Allison Technology Corporation

2006 Finney Vallet Rd., TX. 77471 U.S.A.

800-980-9806 or 281-239-8500

<http://www.atcweb.com> atc@accesscomm.net

ALLTECH ELECTRONICS

WWW.COMPUTERCHOPPER.COM

WE CHOP

PRICE\$!

SCSI CDROM
Matsushita / Apple OEM PC or Mac SCSI
4x \$19

486 Mini System
486SX25 • Great for Linux DX266 Upgradable • 2 ISA Slots • VGA, LPT, 2COMs • FD \$29

250VA Isolation Transformer
115V Pri - 115V 250VA Sec Magnetek Triad 6" x 4" x 5" \$35

PC Game Accessores
Steering Wheels • Flight Sticks • Joysticks Have a ball! Starting at \$19

7 SCSI CD's in a Tower
7 CR-504-L Drives in a SCSI Tower case - 2 50 Pin Connectors \$179

Open Frame Industrial DC P/S +5/12-5/12 +24V \$29

24 Bit Flat Bed Scanner
Win95/98 - ImageWave by Storm Technology. Parallel Port Interface Software Included! 5 Minute Installation \$39

Flat Bed Photo Scanner
Win98/98 - Scan Photos, Slides, Negatives. Small footprint. Great scanner! ISA Slot Req. \$45

8 Port Hub
Refurbished Network Hardware - For PC and Mac. Why pay more? Get Networked Now! \$24

9.75" Mono, 8.6" and 10.4" Color LCDs



\$89 & up.

Great for Servers: ISA Controller Included!! All screens are 640x480. The controller supports 256 Colors. 9.75" Mono Passive.....\$89.00 9.5" Color Passive.....\$199.00 10.4" Color Active.....\$319.00 P200 Motherboard with integrated 24 bit color available. See our web site for more details.

Cheaper Ethernet Stuff Industrial Surplus PC Parts • Mac Parts

For more information on these products and hundreds of other products check out:

WWW.COMPUTERCHOPPER.COM

760/724-2404 Fax 760/724-8808
Computer Circulation Center, Inc. 2618 Temple Heights Drive Oceanside, CA 92056

Mon-Fri 9AM -5:30PM - Or see us on the internet. VISA • Mastercard • Discover • American Express

Prices & Availability subject to change without notice • Government & Educational PO's Accepted. • Not Responsible for Typographical Errors

Write in 135 on Reader Service Card.

Nuts & Volts Magazine/MAY 2000 19

FET PRINCIPLES AND CIRCUITS

E T

Part 2

Field-Effect Transistors

by Ray Marston

Ray Marston looks at practical JFET circuits in this second episode of this four-part series.

Last month's opening episode explained (among other things) the basic operating principles of JFETs. JFETs are low-power devices with a very high input resistance and invariably operate in the depletion mode, i.e., they pass maximum current when the gate bias is zero, and the current is reduced ('depleted') by reverse-biasing the gate terminal.

Most JFETs are n-channel (rather than p-channel) devices. Two of the oldest and best known n-channel JFETs are the 2N3819 and the MPF102, which are usually housed in TO92 plastic packages with the connections shown in Figure 1; Figure 2 lists the basic characteristics of these two devices.


This month's article looks at basic usage information and applications of JFETs. All practical circuits shown here are specifically designed around the 2N3819, but will operate equally well when using the MPF102.

JFET BIASING

The JFET can be used as a linear amplifier by reverse-biasing its gate relative to its source terminal, thus driving it into the linear region. Three basic JFET biasing techniques are in common use. The simplest of these is the 'self-biasing' system shown in Figure 3, in which the gate is grounded via R_g , and any current flowing in R_s drives the source positive relative to the gate, thus generating reverse bias.

Suppose that an I_D of 1mA is wanted, and that a V_{GS} bias of -2V2 is needed to set this condition; the correct bias can obviously be obtained by giving R_s a value of 2k Ω ; if I_D tends to fall for some reason, V_{GS} naturally falls as well, and thus makes I_D increase and counter the original change; the bias is thus self-regulating via negative feedback.

Figure 1. Outline and connections of the 2N3819 and MPF102 JFETs.

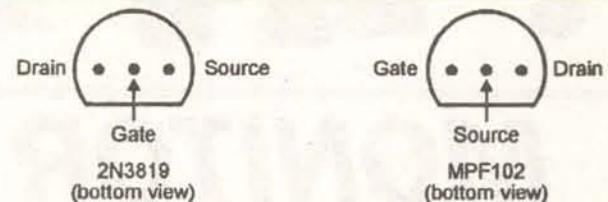

Parameter	2N3819	MPF102
V_{DS} max (= max. drain-to-source voltage)	25V	25V
V_{DG} max (= max. drain-to-gate voltage)	25V	25V
V_{GS} max (= max. gate-to-source voltage)	-25V	-25V
I_{DSS} (= drain-to-source current with $V_{GS} = 0V$)	2-20mA	2-20mA
I_{GSS} max (= gate leakage current at 25° C)	2nA	2nA
P_T max (= max. power dissipation, in free air)	200mW	310mW

Figure 2. Basic characteristics of the 2N3819 and MPF102 n-channel JFETs.

In practice, the V_{GS} value needed to set a given I_D varies widely between individual JFETs, and the only sure way of getting a precise I_D value in this system is to make R_s a variable resistor; the system is, however, accurate enough for many

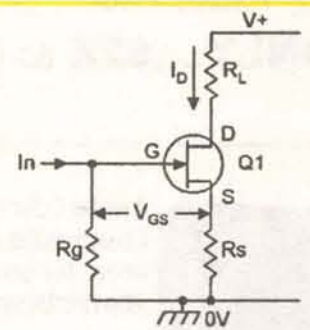


Figure 3. Basic JFET 'self-biasing' system.


applications, and is the most widely used of the three biasing methods.

A more accurate way of biasing the JFET is via the 'offset' system of Figure 4(a), in which divider R_1 - R_2 applies a fixed positive bias to the gate via R_g , and the source voltage equals this voltage minus V_{GS} . If the gate voltage is large relative to V_{GS} , I_D is set mainly by R_s and is not greatly influenced by V_{GS} variations. This system thus enables I_D values to be set with good accuracy and without need for individual component selection. Similar results can be obtained by grounding the gate and taking the bottom of R_s to a large negative voltage, as in Figure 4(b).


The third type of biasing system is shown in Figure 5, in which constant-current generator Q_2 sets the I_D , irrespective of the JFET characteristics. This system gives excellent biasing stability, but at the expense of increased circuit complexity.

PCB LAYOUT Software For Windows - FREE

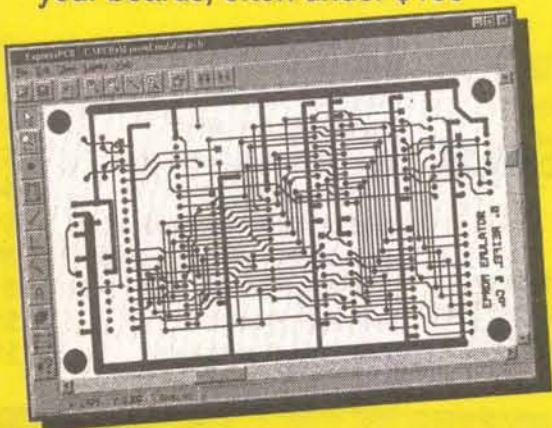- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

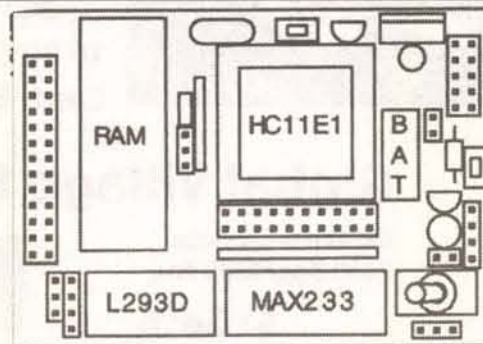

SUPER-TCOMP Single Board Computer

- Completely assembled. NOT A KIT!
- Program in C, assembly, IC, etc.
- 32K RAM chip with 10 year battery backup
- 5 volt low drop-out voltage regulator
- Max233 RS232 converter
- Most signals available at expansion ports
- External mode, reset and power connections
- Available options include I/O expansion and LCD board
- Comes with complete instructions
- Very small package: 2.1" x 3.0"
- 1 year limited warranty

----- ONLY \$145 -----

Ray's Robotic Racers (310) 515-6075
<http://www.teleport.com/~raybutts/>

and cost.

In the three biasing systems described, R_g can have any value up to 10M, the top limit being imposed by the volt drop across R_g caused by gate leakage currents, which may upset the gate bias.

SOURCE FOLLOWER CIRCUITS

When used as linear amplifiers, JFETs are usually used in either the source follower (common drain) or common-source modes. The source follower gives a very high input impedance and near-unity voltage gain (hence the alternative title of 'voltage follower').

Figure 6 shows a simple self-biasing (via RV1) source follower; RV1 is used to set a quiescent R_2 volt-drop of 5V6. The circuit's actual input-to-output voltage gain is 0.95. A degree of bootstrapping is applied to R_3 and increases its effective impedance; the circuit's actual input impedance is 10M shunted by 10pF, i.e., it is 10M at very low frequencies, falling to 1M Ω at about 16kHz and 100k Ω at 160kHz, etc.

Figure 7 shows a source follower with offset gate biasing. Overall voltage gain is about 0.95. C_2 is a bootstrapping capacitor and raises the input impedance to 44M, shunted by 10pF.

Figure 8 shows a hybrid (JFET plus bipolar) source follower. Offset biasing is applied via R_1 - R_2 , and constant-current generator Q_2 acts as a very high-impedance source load, giving the circuit an overall voltage gain of 0.99. C_2 bootstraps R_3 's effective impedance up to 1000M, which is shunted by the JFET's gate impedance; the input impedance of the complete circuit is 500M, shunted by 10pF.

Note then if the high effective value of input impedance of this circuit is to be maintained, the output must either be taken to external loads via an additional emitter follower stage (as shown dotted in the diagram) or must be taken only to fairly high impedance loads.

COMMON SOURCE AMPLIFIERS

Figure 9 shows a simple self-biasing common source amplifier; RV1 is used to set a quiescent 5V6 across R_3 . The RV1- R_2 biasing network is AC-decoupled via C_2 , and the circuit gives a voltage gain of 21dB (= x12), and has a ± 3 dB frequency response that spans 15Hz to 250kHz and an input impedance of 2M Ω shunted by 50pF. (This high shunt value is due to Miller feedback, which multiplies the JFET's effective gate-to-drain capacitance by the circuit's x12 A_v value.)

Figure 10 shows a simple self-biasing headphone amplifier that can be used with headphone impedances of 1k Ω or greater. It has a built-in volume control (RV1), has

an input impedance of 2M Ω , and can use any supply in the 9V to 18V range.

Figure 11 shows a self-biasing add-on pre-amplifier that gives a voltage gain in excess of 20dB, has a bandwidth that extends beyond 100kHz, and has an input impedance of 2M Ω . It can be used with any amplifier that can provide a 9V to 18V power source.

JFET common source amplifiers can — when very high biasing accuracy is needed — be designed using either the 'offset' or 'constant-current' biasing technique. Figures 12 and 13 show circuits of these types. Note that the 'offset' circuit of Figure 12 can be used with supplies in the range 16V to 20V only, while the hybrid circuit of Figure 13 can be used with any supply in the 12V to 20V range. Both circuits give a voltage gain of 21dB, a ± 3 dB bandwidth of 15Hz to 250kHz, and an input impedance of 2M Ω .

DC VOLTMETERS

Figure 14 shows a JFET used to make a very simple and basic three-range DC voltmeter with a maximum FSD sensitivity of 0.5V and an input impedance of 11M Ω . Here, R_6 -RV2 and R_7 form a potential divider across the 12V supply and — if the R_7 -RV2 junction is used as the circuit's zero-voltage

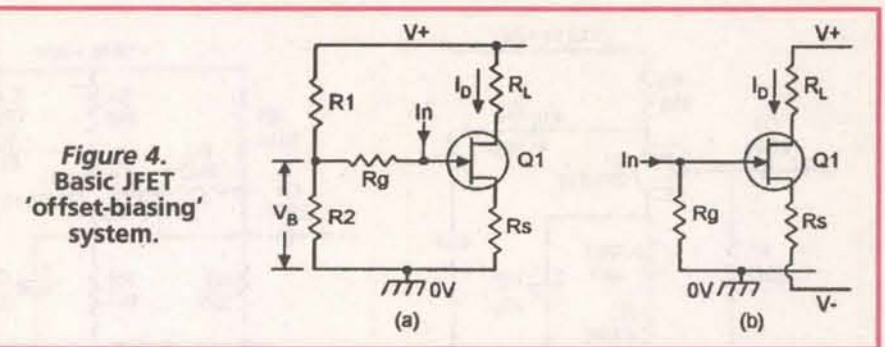


Figure 4. Basic JFET 'offset-biasing' system.

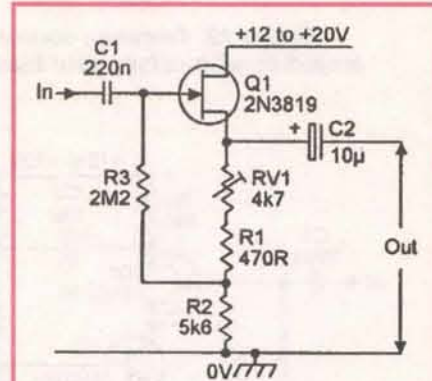


Figure 6. Self-biasing source-follower. $Z_{in} = 10M$.

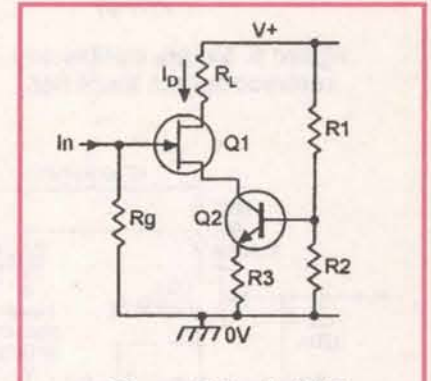


Figure 5. Basic JFET 'constant-current' biasing system.

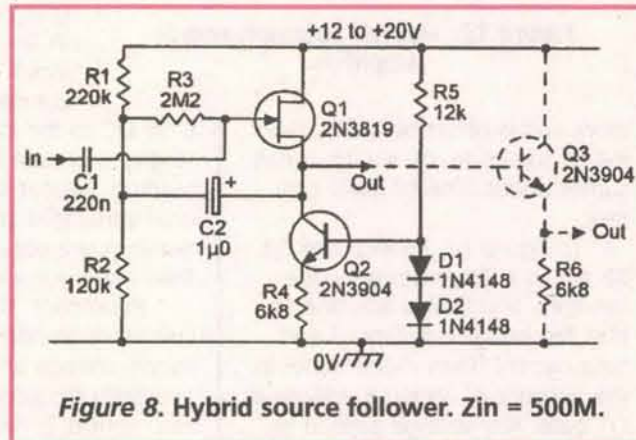


Figure 8. Hybrid source follower. $Z_{in} = 500M$.


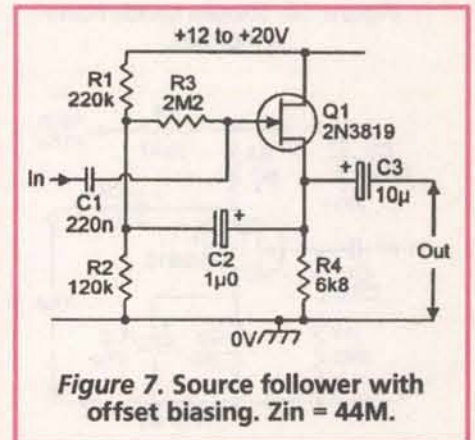


Figure 7. Source follower with offset biasing. $Z_{in} = 44M$.

point — sets the top of R_6 at +8V and the bottom of R_7 at -4V. Q_1 is

used as a source follower, with its gate grounded via the R_1 to R_4 net-

Honey, I
shrank the
COMPUTER!

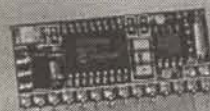

As low as \$29

PicStics are like BASIC Stamps[®] on steroids. They have more speed, more parallel I/O, more code and data space, and more neat features like a real-time clock, 12-bit ADC, and 12-bit DAC.

Call for a
catalog or visit
our Web site
today.

www.micromint.com

Micromint, Inc

740 Florida Central Pkwy., Longwood, FL 32750

(800) 635-3355

(407) 262-0066

BASIC Stamp is a registered trademark of Parallax, Inc.

plug-ins
test sets
counters
generators
oscilloscopes
power supplies
spectrum analyzers
& much more!

www.levylatham.com

PRIVATE MARKETERS OF U.S. GOVERNMENT MILITARY SURPLUS ASSETS

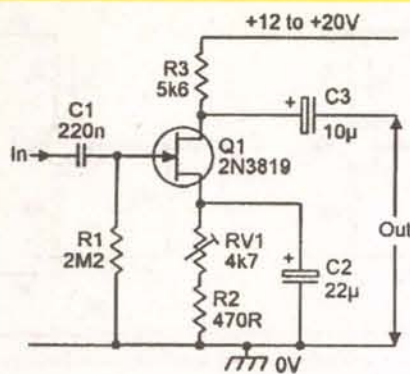


Figure 9. Simple self-biasing common-source amplifier.

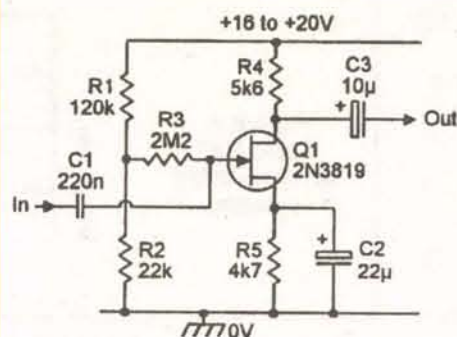


Figure 12. Common-source amplifier with offset gate biasing.

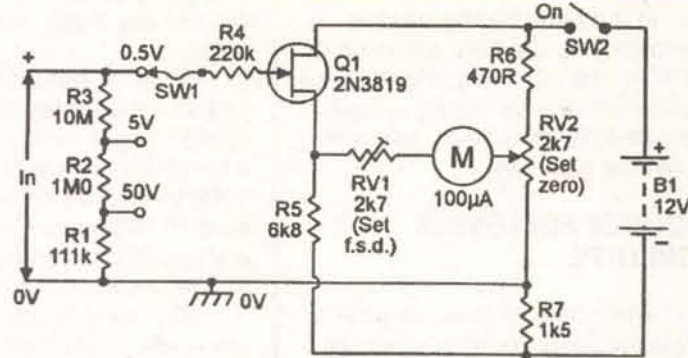


Figure 14. Simple three-range DC voltmeter.

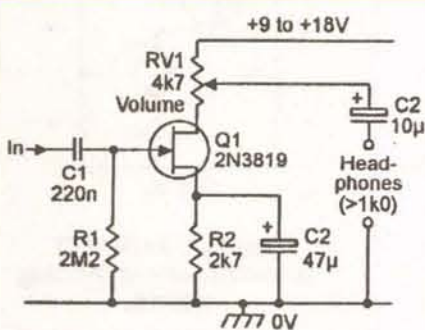


Figure 10. Simple headphone amplifier.

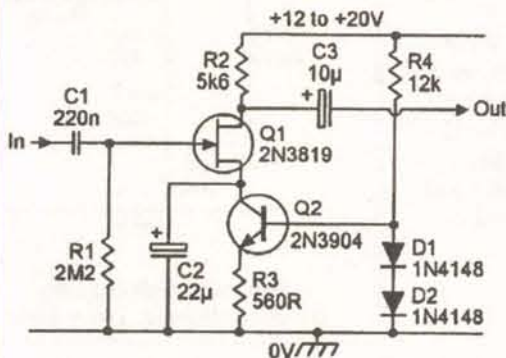


Figure 13. 'Hybrid' common-source amplifier.

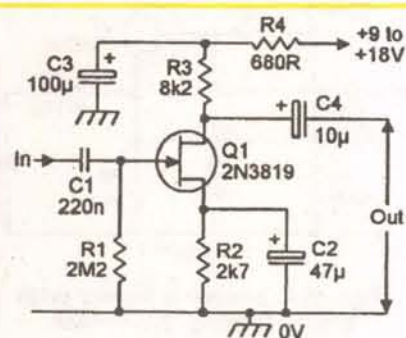


Figure 11. General-purpose add-on pre-amplifier.

work and is offset biased by taking its source to -4V via R5; it consumes about 1mA of drain current.

In Figure 14, R6-RV2 and Q1-R5 act as a Wheatstone bridge network, and RV2 is adjusted so that the bridge is balanced and zero current flows in the meter in the absence of an input voltage at Q1 gate. Any voltage applied to Q1 gate then drives the bridge out of balance by a proportional amount, which can be read direct-

ly on the meter.

R1 to R3 form a range multiplier network that — when RV1 is correctly adjusted — gives FSD ranges of 0.5V, 5V, and 50V. R4 protects Q1's gate against damage if excessive input voltage is applied to the circuit.

To use the Figure 14 circuit, first trim RV2 to give zero meter reading in the absence of an input voltage, and then connect an accurate

0.5V DC to the input and trim RV1 to give a precise full-scale reading. Repeat these adjustments until consistent zero and full-scale readings are obtained; the unit is then ready for use.

In practice, this very simple circuit tends to drift with variations in supply voltage and temperature, and fairly frequent trimming of the zero control is needed. Drift can be greatly reduced by using a zener-stabilized 12V supply.

Figure 15 shows an improved

low-drift version of the JFET voltmeter. Q1 and Q2 are wired as a differential amplifier, so any drift occurring on one side of the circuit is automatically countered by a similar drift on the other side, and good stability is obtained. The circuit uses the 'bridge' principle, with Q1-R5 forming one side of the bridge and Q2-R6 forming the other. Q1 and Q2 should ideally be a matched pair of JFETs, with loss values matched within 10%. The circuit is set up in the same way as that of Figure 14.

MISCELLANEOUS JFET CIRCUITS

To conclude this month's article, Figures 16 to 19 show a miscellaneous collection of useful JFET circuits. The Figure 16 design is that of a very-low-frequency (VLF) astable or free-running multivibrator; its on and off periods are controlled by C1-R4 and C2-R3, and R3 and R4 can have values up to 10M.

With the values shown, the circuit cycles at a rate of once per 20 seconds, i.e., at a frequency of 0.05Hz; start button S1 must be held closed for at least one second to initiate the astable action.

Figure 17 shows — in basic form — how a JFET and a 741 op-amp can be used to make a voltage-controlled amplifier/attenuator. The op-amp is used in the inverting mode, with its voltage gain set by the R2/R3 ratio, and R1 and the JFET are used as a voltage-controlled input attenuator.

When a large negative control voltage is fed to Q1 gate, the JFET acts like a near-infinite resistance and causes zero signal attenuation, so the circuit gives high overall gain but, when the gate bias is zero, the FET acts like a low resistance and causes heavy signal attenuation, so the circuit gives an overall signal loss.

Intermediate values of signal attenuation and overall gain or loss can be obtained by varying the control voltage value.

Figure 18 shows how this voltage-controlled attenuator technique can be used to make a 'constant volume' amplifier that produces an output signal level change of only 7.5dB when the input signal level is varied over a 40dB range (from

Use your PC as a scope and datalogger!

Parallel Port Scope
spectrum analyzer, and digital multimeter



\$79 - \$799

ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333kS/s versions. Great for schools, test depts, etc. Input to Excell! LabView/NT drivers included.

Environmental Logging
record temperature, humidity, etc.



\$129 - \$645

ENVIROMON - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

osziFOX
20MS/s handheld scope



\$129

osziFOX - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

pico
Technology Limited

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See www.saelig.com for Product of the Month!

3mV to 300mV RMS).

The circuit can accept input signal levels up to a maximum of 500mV RMS. Q1 and R4 are wired in series to form a voltage-controlled attenuator that controls the input signal level to common emitter amplifier Q2, which has its output buffered via emitter follower Q3.

Q3's output is used to generate (via C5-R9-D1-D2-C4-R5) a DC control voltage that is fed back to Q1's gate, thus forming a DC negative-feedback loop that automatically adjusts the overall voltage gain so that the output signal level tends to remain constant as the input signal level is varied, as follows.

When a very small input signal is applied to the circuit, Q3's output signal is also small, so negligible DC control voltage is fed to Q1's gate; Q1 thus acts as a low resistance under this condition, so almost the full input signal is applied to Q2 base, and the circuit gives high overall gain.

When a large input signal is applied to the circuit, Q3's output signal tends to be large, so a large DC negative control voltage is fed to Q1's gate; Q1 thus acts as a high resistance under this condition, so only a small part of the input signal is fed to Q2's base, and the circuit gives low overall gain.

Thus, the output level stays fairly constant over a wide range of input signal levels; this characteristic is useful in cassette recorders, intercoms, and telephone amplifiers, etc.

Finally, Figure 19 shows a JFET used to make a DC-to-AC converter or 'chopper' that produces a square-

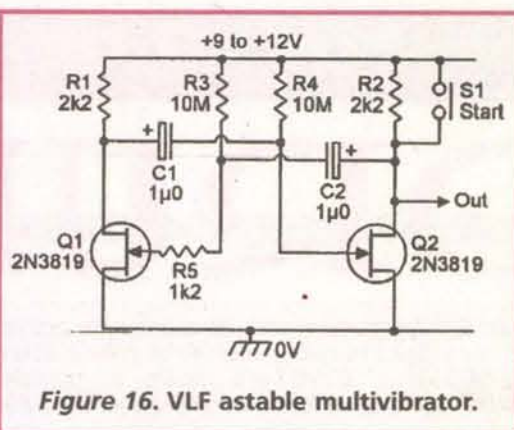


Figure 16. VLF astable multivibrator.

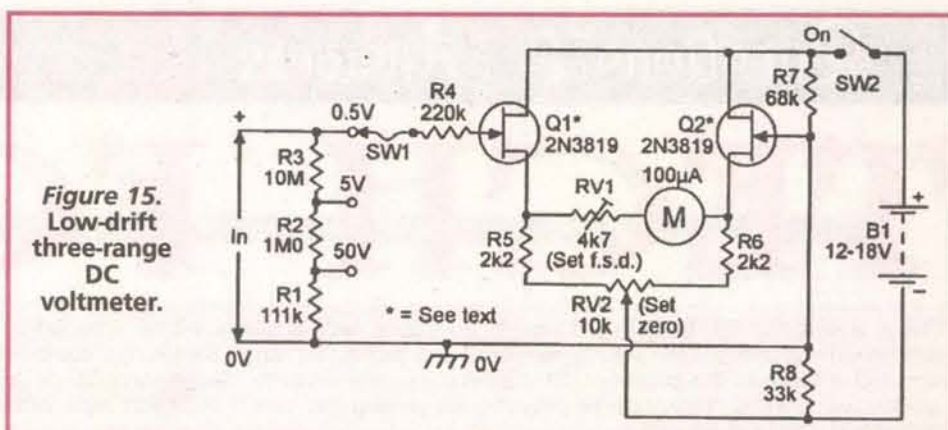


Figure 15. Low-drift three-range DC voltmeter.

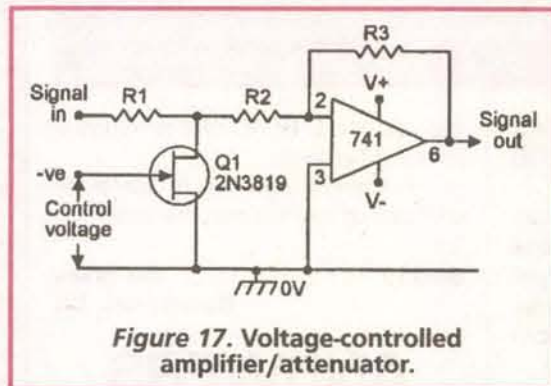


Figure 17. Voltage-controlled amplifier/attenuator.

wave output with a peak amplitude equal to that of the DC input voltage.

In this case, Q1 acts like an electronic switch that is wired in series with R1 and is gated on and off at a 1kHz rate via the Q2-Q3 astable circuit, thus giving the DC-to-AC conversion. Note that Q1's gate-drive signal amplitude can be varied via RV1; if too large a drive is used, Q1's gate-to-source junction starts to avalanche, causing a small spike voltage to break through the drain and give an output even when no DC input is present.

To prevent this, connect a DC input and then trim RV1 until the output is just on the verge of decreasing; once set up in this way, the circuit can be reliably used to chop voltages as small as a fraction of a millivolt. **NV**

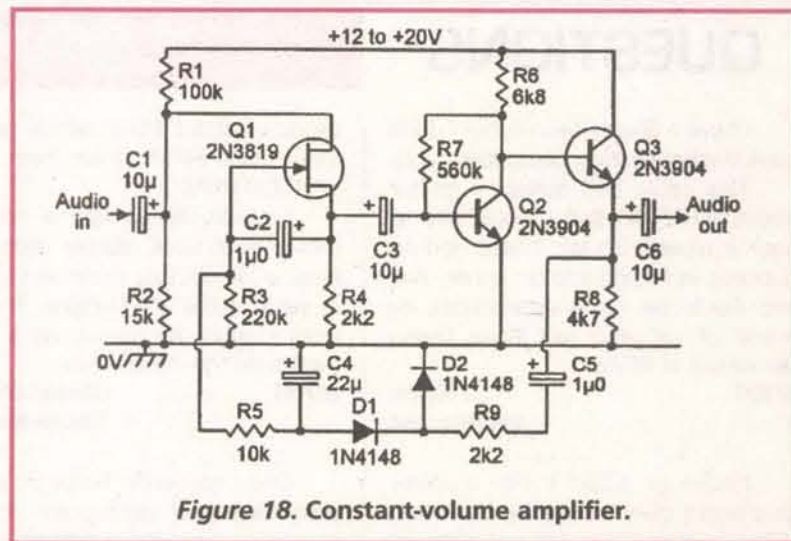


Figure 18. Constant-volume amplifier.


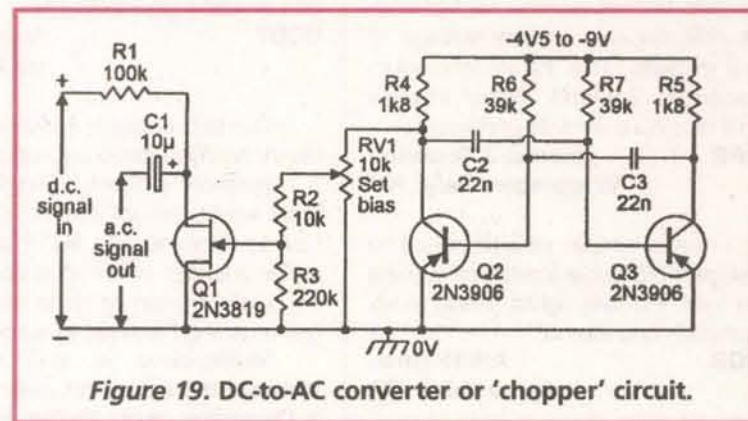


Figure 19. DC-to-AC converter or 'chopper' circuit.

Next time, Ray looks at practical MOSFET and CMOS circuits.

Any waveform you want!

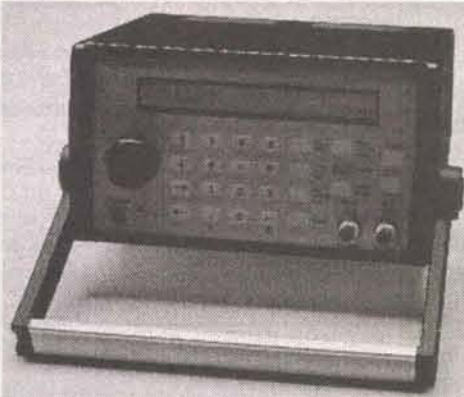

Telulex model SG-100A

New Features:

- ✓ 21.5 MHz
- ✓ .01 Hz steps
- ✓ multi-unit phaselock

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy!
.01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator


Ramps, Triangles, Exponentials, Noise & more.
0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator

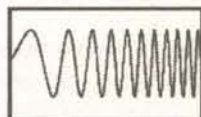
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

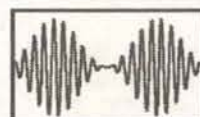


Int/Ext AM, SSB, Dualtone Gen.

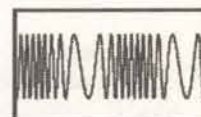

Int/Ext FM, PM, BPSK, Burst

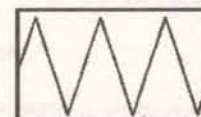


Ramps, Triangles,

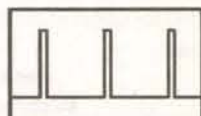


Pulse Generator



Noise

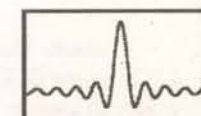

Arbitrary Waveforms

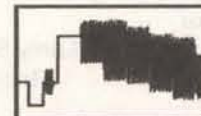

Unlimited Possibilities!

BNC/Telulex Div.

3060 Kerner Blvd., #2
San Rafael, CA 94901

Tel (415) 453-9955
Fax (415) 453-9956

<http://www.Telulex.com>
Email: sales@Telulex.com

FET PRINCIPLES AND CIRCUITS

Part 3

Field-Effect Transistors

by Ray Marston

Ray Marston looks at practical MOSFET and CMOS circuits in this penultimate episode of this four-part series.

Part 1 of this series explained (among other things) the basic operating principles of the MOSFET (or IGFET), and pointed out that complementary enhancement-mode pairs of these devices form the basis of the digital technology known as CMOS.

The present episode of the series looks at practical applications of MOSFETs and CMOS-based MOSFET devices.

A MOSFET INTRODUCTION

MOSFETs are available in both depletion-mode and enhancement-mode versions. Depletion-mode types give a performance similar to a JFET, but with a far higher input resistance (i.e., with a far higher low-frequency input impedance).

Some depletion-mode MOSFETs are equipped with two independent gates, enabling the drain-to-source currents to be controlled via either one or both of



Figure 1. Symbol of the dual-gate or tetrode MOSFET.



Figure 2. Standard symbols of (a) three-pin and (b) four-pin n-channel enhancement-mode MOSFETs.

the gates; these devices (which are often used as signal mixers in VHF tuners) are known as dual-gate or tetrode MOSFETs, and use the symbol shown in Figure 1.

Most modern MOSFETs are enhancement-mode devices, in which the drain-to-source conduction channel is closed when the gate bias is zero, but can be opened by applying a forward gate bias. This 'normally open-circuit' action is implied by the gaps between source and drain in the device's standard symbol, shown in Figure 2(a), which depicts an n-channel MOSFET (the arrow head

is reversed in a p-channel device). In some devices, the semiconductor substrate is made externally available, creating a 'four-terminal' MOSFET, as shown in Figure 2(b).

Figure 3 shows typical transfer characteristics of an n-channel enhancement-mode MOSFET, and Figure 4 shows the V_{GS}/I_D curves of the same device when powered from a 15V supply. Note that no significant I_D current flows

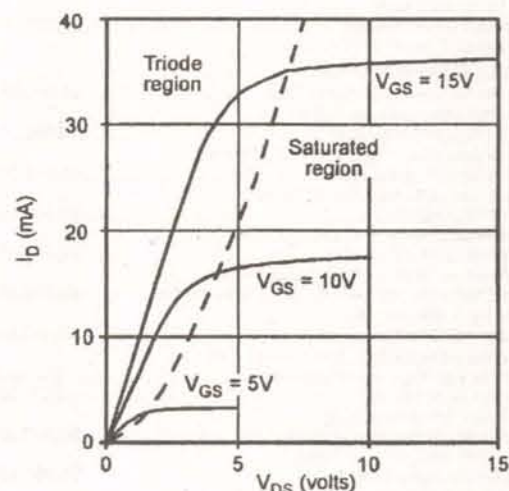


Figure 3. Typical transfer characteristics of 4007UB n-channel enhancement-mode MOSFETs.

until the gate voltage rises to a threshold (V_{TH}) value of a few volts but that, beyond this value, the drain current rises in a non-linear fashion.

Also note that the Figure 3 graph is divided into two characteristic regions, as indicated by the dotted line; these being the 'triode' region, in which the MOSFET acts like a voltage-controlled resistor, and the 'saturated' region, in which it acts like a voltage-controlled constant-current generator.


Because of their very high input resistances, MOSFETs are vulnerable to damage via electrostatic discharges; for this reason, MOSFETs are sometimes provided with integral protection via diodes or zeners.

THE 4007UB

The easiest and cheapest practical way of learning about enhancement-mode MOSFETs is via a 4007UB IC, which is the simplest member of the popular CMOS '4000-series' digital IC range, and actually houses six useful MOSFETs in a single 14-pin DIL package.

Figure 5 shows the functional diagram and pin numbers of the 4007UB, which houses two complementary pairs of independently-accessible MOSFETs and a third complementary MOSFET pair that

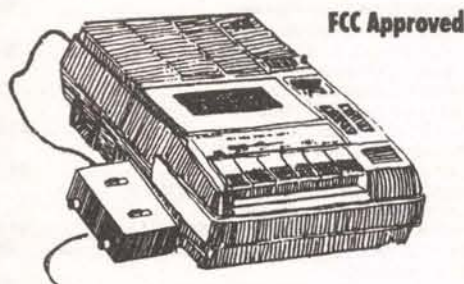TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00


Call 321-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

PCB LAYOUT Software For Windows - FREE

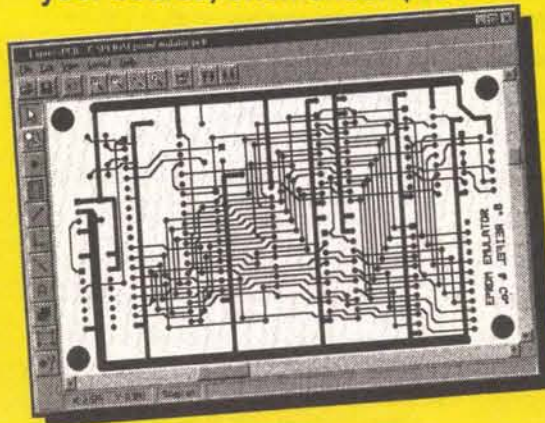- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

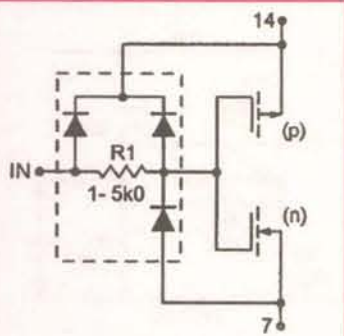


Figure 6. Internal-protection network (within dotted lines) on each input of the 4007UB.

is connected as a standard CMOS inverter stage.

Each of the IC's three independent input terminals is internally connected to the standard CMOS protection network shown in Figure 6.

Within the IC, Q1, Q3, and Q5 are p-channel MOSFETs, and Q2, Q4, and Q6 are n-channel types. Note that the performance graphs of Figures 3 and 4 actually apply to the individual n-channel devices within this CMOS IC.

The 4007UB usage rules are simple. In any given application, all unused IC elements must be disabled. Complementary pairs of MOSFETs can be disabled by connecting them as standard CMOS inverters (i.e., gate-to-gate and source-to-source) and tying their inputs to ground, as shown in Figure 7.

Individual MOSFETs can be disabled by tying their source to their substrate and leaving the drain open circuit. In use, the IC's input terminal must not be allowed to rise above V_{DD} (the supply voltage) or fall below V_{SS} (zero volts).

To use an n-channel MOSFET, the source must be tied to V_{SS} , either directly or via a current-limiting resistor. To use a p-channel MOSFET, the source must be tied to V_{DD} , either directly or via a current-limiting resistor.

LINEAR OPERATION

To fully understand the operation and vagaries of CMOS circuitry, it is necessary to understand the linear characteristics of basic MOSFETs, as shown in the graph of Figure 4.

Note that negligible drain current flows until the gate rises to a 'threshold' value of about 1.5 to 2.5 volts, but that the drain current then increases almost linearly with further increases in gate voltage.

Figure 8 shows how to use an n-channel 4007UB MOSFET as a linear inverting amplifier. R1 acts as Q2's drain load, and R2-Rx bias the gate so that Q2 operates in the linear mode.

The Rx value is selected to give the desired quiescent drain voltage, and is normally in the 18k to

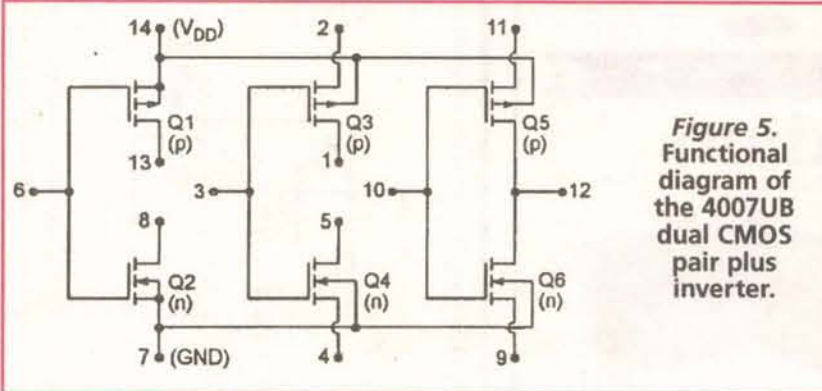


Figure 5. Functional diagram of the 4007UB dual CMOS pair plus inverter.

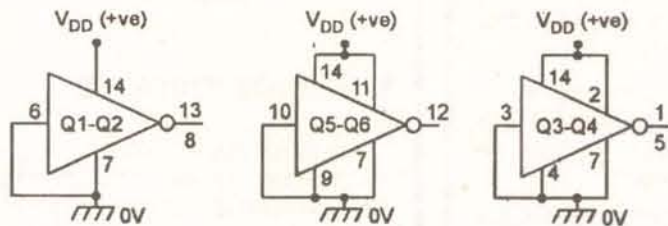


Figure 7. Individual 4007UB complementary pairs can be disabled by connecting them as CMOS inverters and grounding their inputs.

100k range.

The amplifier can be made to give a very high input impedance by wiring a 10M isolating resistor between the R2-Rx junction and Q2 gate, as shown in Figure 9.

Figure 10 shows how to use an n-channel MOSFET as a unity-gain non-inverting common-drain amplifier or source follower.

The MOSFET gate is biased at half-supply volts by the R2-R3 divider, and the source terminal automatically takes up a quiescent value that is slightly more than V_{TH} below the gate value.

The basic circuit has an input impedance equal to the paralleled

values of R2 and R3 (=50k), but can be increased to greater than 10M by wiring R4 as shown.

Alternatively, the input impedance can be raised to several hundred megohms by bootstrapping R4 via C1 as shown in Figure 11.

Note from the above description that the enhancement-mode MOSFET performs like a conventional bipolar transistor, except that it has an ultra-high input impedance and has a substantially larger input-offset voltage (the base-to-

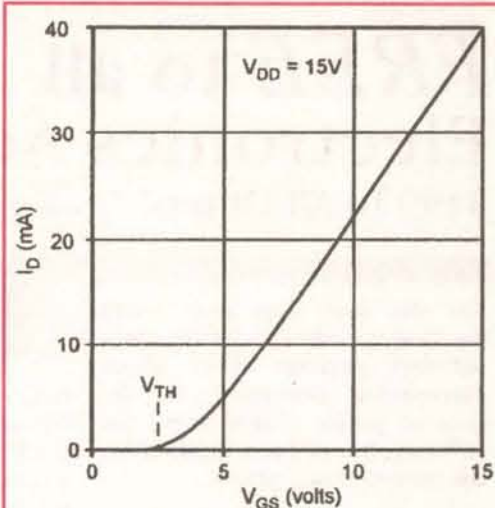


Figure 4. Typical V_{GS}/I_D characteristics of 4007UB n-channel enhancement-mode MOSFET.

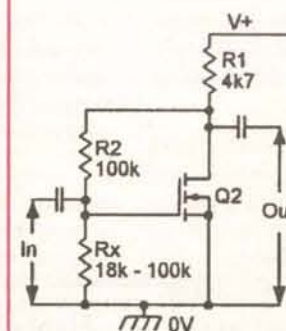


Figure 8. Method of biasing n-channel 4007UB MOSFETs for use as a linear inverting amplifier (with medium input impedance).

emitter offset of a bipolar is typically 600mV, while the gate-to-source offset voltage of a MOSFET is typically two volts).

Allowing for these differences, the enhancement-mode MOSFET can thus be used as a direct replacement in many small-signal bipolar transistor circuits.

BIG POWER

LOW COST

Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5 V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware dock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets

www.micromint.com

To Order Call: **1-800-635-3355**

Micromint, Inc. 740 Florida Central Pkwy., Longwood, FL 32750
(407) 262-0066

Write In 154 on Reader Service Card.

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS

See Table Of Contents: <http://www.sq-1.com>
Secure Online Ordering Is Available

PIC is a trademark of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

Voice (707) 279-8881 Fax (707) 279-8883

<http://www.sq-1.com>

FREE to all Electronics Addicts

\$199 To All Others!

when you mention this special offer #NV2000

For the first time ever we've decided to offer a proprietary software package titled, "Basic Electronics Concepts" to the general public. (Until now, the software hasn't been available to the public, at any price!).

Over 1500 Electronics teachers nationwide use this exact software package to teach Junior High through Graduate Students the basics of electronics, teaching them step by step. The total course of instruction is over 10 full hours and teaches all about resistors, potentiometers, photocells, capacitors, speakers, silicon diodes, SCRs, NPN transistors, PNP transistors, transistor oscillators, and IC timers!

We sell this package day in and day out for \$199 to teachers, parents, and hobbyists that want a detailed, complete method of teaching electronics to themselves, friends or children.

Here's our offer: As part of our "Grand Opening", for a limited time every first time order on the web will receive a copy of this incredible software absolutely free!

We have a limited quantity of the software program in stock, at last check, approximately 1136 units, so place your order today!

Here's a few of the 117 different kits that you can build that we offer ONLINE:

Color Organs • FM Transmitter Kits
Amplifier Kits • Strobe Light Kits
Alarm Kits • Radios Kits • Meter Kits
Keypad Lock Kits • Infrared Kits
and more!

We carry national brands and guarantee that your order will arrive promptly and be exactly what you expected! **ORDER NOW!**

24 Hour Ordering on the web:
www.HobbyTron.com

Build a kit today!

PHONE: 877-606-8766 FAX: 800-470-1606

TRON

HOBBY
TRON.com

Write In 151 on Reader Service Card.

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

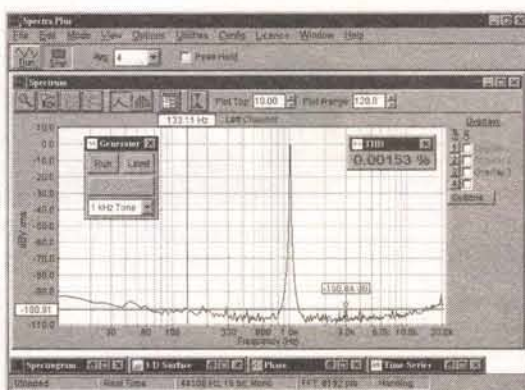- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only – not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.

Spectra Plus
FFT Spectral Analysis System

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

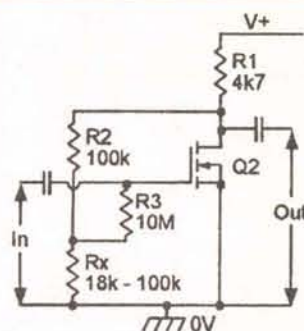


Figure 9. High impedance version of the inverting amplifier.

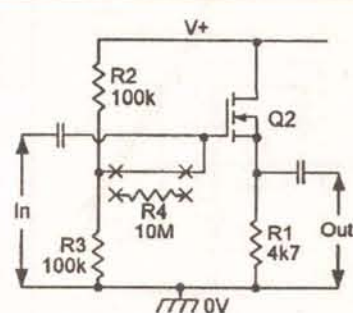


Figure 10. Methods of biasing n-channel 4007UB MOSFET as a unity-gain non-inverting amplifier or source follower.

THE CMOS INVERTER

A major application of enhancement-mode MOSFETs is in the basic CMOS inverting stage of Figure 12(a), in which an n-channel and a p-channel pair of MOSFETs are wired in series but share common input and output terminals.

This basic CMOS circuit is primarily meant for use in digital applications (as described towards the end of Part 1 of this series), in which it consumes negligible quiescent current but can source or sink substantial output currents.

Figures 12(b) and 12(c) show the inverter's digital truth table and its circuit symbol. Note that Q5 and Q6 of the 4007UB IC are fixed-wired in the CMOS inverter configuration.

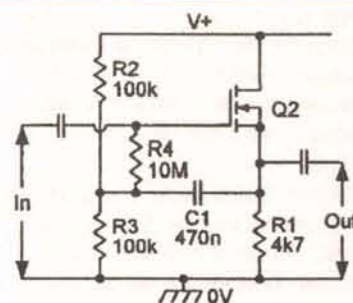


Figure 11. Bootstrapped source follower has ultra-high input impedance.

configuration.

Although intended primarily for digital use, the basic CMOS inverter can be used as a linear


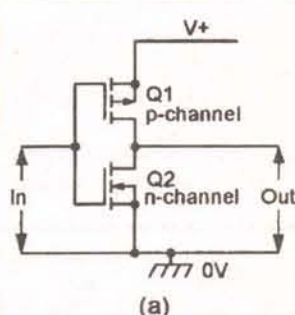


Figure 12. Circuit (a), truth table (b), and symbol (c) of the basic CMOS digital inverter.

In	Out
0	1
1	0

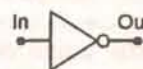

Electro Mavin

Great Buys - Great Products - Great Gadgets
Check Out Our Great WebSite at

<http://mavin.com>

For Computer Items, Hobbies Projects,
Microwave Goodies and Some of the
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

john@mavin.com or mark@mavin.com

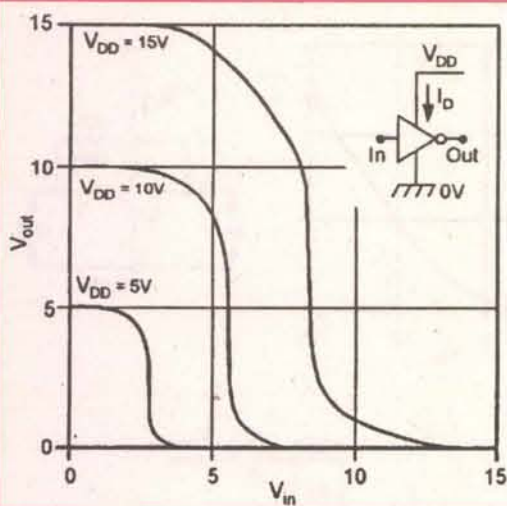


Figure 14. Typical input-to-output voltage transfer characteristics of the 4007UB simple CMOS inverter.

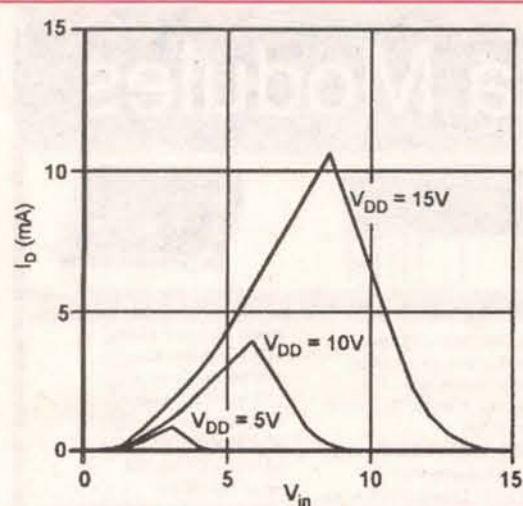


Figure 13. Drain-current transfer characteristics of the simple CMOS inverter.

amplifier by biasing its input to a value between the logic-0 and logic-1 levels; under this condition Q1 and Q2 are both biased partly on, and the inverter thus passes significant quiescent current.


Figure 13 shows the typical drain-current (I_D) transfer characteristics of the circuit under this condition; I_D is zero when the input is at zero or full supply volts, but rises to a maximum value (typically 0.5mA at 5V, or 10.5mA at 15V) when the input is at roughly half-supply volts, under which condition both MOSFETs of the inverter are biased equally.

Figure 14 shows the typical input-to-output voltage-transfer characteristics of the simple CMOS inverter at different supply voltage values. Note that the output voltage changes by only a small amount when the input voltage is shifted around the V_{DD} and 0V levels, but that when V_{in} is biased at roughly half-supply volts, a small change of input voltage causes a large change of output voltage.

Typically, the inverter gives a voltage gain of about 30dB when used with a 15V supply, or 40dB at 5V.

Figure 15 shows a practical linear CMOS inverting amplifier

Figure 16. Typical A_V and frequency characteristics of the linear-mode basic CMOS amplifier.

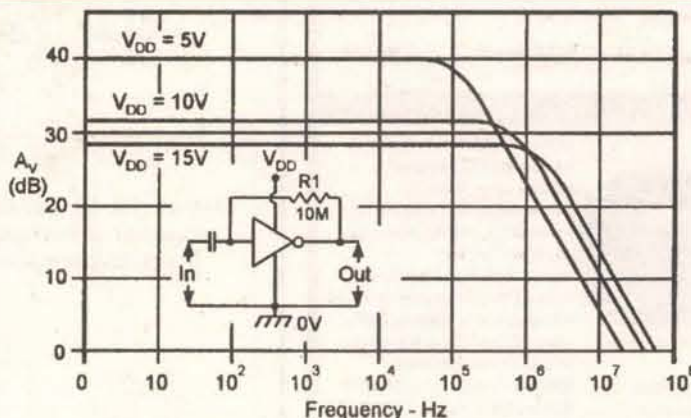

stage. It is biased by wiring 10M resistor R1 between the input and output terminals, so that the output self-biases at approximately half-supply volts.

Figure 16 shows the typical voltage gain and frequency characteristics of this circuit when operated at three alternative supply rail values; this graph assumes that the amplifier output is feeding into the high impedance of a 10M/15pF oscilloscope probe and, under this condition, the circuit has a bandwidth of 2.5MHz when operating from a 15V supply.

As would be expected from the voltage transfer graph of Figure 14, the distortion characteristics of the CMOS linear amplifier are quite good with small-ampli-

tude signals (output amplitudes up to 3V peak-to-peak with a 15V supply), but the distortion then increases as the output approaches the upper and lower supply limits.

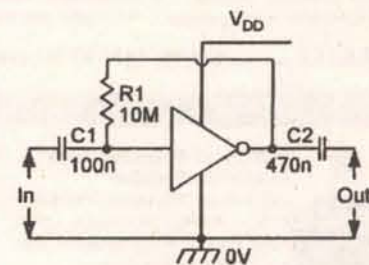


Figure 15. Method of biasing the simple CMOS inverter for linear operation.


Unlike a bipolar transistor circuit, the CMOS amplifier does not 'clip' excessive sinewave signals, but progressively rounds off their peaks.

Figure 17 shows the typical drain-current versus supply-voltage

Digital Storage Oscilloscopes From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

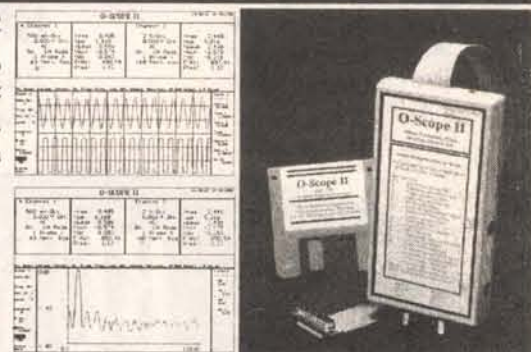O-Scope Ip \$189.
O-Scope II \$349.
Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit. Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, low cost differential amplifier, cuts through common mode noise problems to reveal low voltage signals. With gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems ???
Check out Serial !! Our lowcost serial channel analyzer only \$99.00.

Allison Technology Corporation
2006 Finney Vallet Rd., TX. 77471 U.S.A.
800-980-9806 or 281-239-8500
<http://www.atcweb.com> atc@accesscomm.net

HOT NEW PRODUCTS!!!



Phone Manager - Reverse Caller ID. Now you can keep track of outgoing numbers. Records length, time and date of call. Keep track of the children, the wife, or the phone company. Easy hookup via phone jack.

New low price \$79.95


Phone and Internet Voice Changer - This device is new to the market and provides realistic sounding voices. It allows you to interface directly to your phone jack, or computer via patch cord and mic.

Intro price \$129.95



Order directly from our website at www.electronickits.com
We also have over 200 Electronic Plans, Kits and Spy Products
Carl's Electronics Inc. sales@electronickits.com

RF Data Modules

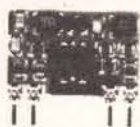

AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current, 4mA typical.
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10

AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery, CMOS
- Low current, 2.4mA typical
- 2kHz data rate, CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95

FM TRANSCIEVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCIEVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



70 x 65 x 15mm

- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation

Transceiver..... RTcom-4xx..... \$247.90
 Transmitter..... RTcomTx-4xx..... \$ 87.15
 Receiver..... RTcomRx-4xx..... \$105.52



Tel: (416)236-3858

Fax: (416)236-8866

www.abacom-tech.com

abacomtech@compuserve.com

Metric
Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886

www.metricsales.com



Scopes, Meters, Analyzers, Power Supplies, Signal Generators, Counters, Recorders and more

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu, Wavetek, Keithley, and more

Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty

Save 30-90% • 5-Day Free Trial

Figure 17. Typical I_D/V_{DD} characteristics of the linear-mode CMOS amplifier.


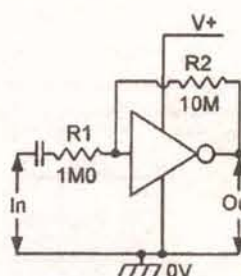
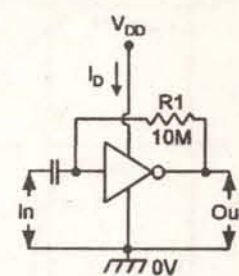
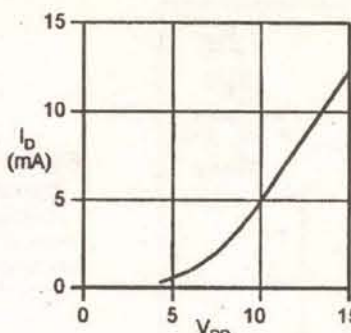


Figure 19. Linear CMOS amplifier wired as 10x inverting amplifier.

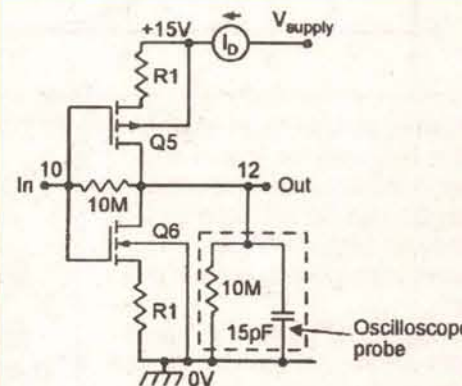

R1	I_D	A_V (V_{out}/V_{in})	Upper 3dB Bandwidth
0	12.5mA	20	2.7MHz
100R	8.2mA	20	1.5MHz
560R	3.9mA	25	300kHz
1k0	2.5mA	30	150kHz
5k6	600 μ A	40	25kHz
10k	370 μ A	40	15kHz
100k	40 μ A	30	2kHz
1M0	4 μ A	10	1kHz

Figure 18. Micropower 4007UB CMOS linear amplifier, showing method of reducing I_D , with performance details.

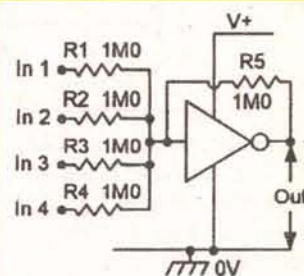


Figure 20. Linear CMOS amplifier wired as unity-gain four-input audio mixer.


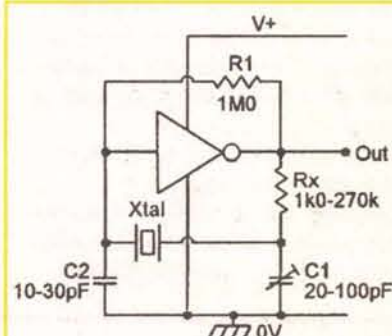


Figure 22. Linear CMOS amplifier wired as a crystal oscillator.

Figure 21. Linear CMOS amplifier wired as an integrator.

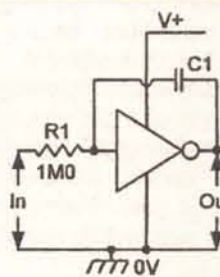

characteristics of the CMOS linear amplifier. The current typically varies from 0.5mA at 5V, to 12.5mA at 15V.

In many applications, the quiescent supply current of the 4007UB CMOS amplifier can be usefully reduced — at the cost of reduced amplifier bandwidth — by wiring external resistors in series with the source terminals of the two MOSFETs of the CMOS stage, as shown in the 'micropower' circuit of Figure 18.

This diagram also lists the effects that different resistor values have on the drain current, voltage gain, and bandwidth of the ampli-

er when operated from a 15V supply and with its output loaded by a 10M/15pF oscilloscope probe.

Note that the additional resistors of the Figure 18 circuit increase the output impedance of the amplifier (the output impedance is roughly equal to the $R1-A_V$ product), and this impedance and the external load resistance/capacitance has a great effect on the overall gain and bandwidth of the circuit.

When using a 10k value for $R1$, for example, if the load capacitance is increased (from 15pF) to 50pF, the bandwidth falls to about 4kHz, but if the capacitance is reduced to 5pF, the bandwidth increases to 45kHz. Similarly, if the resistive load is reduced from 10M to 10k, the voltage gain falls to unity; for significant gain, the load resistance must be large relative to the output impedance of the amplifier.

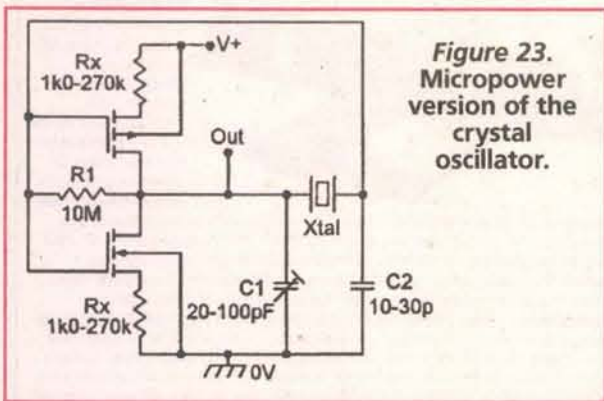


Figure 23.
Micropower
version of the
crystal
oscillator.

The basic (unbiased) CMOS inverter stage has an input capacitance of about 5pF and an input resistance of near-infinity. Thus, if the output of the Figure 18 circuit is fed directly to such a load, it shows a voltage gain of x30 and a bandwidth of 3kHz when R1 has a value of 1M Ω ; it even gives a useful gain and bandwidth when R1 has a value of 10M, but consumes a quiescent current of only 0.4 μ A.

PRACTICAL CMOS

The CMOS linear amplifier can easily be used in either its standard or micropower forms to make a variety of fixed-gain amplifiers, mixers, integrators, active filters, and oscillators, etc. A selection of such circuits is shown in Figures 19 to 23.

Figure 19 shows the practical circuit of an x10 inverting amplifier. The CMOS stage is biased by feedback resistor R2, and the voltage gain is set at x10 by the R1/R2 ratio. The input impedance of the circuit is 1M Ω , and equals the R1 value.

Figure 20 shows the above circuit modified for use as an audio 'mixer' or analog voltage adder. The circuit has four input terminals, and the voltage gain between each input and the output is fixed at unity by the relative values of the 1M Ω input resistor and the 1M Ω feedback resistor.

Figure 21 shows the basic CMOS amplifier used as a simple integrator.

Figure 22 shows the linear CMOS amplifier used as a crystal oscillator. The amplifier is linearly biased via R1 and provides 180° of phase shift at the crystal resonant frequency, thus enabling the circuit to oscillate. If the user wants the crystal to provide a frequency accuracy within 0.1% or so, Rx can be replaced by a short and C1-C2 can be omitted. For ultra-high accuracy, the correct values of Rx-C1-C2 must be individually determined (the diagram shows the typical range of values).

Finally, Figure 23 shows a 'micropower' version of the CMOS crystal oscillator. In this case, Rx is actually incorporated in the amplifier. If desired, the output of this oscillator can be fed directly to the input of an additional CMOS inverter stage, for improved waveform shape/amplitude. **NV**

Enter the Nuts & Volts and ExpressPCB Electronics Design Contest.

Hurry!
Time is
running
out ...

ENTRY DEADLINE: JULY 19TH

See page 10 for details ...

AMAZING DEVICES

Laser Window Bounce Listening System

Powerful listening system, yet simple in operation. You shine a LASER at a window and intercept the reflected beam with our ultra-sensitive filtered OPTICAL RECEIVER. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on the output power of the laser and optics used.

- LWB9 Plans and all Data for 3 Laser Window Bounce Systems.....\$20.00
- LWB6K Kit of Complete 100' System with Visible Laser for Demo/Science Project.....\$129.95
- LLR30 Optical RECEIVER with voice filter.....\$99.95
- LLR3K Kit of Optical Receiver.....\$69.95
- LLR40 Higher performance with low noise preamp, basic optics and deluxe headsets.....\$199.95
- CWL10 10 mw ClassIII B Invisible IR LASER for 500'.....\$199.95
- CWL1K Kit of LASER.....\$149.95
- LM650P5 5 mw ClassIIIA Visible Red Laser Module for up to 100'.....\$19.95
- LM650P10 10 mw ClassIIIB Visible Red Laser Module for up to 200'.....\$69.95

Gravity Motor

Electrical charge reactions produce the effect of "anti gravity." You build a model craft from simple parts and levitate it with our ion power source. Battery or 115vac operation. Great science or fascinating research project includes our gravity handbook.

- GRA3 Plans/Book.....\$20.00
- GRA3K Power Source Kit.....\$99.95
- GRA30 Assembled Above.....\$149.95

Tesla Coil

Produces 30" Sparks
Create a spectacular display of nature own lightning. Many amazing experiments possible. See in action on our web site!

- BTC4 Plans.....\$20.00
- BTC4K kit.....\$799.95
- BTC40 Ready to use.....\$999.95
- Smaller Version (8-10" Sparks)
- BTC3 Plans.....\$15.00
- BTC3K Kit.....\$349.95
- BTC30 Ready to Use.....\$449.95

Ion Ray Guns

Star Wars Technology Directs Energy
Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity, etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments. Handheld battery operated and easy to operate.

- IOG7/9 Plans.....\$10.00
- IOG7K Kit/Plans.....\$99.95
- IOG70 Assembled/Tested.....\$149.95
- Higher Powered Device
- IOG9K Kit/Plans.....\$129.95
- IOG90 Assembled/Tested.....\$199.95

6 Easy FM Xmr Projects!

- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.
- 2 1 Mile+ Telephone Transmitter.
- 3 Line Powered Phone Transmitter Never Needs Batteries!
- 4 Tracking/Homing Beacon Beeping Transmitter
- 5 Video/Audio Broadcaster 1 Mi.
- 6 TV/FM Radio Disrupter. Neat Prank! Discretion Required

Includes Hints Using Wireless Devices

- COMBOX Parts Above 6 Projects.....\$49.95
- COMBOP Plans Above 6 Projects.....\$10.00

TAKE CONTROL Using Electronic Hypnosis

Electronic circuitry induces hypnotic as well as ALPHA relaxed mind states. Place subjects under your control

- HYP2 Plans.....\$10.00
- HYP2K Kit/Plans.....\$49.95
- HYP20 Ready to Use.....\$69.95
- MIND2 Plans for Mind Control.....\$15.00
- MIND2K Kit/Plans.....\$49.95
- MIND20 Ready to Use.....\$79.95

Pain Field Pistol

Caution! Do not aim at people!
Blast out rodents with high power ultrasonics. Handheld and battery operated with all controls. Rental units available.

- PPP1 Plans.....\$8.00
- PPP1K Kit/Plans.....\$49.95
- PPP10 Ready to Use.....\$79.95

Semi-Cond Burning Lasers

10mw to 2 Watts of continuous output!
Use for directed beam of heat, illumination source for night vision, laser window bounce IR driver for ultra-bright green lasers.

- CWL5K Kit/Plans minus diode.....\$199.95
- CWL50 Assembled minus diode.....\$299.95
- LD34 CW 3/4 W 980nm diode.....\$249.95

Mind&Brain Controllers

Incredible device Turbo charges memory, Boost mental powers, Controls stress, Speeds up healing processes and Uncover hidden potentials. High quality unit with many features.

- BWPLUS-APOLLO Ready to use.....\$189.95
- BWII- EINSTEIN Lower cost unit.....\$129.95

Theramagnetic Pulsar™

Complex Magnetic waves are claimed to produce many health benefits. Board level experimental device is sold for research purposes only.

- THMAG10 Lab Assembled.....\$24.95

Amazing Gravitron

Remarkable true levitation without any tethering or external sources of energy. Winning science project. Includes self starter

- GRV10 - Anti Gravity Top.....\$39.95
- GRV30 - Super Levitator.....\$49.95

Cybernetic Ear!

Provides that "extra edge" for many listening applications. Enhances 3 to 4x of normal.

- CYBEREAR.....\$19.95

Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D

- HOVER Plans and Data.....\$25.00

Mini TESLA Coil

Lights up a 4' fluorescent tube-all without any contact!! Yet only 3" tall!

- MTC1K Kit/Plans.....\$19.95
- MTC10 Assembled.....\$34.95

Transistorized TESLA Coil

Amazing and bizarre effects turn a normal light bulb into a spectacular plasma display!! With adjustable frequency control. Safe 12vdc input

- TCL5 Plans.....\$8.00
- TCL5K Kit/Plans.....\$59.95
- TCL50 Assembled and Tested.....\$99.95

Telephone Line Grabber Room Listener Controller and Call Diverter

Listen to your premises. Break in to calls Control household appliances. Remote dial long distance calls-from anywhere!!

- TELCON4 Plans.....\$10.00
- TELCON4K Kit/Plans.....\$129.95
- TELCON40 Ready to Us.....\$169.95

Attention! High Voltage Modules

Battery powered for hovercraft, plasma guns, anti gravity, force fields, pyrotech

- MIMIMAX4 4KV.....\$19.95
- MIMIMAX3 3KV.....\$17.95
- MIMIMAX2 2KV.....\$14.95

Nightstar Night Viewer

Sees in total darkness
• 35000x Light Gain
• Over 100 yds Recognition
• Built in IR Illuminator
• 20 degree Field of View
• 20 Hours Battery Life
• Spectral Response 810-840 nm.

- NSTAR10 - Ready to Use.....\$239.95

Jacobs Ladder

Pyrotechnical traveling fiery plasma expands over 3' before evaporating into space. Solid state circuitry with adjustable arc control. 115/230 volt operation. Uses safe high frequency energy.

- JACK1 Plans.....\$8.00
- JACK1K Supply, Mtg Blks, Ladders.....\$149.95
- JACK10 Ready to Use.....\$249.95

3 Mi FM Voice Transmitter

Crystal clear performance. Many applications. Easy to assemble

- FMV1K Parts and plans.....\$39.95

Burning Cutting Lasers

Current and Future Weapons System
We Stock Parts!
LC3 Plans Poor Mans CO₂ System.....\$15.00
LC7 Plans Lab CO₂ System 30W+.....\$20.00
LAGUN2 Plans Nd,Yag, Ruby 6Kw.....\$20.00
All Three Plans for only.....\$25.00!!

PLASMA FIRE SABER

Patented Moving Light Concept Defies all Logic as it Appears to Evaporate into Space!! Duplicate the STAR WARS effect
Replaceable Blades, Override Switch Interactive Sound Module Available on Request

- SAB15K - Kit 15" Display.....\$29.95+\$5.00 s&h
- SAB24K - Kit 24" Display.....\$59.95+\$5.00 s&h
- SAB36K -Kit 36" Display.....\$129.95+\$15.00 s&h

See Our "Action" Web Site at
www.amazing1.com

Experiment with and Construct Lasers, Phasers, Hypnosis, Mind Control, TESLA COILS, Time Travel, Rail Guns, Magnetic Cannons, Coil and Sleeve Guns, Super High Gravity Pulses, Explode Wires and Water, Antigravity, Levitation, Mass Warping, Magnetic Can Crushing, Plasma Propulsion, High Energy Radio Frequency Guns (Herf), EMP, Lattice Snapping, Force Fields, Ion Ray Guns and all Types of Electrical Pyrotechnics, Plasma and Neon Displays, Sound Blasters, Ultrasonics, Super Hearing, Long Range Transmitters, Jammers, Personal and Property Protection, Surveillance Plus More!!

Ultra Bright Green Laser visible over a mile!!

30 to 50x brighter than the red pointers. Shirt pocket sized pen .55" x 6.3" Full 5mw. Operates for hours from two "AAA" batteries. Call for pricing as we will not be undersold!!!!!!

Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031

1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request
Pay by MC,VISA,Cash, Check, MO, COD. Add \$5.00 S&H plus \$5.00 if COD. Overseas Contact for Proforma

Write in 157 on Reader Service Card.