

# Understanding HEXFET<sup>®</sup> Switching Performance

By S. Clemente, B.R. Pelly, A. Isidori

## Abstract

A simple analytical technique for predicting the switching performance of the HEXFET is presented.

Closed-form solutions for the gate voltage, drain current, and drain voltage during the switching interval, in terms of each of the relevant device and circuit parameters, are derived.

A specific design example is considered, in which the effects are demonstrated of the drive circuit resistance, drain circuit inductance, and drive voltage, on the switching time and switching energy.

## I. Introduction

The HEXFET is an almost ideal switch, which is characterized by very high gain and extremely fast switching characteristics. While users often ignore the intricacies of the switching operation, on the assumption that this is not critical to the overall design, the fact is that a clear understanding of the factors that affect switching can have a profound effect upon the system performance, particularly in high frequency circuits, and is, therefore, of vital interest to the user who needs to optimize his design.

Another reason why many users have a rather incomplete understanding of the HEXFET's switching operation is that the device is still relatively new, and HEXFET circuit design know-how has not yet matured. Users also tend to relate to their experience with bipolar transistors. The switching operation of bipolars is very difficult to analyze, and hence an empirical "try

it and see" approach has generally held sway over more rigorous analytical techniques.

One of the major "incidental" benefits of the HEXFET—in addition to its very real operating advantages—is that it lends itself rather well to analytical modeling; its operation can, therefore, be predicted rather easily at the design stage.

The primary objective of this application note is to show how, starting with a simple model of the HEXFET and using logical reasoning, the principles that govern the HEXFET's operation in a switching circuit can be readily predicted, and approximate mathematical relationships that describe these waveforms can be readily derived. Emphasis will be placed upon an understanding of basic principles.

## II. The HEXFET Model

The electrical model for the HEXFET is shown in Figure 1. The self-capacitances are actually nonlinear functions of the applied voltage; also, to some extent, of the drain current. For purposes of analysis, however, these capacitances will be assumed to have fixed values; this does not detract from our basic objective, which is to understand fundamental principles.

This simple model of the HEXFET is assumed to have a linear transfer characteristic, with slope  $g_{fs}$  and gate threshold voltage  $V_T$ . The external drain current is assumed to be instantaneously responsive to the gate voltage, for operation in the active region.


Under transient switching conditions, charging and discharging currents flow through the various self-capacitive elements. The paths for components of these currents is through the drain-to-source terminals. The presence of these internal capacitive currents is assumed *not* to affect the transfer characteristic between the gate voltage and the external drain current.

The presence of  $C_{DS}$  will also generally be ignored for operations in the active region. This is valid because the effect of the gate-to-drain capacitance  $C_{GD}$ —providing, as it does, a coupling path from the drain circuit to the relatively sensitive gate circuit—generally "swamps" the effect of  $C_{DS}$ .

## III. The Circuit Model

The clamped load is assumed to have sufficient inductance that the current flowing in it has a constant value  $I_Q$  throughout the switching interval (Figure 2). The inductance  $L_l$  represents "unclamped" stray circuit inductance.

The effect of the common source inductance  $L_S$ , shown dashed in Figure 2, will generally be neglected. This is not

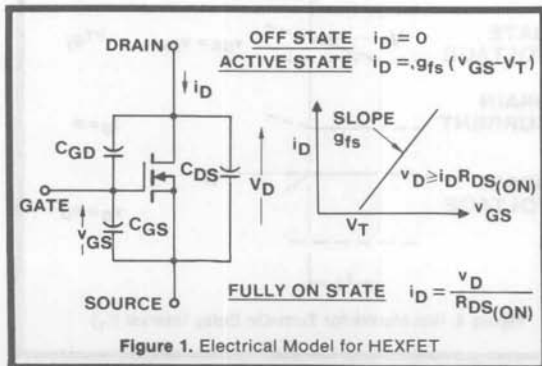

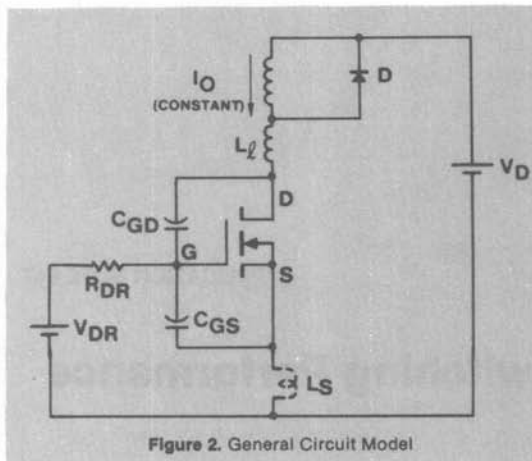


Figure 2. General Circuit Model

because it is necessarily negligible, but because to include it in a general analysis complicates the issue, making clarity of presentation and a grasp of fundamental principles more difficult. We prefer instead to consider the modifying effect of this inductance once the basic analysis is complete.

A number of switching circuits can be resolved into the equivalent circuit shown in Figure 2, or variants thereof, and in this sense the analysis is fairly general. The main point, however, is that the chosen circuit serves as a vehicle for obtaining an understanding of basic principles; once this has been accomplished the designer will be well equipped to deal with the switching operating of the HEXFET in any circuit.

#### IV. Nomenclature

|             |  |
|-------------|--|
| $v_D$       | Instantaneous drain-source voltage                         |
| $v_{GS}$    | Instantaneous gate-source voltage                          |
| $v_{GD}$    | Instantaneous gate-drain voltage                           |
| $V_D$       | Steady applied drain circuit voltage                       |
| $V_{DR}$    | Applied positive gate drive voltage (turn-on)              |
| $V_T$       | Gate threshold voltage                                     |
| $V_F$       | Positive gate drive "forcing" voltage ( $V_{DR} - V_T$ )   |
| $-V_2$      | Applied negative gate drive voltage (turn-off)             |
| $V_{D}^*$   | Initial value of drain-source voltage at start of interval |
| $V_{GS}^*$  | Initial value of gate-source voltage at start of interval  |
| $V_{CLAMP}$ | Drain-source clamping voltage                              |

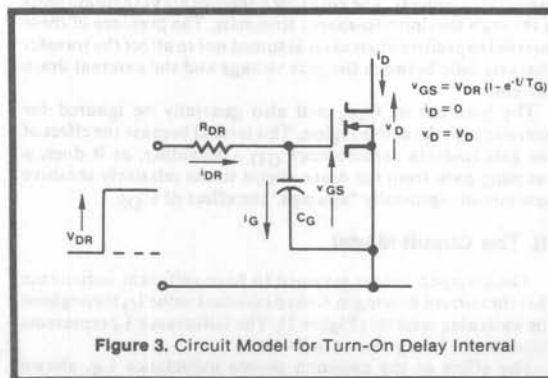


Figure 3. Circuit Model for Turn-On Delay Interval

|              |   |
|--------------|---|
| $i_D$        | Instantaneous current flowing into drain terminal                         |
| $i_{GS}$     | Instantaneous current in $C_{GS}$   |
| $i_{GD}$     | Instantaneous current in $C_{GD}$   |
| $I_O$        | Steady current in clamped inductive load                                  |
| $I_D^*$      | Initial value of current flowing into drain terminal at start of interval |
| $R_{DR}$     | Gate drive circuit resistance   |
| $R_{DS(ON)}$ | On-state resistance of HEXFET   |
| $R_l$        | Stray drain circuit resistance  |
| $L_l$        | Stray drain circuit inductance  |
| $L_s$        | Inductance in series with source that is common to gate circuit           |
| $C_{GS}$     | Gate-source capacitance of HEXFET   |
| $C_{GD}$     | Gate-drain capacitance of HEXFET  |
| $C_{DS}$     | Drain-source capacitance of HEXFET  |
| $C_G$        | $C_{GS} + C_{GD}$   |
| $C_D$        | $C_{DS} + C_{GD}$   |
| $g_{fs}$     | Transconductance of HEXFET  |
| $p$          | Differential operator   |

#### V. Analysis of Switching Operation

Each switching sequence, either from the OFF to the ON condition, or vice versa, is subdivided into a number of separate intervals, for which different constraints and conditions apply. Each interval will be considered in sequence. The end-conditions for one interval become the starting conditions for the next. For simplicity we will take  $t = 0$  at the start of each new interval.

The approach will be to consider each time interval in a qualitative manner, and through a process of reasoning based upon the known conditions and constraints, deduce as much as we can about the general shapes of the dynamic waveforms of drain voltage, drain current and gate voltage.

For certain time intervals this qualitative reasoning leads directly to the parametric analytic solution for that interval; for other time intervals, however, the analytic solutions are not so quickly obtained, except for parametric extremes at each end of the possible spectrum of external circuit conditions; a wide middle range of conditions remains for which derivation of the parametric solutions is rather too lengthy to be presented in its entirety, and in these cases we will simply state the final solutions.

#### A. TURN-ON

##### Turn-On Delay Interval 1

The circuit model for this interval is shown in Figure 3, and operating waveforms are shown in Figure 4. The applied drive

 


Figure 4. Waveforms for Turn-On Delay Interval ( $t_1$ )



Because the rate of change of drain voltage is small (almost zero), virtually no current flows through  $C_{GD}$ , and the drive circuit continues to see the simple parallel combination of  $C_{GD}$  and  $C_{GS}$  (as it did during the turn-on delay period). The gate-to-source voltage,  $v_{GS}$ , therefore, continues to rise exponentially:

$$v_{GS} = V_F \left( 1 - e^{-t/T_G} \right) \quad (3)$$

The drain current rises in sympathy with the gate voltage:

$$i_D = g_{fs} V_F \left( 1 - e^{-t/T_G} \right) \quad (4)$$

The drain voltage is equal to the circuit voltage  $V_D$ , less the small (almost negligible) voltage drop across  $L_l$ :

$$v_D = V_D - \frac{g_{fs} V_F L_l e^{-t/T_G}}{T_G} \quad (5)$$

The period ends when  $i_D = I_O$ .

It remains to quantify how small the ratio  $L_l/R_{DR}$  must be for equations (3) through (5) to remain valid. The essential condition is that the rise of drain current must, for all practical purposes, be exclusively under the influence of the applied drive voltage. This means that whatever voltage change occurs across  $L_l$  should not be noticed in the gate circuit. The current through  $C_{GD}$  will, therefore, be small by comparison with the current through  $C_{GS}$  ( $C_{GS}$  is typically about  $10 \times C_{GD}$ ; however, a sufficiently large voltage change at the drain would produce a current through  $C_{GD}$  which is comparable to or larger than that through  $C_{GS}$ ).

The essential condition therefore is that  $i_{GD} [= C_{GD} (dv_D/dt)]$  should be small by comparison with  $i_{GS} [= C_{GS} (dv_{GS}/dT)]$ .

By differentiation of equations (3) and (5), this yields:

$$\frac{L_l}{R_{DR}} < < \frac{C_{GS}^2}{g_{fs} C_{GD}} \quad (6)$$

Table 1 puts the above criterion into perspective, and shows typical value of  $L_l$  and the corresponding "minimum" values of  $R_{DR}$ , for various HEXFETs. Clearly the values of  $R_{DR}$  needed to satisfy this condition are very high relative to most

**Table 1: Limiting values of  $R_{DR}$  that define which equations (turn-on interval 2, and turn-off interval 3) are applicable, for various HEXFETs.**

|                        |                    | Small $L_l/R_{DR}$                                     |                              | Intermediate $L_l/R_{DR}$                             |                            | Large $L_l/R_{DR}$                                     |  |              |  |
|------------------------|--------------------|--|------------------------------|---|----------------------------|--|--|--------------|--|
|                        |                    | $\frac{L_l}{R_{DR}} < \frac{C_{GS}^2}{10C_{GD}g_{fs}}$ |                              | $\frac{L_l}{R_{DR}} < \frac{C_{GS}^2}{4C_{GD}g_{fs}}$ |                            | $\frac{L_l}{R_{DR}} > \frac{10C_{GS}^2}{C_{GD}g_{fs}}$ |  |              |  |
| Applicable Equations   |                    | 3-5, 37-39   |                              | 8-10, 40-42   |                            | 14-16, 43-45   |  | 24-26, 46-48 |  |
| 1RF510<br>(100V, 2.5A) | $L_l$<br>100 nH    | $R_{DR}$ -2.4k $\Omega$ min                            | $R_{DR}$ -960 $\Omega$ min   | $R_{DR}$ -960 $\Omega$ max                            | $R_{DR}$ -40 $\Omega$ max  |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -24k $\Omega$ min                             | $R_{DR}$ -9.6k $\Omega$ min  | $R_{DR}$ -9.6k $\Omega$ max                           | $R_{DR}$ -400 $\Omega$ max |  |  |              |  |
| 1RF130<br>(100V, 9A)   | $L_l$<br>100 nH    | $R_{DR}$ -1.3k $\Omega$ min                            | $R_{DR}$ -520 $\Omega$ min   | $R_{DR}$ -520 $\Omega$ max                            | $R_{DR}$ -20 $\Omega$ max  |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -13k $\Omega$ min                             | $R_{DR}$ -5.2k $\Omega$ min  | $R_{DR}$ -5.2k $\Omega$ max                           | $R_{DR}$ -200 $\Omega$ max |  |  |              |  |
| 1RF150<br>(100V, 25A)  | $L_l$<br>100 nH    | $R_{DR}$ -410 $\Omega$ min                             | $R_{DR}$ -165 $\Omega$ min   | $R_{DR}$ -165 $\Omega$ max                            | $R_{DR}$ -6 $\Omega$ max   |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -4.1k $\Omega$ min                            | $R_{DR}$ -1.65k $\Omega$ min | $R_{DR}$ -1.65k $\Omega$ max                          | $R_{DR}$ -60 $\Omega$ max  |  |  |              |  |
| 1RF710<br>(400V, 1A)   | $L_l$<br>100 nH    | $R_{DR}$ -620 $\Omega$ min                             | $R_{DR}$ -325 $\Omega$ min   | $R_{DR}$ -325 $\Omega$ max                            | $R_{DR}$ -13 $\Omega$ max  |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -6.2k $\Omega$ min                            | $R_{DR}$ -3.25k $\Omega$ min | $R_{DR}$ -3.25k $\Omega$ max                          | $R_{DR}$ -130 $\Omega$ max |  |  |              |  |
| 1RF330<br>(400V, 3.5A) | $L_l$<br>100 nH    | $R_{DR}$ -420 $\Omega$ min                             | $R_{DR}$ -170 $\Omega$ min   | $R_{DR}$ -170 $\Omega$ max                            | $R_{DR}$ -7 $\Omega$ max   |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -4.2k $\Omega$ min                            | $R_{DR}$ -1.7k $\Omega$ min  | $R_{DR}$ -1.7k $\Omega$ max                           | $R_{DR}$ -70 $\Omega$ max  |  |  |              |  |
| 1RF350<br>(400V, 9A)   | $L_l$<br>100 nH    | $R_{DR}$ -120 $\Omega$ min                             | $R_{DR}$ -50 $\Omega$ min    | $R_{DR}$ -50 $\Omega$ max                             | $R_{DR}$ -2 $\Omega$ max   |  |  |              |  |
|                        | $L_l$<br>1 $\mu$ H | $R_{DR}$ -1.2k $\Omega$ min                            | $R_{DR}$ -500 $\Omega$ min   | $R_{DR}$ -500 $\Omega$ max                            | $R_{DR}$ -20 $\Omega$ max  |  |  |              |  |

 


Figure 8(a). Waveforms for Turn-On Interval 2, Intermediate  $L\ell/R_{DR}$

$$v_{GS} = V_T + V_F - \frac{V_F}{(T_1 - T_2)} \left\{ T_1 e^{-t/T_1} - T_2 e^{-t/T_2} \right\}$$

$$i_D = g_{fs} V_F \left\{ 1 - \frac{1}{(T_1 - T_2)} (T_1 e^{-t/T_1} - T_2 e^{-t/T_2}) \right\}$$

$$v_D = V_D - \frac{g_{fs} V_F L\ell}{(T_1 - T_2)} \left\{ e^{-t/T_2} - e^{-t/T_1} \right\}$$

$$\frac{C_{GS}^2}{10C_{GD}g_{fs}} < \frac{L\ell}{R_{DR}} < \frac{C_{GS}^2}{4C_{GD}g_{fs}}$$

 


Figure 8(b). Waveforms for Turn-On Interval 2, Intermediate  $L\ell/R_{DR}$

$$v_{GS} = V_T + V_F - V_F e^{-t/T_3} \left\{ \cos \omega_3 t + \frac{1}{\omega_3 T_3} \sin \omega_3 t \right\}$$

$$i_D = g_{fs} V_F - g_{fs} V_F e^{-t/T_3} \left\{ \cos \omega_3 t + \frac{1}{\omega_3 T_3} \sin \omega_3 t \right\}$$

$$v_D = V_D - g_{fs} V_F \omega_3 L\ell e^{-t/T_3} \left\{ 1 + \frac{1}{\omega_3^2 T_3^2} \right\} \sin \omega_3 t$$

$$\frac{C_{GS}^2}{4C_{GD}g_{fs}} < \frac{L\ell}{R_{DR}} < 10 \frac{C_{GS}^2}{C_{GD}g_{fs}}$$

normal application requirements. This condition will not, therefore, be frequently met in practice; its consideration here is useful, however, because it helps to introduce the overall problem.

#### Intermediate $L\ell/R_{DR}$

We will now consider the situation when the ratio of  $L\ell/R_{DR}$  is not small, but has some intermediate value; the voltage drop across  $L\ell$  due to the increasing drain current becomes significant, and the current through  $C_{GD}$  cannot be neglected. The general circuit model of Figure 5 applies, and typical switching waves are illustrated in Figure 8(a) and (b).

The mathematical analysis is a little too lengthy to keep touch with physical realities. We will, therefore, confine ourselves to a simple statement of the results.

There are two possible sets of solutions, depending upon whether or not the system is critically damped. If overdamped, then:

$$\frac{L\ell}{R_{DR}} < \frac{C_{GS}^2}{4C_{GD}g_{fs}} \quad (7)$$

Note the similarity of condition (7) to (6). Table I also shows typical values of  $L\ell$  and corresponding minimum values of

$R_{DR}$  that satisfy equation (7). This condition is certainly more likely to be encountered than condition (6), though once again it is generally not representative of most typical practical situations.

The gate voltage,  $v_{GS}$ , the drain current,  $i_D$ , and the drain voltage  $v_D$ , are:

$$v_{GS} = V_T + V_F - \frac{V_F}{(T_1 - T_2)} \left\{ T_1 e^{-t/T_1} - T_2 e^{-t/T_2} \right\} \quad (8)$$

$$i_D = g_{fs} V_F \left\{ 1 - \frac{1}{(T_1 - T_2)} \right\} \left\{ T_1 e^{-t/T_1} - T_2 e^{-t/T_2} \right\} \quad (9)$$

$$v_D = V_D - \frac{g_{fs} V_F L\ell}{(T_1 - T_2)} \left\{ e^{-t/T_2} - e^{-t/T_1} \right\} \quad (10)$$

where

$$T_1 = \frac{2L\ell C_{GD} R_{DR} g_{fs}}{R_{DR} C_{GS} + \sqrt{R_{DR}^2 C_{GS}^2 - 4L\ell C_{GD} R_{DR} g_{fs}}} \quad (11)$$

$$T_2 = \frac{2L\ell C_{GD} R_{DR} g_{fs}}{R_{DR} C_{GS} - \sqrt{R_{DR}^2 C_{GS}^2 - 4L\ell C_{GD} R_{DR} g_{fs}}} \quad (12)$$

The end of the time interval will generally be marked by the drain voltage having fallen all the way to  $i_D \times R_{DS(ON)}$ , with the drain current not having completed its rise.

For an "underdamped" system, the converse of (7) applies:

$$\frac{L_\ell}{R_{DR}} > \frac{C_{GS}^2}{4C_{GD}g_{fs}} \quad (13)$$

The minimum values of  $R_{DR}$  shown in Table 1 that satisfy equation (7) now become the maximum values that satisfy equation (13). Generally, most practical situations will be covered by equation (13).

The gate voltage  $v_{GS}$ , the drain current  $i_D$ , and the drain voltage  $v_D$ , are:

$$v_{GS} = (V_T + V_F) - V_F e^{-t/T_3} \left\{ \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} \right\} \quad (14)$$

$$i_D = g_{fs} V_F - g_{fs} V_F e^{-t/T_3} \left\{ \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} \right\} \quad (15)$$

$$v_D = V_D - g_{fs} V_F \omega_3 L_\ell e^{-t/T_3} \left\{ 1 + \frac{1}{\omega_3^2 T_3^2} \right\} \sin \omega_3 t \quad (16)$$

where

$$T_3 = \frac{2L_\ell C_{GD}g_{fs}}{C_{GS}} \quad (17)$$

$$\omega_3 = \frac{\sqrt{4L_\ell C_{GD}R_{DR}g_{fs} - R_{DR}^2 C_{GS}^2}}{2L_\ell C_{GD}R_{DR}g_{fs}} \quad (18)$$

The end of the time interval will be marked either by the drain circuit  $i_D$  reaching  $I_O$ , or the drain voltage  $v_D$  collapsing to  $i_D \times R_{DS(ON)}$ , whichever occurs first.

### Large $L_\ell/R_{DR}$

Now consider the situation when  $L_\ell/R_{DR}$  has a large value—representing a "fast drive" circuit with a "slow" drain circuit. The equivalent circuit model is shown in Figure 9, and switching waves are illustrated in Figure 10. Note that we are ignoring the gate-to-source capacitance  $C_{GS}$ . This is valid because with large  $L_\ell/R_{DR}$  ratio the "Miller" effect predominates and current through  $C_{GS}$  is small by comparison with that through  $C_{GD}$ .

The inductance  $L_\ell$  now presents such a high impedance that the increase of drain current "requested" by the drive circuit cannot be satisfied; the drive circuit is largely impotent to bring about the drain current that it asks for.

The drain voltage now collapses relatively quickly—generally well before the current rise is completed. The end of the period is marked by the HEXFET reaching the essential condition of a "closed switch"—the voltage across it having collapsed completely.

The mathematics are rather simple; in order to gain insight, it is useful to proceed through the analysis step by step:

$$v_{GS} = (V_T + V_F) - i_{DR} R_{DR} \quad (19)$$

$$i_D = g_{fs}(v_{GS} - V_T)$$

Therefore, from (19):

$$i_D = g_{fs}(V_F - i_{DR} R_{DR}) \quad (20)$$

$$\therefore pL_\ell i_D = -pL_\ell g_{fs} R_{DR} i_{DR} \quad (21)$$

$$v_D = V_D - pL_\ell i_D$$

Therefore from (21):

$$v_D = V_D + pL_\ell g_{fs} R_{DR} i_{DR} \quad (22)$$

$$i_{DR} = -pC_{GD} v_D$$

Therefore from (22):

$$\therefore (p^2 L_\ell C_{GD} g_{fs} R_{DR} + 1) i_{DR} = 0 \quad (23)$$

Equation (23) is a classical second order differential, with purely "oscillatory" terms.

By imposing the appropriate boundary conditions [ $v_{GS} = V_T$  at  $t = 0$ , and  $pL_\ell i_D = 0$  at  $t = 0$  (since  $i_{GD} \neq \infty$ )], the following solutions are obtained:

$$v_{GS} = V_F(1 - \cos \omega_1 t) \quad (24)$$

$$i_D = g_{fs} V_F(1 - \cos \omega_1 t) \quad (25)$$

$$v_D = V_D - \omega_1 L_\ell g_{fs} V_F \sin \omega_1 t \quad (26)$$

 


Figure 9. Circuit Model for Turn-On Interval 2, High  $L_\ell/R_{DR}$

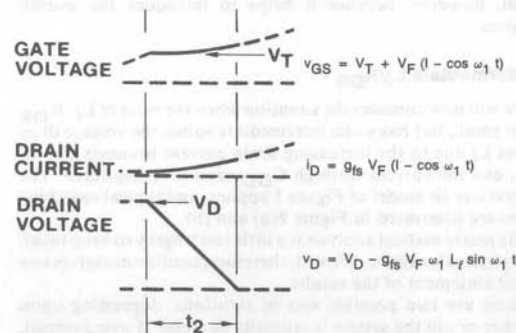


Figure 10. Waveforms for Turn-On Interval 2 Large  $L_\ell/R_{DR}$

$$\frac{L_\ell}{R_{DR}} > \frac{10C_{GS}^2}{C_{GD}g_{fs}}$$

$$= V_D - \sqrt{\frac{g_{fs} L_\ell}{C_{GD} R_{DR}}} \sin \omega_1 t \quad (27)$$

where

$$\omega_1 = \frac{1}{\sqrt{g_{fs} C_{GD} R_{DR} L_\ell}} \quad (28)$$

It remains now to establish how large  $L_\ell/R_{DR}$  must be for the above simple relationships to be valid.

The starting assumption was that the current through  $C_{GS}$  is small by comparison with the "Miller" current  $i_{GD}$  through  $C_{GD}$ . This implies:

$$R_{DR} \ll \frac{1}{\omega_1 C_{GS}}$$

$$\therefore R_{DR} \ll \frac{\sqrt{g_{fs} C_{GD} R_{DR} L_\ell}}{C_{GS}}$$

$$\therefore \frac{L_\ell}{R_{DR}} \gg \frac{C_{GS}^2}{C_{GD} g_{fs}} \quad (29)$$

Table I shows maximum values of  $R_{DR}$  for various HEXFET's for different values of  $L_\ell$  that satisfy the above condition. It is clear that this condition, and hence expressions (24) through (26), will generally apply only to relatively low impedance drive circuits.

Simple qualitative checks on the above relationships will prove their validity. From equation (28),  $\omega_1$  increases as  $R_{DR}$  or  $L_\ell$  decreases. The rate of rise of drain current, therefore, increases as either of these parameters decrease, which is to be expected. From equation (27), the voltage across  $L_\ell$  is proportional to  $L_\ell/R_{DR}$ . Thus increasing  $L_\ell$  or decreasing  $R_{DR}$  gives increasing voltage across  $L_\ell$ —again, to be expected.

The end of the interval occurs when either the drain current  $i_D$  reaches  $I_O$ , or the drain voltage collapses to zero [more precisely when it becomes equal to  $i_D \times R_{DS(ON)}$ ]. If  $I_O$  or  $V_F$ , or both, are small,  $i_D$  could reach  $I_O$  before the collapse of drain voltage is complete. In practice, the voltage collapse will generally occur well before the current has risen to  $I_O$ . To take an example, with the IRF150 HEXFET (rated 25A at 100°C) operating in a 60V circuit, with a gate forcing voltage  $V_F$  of 7V,

$L_\ell = 1 \mu\text{H}$ , and  $R_{DR} = 2\Omega$ , the voltage collapse will be completed by the time the drain current has risen to 0.25A (i.e., about 1% of rated current).

This result is to be expected; we have already reasoned that for large  $L_\ell/R_{DR}$  ratio, the HEXFET essentially acts as a closed switch, the voltage across it collapsing quickly, with the current rising much more slowly, at a rate determined by the external circuit inductance.

### Turn-On Interval 3

The second time interval ends at the completion either of the drain current rise or the drain voltage fall. The completion of the remaining event—voltage fall, or current rise—whichever it is, takes place during the third time interval.

Fortunately, since only the drain voltage or the drain current are now still changing, the analysis is easy, and is independent of the ratio of  $L_\ell/R_{DR}$ . If the drain current is no longer changing, then  $L_\ell$  is irrelevant, since there is no voltage drop across it, whilst if the drain voltage is no longer changing, the HEXFET already acts as a closed switch, and  $R_{DR}$  is irrelevant.

Consider first the situation when the voltage completes its fall during the third interval. The equivalent circuit model is shown in Figure 11. At the start of the period the drain voltage is  $V_D^*$ . Since the drain current is constant,  $v_{GS}$  must also be constant:

$$v_{GS} = V_T + \frac{I_O}{g_{fs}} \quad (30)$$

Therefore  $i_{DR}$  is also constant:


$$i_{DR} = \frac{1}{R_{DR}} (V_{DR} - v_{GS}) = \frac{V_{DR} - (V_T + I_O/g_{fs})}{R_{DR}} \quad (31)$$

Since  $v_{GS}$  is constant, no current flows in  $C_{GS}$ , and all of  $i_{DR}$  flows in  $C_{GD}$ . The rate of change of voltage across  $C_{GD}$  is therefore:

$$\frac{dv_{GD}}{dt} = \frac{i_{DR}}{C_{GD}} = \frac{V_{DR} - (V_T + I_O/g_{fs})}{R_{DR} C_{GD}} \quad (32)$$

The rate of change of drain-source voltage is equal to the rate of change of drain-gate voltage, since  $v_{GS}$  is constant. Therefore, the drain voltage is:
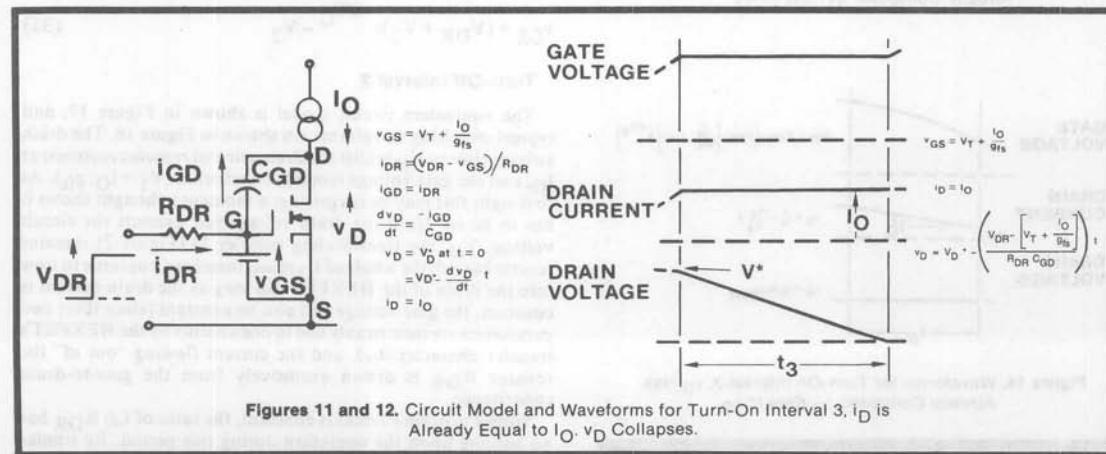
$$v_D = V_D^* - \left( \frac{V_{DR} - (V_T + I_O/g_{fs})}{R_{DR} C_{GD}} \right) t \quad (33)$$



Figures 11 and 12. Circuit Model and Waveforms for Turn-On Interval 3,  $i_D$  is Already Equal to  $I_O$ .  $v_D$  Collapses.

We will now consider the situation when the current completes its rise during the third time interval, the drain voltage having already collapsed.

The equivalent circuit model is shown in Figure 13 and switching waveforms are shown in Figure 14. The drain current  $i_D$  is:

$$i_D = I_D^* + \frac{V_D}{L_\ell} t \quad (34)$$

The gate voltage continues to increase exponentially during the third interval, at time constant  $T_G$  [equation (2)]. This, however, has no influence over the drain current or voltage, since the HEXFET is already "fully on."

#### Turn-On Interval 4

The gate voltage completes its exponential charge, at time constant  $T_G$ , to the level of the applied drive voltage  $V_{DR}$ . This has no influence over the drain current or voltage, since the switching sequence in the drain circuit has already been completed.

## B. TURN-OFF

#### Turn-Off Delay Interval 1

The equivalent circuit model is shown in Figure 15, and operating waveforms are shown in Figure 16. The applied drive voltage  $V_{DR}$  is assumed to fall instantaneously to a negative

 


Figure 13. Circuit Model for Turn-On Interval 3,  $v_D$  Has Already Collapsed.  $i_D$  rises to  $I_D$ .

 


Figure 14. Waveforms for Turn-On Interval 3,  $v_D$  Has Already Collapsed.  $i_D$  rises to  $I_D$ .

 


Figure 15. Circuit Model for Turn-Off Delay Interval

 


Figure 16. Waveforms for Turn-Off Delay Interval ( $t_1$ )

voltage  $-V_2$  (this could, of course, be zero, or even positive, representing a small residual positive drive voltage). The voltage appearing between the gate and source terminals falls at a rate determined by the time constant  $R_{DR}C_G$ , and nothing happens in the drain circuit until the gate voltage falls to  $V_T + (I_D/g_{fs})$ , which corresponds to the gate voltage needed to sustain the drain current  $I_D$ . This point marks the end of the turn-off delay period. The gate voltage during the turn-off delay interval is given by:

$$v_{GS} = (V_{DR} + V_2)e^{-t/T_G} - V_2 \quad (35)$$

#### Turn-Off Interval 2

The equivalent circuit model is shown in Figure 17, and typical switching waveforms are shown in Figure 18. The drain voltage rises to  $V_D$  whilst the drain current *remains constant* at  $I_D$ , and the gate voltage *remains constant* at  $(V_T + I_D/g_{fs})$ . At first sight this may be surprising; a moment's thought shows it has to be so. Until the drain voltage just exceeds the circuit voltage,  $V_D$ , the freewheeling rectifier D (Figure 2) remains reverse biased; the whole of  $I_D$  must, therefore, continue to flow into the drain of the HEXFET. So long as the drain current is constant, the gate voltage will also be constant (since these two parameters are inextricably tied to one another by the HEXFET's transfer characteristic), and the current flowing "out of" the resistor  $R_{DR}$  is drawn exclusively from the gate-to-drain capacitance.

Since the drain current is constant, the ratio of  $L_\ell/R_{DR}$  has no bearing upon the operation during this period. By similar



reasoning used to analyze the voltage fall during the third interval of switch-on, the following relationship is derived:

$$v_D = \frac{(I_O/g_{fs} + V_T + V_2)}{C_{GD}R_{DR}} t \quad (36)$$

### Turn-Off Interval 3

The general circuit model for this interval is shown in Figure 19. At the end of the second interval, the drain voltage is just equal to the supply voltage  $V_D$ , while the current is equal to the full load value,  $I_O$ . The freewheeling rectifier D (Figure 2) is now poised at the point of conduction, ready to receive the load current  $I_O$ , and the potential at the "top" of  $L_L$  is now fixed essentially at  $V_D$ . In order for the drain current to be commutated into the freewheeling rectifier, it is axiomatic that the drain voltage must increase above  $V_D$ . This reflects the fundamental property of inductance  $L_L$ ; the voltage across it must reverse in order for the current in it to reduce; a voltage-time integral must be developed, equal to  $I_O \times L_L$ , for the drain current to be returned to zero. This fundamental consideration relates directly to the inductance  $L_L$ , and is quite independent of any other circuit considerations. The magnitude of the peak overvoltage developed across the HEXFET will be proportional to the size of the inductance  $L_L$ , the magnitude of the current  $I_O$ , and the speed of switching.

In most practical circuits, the voltage transient at the drain can easily exceed the voltage rating of the HEXFET. In the absence of an externally connected local voltage clamp, the HEXFET will likely be driven into avalanche, acting, in effect,

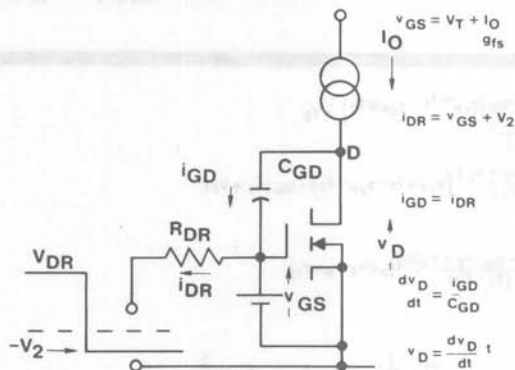


Figure 17. Circuit Model for Turn-Off Interval 2

 


Figure 18. Waveforms for Turn-Off Interval 2

 


Figure 19. General Circuit Model for Turn-Off Interval 3

 


Figure 20. Circuit Model for Turn-Off Interval 3 Small  $L_L/R_{DR}$

as its own voltage clamp, and preventing further substantial increase of voltage. This may or may not be permissible, depending upon whether the HEXFET is rated to handle the avalanche energy. If it cannot do so, then a local external voltage clamp, such as a zener diode, connected physically close to the drain and source terminals will be needed, and this will be functionally equivalent to the HEXFET itself avalanching, save that the energy is absorbed by the clamp, rather than by the HEXFET.

In this third time interval of turn-off, as during the second time interval of turn-on, both the drain current and the drain voltage change. Again, these two events are dynamically intertwined. A change of drain current produces a change of voltage across  $L_L$ ; this produces a current flow through the "Miller" capacitance  $C_{GD}$ ; this restrains the rate of decrease of gate voltage, which in turn restrains the original rate of change of drain current.

As we would expect, the form of the analytic solutions depends upon the ratio of  $L_L/R_{DR}$ . We will simply state the results, since the derivation follows the same general procedures covered for the second turn-on interval.

### Small $L_L/R_{DR}$

The equivalent circuit model is shown in Figure 20, and operating waveforms are shown in Figure 21.

For small  $L_L/R_{DR}$ , equation (6) must be satisfied:

$$v_{GS} = (I_O/g_{fs} + V_T + V_2) e^{-t/T_G} - V_2 \quad (37)$$

 


Figure 21. Waveforms for Turn-Off Interval 3 Small  $L_l/R_{DR}$

$$\frac{L_l}{R_{DR}} < \frac{C_{GS}^2}{10C_{GD}g_{fs}}$$

$$i_D = (I_0 + g_{fs}[V_T + V_2])e^{-t/T_G} - g_{fs}[V_T + V_2] \quad (38)$$

$$v_D = V_D + \frac{(I_0 + g_{fs}[V_T + V_2])e^{-t/T_G}}{T_G} \quad (39)$$

The interval ends when the drain current  $i_D$  falls to zero.

#### Intermediate $L_l/R_{DR}$

The general circuit model shown in Figure 19 applies. Either equation (7) or (13) must be satisfied. Operating waveforms for

$L_l/R_{DR}$  that satisfy equation (7) are shown in Figure 22(a). Expressions for the gate voltage  $v_{GS}$ , the drain current  $i_D$ , and the drain voltage  $v_D$  are as follows:

$$v_{GS} = \frac{(I_0/g_{fs} + V_T + V_2)}{(T_1 - T_2)} T_1 e^{-t/T_1} - T_2 e^{-t/T_2} - V_2 \quad (40)$$

$$i_D = \frac{(I_0 + g_{fs}[V_T + V_2])}{(T_1 - T_2)} T_1 e^{-t/T_1} - T_2 e^{-t/T_2} \dots \dots - g_{fs}[V_T + V_2] \quad (41)$$

$$v_D = V_D + \frac{(I_0 + g_{fs}[V_T + V_2])L_l}{(T_1 - T_2)} e^{-t/T_2} - e^{-t/T_1} \quad (42)$$

where  $T_1$  and  $T_2$  are given by equations (11) and (12), respectively.

Operating waveforms for  $L_l/R_{DR}$  given by equation (13) are shown in Figure 22(b). Expressions for the gate voltage  $v_{GS}$ , the drain current  $i_D$ , and the drain voltage  $v_D$  are as follows:

$$v_{GS} = (I_0/g_{fs} + V_T + V_2)e^{-t/T_3} \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} - V_2 \quad (43)$$

$$i_D = (I_0 + g_{fs}[V_T + V_2])e^{-t/T_3} \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} \dots \dots - g_{fs}[V_T + V_2] \quad (44)$$

 


Figure 22(a). Waveforms for Turn-Off Interval 3 Intermediate  $L_l/R_{DR}$

$$v_{GS} = \frac{(I_0 + V_T + V_2)}{(T_1 - T_2)} (T_1 e^{-t/T_1} - T_2 e^{-t/T_2}) - V_2$$

$$i_D = \frac{(I_0 + g_{fs}[V_T + V_2])}{(T_1 - T_2)} (T_1 e^{-t/T_1} - T_2 e^{-t/T_2}) - g_{fs}(V_2 + V_T)$$

$$v_D = V_D + \frac{(I_0 + g_{fs}[V_T + V_2])L_l}{(T_1 - T_2)} (e^{-t/T_2} - e^{-t/T_1})$$

$$\frac{C_{GS}^2}{10C_{GD}g_{fs}} < \frac{L_l}{R_{DR}} < \frac{C_{GS}^2}{4C_{GD}g_{fs}}$$

 


Figure 22(b). Waveforms for Turn-Off Interval 3 Intermediate  $L_l/R_{DR}$

$$v_{GS} = \frac{(I_0 + V_T + V_2)}{g_{fs}} e^{-t/T_3} \left( \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} \right) - V_2$$

$$i_D = (I_0 + g_{fs}[V_T + V_2])e^{-t/T_3} \left( \cos \omega_3 t + \frac{\sin \omega_3 t}{\omega_3 T_3} \right) - g_{fs}(V_T + V_2)$$

$$v_D = V_D + (I_0 + g_{fs}[V_T + V_2])\omega_3 L_l e^{-t/T_3} \left( 1 + \frac{1}{\omega_3^2 T_3^2} \right) \sin \omega_3 t$$

$$\frac{C_{GS}^2}{4C_{GD}g_{fs}} < \frac{L_l}{R_{DR}} < \frac{10C_{GS}^2}{C_{GD}g_{fs}}$$



voltage  $V_D$ . The drain capacitance  $C_D$  then "rings" with the stray circuit inductance  $L_\ell$ , the oscillation being damped by the stray circuit resistance  $R_\ell$ . Figure 27 shows the equivalent circuit for this interval, and Figure 28 shows a typical drain voltage waveform.

$$v_D = V_D + (V_D^* - V_D)e^{-t/T_4} \cos \omega_4 t \quad (50)$$

where

$$T_4 = \frac{2L_\ell}{R_\ell} \quad (51)$$

$$\omega_4 = \frac{\sqrt{4L_\ell C_D - C_D^2 R_\ell^2}}{2L_\ell C_D} \quad (52)$$

During this interval the gate voltage discharges exponentially with time constant  $T_G$  towards a final value of  $-V_2$ .

### VI. A Worked Design Example

Figures 29 through 32 show switching waveforms for a specific design example, obtained from the analytic expressions presented in this paper. Various combinations of  $L_\ell/R_{DR}$ , and amplitude of drive voltage, are considered in order to illustrate the effects of these parameters on the switching performance. The following data is used:

HEXFET type: IRF150

$C_{GS}$ : 2650 pF

$C_{GD}$ : 350 pF

$V_T$ : 3 V

$g_{fs}$ : 8 A/V

$V_D$ : 50 V

$I_O$ : 35 A

 


Figure 27. Circuit Model for Turn-Off Interval 4

 


Figure 28. Drain Voltage for Turn-Off Interval 4

 


Figure 29. Turn-On Waveforms For Various Circuit Conditions

- (a)  $R_{DR} = 5 \Omega$ ,  $L_\ell = 200 \text{ nH}$
- (b)  $R_{DR} = 50 \Omega$ ,  $L_\ell = 200 \text{ nH}$
- (c)  $R_{DR} = 50 \Omega$ ,  $L_\ell = 1 \mu\text{H}$

IRF 150,  $V_{DR} = 10\text{V}$   
 $V_2 = 0$

Figure 29 shows waveforms calculated for the turn-on interval for: (a)  $R_{DR} = 5$  ohms,  $L_\ell = 200$  nH; (b)  $R_{DR} = 50$  ohms,  $L_\ell = 200$  nH; and (c)  $R_{DR} = 50$  ohms,  $L_\ell = 1$   $\mu\text{H}$ . The drive voltage  $V_{DR}$  is 10 volts.

Condition (a) is representative of a fast drive circuit, and a relatively high impedance of  $L_\ell$ . The drain voltage falls rapidly, and most of the current rise time occurs subsequent to the collapse of drain voltage. The switching energy is almost negligible—a mere  $0.12 \mu\text{J}$ . In Figure 29(b), the inductance is the same, but the drive resistance has increased to 50 ohms. The gate drive circuit is now much slower, and the drain voltage collapses much less rapidly; in fact, the drain current now completes its rise before the drain voltage collapses completely. The total switching time (current rise + voltage fall) increases from 150 ns in Figure 29(a) to 360 ns in Figure 29(b). More significantly, the switching energy increases from  $0.12 \mu\text{J}$  to  $55 \mu\text{J}$ .



In Figure 29(c), the drive circuit resistance is still 50 ohms, while the drain inductance  $L_\ell$  has increased from 200 nH to 1  $\mu\text{H}$ . The speed of the drive circuit is, therefore, the same as in Figure 29(b), but the impedance of  $L_\ell$  increases by a factor of 5. The voltage drop in the drain circuit is, therefore, once again very significant, and the drain voltage collapses much more

rapidly. Because of the increased inductance, however, the current rise time is much longer. The switching energy decreases from  $55 \mu\text{J}$  in Figure 29(b) to  $1.8 \mu\text{J}$  in Figure 29(c), because of the much faster voltage collapse. It would be wrong to believe, however, that the overall switching losses can be decreased by increasing  $L_\ell$ . The energy saved during turn-on by increasing  $L_\ell$  is more than offset by increased energy at turn-off. Increasing  $L_\ell$  to reduce the turn-on losses is counterproductive; it simply postpones the "day of reckoning" to the turn-off interval.

Before studying the details of the turn-off waveforms in Figure 30, it will be instructive to make some basic comparisons between the operation during the turn-on and turn-off intervals.

At turn-on the peak dissipation is drastically effected by the  $L_\ell/R_{DR}$  ratio, and is very small if this ratio is large. At turn-off, however,  $L_\ell/R_{DR}$  has no real influence on the peak dissipation, and this is *always* relatively high. This is because the drain current cannot start to decrease until the drain voltage has risen all the way to the circuit voltage. The peak dissipation during the voltage rise interval (turn-off interval 2) will, therefore, always be  $V_D \times I_O$ . While the value of drive resistance,  $R_{DR}$ , controls the duration of this period,  $L_\ell$  has no effect upon it.

The next turn-off interval ( $t_3$ ), is also one of relatively high power dissipation. Even with no drain inductance, the drain current must decay from  $I_O$  to zero with the drain voltage at the full circuit value,  $V_D$ . In practice  $L_\ell$  will never be zero, and the energy stored in this inductance ( $1/2 L_\ell I_O^2$ ) will also be dissipated during this period. It is evident, therefore, that while the turn-on energy depends strongly upon the  $L_\ell/R_{DR}$  ratio, and can be very small if  $L_\ell/R_{DR}$  is large, there is no way of avoiding a much more significant turn-off energy. Generally, the larger is  $L_\ell$ , the greater will be the *total* energy dissipation, even though the turn-on dissipation may be very low.

  

Figures 30(a) through (c) show waveforms at turn-off that correspond to the same three sets of values of  $R_{DR}$  and  $L_\ell$  as in Figure 29(a) through (c). The waveforms in Figure 30(a) are for a fast drive circuit ( $R_{DR} = 5 \text{ ohms}$ ). The drain voltage rises rapidly to the clamping level of 95V. Note that in the absence of a clamp the drain voltage would rise to a hypothetical peak of 235V (assuming that this 100V rated HEXFET would take it!). The energy dissipated in the HEXFET during the time the drain voltage rises to the 95V clamp level is referred to in Figure 31 as "switching" energy, and is  $45 \mu\text{J}$ —more than two orders of magnitude greater than the energy at turn-on for the same values of  $R_{DR}$  and  $L_\ell$  [Figure 29(a)].

Once the 95V clamp level is reached, the current decays approximately linearly, and an additional  $235 \mu\text{J}$  of energy is dissipated during the clamping period. This energy would be dissipated either in an external clamp, if this is used, or in the HEXFET itself—assuming that it is capable of operating in its avalanche mode.

Note that the energy stored in  $L_\ell$ ,  $1/2 L_\ell I_O^2 = 122 \mu\text{J}$ , is about half the total energy dissipated during the clamping period. Simple physical reasoning confirms the correctness of this; not only must the energy stored in  $L_\ell$  be dissipated, but since the supply voltage  $V_D$  continues to feed energy to the circuit ( $i_D$  continues to be drawn from  $V_D$ ), this energy also must end up being dissipated during this period.

Figure 30(b) shows waveforms for  $R_{DR} = 50 \text{ ohms}$ , with  $L_\ell$  the same as for Figure 30(a). The response of the gate drive circuit is much slower, and hence the rate of rise of drain voltage is also much slower—so slow, in fact, that the drain voltage never reaches the clamping level of 95V. In this case, all the switching energy must be dissipated in the device itself, and there is no opportunity for shunting some of this into an external clamp. The total switching time increases from 175 ns [Figure 30(a)] to 400 ns, and the total switching energy increases from 280 to  $450 \mu\text{J}$ . Once again, the turn-off energy of  $450 \mu\text{J}$  is much greater than the turn-on energy of  $55 \mu\text{J}$  for the same value of  $L_\ell$  and  $R_{DR}$  [Figure 29(b)].

 


Figure 30(c) shows turn-off waveforms for  $R_{DR} = 50$  ohms, but with  $L_\ell$  increased to  $1 \mu\text{H}$ . As would be expected, the initial rate of change of drain voltage is the same as in Figure 30(b); until the drain voltage becomes equal to the circuit voltage of 50V, the drain current remains constant at  $I_O$ , and  $L_\ell$  has no effect. Thereafter, however, the drain voltage moves much more rapidly upwards, and has no difficulty in reaching the clamp level of 95V. The total switching time increases to 950 ns, because of the increased value of  $L_\ell$ , and the total switching energy increases from  $450 \mu\text{J}$  in Figure 30(b) to  $1435 \mu\text{J}$  in Figure 30(c).

It is interesting to compare the energy reduction at turn-on when  $L_\ell$  is increased from 200 nH to  $1 \mu\text{H}$ , Figures 29(b) and (c), versus the energy increase at turn-off [Figures 30(b) and (c)]. The energy reduction at turn-on is  $(55 - 1.8) = 53.2 \mu\text{J}$ , while the energy increase at turn-off is  $(1435 - 450) = 985 \mu\text{J}$ . The net effect of increasing drain circuit inductance is a very substantial increase in the total energy dissipation.

The waveforms in Figure 31 show the effect of increasing the applied drive voltage from 10V to 15V, for  $R_{DR} = 50$  ohms and  $L_\ell = 200$  nH. The total switching time decreases from 360 ns to 160 ns, and the switching energy decreases from  $55 \mu\text{J}$  to  $6 \mu\text{J}$ .

Figure 32 shows the same comparison for the turn-off interval. The waveforms in Figure 32(a) are for no applied drive voltage during the turn-off interval, while those in Figure 32(b) are for a negative drive voltage of -15V. The total switching time decreases from 400 to 250 ns, and the switching energy from  $450$  to  $305 \mu\text{J}$ . The negative gate drive voltage not only reduces the total switching energy, but also, because it forces the drain voltage to reach the 95V clamping level, it offers the possibility for "dumping"  $195 \mu\text{J}$  of energy which would otherwise be dissipated in the HEXFET, into an external clamp.

## VII. The Effect of Common Source Inductance

So far we have ignored the effect of the common source inductance  $L_S$ , shown dashed in Figure 2. This inductance will always be present to some extent; even with careful circuit layout, the user will have to accept, at a minimum, the internal lead inductance within the package of the device. For a TO-3 package, this inductance is in the order of 10 to 15 nH. We will now consider briefly the modifying effect of  $L_S$  on the switching operation.

Figure 33 shows the general equivalent circuit which includes  $L_S$ . As the drain current  $i_D$  starts to increase at turn-on, a voltage will be developed across  $L_S$  due to the rate of change of drain current. This voltage is common to the gate circuit, and its polarity is such to reduce the net voltage appearing between the gate and source terminals. Like the "Miller" effect, which provides a negative feedback from the drain to the gate, slowing down the rate of change of current, so the common source inductance also provides a negative feedback, from the source circuit to the gate, also slowing down the change of drain current.

A complete analysis of the switching operation that includes the effect of the common source inductance can be accomplished by means of the procedures already presented. This is beyond the scope of this paper. We will content ourselves instead with an approximate analysis, the main benefit of which is the extreme simplicity of the result.

Referring to the equivalent circuit in Figure 33, it is evident that  $L_S$  only has an effect when the drain current is changing, and the HEXFET is in its active region. This restricts the analysis to interval 2 during turn-on, and interval 3 during turn-off.

The loop equation for the gate circuit is:

$$i_{DR}R_{DR} + \frac{i_{GS}}{pC_{GS}} + pL_S i_{GS} + pL_S i_D = V_{DR} \quad (53)$$

By making the approximation (valid for practical operating conditions)  $pL_S i_D \gg pL_S i_{GS}$ , equation (53) becomes:

$$i_{DR}R_{DR} + \frac{i_{GS}}{pC_{GS}} = V_{DR} \quad (54)$$

Now

$$i_D = g_{fs} v_{GS} = \frac{g_{fs} i_{GS}}{pC_{GS}} \quad (55)$$

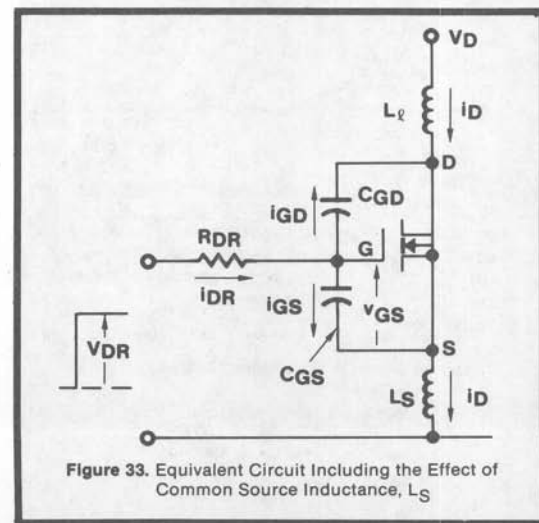


Figure 33. Equivalent Circuit Including the Effect of Common Source Inductance,  $L_S$