

Output Transformer for 12V

- ① - Determine desired power output $E_g = 15W$
 - ② Assume transformer efficiency = 80%
 \therefore transistor O/P power required = $\frac{P_o}{.8}$ $E_g = 18.8W = P_o$
 - ③ - Calculate transistor dissipation = $\frac{P_o}{4}$ $E_g = \frac{18.8W}{4} = 4.7W$
per transistor.
 - ④ Calculate heat sink by $\theta_{c/w} \text{ TOTAL} = \frac{T_{max} - T_{amb}}{P}$
 - ⑤ Calculate primary Z by V_{cc}^2 / P_o CT. $E_g = \frac{144}{18.8} = 7.8 \Omega$ CT
 - ⑥ For core area calculation double P_o $E_g \rightarrow 18.8 \times 2 = 37.6W = P_o$
 - ⑦ Calculate core area by $\frac{\sqrt{P_o}}{5.58}$ $E_g = \frac{\sqrt{37.6}}{5.58} = 1.1 \text{ sq"}$
 - ⑧ Calculate turns ratio $4r = \sqrt{\frac{P_o}{Z_p}}$ $E_g = \sqrt{\frac{9}{7.8}} = .715$
 - ⑨ Calculate turns ratio Z_s / Z_p by $\sqrt{\frac{P_o}{Z_p}}$ $E_g = \sqrt{\frac{9}{7.8}} = 1.01$
 - ⑩ Calculate for $16r$ if desired by $\sqrt{\frac{P_o}{Z_p}}$ $E_g = \sqrt{\frac{16}{7.8}} = 1.413$
 - ⑪ Take supply voltage and double $E_g \quad 12V = 24V$
 - ⑫ Determine primary current by $\frac{P_o}{V_{II}}$ $E_g = \frac{18.8W}{24V} = 780mA$
- This is the current per section - total current draw would be 1560mA. for our example.
- ⑬ Determine secondary currents by $I_s = \frac{I_p}{\text{Turns ratio}}$
 $E_g - 4r = \frac{1560}{.715} = 2.2A \quad 8r = \frac{1560}{1.01} = 1.55A \quad 16r = \frac{1560}{2.47} = 1.09A$
 - ⑭ Choose wire size by the rate of 700 to 1000 circular mils / ampere though 600 is permissible with very neat winding.

AWG	AREA (cm)	AWG	AREA (cm)	AWG	AREA (cm)
14	4107	25	320	36	25
15	3257	26	254	37	20
16	2583	27	201	38	15
17	2048	28	160	39	12
18	1624	29	126	40	10
19	1288	30	100		
20	1022	31	79		
21	810	32	63		
22	642	33	50		
23	509	34	39		
24	404	35	31		

ELCOM BOOK

42.387 50 SHEETS 5 SQUARE
 42.388 100 SHEETS 5 SQUARE
 42.389 200 SHEETS 5 SQUARE



By this we find we need $\frac{178A}{A} \times 700 = \frac{543}{1000} \text{ cm}$ showing we need number 22 wire for the primary.

- 4r sec = $2.2 \times 700 = \#18 \text{ wire}$
- 8r = $1.55 \times 700 = \#19 \text{ wire}$
- 16r = $1.09 \times 700 = \#21 \text{ wire}$

- use largest size possible though to prevent DC losses in the primary.

(15) Determine primary turns by $PT^{15} = \frac{2V_{CC} \times 10^5}{4.44(A)(f)(BM)}$

Eg $\frac{24 \times 10^5}{4.44 \times 1.1 \times 100 \times 70,000} = 70 \text{ turns CT.}$

A = core area.

f = 3db frequency (low end).

BM = flux density, 40,000 to 100,000 (gauss/cm²) (70,000 is a good number)


70 turns means 35 bifilar double turns

(16) Determine secondary turns by Primary turns x turns ratio

Eg 4r = $70 \times 1.715 = 50 \text{ turns}$
 8r = $70 \times 1.41 = 70 \text{ turns}$
 16r = $70 \times 1.43 = 100 \text{ turns}$

This completes calculation of the OPT trans

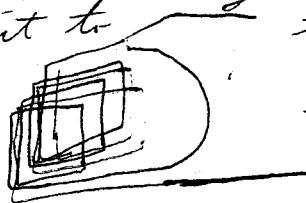- A bifilar wind is where 2 separate winds are made at the same time - side by side, interwound - then, the two windings are put in series to get a center tapped winding - this is done by taking one end and connecting it to the opposite end of the other winding. They could also be left separate if desired.



ELCOM - Driver trans for a CE - Push Pull amp.

a - $R_{in} = 4(h_{ie} + (R_E)(h_{FE}))$

Eg - Let $h_{ie} = 200 \Omega$ & $h_{FE} = 40$
 $R_E = 1r.$

$\therefore R_{in} = 4(200) = 960 \Omega \text{ CT}$

b Find $P_{in} = \frac{4V_{CC}^2}{2I_C / \beta \times V_{CC}}$
 $I_C = I_C \text{ per transistor}$

Eg = $\frac{4 \times 200^2 \times 15.8}{1600 \times 7.8 \times 78A} = 1.2W$
 $2 \times 40 \times 12 = 235W \times 2 = 47W$
 say 1.5W is needed.

If a darlington is used - let $\beta = 400$ - $P_{in} = \frac{4V_{CC}^2}{2\beta I_C} = 126mW$

Find R_{in} by $\frac{V_{CC}^2}{2P_{in}}$

Eg = $\frac{144}{2 \times 1.2} = 154 \Omega$