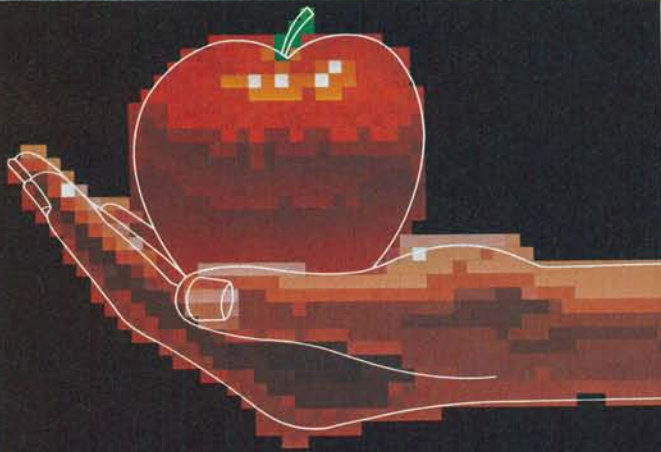


# POLISH YOUR APPLE WITH A LUMINANCE BOARD




*A low-cost plug-in board  
turns an Apple II computer into  
a graphics giant  
with 240 color choices*

*By Ray Dahlby*








**E**NHANCING the utility of his/her computer is among the most fruitful accomplishments that a computerist can achieve. It separates the appliance operator from the innovative enthusiast. An Apple II micro-computer, for example, can produce the dramatic displays shown at right by simply plugging in an under-\$100 hardware board (assembled in about an hour with the plans presented here) and running some software.

This accessory luminance board enables an Apple II to block-shade text with one of 16 brightness levels for 240 low-resolution colors in place of the normal 16 colors, and simultaneously display bar graphs with high resolution. In addition to luminance control, the circuit adds a video interrupt mechanism for synchronous video-screen page flipping and screen splits. This makes it possible to expand the Apple's mixed text and graphics mode so that text can be displayed above or below the graphics.

Using the board you can even display part of page-1 hi-res graphics with part of the graphics on page 2, or you

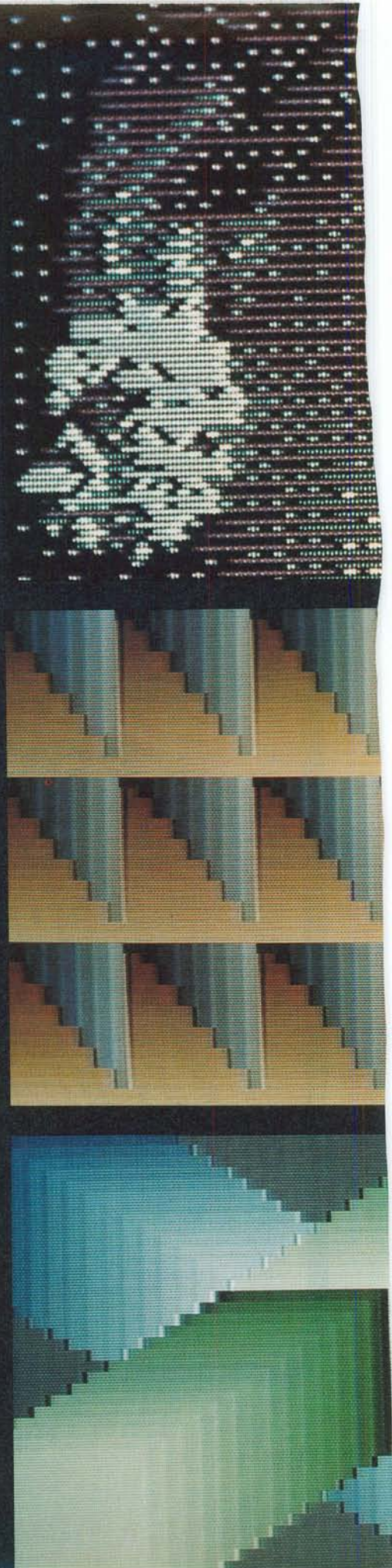



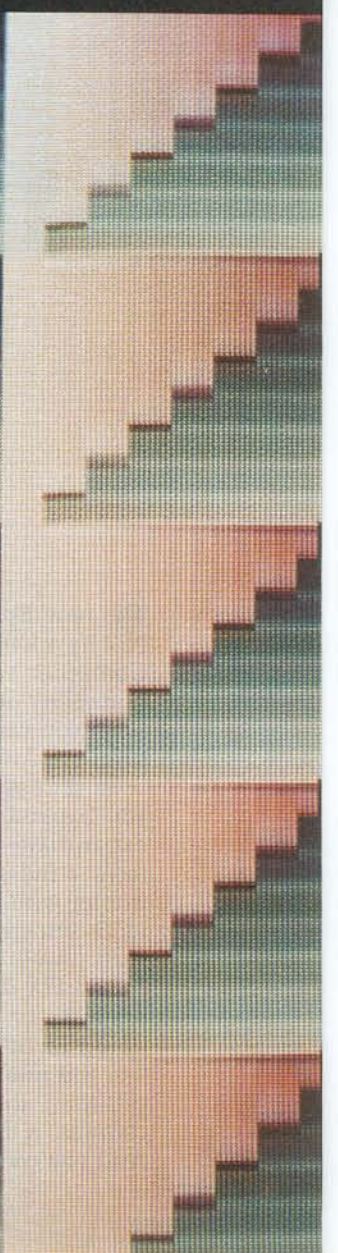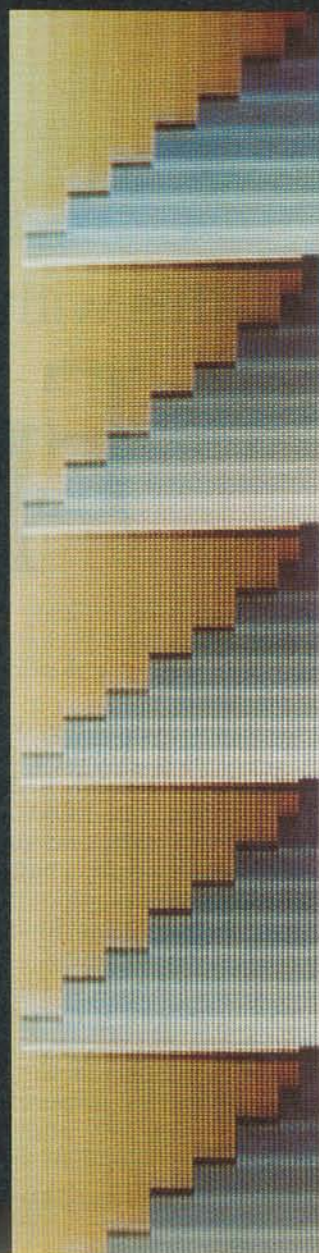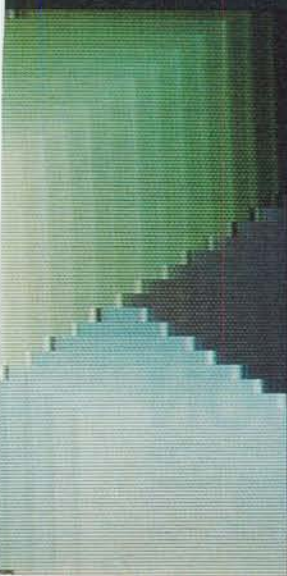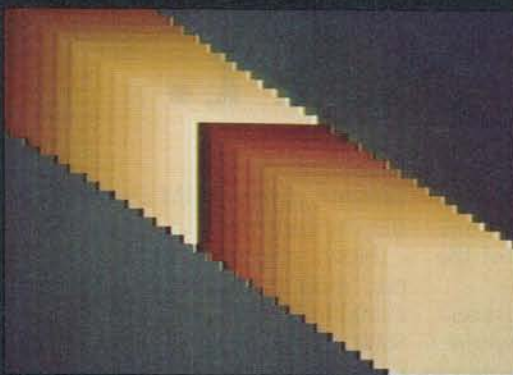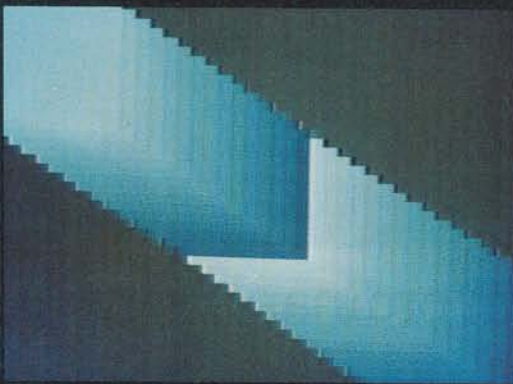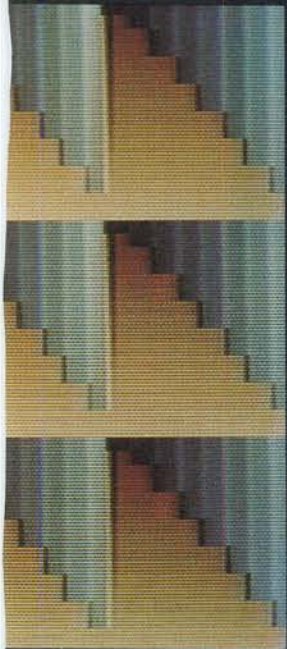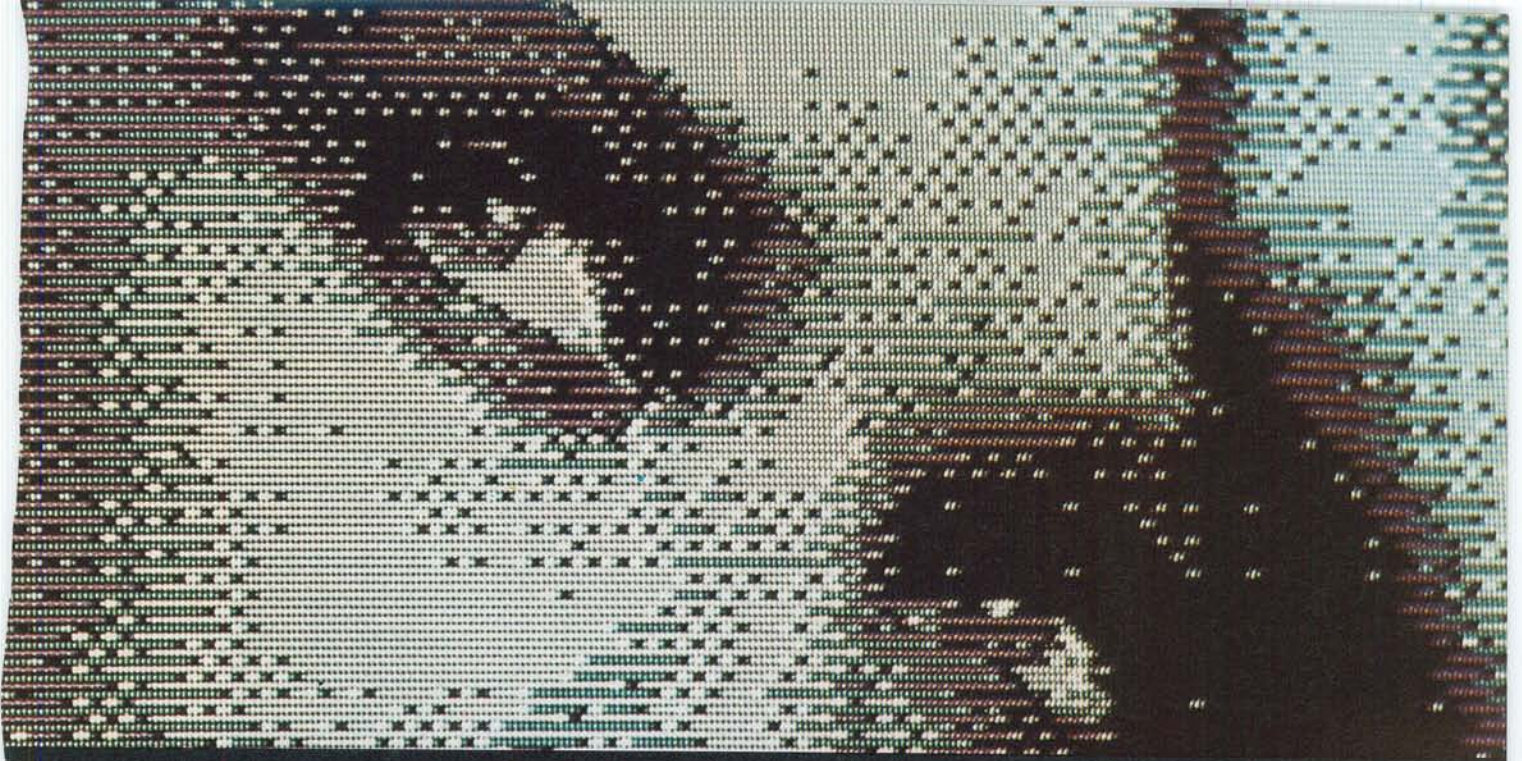



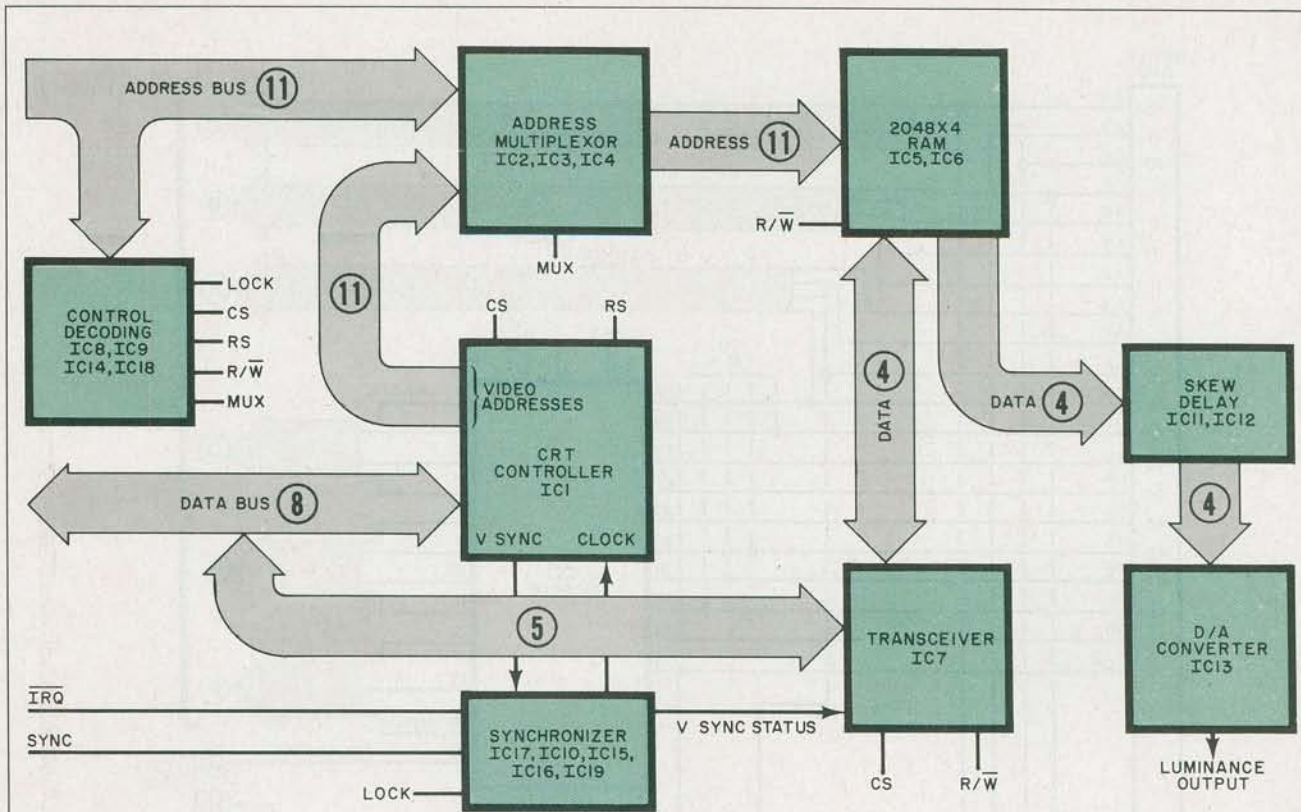



Fig. 1. The most important element of the system is the 6845 CRT controller.

can display them simultaneously for a double-resolution graphics display of 560 x 192 pixels. All of this is accomplished without complex modifications to existing Apple equipment and without losing the normal display modes. The

card plugs into slot 7 as shown in the photo below.

The luminance component of a television signal contains brightness information about the image being viewed. Similarly, to add luminance capabilities to a computer,

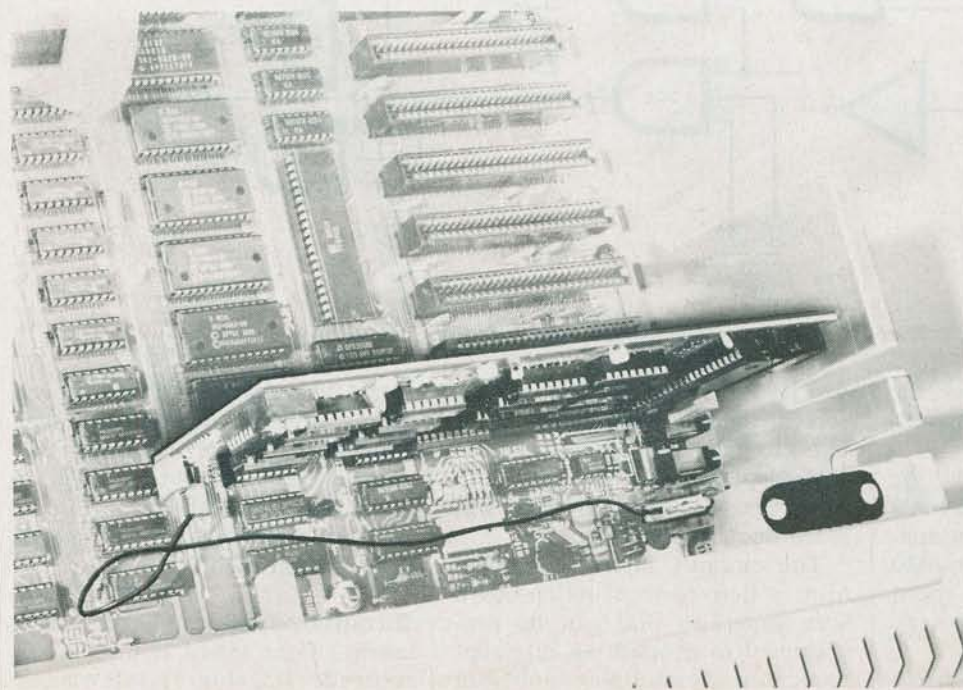brightness information must be added to its video output. The circuit card supplies this information from a 2048 x 4-bit RAM memory. Data is mapped to overlay the Apple's screen in a 40 x 48 array of pixels. Data written to each



The accessory luminance board plugs into slot 7 on the Apple bus.



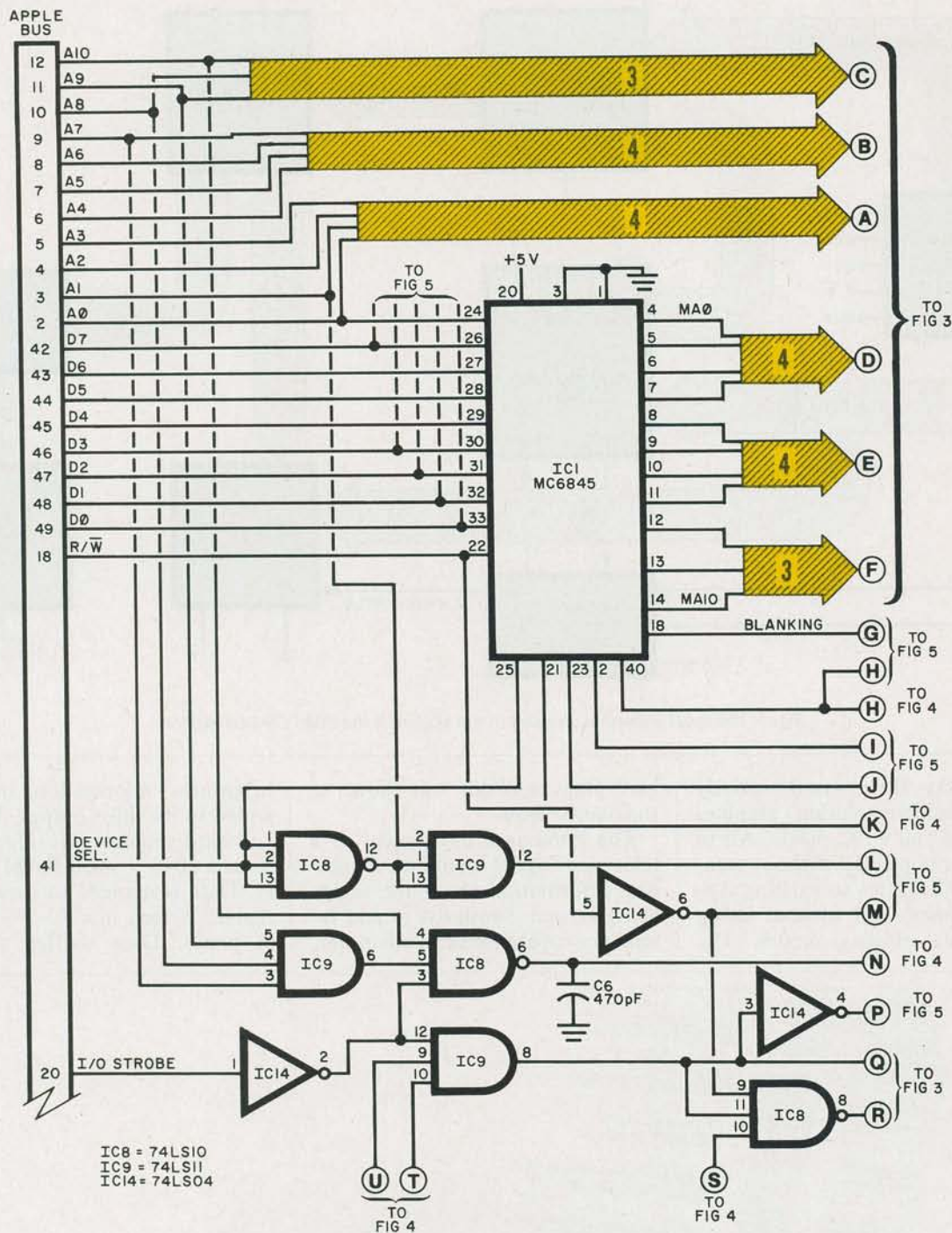


Fig. 2. The 6845 synchronously regenerates the video RAM addressing.

memory location determines the brightness level of the corresponding pixel.

Since 16 tone levels rival the quality of photographic film, 4 bits was considered adequate. The spatial resolution of  $40 \times 48$  or 1920 pixels was chosen for high-speed animation and memory-size reduction.

Each luminance pixel precisely

overlays a  $7 \times 4$  dot area of the screen, adding luminance attributes to one block of low-res or an equivalent area of hi-res. Two luminance pixels stacked vertically will shade one text character.

The circuit's interrupt mechanism is derived from its on-board scan generator and can be programmed to produce an interrupt request on any multiple of four scan

lines. This feature allows smooth animation plus synchronous page flipping. The 60-Hz interrupts can also be used as a real-time clock. A block diagram is shown in Fig. 1, with the complete schematic shown in Figs. 2 through 5.

**Circuit Operation.** The central element of the board is 6845 CRT controller IC1 (Fig. 1). It is used to



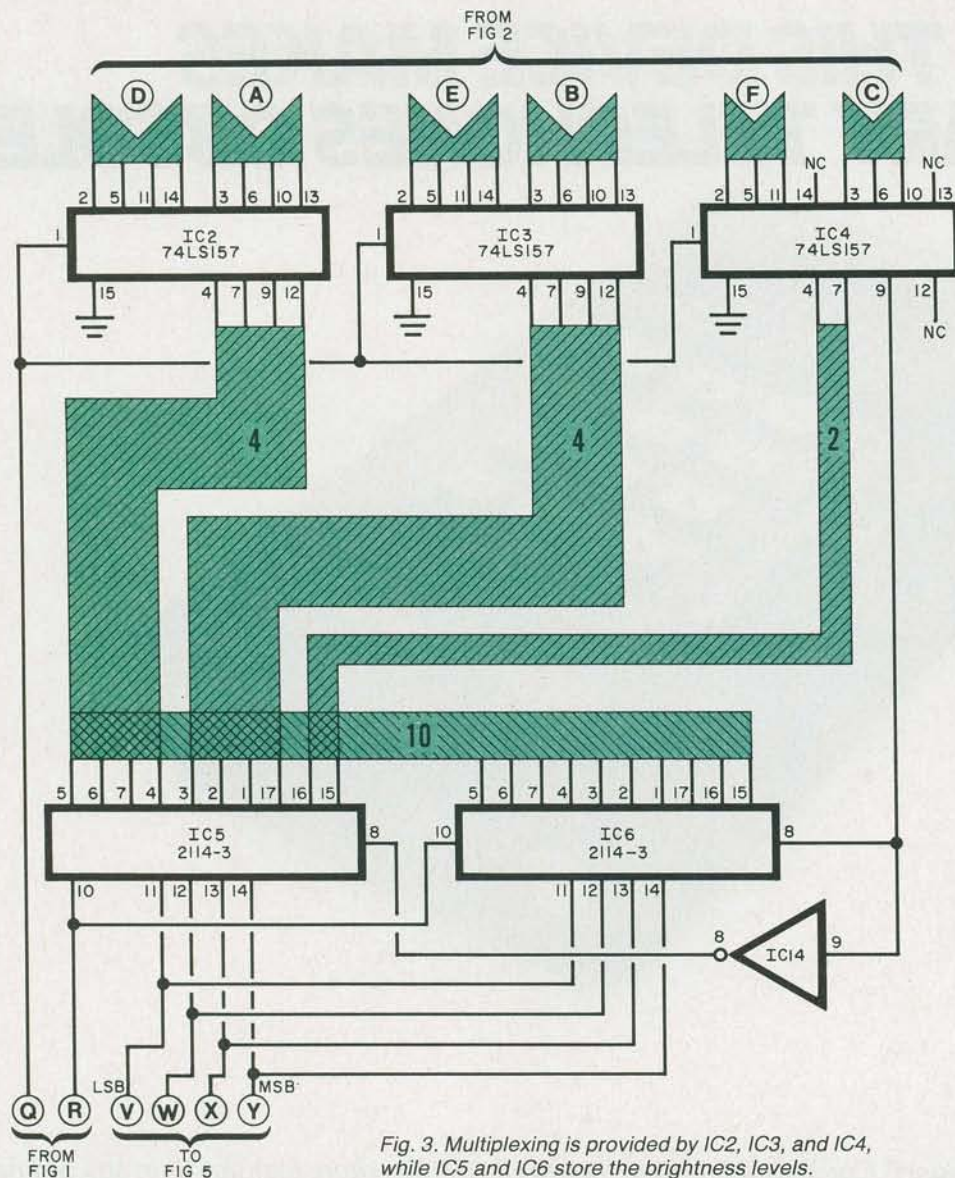


Fig. 3. Multiplexing is provided by IC2, IC3, and IC4, while IC5 and IC6 store the brightness levels.

synchronously regenerate the video RAM addressing not available on the Apple bus. This IC is programmed for the Apple video timing, then phase locked to the sync pulse on pin 19 of slot 7.

The circuit then runs in step with the Apple video, providing addressing for the on-board  $2K \times 4$  luminance RAMs IC5 and IC6, which store the brightness level of each luminance pixel. The RAMs can be read from, or written to, transparently by the Apple during phase 2 of the processor clock. This removes the "glitches" that are common to many 80-column plug-in boards. Address multiplexing is taken care of by IC2, IC3, and IC4 (Fig. 3).

During phase 1 of the processor

clock, contents of the luminance RAM addressed by IC1 are fed to IC12 (Fig. 5) which in turn drives the four-bit D/A comprised of elements of IC13 and its associated resistor/ladder network. This converts the digital data into a 16-level analog signal. The output of this network, preset by R11, is coupled

to the Apple baseband video output.

In IC17 (Fig. 4) and its associated circuit the vertical sync signal is extracted from the composite signal that appears on pin 19 of slot 7. The resulting output provides a reference for the phase locking. The remainder of the phase-lock circuit is formed from IC10, IC15A, IC16, and elements of IC19 in Fig. 4, and a portion of IC12 of Fig. 5.

**Construction.** The circuit can be built on any Apple prototyping board using wire wrap or, alternatively, on a pc board such as that shown in Fig. 6. Since some elements of the circuit operate at 7 MHz, take care when using the point-to-point wiring technique.

TABLE I  
SWITCH POSITIONS

Revision	S1	S2	S3	S4
0-6	On	Off	*	On
7	Off	On		Off
8 and up	On	Off		Off
Future	Off	On		On

\*S3 enable interrupts and is independent of revision number.



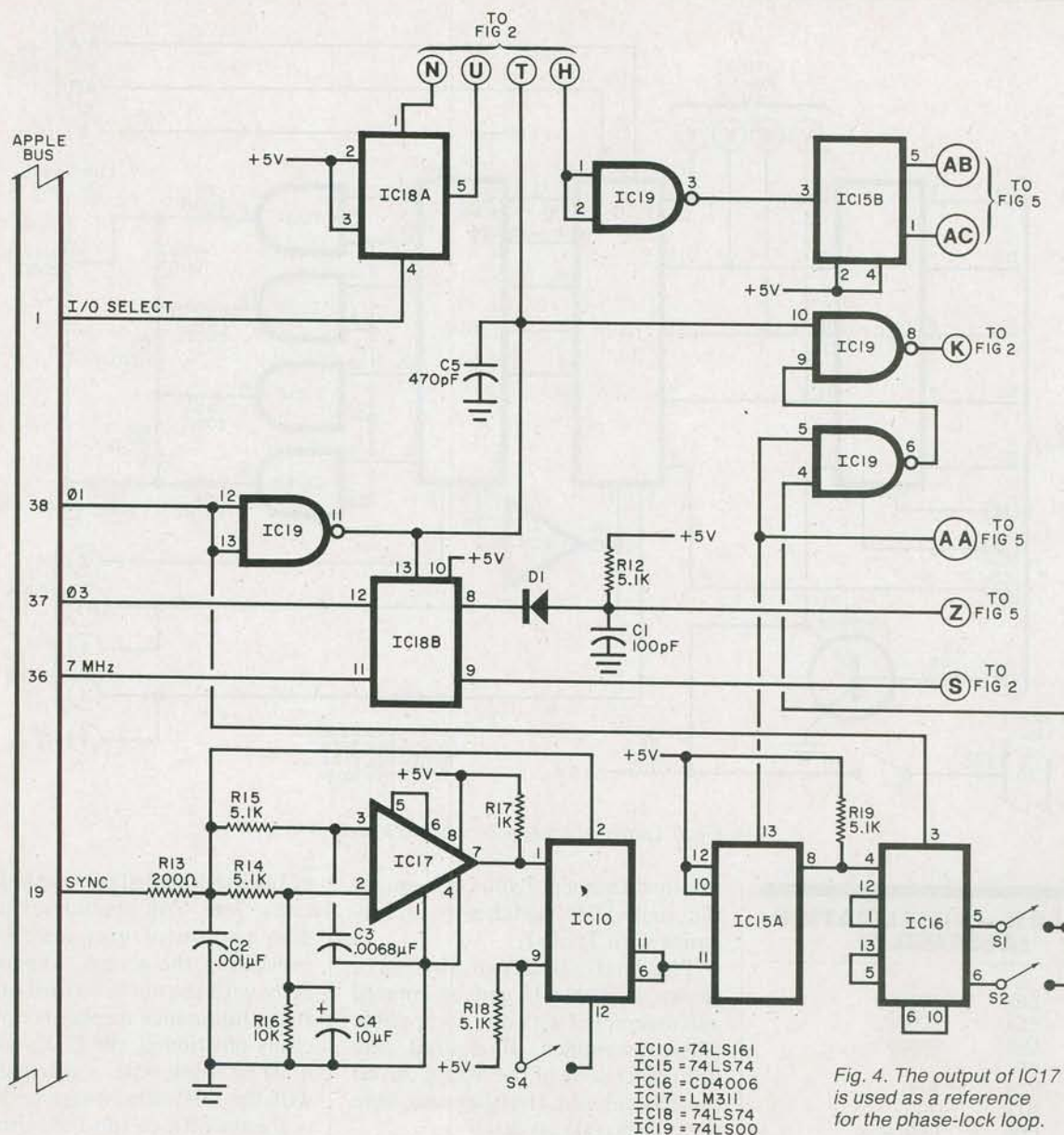


Fig. 4. The output of IC17 is used as a reference for the phase-lock loop.

### PARTS LIST

C1—100-pF ceramic disc capacitor  
 C2—0.001- $\mu$ F capacitor  
 C3—0.0068- $\mu$ F capacitor  
 C4—10- $\mu$ F, 15-V electrolytic  
 C5, C6—470-pF ceramic disc capacitor  
 C7 through C11—0.1- $\mu$ F ceramic disc capacitor  
 D1—1N914 diode  
 IC1—MC6845 CRT controller  
 IC2 through IC4—74LS157 quad 2-input data selector  
 IC5, IC6—2114-3 1024 x 4 static RAM  
 IC7—74LS245 octal bus transceiver  
 IC8—74LS10 triple 3-input NAND  
 IC9—74LS11 triple 3-input AND  
 IC10—74LS161 4-bit binary counter  
 IC11, IC12—74LS174 hex D flip-flop  
 IC13—74LS08 quad 2-input AND  
 IC14—74LS04 hex inverter  
 IC15, IC18—74LS74 hex D flip-flop  
 IC16—CD4006 shift register  
 IC17—LM311N comparator

IC19—74LS00 quad 2-input NAND  
 Q1—2N3904  
 The following are 1/4-W, 5% resistors unless otherwise noted:  
 R1, R16—10 kilohms  
 R2, R12, R14, R15, R18, R19—5.1 kilohms  
 R3 through R7, R13—200 ohms  
 R8, R9, R10—100 ohms  
 R11—200-ohm trimmer potentiometer (Bourns 3386W or equiv.)  
 R17—1 kilohm  
 S1 through S4—4-position DIP spst switch  
 Misc.—Sockets, 6" to 8" length of insulated lead, small alligator clip.  
**Note: The following is available from Ray Dahlby Electronics, Box 7600, Vancouver, B.C. V6B 4X9, Canada: Printed-circuit board, \$29.95; sub-interpretor diskette, \$10 check or money order in U.S. funds.**

The use of sockets is recommended for the ICs, and caution must be observed with static-sensitive MOS devices IC1, IC5, IC6, and IC16.

After all components are installed (Fig. 7), carefully check all connections. A miniature DIP switch can be used for the four switches called for in the circuit. Attach a short length (6" to 8") of insulated lead to the luminance output (top of R11), and terminate the lead with a small alligator clip.

The Apple II has undergone several revisions in video timing to accommodate new TV receivers. This circuit handles these timing changes via the four DIP switches on the board. After determining the



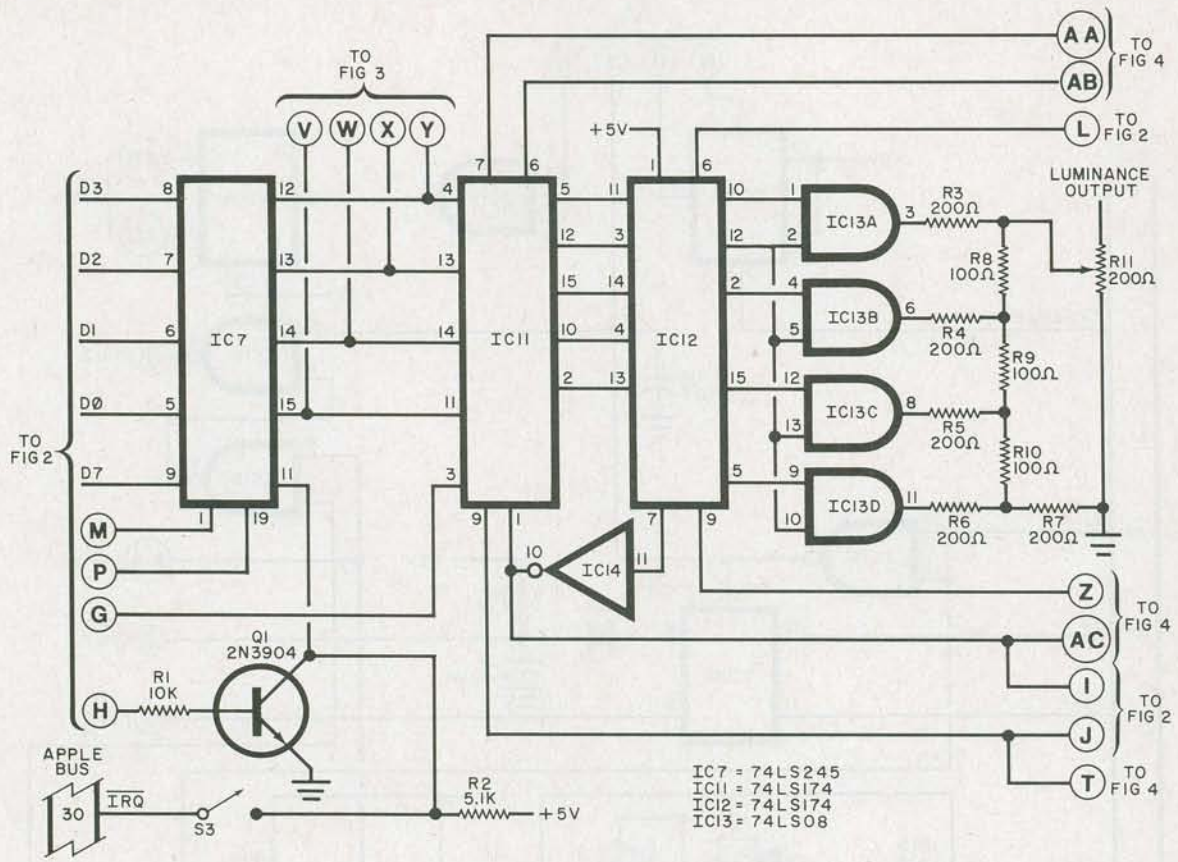


Fig. 5. Luminance output is obtained from D/A IC13.

**TABLE II—INITIALIZATION (ASSEMBLY)**

RS	EQU	\$C0F0
LOCK	EQU	\$C0F2
	ORG	\$0300
	SEI	
	LDX	#00
INIT	STX	RS
	LDA	TABLE, X
	STA	RS+1
	INX	
	CPX	#16
	BNE	INIT
	JSR	WAIT
	BIT	LOCK
	RTS	
WAIT	LDX	#01
	LDY	#255
HERE	DEX	
	BNE	HERE
	DEY	
	BNE	HERE
	RTS	
TABLE	DFB	64,40,48,08,63,06 48,53,00,03,32,00 00,00,00,00

**(HEX OBJECT CODE)**

78, A2, 00, 8E, F0, C0, BD, 23, 03, 8D, F1, C0, E8, E0, 10, D0, F2, 20, 18, 03, 2C, F2, C0, 60, A2, 01, A0, FF, CA, D0, FD, 88, D0, FA, 60, 40, 28, 30, 08, 3F, 06, 30, 35, 00, 03, 20, 00, 00, 00, 00, 00
--

revision number of your system, set the four DIP switches in accordance with Table I.

The initialization software shown in Table II can be entered and assembled with any compatible editor/assembler. If desired, the hex object code of the listing can be directly entered. In either case, save the object code on disk.

With the Apple II power turned off, connect the luminance lead alligator clip to the center connector of the video output connector at the rear of the motherboard. Install the Syncard in slot 7.

If you are using a video modulator that gets its video from the four-pin connector in the Apple, it will have to be modified. In the case of an M&R Supr-Mod, cut the brown lead coming from the modulator and patch the video from the rear of the Apple to the auxiliary input of the Supr-Mod. Rotate the modulator level control full clockwise and re-install it. Even without the board, the modulator will work normally. Other r-f modulators should be similar.

With the initialization program

of Listing 1 loaded in the computer, CALL 768. You should see a random pattern of gray-scale blocks overlaying the screen, aligned exactly with the normal video output. If the luminance display is not precisely positioned, the DIP switches must be reset. After experimenting with the DIP switches (note that S3 is always off), re-run the initialization routine.

When the board is running, adjust luminance control R11, and the video output level of the Apple for a good picture without tearing. There will be a loss of vertical sync until the Syncard is initialized. If desired, this can be avoided by tem-

**TABLE III PROGRAM PARAMETERS**

\$C0F0	6845 register select*
\$C0F1	6845 data register*
\$C0F2	Lock
\$CFFF	Disable access to luminance RAM
\$C700	Enable access to luminance RAM
\$C800-\$CF7F	Luminance RAM

\*See 6845 data sheet.



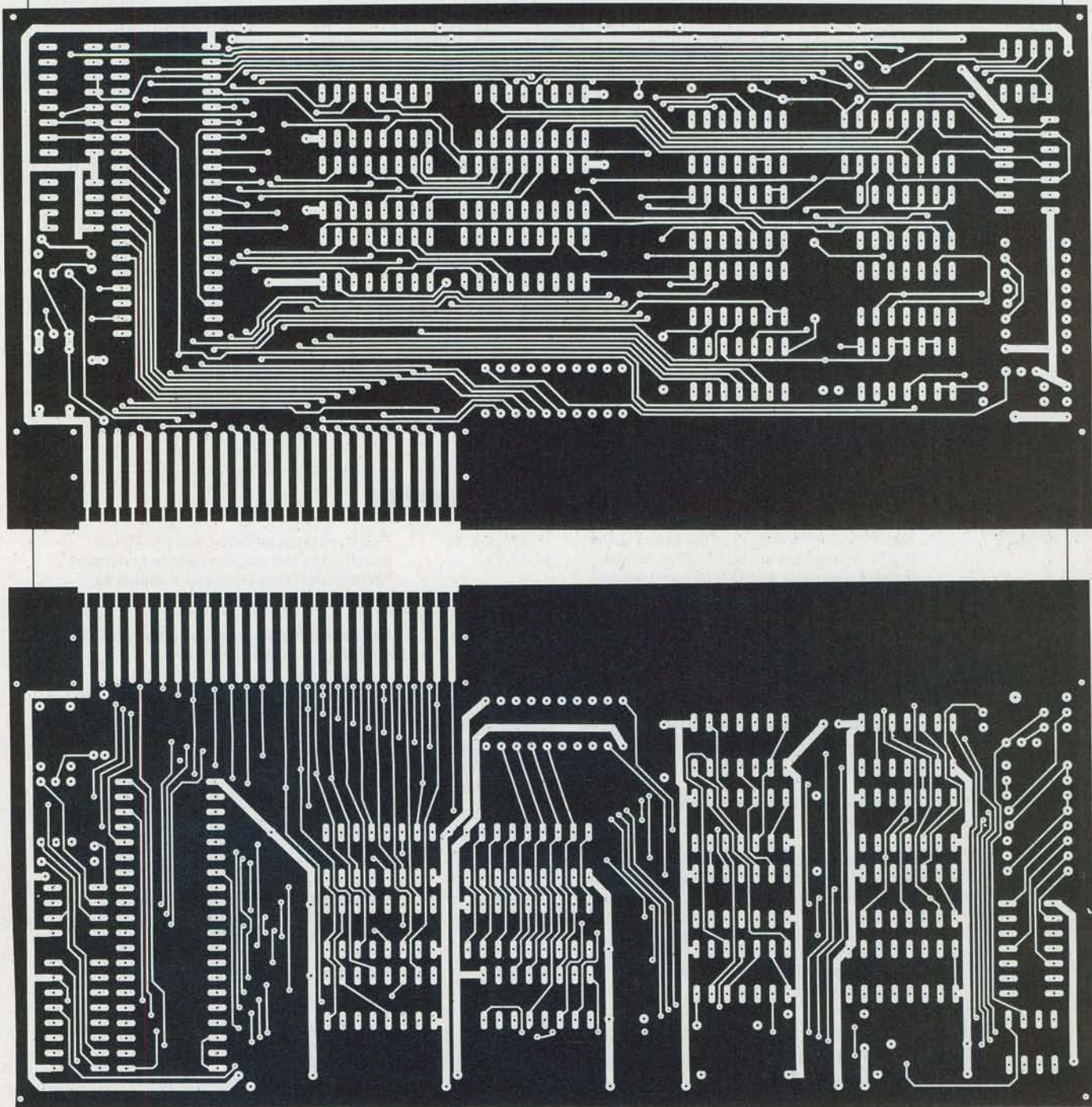


Fig. 6. Foil patterns for the double-sided printed circuit board.

porarily disconnecting the alligator clip from the video connector (the board will not deliver an output when this is done).

**Programming.** With the luminance board running, a machine-language programmer can start experimenting immediately. Program

parameters are shown in Table III.

The gray-scale RAM is located in \$C800 to \$CFFF. By writing values between 0 and 15 into this area,



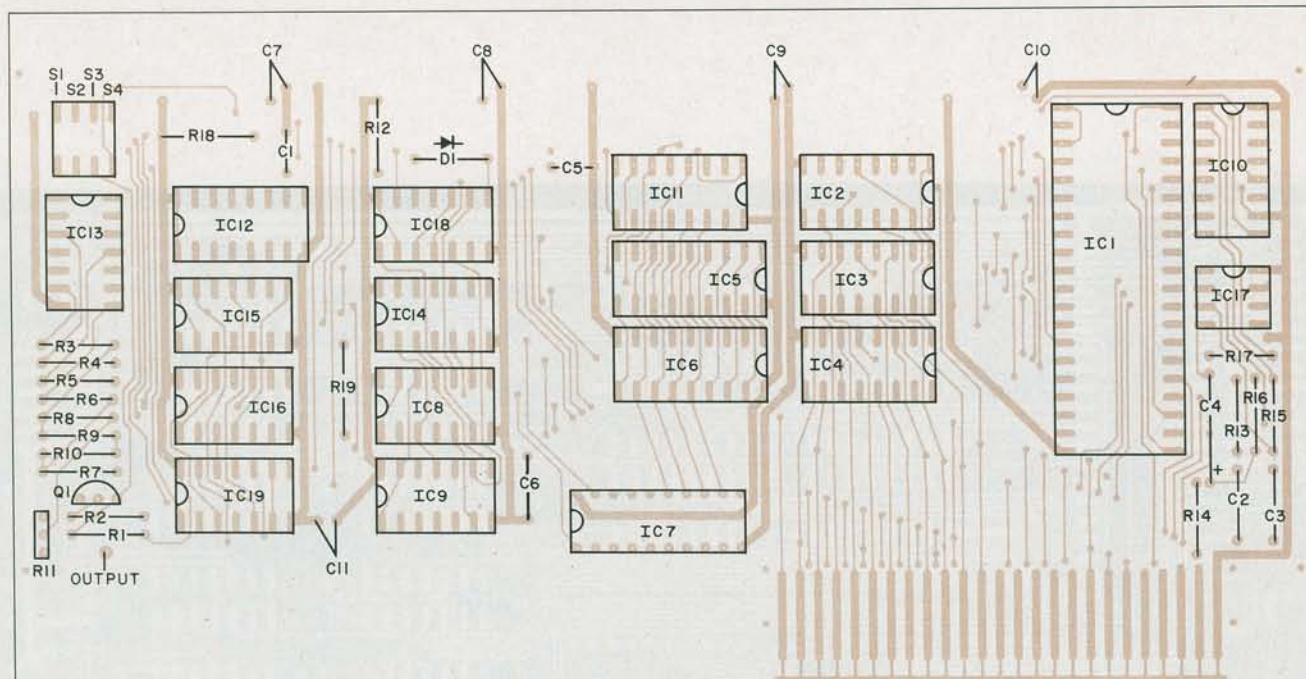


Fig. 7. Component layout for the printed circuit board.

#### TABLE IV—SPECIAL COMMANDS

&LOCK	Synchronizes the timing of the board to the Apple. It executes an &NOSHOW, so after locking, you must &SHOW to see the luminance screen.	&FILL,X,Y, X1,Y1	Fills a rectangular block with the shade specified by the previous shade command. Same restrictions on X and Y values as lo-res.
&SHOW &NOSHOW	Switches the luminance display on and off. Does not alter the content of the luminance RAM.	&MOSAIC,1 &MOSAIC,2	Converts a picture on hi-res page 1 or 2 to a 40 x 48 grey scale mosaic.
&CLR,X	Clears the luminance screen to the shade indicated by the expression after the comma. (0-15)	&S1 (text1) &S2 (text2) &S3 (lo-res 1) &S4 (lo-res 2) &S5 (hi-res 1) &S6 (hi-res 2)	Synchronous screen switches used for flipping pages.
&SHADE,X	Sets the shade for the &PLT and &FILL commands.	&I1,X	Split screen into text and hi-res 1
&PLT,X,Y	Plots a pixel of the shade specified by the last &SHADE command. Same screen coordinates as lo-res	&I2,X	Split screen into text and hi-res 2
&RTN,X,Y	Used to return the shade of the indicated X,Y location. Like the "SCRN" function of Applesoft except the value is returned through location 255 (\$FF)	&I3,X	Split screen into hi-res 1 and hi-res 2
		&SEI	Sets the interrupt disable flag
		&CLI	Resets the interrupt disable flag

pixels can be set to the desired brightness level. The screen is linearly mapped with \$C800 at the upper left corner. The high bit of each location in the luminance RAM indicates vertical synchronization status. This signal can be used to flip pages synchronously with the video frame rate.

If you don't use machine language, a special operating system has been written for the Apple that

forms a subset of Applesoft BASIC. Twenty special commands have been added, as shown in Table IV. This sub-interpreter is too lengthy to be listed here, so it is being made available on diskette from the source shown in the Parts List. The floppy diskette also contains demonstrations.

When the sub-interpreter is run, it installs itself just below DOS, and it resets Hi-Mem so that BASIC

programs will not overwrite it. Three demonstration programs and pictures of the results accompany this article to show what can be done with the luminance board and the sub-interpreter.

The result of "polishing" your Apple with these low-cost additions will clearly expand the utility of your computer, providing you with astounding video results and a new challenge. ◇