

Linear v-f converter

In this circuit a NE556 timer is used in a dual mode. Frequency of operation is $0.91/2RC$ where R is the resistance of the f.e.t. Because the resistance R is indirectly proportional to the input voltage, the circuit is very linear. Frequency range is from 0.1Hz to 100kHz and the linearity is within 0.005%.

Kamil Kraus,
Rokycany,
Czechoslovakia.

