

Read isolated digital signals without power drain

Alfredo H Saab and Joseph Neubauer, Maxim Integrated Products Inc, Sunnyvale, CA

ALTHOUGH OPTOCOUPLERS offer designers a straightforward method of establishing galvanic isolation between circuits that operate at different ground potentials, they do not provide an ideal approach. An optocoupler draws power from the isolated circuit, switches relatively slowly, and loses current-transfer ratio as its light emitter ages.

The circuit in **Figure 1** overcomes these limitations by replicating a digital signal's state, drawing no power from the isolated input, and consuming only modest power on the nonisolated side. As **Figure 2** shows, the circuit imposes only a 20-nsec input-to-output delay from the positive edge of SENSE_CLK to DATA_OUT.

MOSFET transistor Q_1 operates in either of two states—high resistance between source and drain ($R_{DS(OFF)}$), or low resistance ($R_{DS(ON)}$) when a control signal drives Q_1 into conduction. When conducting, Q_1 imposes a low resistance across T_1 's secondary winding, W_3 . The remainder of the circuit senses the state of T_1 's secondary resistance. Resistor R_1 , capacitor C_1 , and the complementary in-

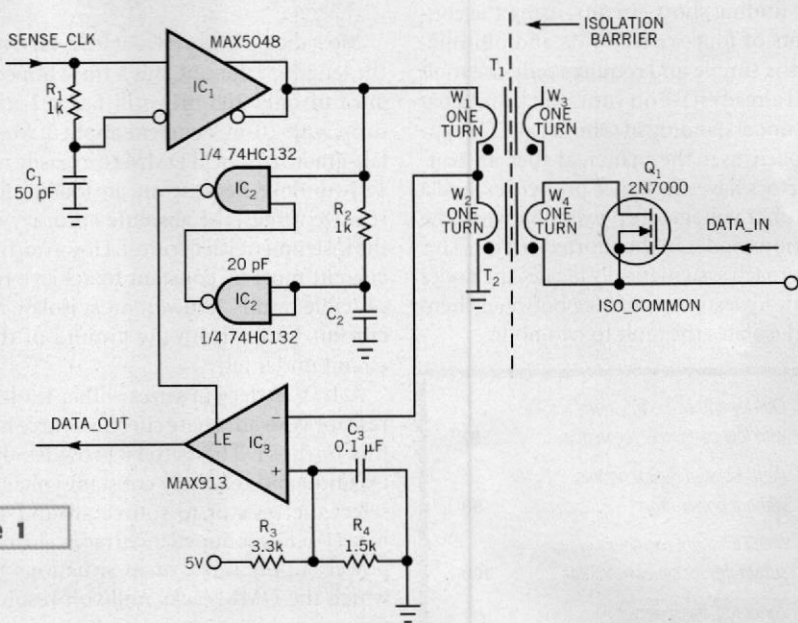


Figure 1

You can use a simple ferrite-bead transformer to isolate logic-level signals.

puts of MOSFET-driver IC_1 differentiate the SENSE_CLK signal's positive-going input edge, producing a positive-going 5V pulse at IC_3 's output and driving one

end of winding W_1 . **Figure 2** shows the relationship among the circuit's signals.

Connected in series-aiding mode, the two primary windings W_1 and W_2 of T_1

form a 2-to-1 inductive voltage divider whose center tap drives the inverting input of IC₃, a high-speed comparator. With Q₁ off and thus presenting an open circuit across the secondary of T₁, the junction of windings W₁ and W₂ applies a pulse of approximately 2.5V to comparator IC₃'s inverting input and drives IC₃'s internal state low. Meanwhile, IC₂'s two gates, resistor R₂ and capacitor C₂ generate a short strobe pulse in the middle of IC₁'s output pulse and applied to IC₃'s LE (latch-enable) input.

Latching IC₃'s internal state to its external output (DATA_OUT) produces a logic-low output that follows DATA_IN. If DATA_IN goes sufficiently positive to bias Q₁ on, Q₁'s low resistance across W₃ reflects a low impedance to windings W₁ and W₂ of T₁. The reduced pulse amplitude at the junction of W₁ and W₂ and IC₃'s inverting input of approximately 0.5V is insufficient to trigger IC₃, and IC₃'s internal state goes high. The latch-

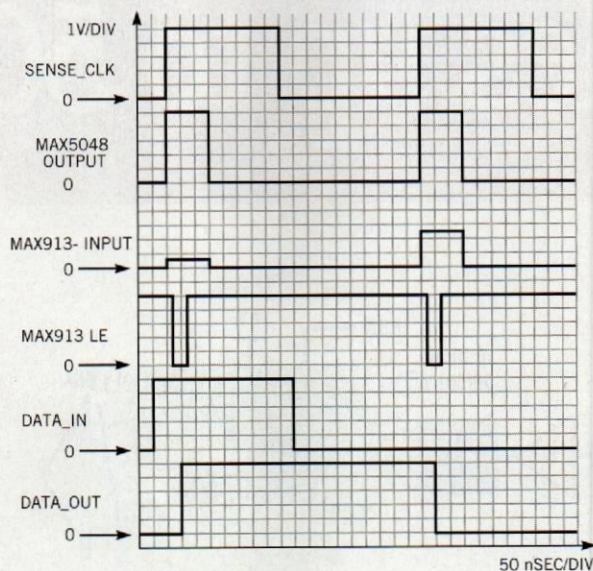


Figure 2 Each positive-going transition of SENSE_CLK transfers the state of the galvanically isolated digital signal at DATA_IN to DATA_OUT.

ing pulse at LE forces IC₃'s DATA_OUT high, again following the state of DATA_IN.

IC₁, IC₂, and IC₃ operate from a single 5V power supply. Separate bypass capacitors placed adjacent to each device's power pins minimize noise. Resistors R₃

and R₄ set IC₃'s trigger-voltage threshold. Transformer T₁ provides a 1-to-1-to-1 turns ratio and comprises a single-hole ferrite bead (Fair-Rite part number 2673000101) with three identical single-turn windings. To minimize stray inductance, keep the connection to the junction of windings W₁, W₂, and IC₁ as short as possible. Also, the grounded end of W₂ should return to IC₁'s ground connection.

The circuit's isolation capabilities depend on its pc-board layout and the properties of transformer T₁, whose type 73 ferrite core is moderately conductive. Thus, T₁'s isolation properties depend on its windings' insulation. For example, Teflon or Kapton-insulated wire can withstand several kilovolts. If you carefully construct T₁ using the specified core and Teflon-insulated AWG #24 wire, the transformer can exhibit interwinding capacitances of 0.2 pF or less. □

MOSFET shunt regulator substitutes for series regulator

Stuart R Michaels, SRM Consulting

YOU WOULD NORMALLY use a series linear regulator or a dc/dc converter to obtain 3V dc from a higher supply. However, when breadboarding a concept, you may be able to use a shunt regulator, especially if a series regulator of the correct voltage is unavailable. The MOSFET in **Figure 1** can replace a zener diode in a shunt regulator and provide lower output impedance than a zener diode.

The MOSFET is self-biased by connecting its drain to its source. The difference between the input voltage and the gate-to-source threshold voltage, V_{GS}, sets the current. The IRF521 in this example

has a threshold voltage of 2 to 4V at 250 μA. The upper curve of **Figure 2** shows that the IRF521 achieves a gate-to-source voltage of 3V at a current of about 200 μA. MOSFETs can vary from device to device, but the typical MOSFET has a threshold at approximately the mean between the maximum and the minimum limits.

The lower curve in **Figure 2** is the output impedance, which you obtain from the upper curve by differentiating the upper curve. Although the output impedance, R_{OUT}, is near 800Ω at a current of 100 μA, it rapidly drops to less than 6Ω

at 50 mA. Because you operate the MOSFET at or near threshold, its on-resistance spec doesn't apply, and the output impedance of this circuit is far higher than you would expect from the on-resistance. However, in general, the lower the on-resistance, the lower the output impedance at a specific current near threshold.

This circuit may require that R₂ and C₁ stop the oscillation in the MOSFET. Add a filter capacitor to the output to minimize the effect of load transients. Connecting a large filter capacitor from the gate to the source with short leads eliminates the need for R₂. You can use other