

# Two diodes protect logic-level translator

by P. R. K. Chetty


Indian Scientific Satellite Project, Bangalore, India

A level translator is used to interface between two circuits that operate at different logic levels. But the translating transistor (or level-up transistor) is often burned out when its load is accidentally short-circuited to ground. The addition of two diodes to the conventional level-up circuit can protect the transistor. Even a transistor that operates at 30 volts (as well as those meeting lower voltage requirements) can be safeguarded by the circuit modification described here.

The conventional translation circuit (or logic level-up

circuit) is shown in Fig. 1(a), and a modified version with two protection diodes added is shown in Fig. 1(b). The component values shown are chosen to provide a normal load current of about 100 milliamperes. In normal operation, when the input logic is high (logic 1), diode  $D_1$  is forward-biased;  $Q_1$  is turned on, and therefore  $Q_2$  is turned on. Diode  $D_2$  is reverse-biased, so the output-logic voltage across the load is nearly  $V_{CC}$ . When the input logic is low (logic 0), the transistors are turned off, and the output logic is zero.

If the output load is shorted to ground when the input is a logic 1, the anode of  $D_1$  is above ground only by the amount of the forward-voltage drop through  $D_2$ . This voltage is not great enough to let  $Q_1$  conduct because a voltage of at least two diode drops,  $V_{D1}$  and  $V_{BE}$ , would be required to turn on  $Q_1$ . Therefore  $Q_1$  is turned off, and, as a result, transistor  $Q_2$  is turned off too, which prevents it from conducting a destructive current straight to ground. The circuit remains shut down as

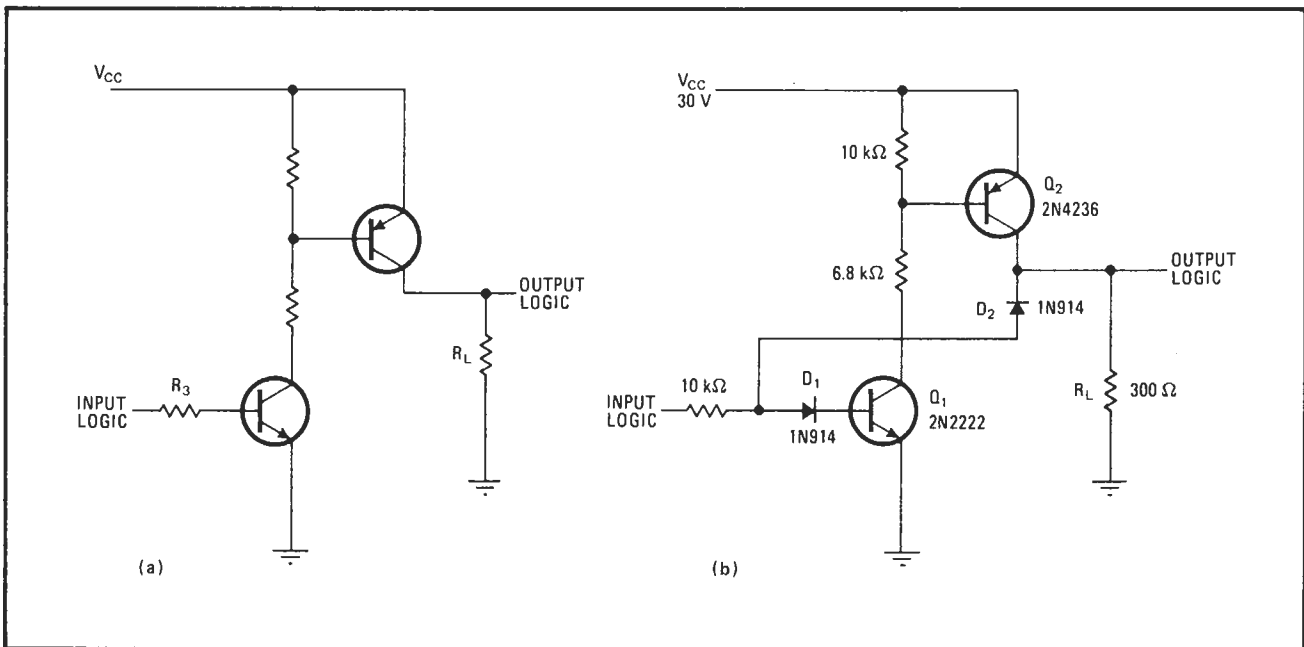

**1. Protection.** Conventional logic-level translator shown in (a) is modified by addition of two diodes in (b). Diodes protect translation transistor  $Q_2$  from destructive current that would otherwise flow if load resistor were short-circuited. Diodes turn off both transistors, so no current is drawn from supply while load is shorted. In normal operation, load current of about 100 milliamperes is unaffected by diodes.