

# Cross-coupled gates prevent push-pull-driver overlap


Richard Rice, Oconomowoc, WI



Overlap—the short period during which a push-pull drive's two transistors are both simultaneously on—is a common problem with

these drives in a center-tapped transformer's primary. Overlap causes a large current spike and increased switching losses. The fact that saturated transis-

tors turn off more slowly than they turn on causes the problem. One method of preventing overlap is to provide a time delay after turning off one transistor and before turning on the other one. This method requires several extra components and must include enough delay for a worst-case scenario. This Design Idea uses cross-coupled gates to prevent one transistor from turning

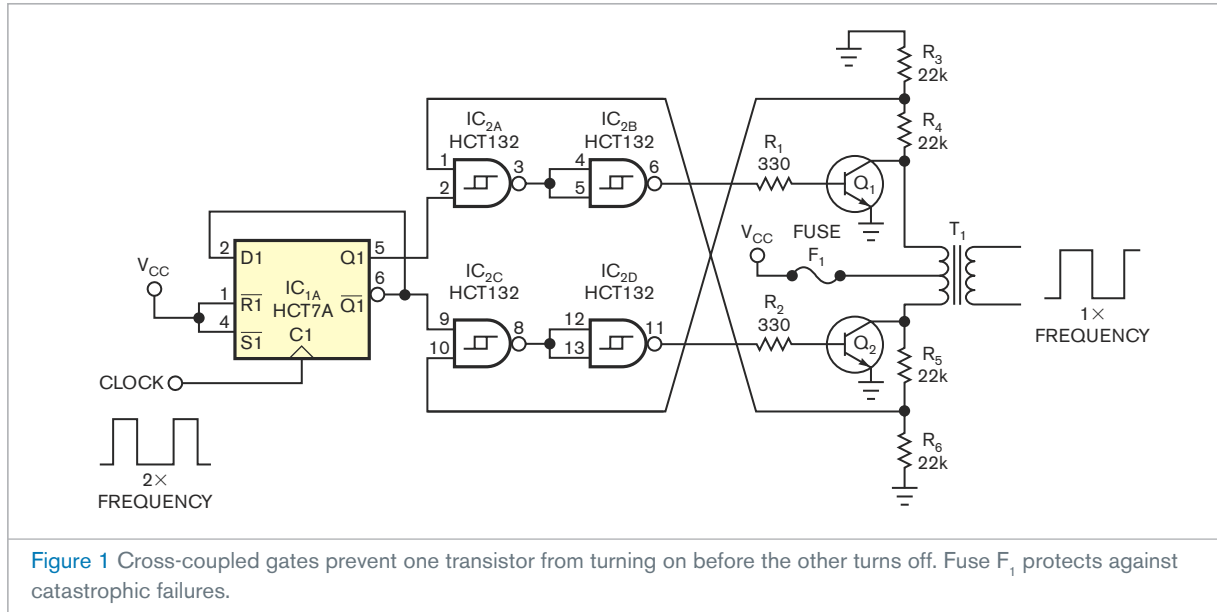

**Figure 1** Cross-coupled gates prevent one transistor from turning on before the other turns off. Fuse  $F_1$  protects against catastrophic failures.

on before the other turns off (**Figure 1**). For simplicity, the **figure** omits the depiction of bypass capacitors, snubber networks, and other components unnecessary for illustrating the method.

Gate IC<sub>2A</sub> prevents Q<sub>1</sub> from turning on until Q<sub>2</sub> turns off. Likewise, gate IC<sub>2C</sub> prevents Q<sub>2</sub> from turning on until Q<sub>1</sub> turns off. Gates IC<sub>2B</sub> and IC<sub>2D</sub> function as inverters to provide the correct

polarity to drive the switching transistors. Monitoring the transistors' collector voltages senses the turn-off of each transistor using the voltage dividers R<sub>3</sub>/R<sub>4</sub> and R<sub>5</sub>/R<sub>6</sub>. Because the collector voltage swings to twice the supply voltage, the voltage dividers halve the voltage. The impedance of the voltage dividers also limits the gates' input current to a safe level during overshoot.

The switching frequency is one-half the input-clock frequency. D-type flip-flop IC<sub>1A</sub> divides the input-clock frequency by two and provides complementary outputs with a 50% duty cycle. The complementary outputs drive the switching transistors in an alternating sequence. The secondary of transformer T<sub>1</sub> provides an isolated square-wave output. **EDN**