

Series Resistors, Body Capacitance Scan 16 Buttons With Two MCU Pins

In an application using a pin-limited microcontroller (MCU), I needed to scan an array of 16 buttons. The technique I used involved a series string of resistors of identical value connected between two bidirectional pins of the MCU.

For simplicity, the example shown uses five resistors to scan four buttons (*see the figure*). A metal pad is created at each juncture between the resistors. When a person touches one of the metal pads, body capacitance creates an RC circuit that the MCU can sense.


P1 is first configured as an output, and P2 as an input. P1 drives a high level that charges the capacitor through the resistors in the

string connecting P1 and the metal pad that's being touched. In the example, this resistance is $2R$. The voltage level on P2 is sensed and the time at which the capacitor reaches a logic 1 is recorded. This time, T_2 , is proportional to $2R \times C$. Because P2 is a high-impedance input, the remaining resistors in the string have no appreciable effect on the time constant.

P1 and P2 are then turned into outputs and driven to a low level to dump the charge on the capacitance as quickly as possible. After that, the situation is reversed, with P2 becoming the output and P1 becoming the input. The capacitor charging time, T_1 , sensed by

COTS POWER SOLUTIONS

For Military and Avionics Applications

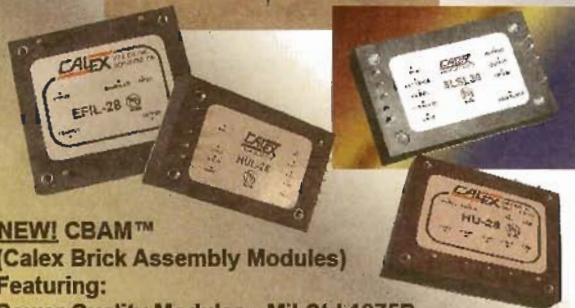

NEW! CBAM™ (Calex Brick Assembly Modules)

Featuring:

- Power Quality Modules - Mil-Std 1275B
- Filter Modules - Mil-Std 461E
- Hold-up Modules
- Load Share Modules
- DC/DC Converters
- AC/DC Power Supplies
- Custom Power Solutions
- Power Accessories




www.calex.com
(925) 687-4411 (800) 542-3355
e-mail: sales@calex.com

Ask us about our new 200W Half Brick!

READER SERVICE 90

Ideas For Design

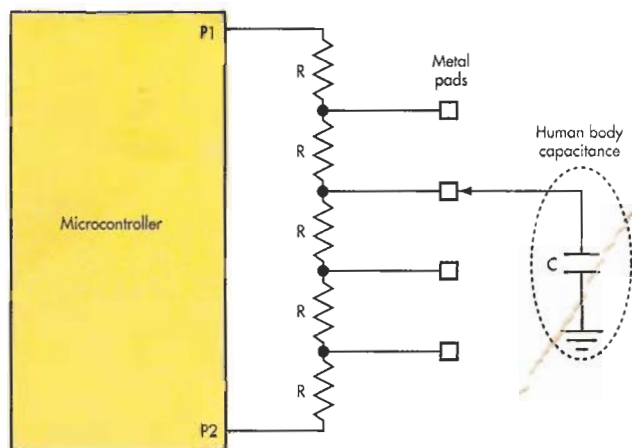

This arrangement uses two MCU pins that switch between output and input, which lets the device calculate the differences in the RC time constants to determine which button is pushed.

P1 in this condition, is proportional to $3R \times C$.

The MCU computes the ratio of T1 and T2:

$$T1/T2 = (3RC)/(2RC) = 3/2.$$

The ratio is independent of the actual human body capacitance or the resistor value (as long as all the resistor values are identical). The MCU looks for the closest match of the ratio in a table to determine which button was touched.

Assuming a human body capacitance of 100 pF, a value of 10 kΩ for R gives a time increment of about a microsecond, something most microcontrollers can sense.

As noted, I used this technique to scan as many as 16 buttons. An obvious limiting factor is stray capacitance along the resistor string and on the MCU I/O pins. You also need resistors with well-matched values, at least 1% or even 0.1%, depending on how many buttons you are scanning. The MCU pins also have to trigger at the same threshold voltage. If your production environment and MCU allow it, you can use a training session to teach the controller what ratio corresponds to each button and have it stored into the EEPROM or flash.

The resistors in the string serve to attenuate the effects of electrostatic discharge (ESD) when a person touches a bare metal pad connected directly to the circuit. If ESD is a concern, replace the metal pads with pushbuttons that connect a common capacitor to ground. In this case, you can make C larger and reduce R to reduce the effect of stray capacitance.

If an additional pin (P3) is available, you can scan up to 32 buttons by using resistor strings between P1-P2 and P1-P3. With N pins, you could scan $16N(N - 1)$ buttons.

DAVE VANDEN BOUT, president, holds a BS, MS, and PhD in electrical engineering. He attended North Carolina State University, Raleigh, and the Massachusetts Institute of Technology, Cambridge.

Design & Development

Engineers

SUPERSOURCE

ASAP
RUSH
SERVICE



Development
Sockets

Adapters



HiLo PGA/BGA
Socketing System



PC104 & PC104+
Connectors



Test accessories
for every package

Mictor probing &
cable accessories

FIND IT FAST
GET IT FAST

ET Emulation Technology, Inc.

(800) 232-7837

www.emulation.com

READER SERVICE 95