

USING MICROPROCESSORS IN YOUR home projects often turns out to be a complex ordeal. The typical microprocessor project consists of the processor, EPROM, RAM, address decoder circuitry, clock circuitry, input/output ports, and the ever present but essential "glue" components. Things can get a little more complicated if a special-purpose IC like an analog-to-digital converter is thrown in. Then comes the pleasure of putting everything on a circuit board—and most of the time the complexity of the circuit necessitates the use of a double-sided board!

But don't despair. There is an easier and more enjoyable way to exercise your hobby. This article will open the door to a more efficient hobbyist approach to designing microprocessor-based projects. Imagine how much de-

sign time could be saved if you had a processor, EPROM, RAM, clock, and input/output ports already integrated into a standard 40-pin package.

Such devices already exist, of course—they're called microcontrollers. Several different varieties of these microcontrollers are now readily and inexpensively available. All you really need to use them is a microcontroller programmer, and we're going to show you how to build one in just one evening for under \$50. The programmer is good for the 8748H and 8749H series of microcontrollers made by Intel.

#### The 8748/49H

The 8748/49H is commonly referred to as a single-component 8-bit microcomputer. The instruction sets for the 8748H and 8749H are identical. The 8749H

contains 2K of EPROM and 128 bytes of RAM, while the 8748H contains 1K of EPROM and 64 bytes of RAM. Although that doesn't sound like a lot of memory, you'll find the amount of EPROM and RAM to be more than adequate for most controller applications. And if you do require extra RAM, you can hang it out-board just as you would with any other processor IC.

Both IC's include an interval timer/event counter, two single-level interrupts, an internal oscillator, a true bi-directional bus, two latched quasi-bidirectional I/O ports, two testable input pins, and an 8-bit processor that executes over 96 instructions with most of them consisting of a single byte. If you're short on I/O or memory, the 8748H/49H will accommodate most common peripheral circuitry available for other microprocessors. A minimum circuit configuration consists of the 8748H/49H, a crystal, two 27-pF disk capacitors, a 5-volt DC power source, and a 1- $\mu$ F reset capacitor.

#### Software

There are many cross assemblers for the 8748H/49H available in the public domain, and many more advertised by reputable electronics distributors. Just choose one that fits your needs and budget. One cross-assembler software package that can be used with PC-compatible computers is contained in a ZIP file (TASM.ZIP) that's included as part of a larger ZIP file containing all software relevant to this article. The larger ZIP file (874XPGR.ZIP) is available on the RE-BBS (516) 293-2283, 1200/2400, 8N1.

The 8748H/49H lends itself well to applications that require I/O port activity and serial communications (RS-232) with a terminal or supervisory program. This project was designed to take advantage of both. Most of the data storage and screen information are maintained and presented to the user by the terminal program, PROG.EXE, which runs on a PC-compatible computer. The terminal program is DOS based, so you may have to modify the source code (PROG.BAS) to run on a different computer. The software listing

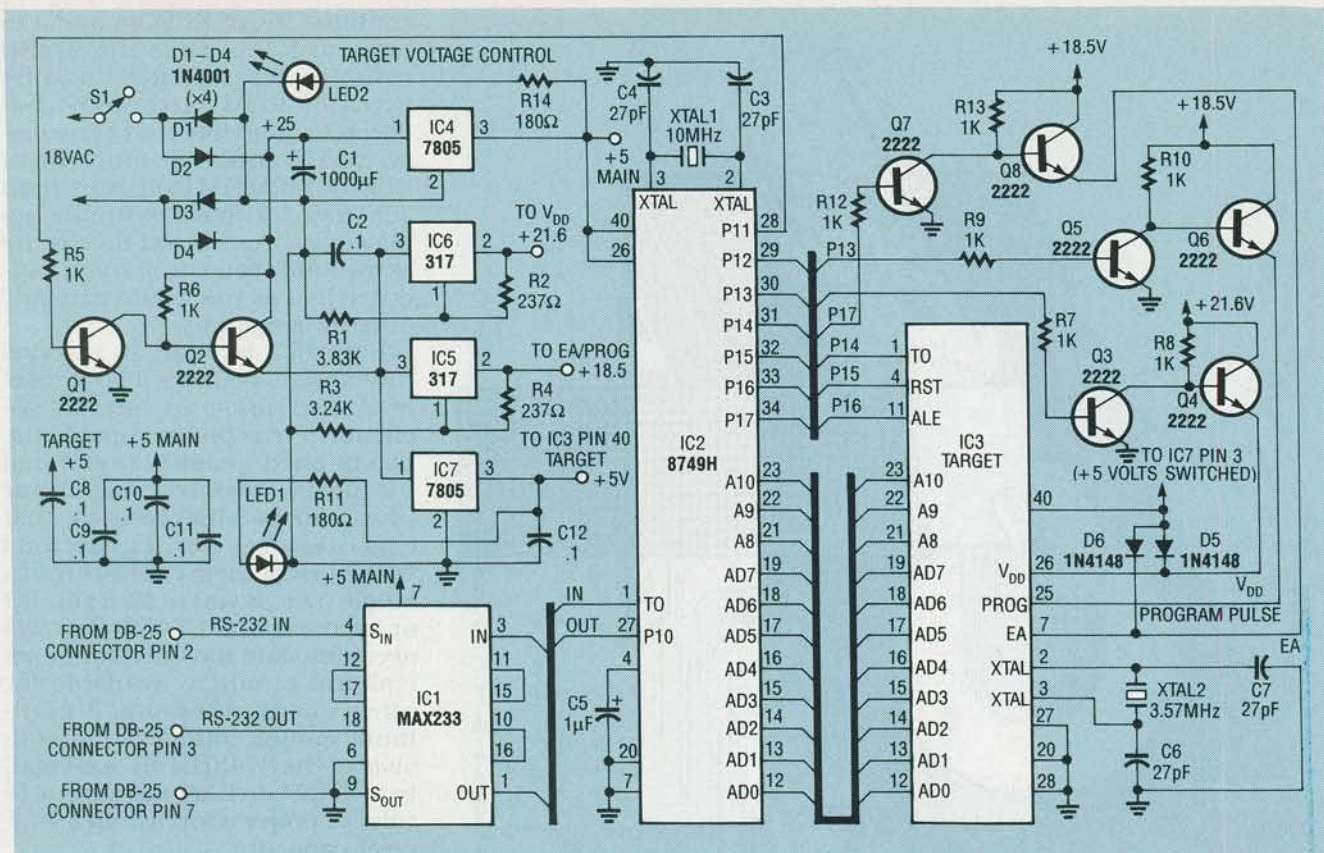


FIG. 1—PROGRAMMER SCHEMATIC. The MAX233 RS-232 driver/receiver (IC1) converts the signals from your serial port to TTL levels for the 8749H and vice versa.

for the terminal program is unfortunately too large to print here, but it is contained in the main ZIP file (874XPGR.ZIP).

Any data or commands are sent serially at 2400 bits per second from the terminal program via serial port to the programmer. The programmer's processor acts on the received data and returns any necessary data to the terminal program. This eliminates the housekeeping functions that would normally be performed by the programmer's processor, and thus simplifies both the hardware and the software of the programmer module.

### Circuitry

Looking at the schematic in Fig. 1, IC1 is a MAX233 RS-232 driver/receiver. Its purpose is to convert the signals from your serial port to TTL levels for the 8749H and vice versa. The input serial data stream is fed into the  $T_0$  input of the 8749H programmer while the output data stream is fed from I/O Port 1.0. The combination of the driver/receiver IC, the built-in hardware of the 8749H, and firmware in EPROM

allows the terminal program to communicate with the 8748H/49H programmer.

Microcomputer IC2 (an 8749H) controls the application of the proper programming voltage levels, pulses, address information, and data to IC3 (the target device), which is installed in a ZIF (zero insertion force) socket when programming. The code for IC2 (874XCODE.HEX) is also contained in the ZIP file 874XPGR.ZIP. (There is also a binary version of the code, 874XCODE.BIN, which is also contained in the ZIP file.) The bidirectional ports contained in IC2 latch output data and read input data that is latched onto an external port by another device. Traditionally that would be handled by both a 74LS373 octal latch used as an output port and a companion 74LS244 used as an input port. Our programmer contains no external latches or address decode circuitry in either the data bus or control ports.

Data and address information are multiplexed on the bus pins  $AD_0$ – $AD_7$ . The bus pins behave in

a similar fashion to the bidirectional port pins but tend to be more TTL-like in nature. If you get a data sheet, study the differences in internal hardware construction as it pertains to the bus and quasi-bidirectional I/O ports. In the case of the programmer hardware, the target, IC3, and main processor, IC2, alternately latch output data on their respective busses to be read by the opposing processor's bus. Address pins  $A_8$ – $A_{10}$  are actually IC2's I/O port pins  $P_0$ – $P_2$ , and are used as latched output pins. I/O port  $P_1$  is used to control the transistor pairs that supply the correct programming voltages to the target device. Since all of the bidirectional I/O pins can drive one TTL load, port  $P_1$  is also used to set up TTL logic levels on IC2's port pins  $P_{1.4}$ – $P_{1.6}$  that connect to the target device directly.

Power for IC1 and IC2 is supplied via voltage regulator IC4 and associated circuitry. Crystal XTAL1 along with the two 27-pF capacitors supply the feedback path for the on-chip oscillator. Since precise clock periods are required to generate timing for

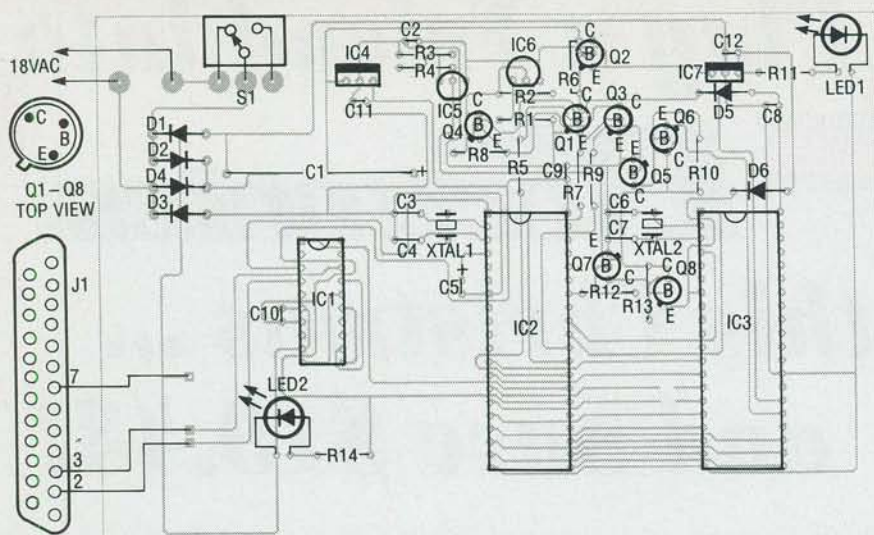


FIG. 2—FIRST INSTALL THE POWER SUPPLY DIODES D1–D4, filter capacitor C1, switch S1, and connect the 18-VAC transformer. With no other parts installed, you should have a full-wave bridge circuit with a +25-volt DC output across C1.

the serial data stream and programming pulses, a crystal-controlled oscillator is essential.

The 1- $\mu$ F tantalum capacitor, C5, resets the microcomputer. Note the absence of the reset switch, and don't be tempted to add one. If the power is toggled or the processor is reset while a target device is socketed, permanent damage will result to the target due to transient voltages on the transistor pairs generated by a main processor reset. Therefore, NEVER apply or terminate power while a target is socketed. You may add a reset switch across the 1- $\mu$ F capacitor as shown in the example circuits we'll look at later.

The device to be programmed, IC3, can be either a 8748H or 8749H. You select the type when you run the terminal program. The target device needs +5-, +18-, and +21-volt DC power sources to effect the programming/verify process. The voltages are derived from voltage regulators IC5–IC7; IC5 and IC6 are standard configurations of the low-power "LZ" version of the LM317.

Transistor pairs Q3–Q4, Q5–Q6, and Q7–Q8 provide the high-voltage switching functions necessary for the programming and verification of the target device. Voltage regulator IC7, a 7805T, supplies +5-volts DC to the target during programming and verification. Light-emitting diode LED1 is active when power is applied to the target device. Tran-

sistor pair Q1–Q2 is used to switch all operating power to the target device (IC3).

The 8748H/49H needs a clock signal to move data internally. Crystal XTAL2 along with its 27-pF capacitors are used to supply a clock signal for the target device. Any crystal between 3 and 4 MHz will suffice. The target clock period is not critical to the programming process.

The sequence used to program IC3 is similar to programming an ordinary EPROM; the target device is powered up in program mode. Address information is passed to the target by IC2. Then, data information is latched out of IC2 to the target. A pulse is applied to the target's PROG pin and the verification process follows. If verification is good, then the process is repeated for the next byte, and so on.

To sum it up, IC1 converts RS-232 voltage levels to TTL voltage levels and vice versa. Controller IC2 provides communication with the terminal program via a 2400 bits-per-second serial link, provides address and data information to the target, provides precisely timed pulses to the target, and provides voltage-switching information to the transistor pairs that interface with the target. Target IC3 is programmed with the data you specify using the terminal program in conjunction with IC2. All of this is done with a single-component microcomputer on a single sided board!

## PARTS LIST

### All resistors are 1/4-watt.

- R1—3830 ohms, 1%
- R2, R4—237 ohms, 1%
- R3—3240 ohms, 1%
- R5–R10, R12, R13—1000 ohms, 5%
- R11, R14—180 ohms, 5%

### Capacitors

- C1—1000  $\mu$ F, 35V, electrolytic
- C2, C8–C12—0.1  $\mu$ F, 50V, Mylar
- C3, C4, C6, C7—27 pF, disk
- C5—1  $\mu$ F, 35V, tantalum

### Semiconductors

- IC1—MAX232 RS-232 driver/receiver
- IC2—8749H microcontroller (programmed)
- IC3—8748H or 8749H microcontroller
- IC4, IC7—7805T 5-volt regulator
- IC5, IC6—LM317LZ low-power adjustable regulator
- D1–D4—1N4001 diode
- D5, D6—1N4148 diode
- LED1, LED2—light-emitting diodes, choose color to suit taste
- Q1–Q8—2N2222A NPN transistor

### Other components

- S1—SPST toggle switch
- XTAL1—10-MHz crystal
- XTAL2—3.57-MHz crystal

**Miscellaneous:** 18VAC transformer, heatsink for IC4, 40-pin ZIF socket (for target IC3), 40-pin IC socket (for IC2), 20-pin IC socket (for IC1), 25-pin right-angle female DB-25 connector (optional), serial cable, PC board, wire, solder, etc.

**Note:** The following items are available from F. Eady, PO Box 541222, Merritt Island, FL 32954:

- A kit of parts including a pre-programmed microcontroller (not including the transformer, ZIF socket, serial cable, or 25-pin connector)—\$49.95 + \$5.00 S&H.
- PC board only—\$15.00 + \$5.00 S&H.
- Software on floppy disk—\$5.00 postpaid.

Check or money orders only.  
For technical assistance call (407) 454-9905.

## Construction

The first thing you must do is etch and drill a PC board from the pattern we've provided—or purchase a ready-to-use PC board from the source mentioned in the parts list. As shown in Fig. 2, start assembly by installing power supply diodes D1–D4 and filter capacitor C1. Mount the switch S1 and connect the 18-VAC transformer. At this point,






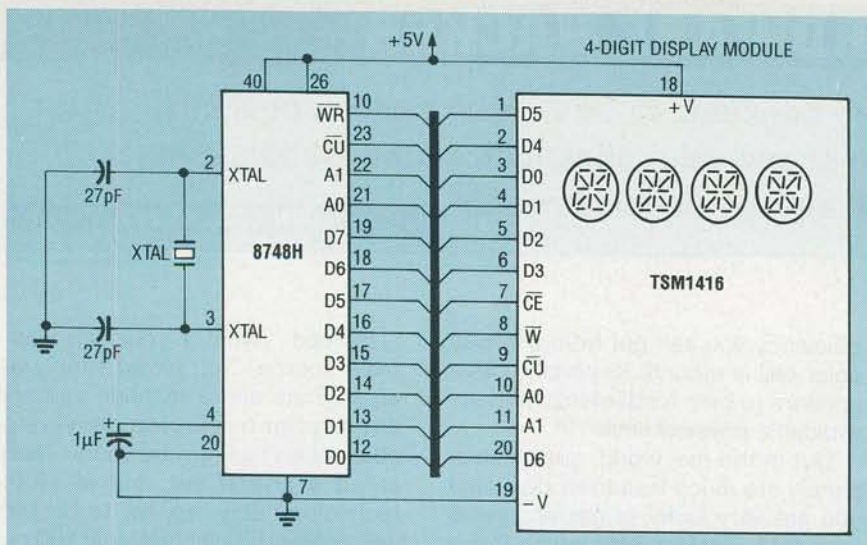


FIG. 4—INTELLIGENT DRIVER for a 4-digit display module. The circuit will first put an "X" in all four digits and then display "8748." The accompanying software is shown in Listing 1. The TSM1416 4-digit display module is manufactured by Three-Five Systems, Inc.

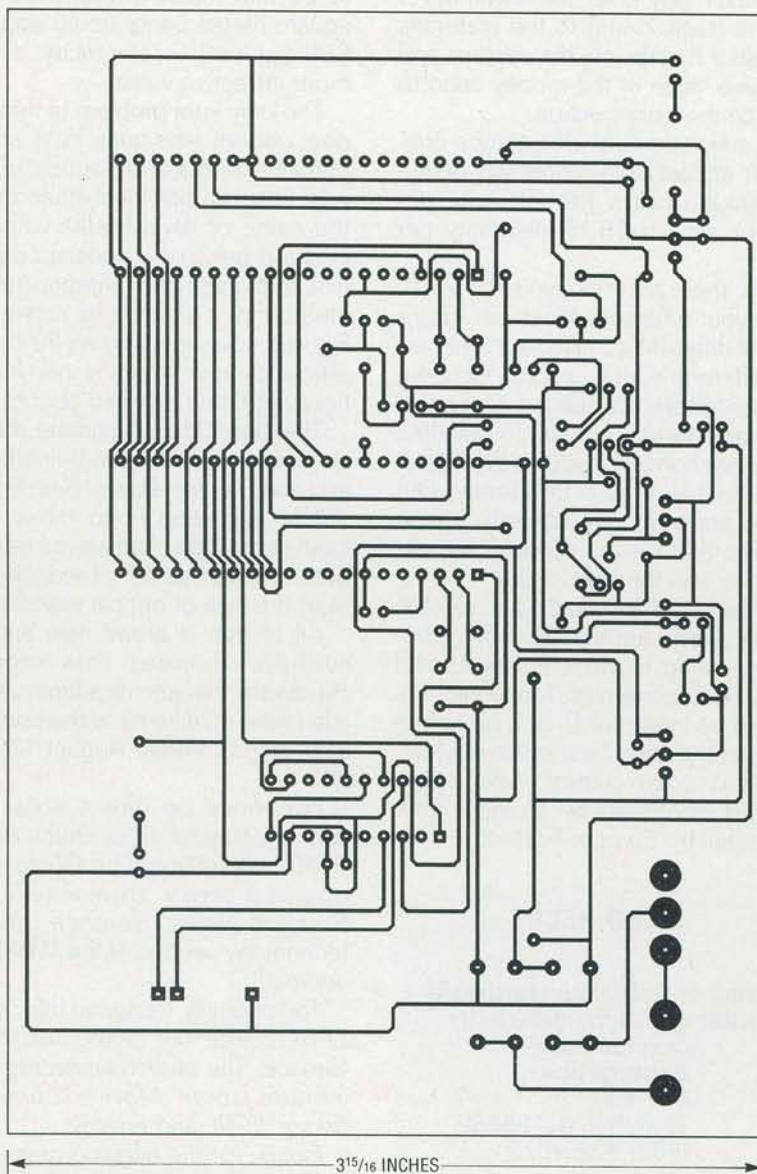

FOIL PATTERN for the microcontroller programmer, shown actual size.

binary editor and then program that file into a target 8748H. This eliminates the initial need for a cross assembler and gives you the opportunity to experiment with minimum cost and effort. The circuits presented illustrate the advantages of using an integrated microcomputer like the 8748H—and they're simple enough to be built on an experimenter's breadboard.

Figure 4 shows an intelligent driver for a 4-digit display module, and Listing 1 shows the accompanying software. The circuit will first put an "X" in all four digits and then display "8748." While it's nothing fancy, it does show you how to make the display work. The TSM1416 4-digit display module is manufactured by Three-Five Systems, Inc.

Our second example circuit, shown in Fig. 5, is our "expensive LED blinker circuit." We say "expensive" because you certainly

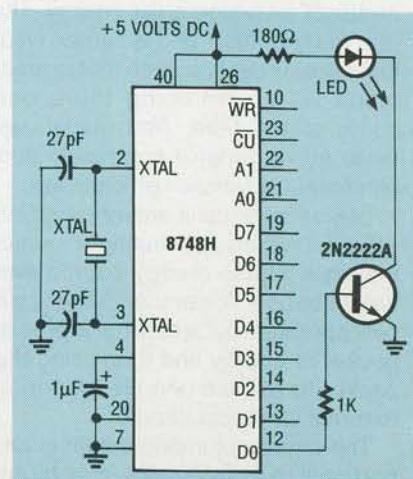


FIG. 5—EXPENSIVE LED BLINKER circuit. While it is somewhat overkill, it is very useful as a teaching tool. The software for this circuit is shown in Listing 2.

don't need a microcontroller to turn an LED on and off—the circuit is somewhat of an overkill. However, the circuit's simplicity becomes extremely beneficial when it's being used as a teaching tool. That way you can concentrate on the microcontroller's operation. The software for the Fig. 5 example is shown in Listing 2.

For the two example circuits we've provided, you can copy the software routines directly from the listings or download them from the RE-BBS as part of the main ZIP file (874XPGR.ZIP). R-E