

SPECIAL SUPPLEMENT - ULTRA HI-FI DESIGN

electronics today

SEPTEMBER 1978

INTERNATIONAL

\$1.25*

NZ \$1.50

Windscreen Wiper
Delay Unit

Space Shuttle
Communications

Light Chaser
Project



LED Pendant

LED Pendant

WANTING TO IMPRESS upon one's partner that electronics is not a boring useless occupation, has inspired many an electronic engineer to build egg-timers and liquid overflow indicators, etc. for their loved ones.

However, such devices, appreciated though they may be, cannot usefully be exhibited at parties and pubs to achieve maximum admiration. An obvious solution is electronic jewellery.

Before LEDs became commonly available it was possible to build illuminated jewellery using miniature catheter bulbs. But the current drain still involved the inelegant strapping-on of bulky power supplies and concealed switches.

Nowadays, by using LEDs and CMOS 'chips', it is possible to build a piece of self-contained jewellery that doesn't even need an on/off switch.

Electronic jewellery may take virtually any form that the designer seeks — the main limitation being availability of miniature resistors which are often hard to find in this country.

The example shown was in fact built using 1/8th watt resistors obtained from the UK. IRH manufacture a range of 1/4 watt resistors which are marketed via A & R-Soanar and only minor changes are needed to the mechanical details shown to accommodate these.

The operation is as follows. Upon touching the contact plates the seven-segment LED flashes between the two sections of the design for about eight seconds and then switches off again.

The pendant is not limited to letters that the seven segment display can handle. There is nothing to stop the reader from hard-wiring LEDs into dot patterns of any desired form.


(The prototype shown here was designed to flash the initials BJ).



Finishing It Off

When all the wiring is complete the battery compartments need to be constructed. Make up two tubes of the same external diameter as the batteries from cellophane or plastic and position them on the facia over the battery contacts, then pour quick-set epoxy around the tubes. When the epoxy has set remove the tubes and you have two battery compartments.

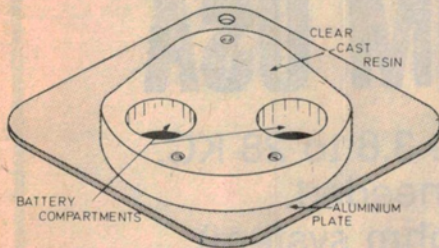Make up another cellophane or plastic tube about 37 mm in diameter. Place this around the finished electronics and battery compartments and pour more clear cast over to cover everything to the depth of the battery compartments. When this has set a thin sheet of aluminium can be screwed down with countersunk self-tappers. (This sheet forms the common connector for the two cells).



LED Pendant as seen from rear after potting, note battery compartments.

Presentation

Having built the device, and given it to your loved one, all that remains is for you to reap your just rewards, preferably in dimly lit surroundings where the pulsating red glow will hopefully produce the desired effect!

Note

This project could have been made much smaller by using a flat pack version of the 4011 and miniature hearing aid type transistors, and 1/20th watt resistors. This would reduce the size to almost the display and battery dimensions. But by using commonly available components a respectable size has been achieved.

PARTS LIST – ETI 552

Resistors all 1/8 W 5% or smaller

R1	2M2
R2	1M
R3	47k
R4	100k
R5,6	4k7
R7	120R
R8	150R

Capacitors

C1	10 μ 6V3 tantalum
C2	4 μ 7 16V tantalum

Semiconductors


IC1	4011
D1	1N914
Q1,2	BC214
DISPLAY	7-segment common cathode type

Additional components for the circuit shown in Fig. 1(c)

R9	470R
R10	4k7
R11	220R
R12	120R
Q3	BC214

Miscellaneous

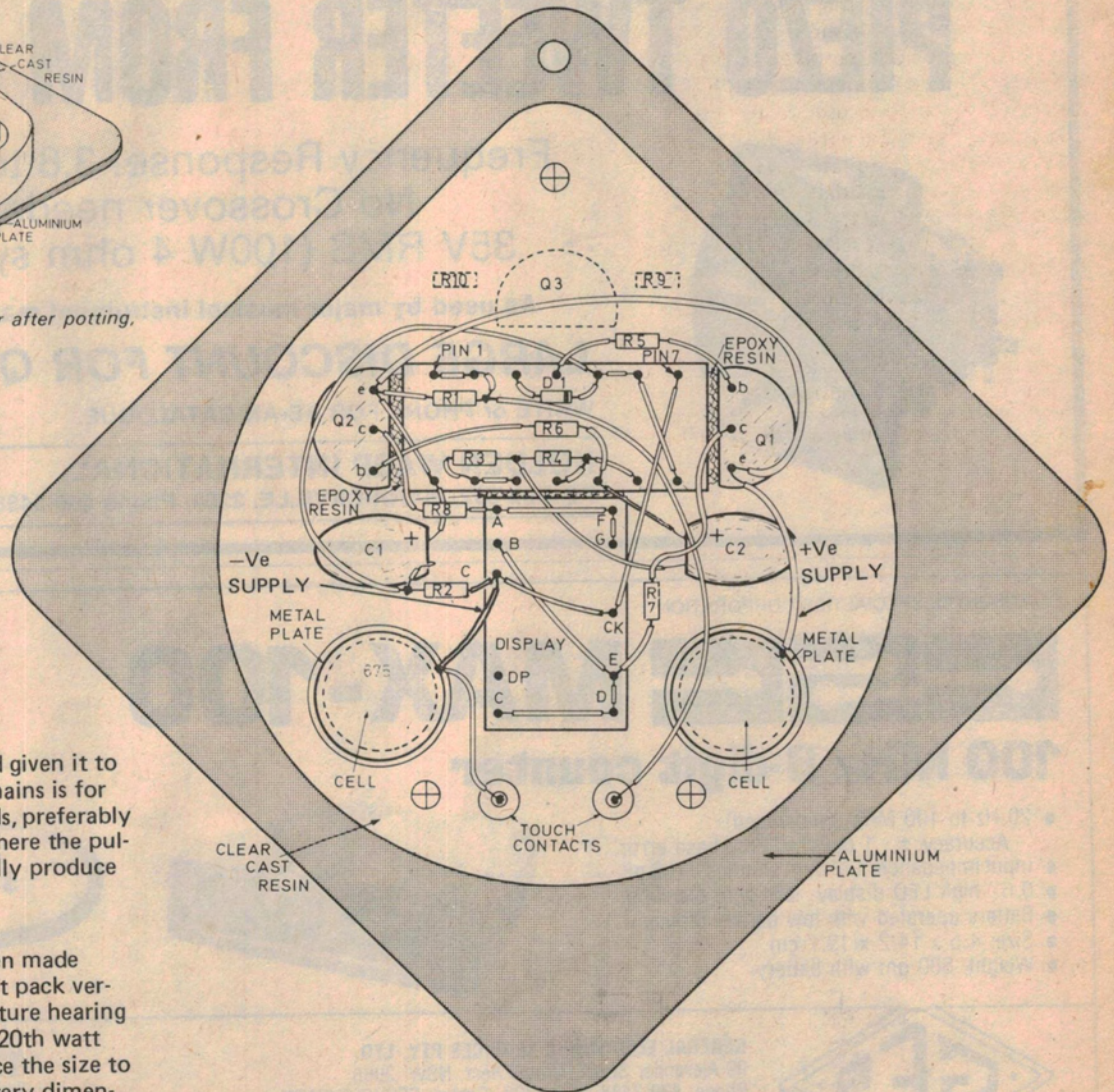Piece aluminium 14 B&S 50 mm square, piece red perspex 21 mm x 12 mm, epoxy resin, 2 off 6 BA brass cheese-head bolts, 19 B&S tin plate, 28 B&S tinned copper wire, PTFE sleeving, 2 off Mallory MS76M cells.



Component layout, shown at twice times life size.