

# designideas

READERS SOLVE DESIGN PROBLEMS

## Platinum-RTD-based circuit provides high performance with few components

Jordan Dimitrov, Toronto, ON, Canada

The standard way of using an RTD (resistance-temperature-detector) sensor is to include it in a bridge followed by a differential amplifier. The problem is that two nonlinearities—one from the sensor and another from the bridge—affect the transfer function. Some approaches are available that attempt to avoid the problem, but they tend to be bulky and expensive (references 1, 2, and 3). An alternative circuit proposes adding only one extra resistor to the differential amplifier but provides neither design guidelines nor results (Reference 4). This Design Idea fills the gap. Although circuit analysis is somewhat complex, performance is good, and the circuit uses few components.

Besides the platinum RTD,  $R_{\theta}$ , the circuit features only six precision resistors, an op amp, and a voltage reference (Figure 1).  $R_4$ , the extra resistor for the differential amplifier, delivers

additional current to the sensor that relates to the temperature you are measuring. With proper design, the circuit can provide good linearity and stability over a wide range of input temperatures. The output voltage,  $V_O$ , depends on circuit components in the following way:

$$V_O = V_{REF} \times \frac{Y_1}{Y_2} \times \frac{R_{\theta}(Y_0 + Y_2 - Y_3 - Y_4) - 1}{R_{\theta}[Y_1 + Y_3 - R_2 Y_4(Y_0 + Y_1)] + 1}$$

where  $Y_i = 1/R_i$  and  $i=0$  to 4.

For positive temperatures, a second-degree polynomial of the following form can approximate RTD characteristics:

$$R_{\theta} = R_0(1 + \alpha \times \theta + \beta \times \theta^2),$$

where  $R_0$  is sensor resistance at  $0^{\circ}\text{C}$ ,  $\alpha$  and  $\beta$  are coefficients, and  $\theta$  is the measured temperature.

After replacing the second equation

### Dis Inside

72 Proportional-ac-power controller does out whole cycles of ac line

78 Extend monolithic programmable-resistor-adjustment range with active negative resistance

78 1-Wire network controls remote SPI peripherals

>What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to [edndesignideas@reedbusiness.com](mailto:edndesignideas@reedbusiness.com).

>To see all of EDN's Design Ideas, visit [www.edn.com/designideas](http://www.edn.com/designideas).

in the first and doing some rearrangements, you get:

$$V_O = \frac{\theta - B}{\theta^2 - B\theta - C} \times K \times \theta = f(\theta)K\theta,$$

where  $B$ ,  $C$ , and  $K$  are constants and  $f(\theta)$  is a function of temperature. Figure 2 shows the general shape of  $f(\theta)$ . The output voltage depends linearly on temperature when  $f(\theta)$  is as close

as possible to a constant. This situation is most true around the minimum point of  $f(\theta)$ .

Some additional relations provide that the output voltage is  $0\text{V}$  at temperature  $0^{\circ}\text{C}$ , the conversion coefficient is  $10\text{ mV}/^{\circ}\text{C}$ , the minimum of function  $f(\theta)$  is in the middle of the measurement span, and

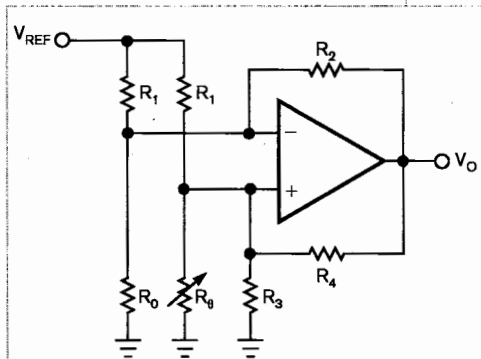


Figure 1 This generic RTD circuit needs few components.

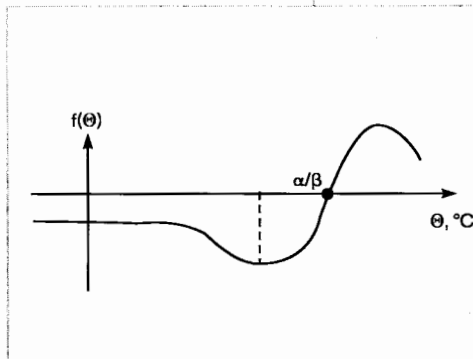


Figure 2 The general shape of function  $f(\theta)$  varies with temperature.

the current through  $R_\theta$  causes negligible self-heating of the sensor.

Figure 3 shows the circuit that meets these requirements. The sensor is a DIN-IEC 751 platinum RTD. Microsoft (www.microsoft.com) Excel software fits 13 points of 0 to 600°C in steps of 50° from the RTD's calibration table. The spreadsheet software determined  $R_0$  to have a value of 100Ω,  $\alpha$  to have a value of  $3.908 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$ , and  $\beta$  to have a value of  $-5.801 \times 10^{-7} \text{ } ^\circ\text{C}^{-2}$  with an  $R^2$  factor of one.

All the circuit's resistors have tolerances of 0.02%, and the temperature

coefficient is 50 ppm/°C. You can use two trimming potentiometers,  $V_{R1}$  and  $V_{R2}$ , to independently adjust zero and span readings. You should perform span

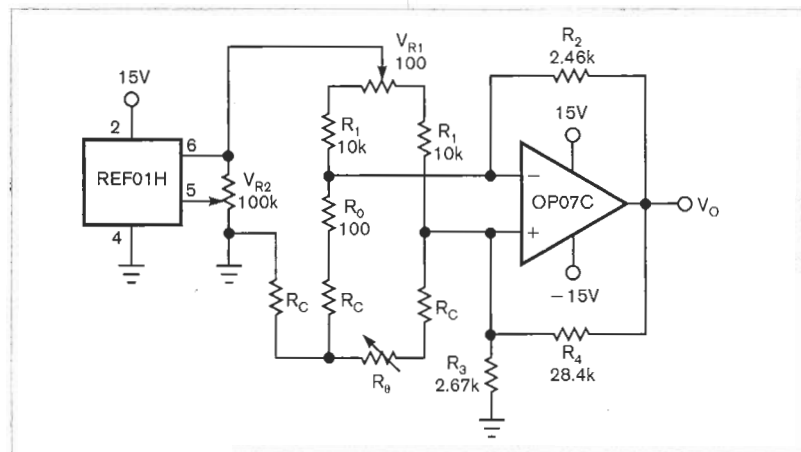


Figure 3 The full circuit needs trimming potentiometers  $V_{R1}$  and  $V_{R2}$  to adjust zero and span, respectively, and a three-lead cable for sensor connection.  $R_C$  is the cable's resistance.

TABLE 1 EXPERIMENTAL RESULTS

Measurement range	-100 to +600°C
Nominal sensitivity	10 mV/°C
Basic accuracy (nonlinearity)	Well below ±1°C
Ambient-temperature effect	0.05°C/10°C
Power-supply effect	0.1°C/V
Cable effect (three-lead connection)	0.7°C/Ω
Power-supply range	±12 to ±18V
Consumption (600°C input)	9 and -3 mA
Operating temperature	-40 to +85°C

adjustment at 550°C to match the magnitudes of the positive and the negative errors. You can also extend the temperature range to start from -100°C instead of 0°C without exceeding the basic nonlinearity. The three-lead connection to the sensor significantly reduces the influence of connection-cable resistance,  $R_C$ , on accuracy.

Table 1 shows the results of evaluating this circuit's performance with a calibrated, precision-decade resistance and a calibrated, 4.5-digit multimeter with readings at ambient temperatures of 24 and 68°C; power supplies of ±12, ±15, and ±18V; and cable resistances of 0 and 5Ω. **EDN**

## REFERENCES

1. Bryant, James, Walt Jung, and Walter Kester, *Op Amp Applications*, Analog Devices, 2002.
2. Villanucci, Robert S, "Design an RTD interface with a spreadsheet," *EDN*, Feb 7, 2008, pg 57, www.edn.com/article/CA6526816.
3. Moghimi, Riza, "Low-error platinum RTD circuit has shutdown capability," *EDN*, Sept 14, 2000, pg 186, www.edn.com/article/CA47186.
4. Gutnikov, VS, *Integrated Electronics in Measuring Devices*, Leningrad, 1980.