

# Build the Muscle Whistler

LISTEN TO YOUR BICEPS DO THEIR THING

BY HARRY GARLAND  
AND ROGER MELEN

There are 656 muscles in the human body and all of them generate a small voltage potential when they are activated. This voltage, called myoelectricity or EMG, is present on the surface of the skin surrounding the muscle. The detection of this signal is important in both clinical medicine and medical research.


Reaction time, for example, can be measured by noting the time lag between a stimulus and the onset of EMG activity. Audible EMG monitoring has been used experimentally in training athletes—it has been hypothesized that athletes can learn complicated, coordinated muscle skills faster by listening to their muscles during training.

The Muscle Whistler, described here, can monitor many of the muscles in the body, producing a whistling tone each time a muscle is activated. Try it, for instance, with the electrodes on the biceps

muscle (upper arm) and lift a heavy object. Signals can also be picked up with the electrodes on the triceps (back of upper arm) when you try to push something. The flexor muscles (on the front of the lower arm) are active when you clench your fist, and the gastrocnemius muscle (in the calf of the lower leg) is active when you stand on your toes. You may be surprised to hear muscle activity even when you think a muscle is relaxed. This is called "muscle tone" and is characteristic of all muscles.

Whether you listen to the Muscle Whistler to monitor the force generated by your muscles, measure your reaction time, or improve your golf swing, this project will provide an entertaining introduction to an important area of medical electronics.

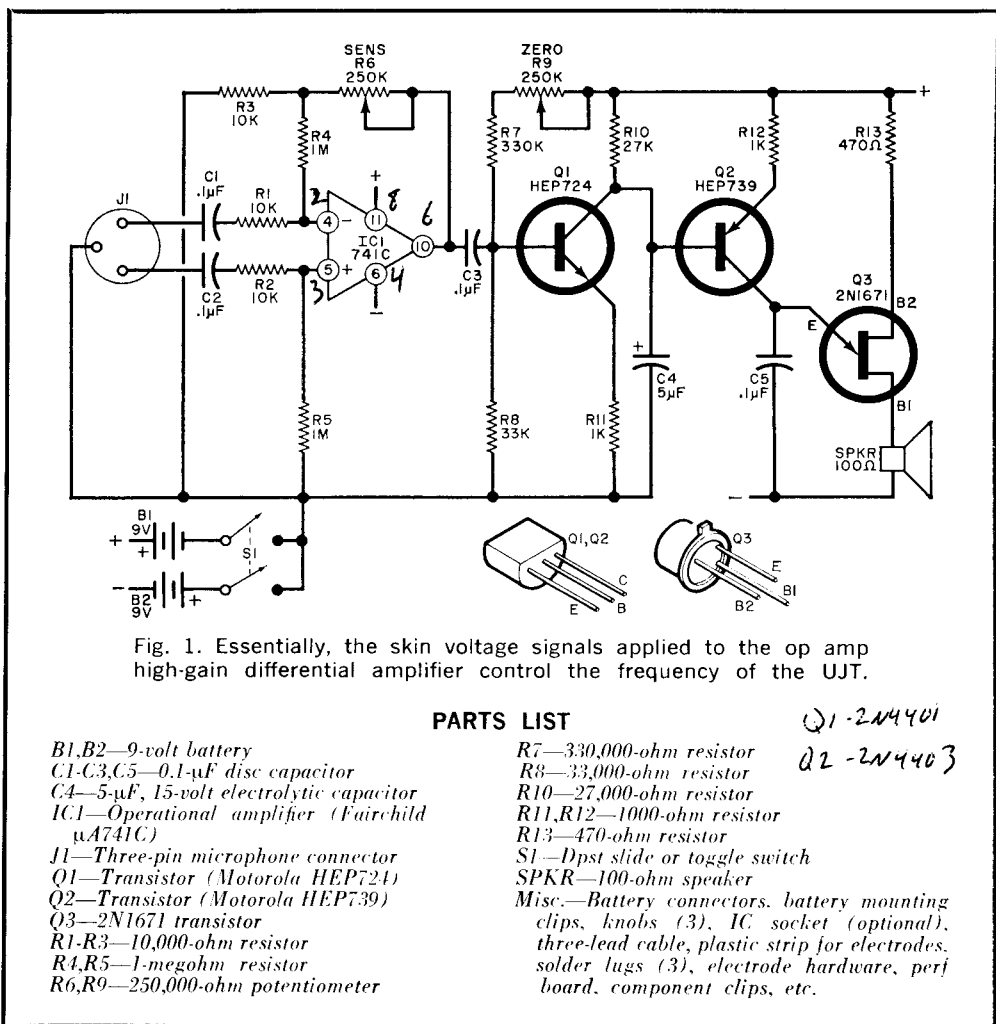**Construction.** The circuit of the Muscle



#### PARTS LIST

B1, B2—9-volt battery  
 C1-C3, C5—0.1- $\mu$ F disc capacitor  
 C4—5- $\mu$ F, 15-volt electrolytic capacitor  
 IC1—Operational amplifier (Fairchild  $\mu$ A741C)  
 J1—Three-pin microphone connector  
 Q1—Transistor (Motorola HEP724)  
 Q2—Transistor (Motorola HEP739)  
 Q3—2N1671 transistor  
 R1-R3—10,000-ohm resistor  
 R4, R5—1-megohm resistor  
 R6, R9—250,000-ohm potentiometer

R7—330,000-ohm resistor  
 R8—33,000-ohm resistor  
 R10—27,000-ohm resistor  
 R11, R12—1000-ohm resistor  
 R13—470-ohm resistor  
 S1—Dpst slide or toggle switch  
 SPKR—100-ohm speaker  
 Misc.—Battery connectors, battery mounting clips, knobs (3), IC socket (optional), three-lead cable, plastic strip for electrodes, solder lugs (3), electrode hardware, perf board, component clips, etc.

Q1-2N4401  
 Q2-2N4403

Whistler is shown in Fig. 1. The prototype was built on a piece of perf board, though any other method may be used. The components are mounted on small clips, except that a 14-pin dual in-line socket may be used for the IC if desired. The input connector (J1), the speaker, the zero and sensitivity potentiometers (R9 and R6, respectively), and the on-off switch (S1) are mounted on the front panel of the selected chassis.

A conventional three-lead microphone jack with an associated three-lead microphone connector and a few feet of three-lead cable are used to connect the muscle electrodes to the circuit.

The electrodes are fashioned from two screws mounted 3 or 4 inches apart on a

narrow piece of plastic as shown in Fig. 2. A third screw midway between the other two forms the ground electrode. Solder lugs under the nuts are used to connect the three color-coded leads from the circuit. The center screw is longer than the other two so that a knob, or some other type of handle, can be attached.

**Operation.** With power applied to the circuit, adjust R9 so that there is no output from the speaker when there is no input signal. The output varies from a whistle down to a series of slow clicks. Adjust R9 until the clicks just stop. With the sensitivity control (R6) turned up  
 (Continued on page 103)

## MUSCLE WHISTLER

(Continued from page 61)

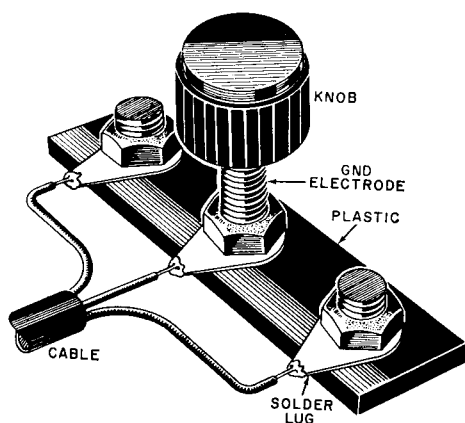


Fig. 2. Electrodes are mounted on a small length of plastic as shown here. An insulated knob on the ground screw acts as the handle.

slightly, touching one of the end electrodes on the muscle probe should cause the circuit to squeal due to imbalance in the operational amplifier circuit. (It is actually pickup from the field created by the 60-Hz power line.) However, when both electrodes are touching the skin, virtually all of this ambient noise is rejected by the differential amplifier.

Good electrical contact must be made between the electrodes and the skin. Use a commercial electrode paste or make your own by mixing salt, water, and flour in a good pasty consistency. The

paste is rubbed into the area of skin where the electrodes are to be applied.

Before the electrodes are placed against the skin, set *R6* partially up and be sure *R9* is adjusted to give no output. Place the electrodes against the skin. There will be a change in the tone of the output. Adjust *R9* just below the oscillation point and adjust *R6* until the output changes frequency as the muscle is activated. Each time the muscle is flexed, the whistle changes frequency—the tenser the muscle, the higher the frequency.


**Theory of Circuit Design.** Operational amplifier *IC1* is a very high gain differential amplifier whose gain (sensitivity) is controlled by feedback potentiometer *R6*. The differential input to the op amp is picked up by the electrodes applied to the skin.

Unijunction transistor *Q3* is wired in the classical UJT oscillator configuration with *C5* determining the frequency and the emitter-collector resistance of *Q2* (with limiting resistor *R12*) acting as the charging resistor. The interelement resistance of *Q2* is a function of the applied base current and the voltage to move this current is stored in capacitor *C4*, which is charged up by amplifier *Q1*. The size of the steady-state charge on *C4* is determined by the setting of *R9*.

When a muscle voltage is amplified by *IC1* and fed to *Q1*, the collector voltage on *Q1* varies, thus changing the charge on *C4*. This, in turn, varies the UJT oscillator frequency. The speaker forms the load for *Q3*, and the audible tone consists of a series of spikes, each occurring as the UJT fires. ♦

## FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.

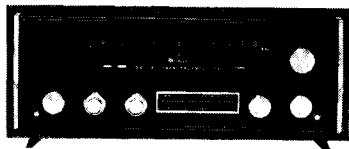

MX 114

FM/FM STEREO TUNER  
and STEREO PREAMPLIFIER

### SEND TODAY!

McIntosh Laboratory Inc.  
2 Chambers St., Dept. PT-1171  
Binghamton, N.Y. 13903

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE NO. 23 ON READER SERVICE PAGE