

emitter follower with current source

In its standard version an emitter follower is provided with an emitter resistor. This resistor and the base potential determine the emitter current I_e of the emitter follower. The gain of the emitter follower is always less than unity, but approaches unity as the product $S \cdot R_e$ is greater. S is the slope, which equals $40 \cdot I_e$. The product $S R_e = 40 I_e R_e$, and thus the gain, corresponds to a certain base potential.

If R_e is replaced by a current source, S can be chosen independently of R_e . The value of R_e is then determined by the load impedance of the emitter follower which is usually much higher than the value required for the DC-setting. It is now possible to obtain a gain closely approaching unity. This is of importance for certain types of active filter.

The circuit has an additional advantage. It can be shown that the distortion of an emitter follower is inversely proportional to the square of the emitter impedance R_e . As already said, R_e is much higher than usual when a current source is used. Hence distortion, too, is much less than usual. At the indicated value of R_e the emitter current is about 2 mA. Reduction of R_3 involves a proportional increase in emitter current.

