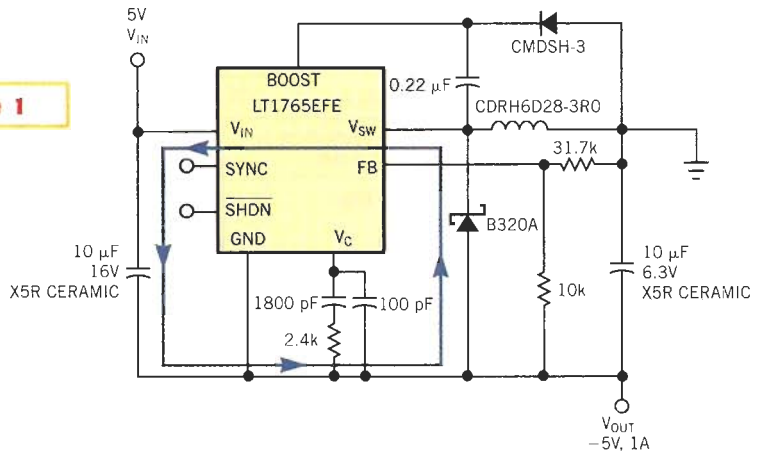


# Lower dc/dc-converter ripple by using optimum capacitor hookup

Keith Szolusha, Linear Technology Corp, Milpitas, CA

**L**OW-RIPPLE-VOLTAGE positive-to-negative dc/dc converters find use in many of today's high-frequency and noise-sensitive disk drives, battery-powered devices, portable computers, and automotive applications. Like a positive buck converter, a positive-to-negative converter can have low output-ripple voltage if you place the bulk input capacitor between  $V_{IN}$  and  $V_{OUT}$  rather than between  $V_{IN}$  and ground. A common misconception is that positive-to-negative converters in the first configuration have noisy outputs. This configuration actually solves noise problems rather than introducing them. In either configuration, the  $V_{IN}$  and ground pins of the IC connect to  $V_{IN}$  and  $V_{OUT}$ , respectively (figures 1 and 2). Therefore,

Figure 1



This +5-to- $-5V$  converter with the bulk input capacitor between  $V_{IN}$  and  $V_{OUT}$  has low output ripple. The high-di/dt path, indicated here with blue lines, does not include the output capacitor.