



the count-up interval must be greater than that encountered during the count-down time.

If the period between  $A_1$ 's toggling times, and thus the measuring cycle  $t = (T_1 + T_2)$ , are small, then the derivative of the input wave,  $f'(t)$ , may be assumed to be constant over the measuring cycle, and  $f'(t) = K$ . Therefore the change in the average frequency with respect to time  $t$  is:

$$\frac{f_u - f_d}{t} \rightarrow f'(t) = K \quad (2)$$

Substituting for  $f_u - f_d$  in Eq. 1 yields:

$$R = KT_1 t \quad (3)$$

where  $R$  now represents acceleration and  $T_1$  and  $t$  are known constants.

If the change in  $f(t)$  is negative (deceleration), the

number of pulses received during the first (down) counting interval will be greater than that received during the next (up) counting time. Hence, neither a carry nor a borrow pulse will appear at  $A_2$ , and  $A_5$  is not triggered. Therefore  $G_4$  is disabled,  $G_5$  is enabled, and  $A_3$  is triggered at the end of every other  $T_1$  period.

The end result of this operation is that  $A_2$  first counts up during the initial  $T_1$  period and down for the second  $T_1$  period, at the end of which time the  $Q$  output of  $A_1$  moves low and the next measuring cycle starts. Thus the latched output of  $A_2$  is still given by Eq. 3, where  $K$  now represents the rate of decrease of  $f(t)$ . The state of the retriggered  $A_5$  indicates whether  $f(t)$  is accelerating or decelerating ( $Q = 1$  or  $Q = 0$ , respectively).  $\square$

---

Engineer's notebook is a regular feature in *Electronics*. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.