

# designideas

READERS SOLVE DESIGN PROBLEMS

## Two-channel audio amplifier drives stepper motor

Phill Leyva and Bill Quach, Maxim Integrated Products, Sunnyvale, CA

Although relatively expensive, monofilar-wound, bipolar stepper motors provide strong torque for a given physical size. However, each of the motor's two windings requires eight driving transistors connected in groups of four in an H-bridge configuration. Each transistor must withstand and quickly recover from overloads and short-circuit conditions, and a driver must consequently include complex and large discrete-component protective circuitry.

As an alternative, **Figure 1** shows a motor-driver circuit based on Maxim's ([www.maxim-ic.com](http://www.maxim-ic.com)) MAX9715, a tiny, surface-mount, 2.8W Class D audio amplifier, which typically drives 4 or 8Ω speakers. Each of IC<sub>1</sub>'s two outputs consists of a MOSFET H-bridge that drives a pair of output lines, OUTR+ and OUTR- and OUTL+ and OUTL-, that connect to the stepper motor's A and B windings, respectively. Each pair delivers a differential-pulse-width-modulated signal

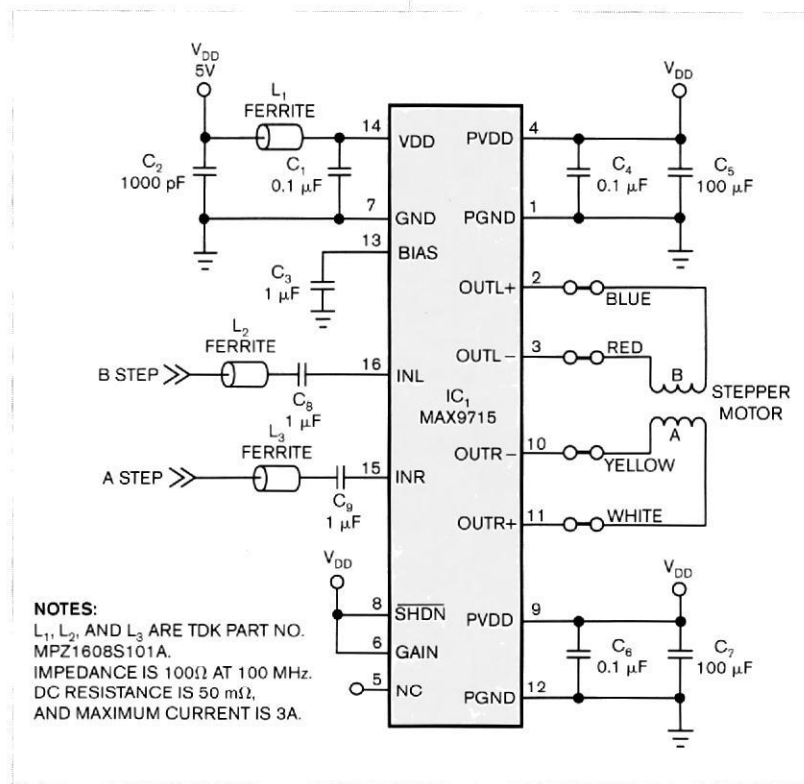


Figure 1 A single surface-mount circuit and a few passive components can drive a bipolar, monofilar-wound stepper motor.

### DI's Inside

98 Get power from a telephone line without disturbing it

100 Active-filter circuit and oscilloscope inspect a Class D amplifier's output

102 Voltage-to-pulse-width converter spares microprocessor's resources

104 Precision voltage reference delivers 80 mA

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to [edndesignideas@reedbusiness.com](mailto:edndesignideas@reedbusiness.com).

with a nominal switching frequency of 1.22 MHz. The circuit's low-interference design eliminates the requirement for output-line filters.

Capacitors C<sub>1</sub>, C<sub>3</sub>, C<sub>4</sub>, and C<sub>6</sub> provide bypassing for IC<sub>1</sub>'s power input and bias pins, and C<sub>5</sub> and C<sub>7</sub> provide bulk-holdup capacitance for the Class D power amplifiers' outputs. Capacitors C<sub>8</sub> and C<sub>9</sub> limit the amplifiers' input bandwidth to 16 Hz, and L<sub>2</sub> and L<sub>3</sub> suppress electrical-noise pickup by the long input cables. Comprising C<sub>1</sub>, C<sub>2</sub>, and ferrite bead L<sub>1</sub>, a pi-section noise filter suppresses noise on IC<sub>1</sub>'s power-sup-

TABLE 1 A\_STEP AND B\_STEP PULSE SEQUENCE

Step	A_Step	B_Step
0	H	L
1	L	L
2	L	H
3	H	H
4	H	L

ply input. A suitable controller feeds digital pulses to IC<sub>1</sub>'s A\_Step and B\_Step inputs, which respectively drive the motor's right and left channels. Internal short-circuit and thermal protection guards the amplifier against overcurrent and short circuits caused by the stepper motor or its connecting leads.

Table 1 illustrates the A\_Step and B\_Step pulse sequence that rotates a typical stepper motor in one direction by continuous application of steps 0 through 4. Step 4 returns the motor's shaft to its starting position and completes its 360° rotation. To reverse the motor, begin at the bottom of the table to reverse the pulse pattern and work upward. You can disable both of the amplifier's channels by applying a logic-low signal to Pin 8, IC<sub>1</sub>'s active-low SHDN input. Figure 2 illustrates the circuit's input and output waveforms. EDN

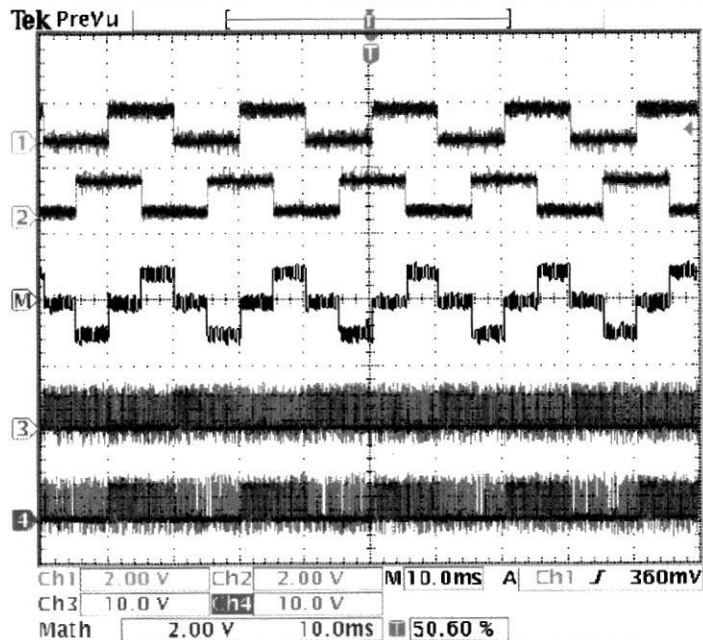


Figure 2 Waveforms from the circuit in Figure 1 include the A\_Step input (Channel 1), B\_Step input (Channel 2), outputs OTR+ (Channel 3) and OTR- (Channel 4), and the signal that arrives at the motor's windings (OTR+ minus OTR-, middle trace), which the oscilloscope's math function computes.