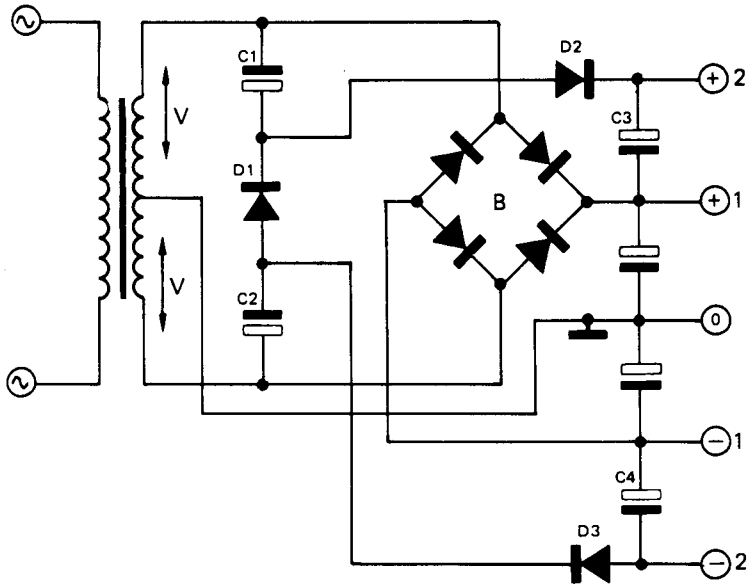


**99** Besides the set of symmetrical supply voltages ( $\pm 1$  in the figure), it is often handy to have available a second set of symmetrical supply voltages ( $\pm 2$  in the figure). These voltages are higher than the  $\pm 1$  voltages, and can supply only a relatively low current. With this circuit it is possible to obtain these auxiliary voltages from the same transformer windings as used for the main voltages.

The circuit operates as a symmetrical voltage doubler. Suppose the secondary of the transformer gives  $2 \times V$  volts rms and that the diode threshold voltages are



9642

neglected. Then the voltages  $\pm 1$  are equal to  $\pm V \times \sqrt{2}$ . Capacitor C3 is charged from C1 via D2 during one half cycle; during the next half cycle C4 is charged from C2 via D3. Consequently the points  $\pm 2$  carry a voltage of  $\pm 2 V \times \sqrt{2}$  relative to supply common. For the practical circuit IN4000 series diodes can be used for D1, D2 and D3. The values of C1, C2 and C3 are 100 to 470  $\mu\text{F}$  with a maximum voltage rating of at least  $V \times \sqrt{2}$  volts.