

Get Low-Noise, Low-Ripple, High-PSRR Power with a Linear Regulator

By Jeff Falin, Senior Applications Engineer

Introduction

Audio circuitry, PLLs, RF transceivers, and DACs are just a few examples of devices that can be sensitive to noise and therefore may not operate properly when powered from a switching power supply. Linear regulators are ideal for powering these circuits. This abbreviated article explores design factors required to achieve a high power-supply rejection ratio (PSRR) over a wide bandwidth with very low noise and quiescent current.

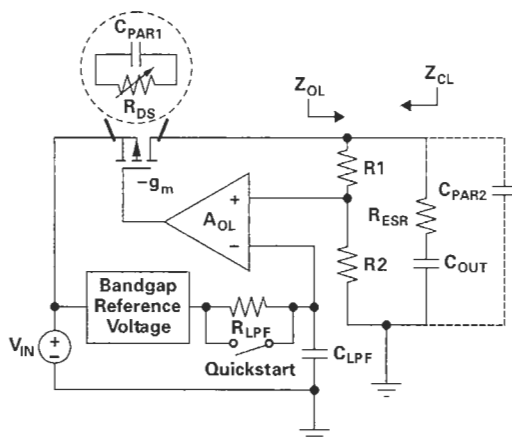


Figure 1. Simplified block diagram of a linear regulator


Figure 1 shows a simplified block diagram of a linear regulator using a p-channel MOSFET (pFET) as a pass element. A_{OL} is the open-loop gain of the error amplifier, and g_m is the pass-element transconductance. The error amplifier controls the voltage at the gate of the pass element so that the current through the FET keeps the output voltage regulated relative to the internal reference voltage. Assuming that the low-pass filter (LPF) formed by R_{LPF} and C_{LPF} eliminates nearly all internal-reference noise, the output voltage should be ripple- and noise-free for frequencies within the bandwidth of the regulator's control loop.

What is the PSRR?

The PSRR is a measure of a circuit's PSR expressed as a ratio of output noise to noise at the power-supply input. It provides a measure of how well a circuit rejects ripple at various frequencies injected from its input power supply. In the case of linear regulators, PSRR is a measure of the

Featured in the latest online issue

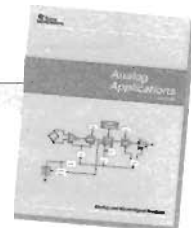- Using a touch-screen controller's auxiliary inputs
- Driving a WLED does not always require 4 V
- Host-side gas-gauge-system design considerations for single-cell handheld applications
- Using a buck converter in an inverting buck-boost topology
- Download your copy now at www.ti.com/aa



regulated output-voltage ripple compared to the input-voltage ripple over a wide frequency range and is expressed in decibels (dB). If the pass element in Figure 1 is treated as a variable resistance, R_{DS} , and the error amplifier and bandgap reference are assumed to have been designed to minimize pass-through of the input-voltage ripple, then the PSR is simply a voltage divider, expressed as

$$PSR = \frac{Z_{OL} \parallel Z_{CL}}{Z_{OL} \parallel Z_{CL} + R_{DS}}$$

In this equation, Z_{OL} is the output impedance at the regulator's output, ignoring the effect of the regulator's feedback loop:

$$Z_{OL} = (Z_{COUT} + R_{ESR}) \parallel (R1 + R2) \parallel C_{PAR2}$$

where Z_{COUT} and R_{ESR} are the output capacitor's impedance and equivalent series resistance (ESR), respectively, and C_{PAR2} is the parasitic capacitance of the output components and PCB. Z_{CL} is the impedance looking back into the output of the regulator, including the effect of the regulator's feedback loop:

$$Z_{CL} = \frac{Z_{OL} \parallel R_{DS} \parallel C_{PAR1}}{g_m \times A_{OL} \times f \times \beta}$$

where C_{PAR1} is the passive-element parasitic capacitance, f is the ripple frequency, and β is the feedback factor,

$$\beta = \frac{R2}{R1 + R2}$$

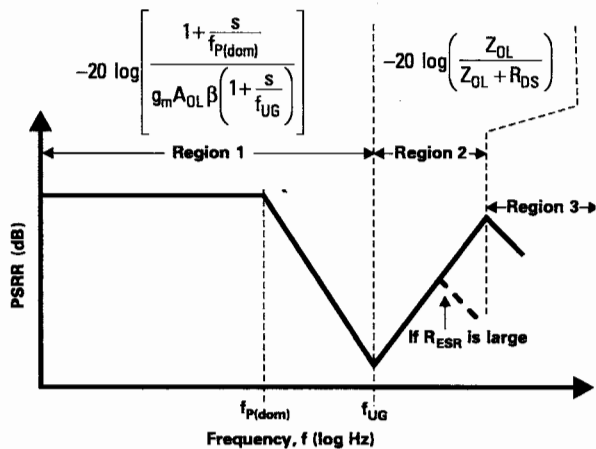


Figure 2. PSRR graph

Figure 2 shows the general shape of a PSRR curve, where $f_{P(dom)}$ is the dominant pole and f_{UG} is the unity-gain bandwidth. If the error amplifier is compensated to have a single-pole response, then the Region 1 PSR for amplifier frequencies below f_{UG} can be approximated by the equation on the left side of the graph. Designing the regulator with a high-gain, wide-bandwidth error amplifier can therefore provide high PSR over a wide range of frequencies. In Region 2, above the control-loop bandwidth, the regulator is no longer effective at providing PSR, so the PSRR reduces to a simple voltage divider as shown on the right side of the curve. As Z_{COUT} decreases relative to R_{DS} , the PSR provided by the passive components on the board increases. If C_{OUT} has high R_{ESR} , the PSR peaks sooner. In Region 3, the IC and board parasitic capacitances (C_{PAR1} and C_{PAR2}) dominate, resulting in a capacitive voltage divider, which typically causes the PSR to decrease again.

Maximizing PSR

The TPS717xx family of regulators has incorporated circuit techniques to provide high PSR over a wide frequency range. An example of the PSRR is shown in Figure 3.

With the simple model previously explained, it can be shown that the TPS717xx's dominant pole with $C_{OUT} = 1 \mu F$ is at approximately 20 to 30 kHz and the unity-gain frequency is near 400 kHz. Since PSR is a function of the open-loop gain, as the gain varies so will the PSR in Regions 1 and 2 of Figure 2. Figure 3 shows the TPS717xx's PSRR varying with load current. As load current increases, R_{DS} decreases; therefore Z_{CL} decreases, since a MOSFET's output impedance is inversely proportional to its drain current. In many regulators, where $f_{P(dom)}$ varies with Z_{CL} , increasing the load current also pushes $f_{P(dom)}$ to higher frequencies, which increases the feedback-loop bandwidth. As shown in Figure 3, the net effect of increasing the load current is reduced PSRR.

The differential DC voltage between input and output also affects PSR. As $V_{IN} - V_{OUT}$ is lowered, the pFET (which provides gain) is driven out of the active (saturation) region of operation and into the triode/linear region, which causes the feedback loop to lose gain. Therefore, the PSR of the regulator decreases as V_{IN} approaches V_{OUT} . The lowest

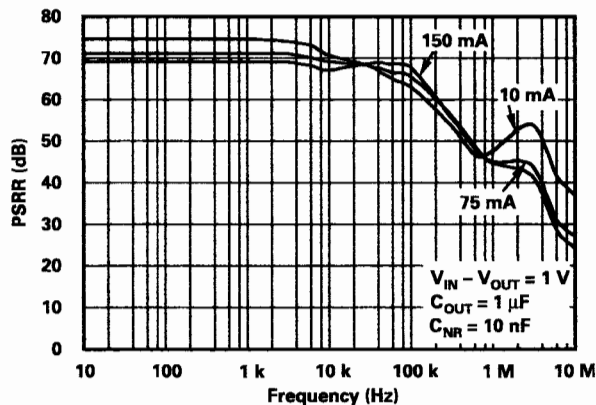


Figure 3. TPS717xx PSRR graph

PSR, approaching 0 dB, occurs when the device is in dropout ($V_{IN} = V_{OUT}$). In this situation, the RC filter formed by the linear regulator's pass-element R_{DS} and output capacitor determines PSR.

Low Noise

Noise is generated by the transistors and resistors in the regulator's internal circuitry as well as by the external feedback resistors. Transistors generate shot noise and flicker noise, both of which are directly proportional to current flow. Flicker noise is indirectly proportional to frequency and so is higher at low frequencies. The resistive element of MOSFETs also generates thermal noise like resistors. Thermal noise is directly proportional to temperature, the resistor's resistance value, and the current flow through the transistors. Transistors and resistors closest to the error-amplifier inputs cause the most output noise because their noise is amplified by the regulator's closed-loop gain ($A_{CL} = V_{OUT}/V_{Bandgap} = 1/\beta = 1 + R1/R2$). The noise contribution from components later in the signal path is insignificant when compared to the noise at the error-amplifier inputs. In fact, when modest-sized feedback resistors are used, most of the regulator's noise comes from the amplified bandgap reference. As shown in Figure 1, the simplest way to reduce the bandgap noise is to use a low-pass filter (LPF) consisting of an internal resistor, R_{LPF} , and an external capacitor, C_{LPF} . At startup, this filter would slow down the output-voltage rise without the aid of the "quickstart" transistor. When the quickstart transistor is used, it shorts out the R_{LPF} for a short time at startup so the regulator output can rise quickly.

Conclusion

Linear regulators like the TPS717xx are ideal for providing a low-ripple, low-noise power rail to sensitive analog circuitry. These linear regulators consume very little quiescent current when powered and even less when shut down.

Please see Reference 1 for the complete version of this article, which discusses spectral noise density, component selection, and board layout.

Reference

1. View the complete article at <http://www-s.ti.com/sc/techlit/slyt280>