 


# Section 7.0 Application Circuits & Description Information

...ed for from a  
ector is needed  
use 0.1 μF. ca



High Voltage Short Circuit Protected Regulator

V<sub>IN</sub> = 40V DC

\*\*\*Solid tantalum  
\*\*\*Heat sink Q2  
\*\*\*Since the 100V

## 7.0 APPLICATIONS

Voltage regulator use can be expanded beyond that of the simple three-terminal fixed voltage regulator. Some of the circuits which are practical and useful are described in this section. Pertinent equations are included rather than providing fixed component values as the circuits are equally applicable to all regulators within a family.

### 7.1 POSITIVE REGULATORS

#### 7.1.1 Basic Regulator

 


FIGURE 7.1. Basic Regulator Connection

Normal connections are indicated in Figure 7.1. If the regulator is located more than two inches from the supply filter capacitor, a supply bypass capacitor is required to maintain stability (much as is the case with op-amps). This should be a 0.22  $\mu\text{F}$  or larger disc ceramic, 2  $\mu\text{F}$  or larger solid tantalum, or 25  $\mu\text{F}$  or larger aluminum electrolytic capacitor (the LM120 and LM123 series require the solid tantalum or aluminum electrolytics). Progressively larger values are required of ceramic, solid tantalum and aluminum electrolytic capacitors because the effective series resistance ESR increases respectively in each type capacitor. The LM120 series alone of all the group requires an output capacitor to insure stable operation. The others are stable when operating into a resistive load. The LM120 output capacitor should be a 1  $\mu\text{F}$  or larger solid tantalum or 25  $\mu\text{F}$  or larger aluminum electrolytic. Transient response of all the regulators is improved when output capacitors are added. To minimize high-frequency noise, a 0.01  $\mu\text{F}$  output capacitor is recommended on the LM78LXX and LM140L series.

#### 7.1.2 Current Source

 


FIGURE 7.2. Current Source

A constant output current  $I_L$  is delivered to a variable load impedance  $Z_L$ .

$$I_L = \frac{V_{REG}}{R} + I_Q \quad (7.1)$$

$$\text{for } 0 \leq Z_L \leq \frac{V_{IN} - (V_{REG} + V_{dropout})}{I_L}$$

The output impedance is:

$$Z_O = \frac{\Delta V_O}{\Delta I_L} = \frac{1}{\frac{\Delta I_Q}{\Delta V_{IN}} + \frac{L'_r}{R}} \quad (7.2)$$

where:  $\frac{\Delta I_Q}{\Delta V_{IN}}$  = quiescent current change per volt of input voltage change of the regulator

$L'_r = \frac{\Delta V_O}{\Delta V_{IN}}$  = line regulation, the change in regulator output per volt of input voltage change at a given  $I_O$

#### 7.1.3 High Current Regulator

 


FIGURE 7.3. High Current Regulator with Short Circuit Limit During Output Shorts

This current boost circuit takes advantage of the internal current limiting characteristics of the regulator to provide short-circuit current protection for the booster as well. The regulator and  $Q_1$  share load current in the ratio set between  $R_2$  and  $R_1$  if  $V_D = V_{BE}(Q_1)$ .

$$I_1 = \frac{R_2}{R_1} I_{REG} \quad (7.3)$$

During output shorts

$$I_{1(SC)} = \frac{R_2}{R_1} I_{REG(SC)} \quad (7.4)$$

If the regulator and  $Q_1$  have the same thermal resistance  $\theta_{JC}$  and the pass transistor heat sink has  $R_2/R_1$  times the capacity of the regulator heat sink, the thermal protection (shutdown) of the regulator will also be extended to  $Q_1$ . Some suggested transistors are listed below.

$Q_1$	D	$I_1$	$I_{REG}$	$R_2/R_1$	$R_3$
2N4398	IN4719	$\geq 3$ A	1 A	$\geq 3$	5 - 10 $\Omega$
NSD32	IN4719	2 A	1 A	2	5 - 10 $\Omega$
NSDU51A	IN4003	1 A	0.5 A	2	5 - 10 $\Omega$

 


FIGURE 7.4. Equivalent of Power PNP Transistor

The minimum input-to-output voltage differential of the regulator circuit is increased by a diode drop plus the  $V_{R1}$  drop. For high current applications a low priced PNP/NPN combination may be used to replace the expensive single PNP 2N4398 as illustrated in Figure 7.4.

### 7.1.4 Adjustable Output Voltage

 


FIGURE 7.5. Adjustable  $V_{OUT}$

A fraction of the regulator current  $V_{REG}/R_1$  is used to raise the ground pin of the regulator and provide, through voltage drop across  $R_2$ , an adjustable output voltage.

$$V_O = V_{REG} + R_2(I_Q + \frac{V_{REG}}{R_1}) \quad (7.5)$$

Line regulation is

$$\frac{\Delta V_O}{\Delta V_{IN}} = (L'_r) \left( \frac{R_1 + R_2}{R_1} \right) + \left( \frac{\Delta I_Q}{\Delta V_{IN}} \right) R_2 \quad (7.6)$$

Load regulation is


$$\frac{\Delta V_O}{\Delta I_L} = (L_r) \left( \frac{R_1 + R_2}{R_1} \right) + \left( \frac{\Delta I_Q}{\Delta I_O} \right) R_2 \quad (7.7)$$

where:  $L_r = \frac{\Delta V_O}{\Delta I_O}$ , the regulator load regulation per amp of load change

$\frac{\Delta I_Q}{\Delta I_O}$  = quiescent current change per amp of load current change

$\frac{\Delta I_Q}{\Delta V_{IN}}$  = quiescent current change per volt of input voltage change

### 7.1.5 Variable Output Voltage

 

\* Required if the regulator far from power supply filter  
\*\* Solid tantalum

FIGURE 7.6. Variable Output Regulator

The ground terminal of the regulator is raised above common by an amount equal to the voltage applied at the non-inverting input of the op-amp. For  $I \gg I_B$ , the output voltage is:

$$V_O = \left( \frac{R_1 + R_2 + R_3}{R_1} \right) V_{REG} \quad (7.8)$$

The minimum output voltage will be determined by the  $V_{REG}$  and  $V_{B(MIN)}$ , where  $V_{B(MIN)}$  is the op-amp common-mode voltage lower limit ( $\approx 2$  V for LM301A used with single supply).

$$V_{O(MIN)} = V_{REG} + V_{B(MIN)} \quad (7.9)$$

$$\text{when } R_2 = 0, \quad \frac{R_3}{R_1} = \frac{V_{B(MIN)}}{V_{REG}} \quad (7.10a)$$

$$V_{O(MAX)} = \quad (7.10b)$$

$$\left( \frac{R_1 + R_2(MAX) + R_3}{R_1} \right) V_{REG} = V_{IN} - V_{dropout}$$

To choose  $R_1$ ,  $R_2$ ,  $R_3$  for a specified  $V_{IN}$ , start with an arbitrary value for  $R_1$ . Determine  $R_2$  and  $R_3$  from Eqn 7.10 and finally check to insure that

$$\frac{V_{O(MIN)}}{R_1 + R_3} \gg I_B, \quad \frac{V_{O(MAX)}}{R_1 + R_2 + R_3} \gg I_B$$

Example:  $V_{IN} = 25$  V LM341P-05

$V_O = 7.23$  V  $R_1 = 3$  K

$R_2 = 10$  K

$R_3 = 1.2$  K

The load and line regulation can be determined by:

$$\frac{\Delta V_O}{\Delta V_{IN}} = (L'_r) \left( \frac{R_1 + R_2 + R_3}{R_1} \right) \quad (7.11)$$

$$\frac{\Delta V_O}{\Delta I_L} = (L_r) \left( \frac{R_1 + R_2 + R_3}{R_1} \right) \quad (7.12)$$

The  $\Delta I_Q$  factor (see previous paragraph) is neglected because the op-amp output impedance is very low.

### 7.1.6 Variable Output Voltage with $V_{O(MIN)} \approx 0$

 


FIGURE 7.7. Variable Output Voltage of 0.5 - 28 V

A wide range of output voltages can be obtained with the circuit of Figure 7.7. A 0- to 20-volt supply can be built using a -7-volt supply and a conventional op-amp. For higher output voltages, a high-voltage op-amp, such as LM143, is required. If

$$R_2 + R_3 = R_4 + R_5 = R, \quad \text{and} \quad R_2/R_3 = 1/10,$$

$$\text{then } V_O = V_{REG} \left( \frac{R_2}{R_4} \right) = V_{REG} \left( \frac{1}{11} \right) \left( \frac{R_4 + R_5}{R_4} \right) \quad (7.13)$$

Since  $V_O$  is inversely proportional to  $R_4$ , low output voltages can be very accurately set. The required  $R_1$  is

$$R_1 = \frac{V_{IN}^-}{I_Q}$$

The  $V_{O(MAX)}$  is dependent on  $V_{IN}$  and  $V_{dropout}$ , provided that the amplifier can source the current required to raise  $V_G$  to  $V_O - V_{REG}$ .

Example:

$V_{IN}^- = -15 \text{ V}$	$R_1 = 2.1 \text{ K}$
$V_{IN}^+ = +30 \text{ V}$	$R_2 = 910 \text{ } \Omega$
$V_O = 0.5\text{-}28 \text{ V}$	$R_3 = 9.1 \text{ K}$
LM340K-05	$R_4 + R_5 = 10 \text{ K}$

### 7.1.7 High Input Voltage

 


FIGURE 7.8. High Input Voltage

For input voltages higher than  $V_{IN(MAX)}$  as specified for the regulator, a transistor/low-power zener combination can be used (instead of an expensive power zener) to reduce the input voltage seen by the regulator. Transistor Q conducts full load current, and therefore requires a power device with adequate heat sink.

Example: In Figure 7.8b

$$V_{IN} = 48 \text{ V} \quad \text{LM341P-15}$$

$$I_L = 400 \text{ mA} \quad Z = 1\text{N}4745 \text{ (16 V)}$$

Q would dissipate 7 W, therefore use an NSD31 power transistor. For higher dissipation, use a 2N3055.

### 7.1.8 High Output Voltage

 


FIGURE 7.9. High-Voltage Regulator

With the circuit of Figure 7.6, one can obtain high output voltages if a high-voltage op-amp is used (LM343). Another approach is to raise the ground terminal with a zener diode as illustrated in Figure 7.9. Transistor Q and  $Z_2$  set  $V_{IN} \approx V_{Z2} + V_{Z1} - 1 \text{ V}$ .  $D_3$  aids full load start-up and also holds  $V_G$  to a diode drop above ground during short circuits, thus protecting the regulator from high input-to-output voltage differentials.

Example:

LM340T-24	$Z_1 = 1\text{N}5359 \text{ (24 V)}$
$V_{IN} = 80 \text{ V}$	$Z_2 = 1\text{N}5365 \text{ (36 V)}$
$V_O = 48 \text{ V}$	$Q = 2\text{N}3055$
$R = 600 \text{ } \Omega$	

Under short-circuit conditions,  $V_{IN}$  reduces to 35 V.

Figure 7.10 illustrates another circuit for a high-voltage regulator with better input voltage limiting under short circuit conditions. In normal operation,  $Q_2$  is OFF and  $Q_1$  conducts full load current.  $Q_2$  saturates when the output is shorted, thus dropping the voltage at  $Q_1$  base and limiting regulator  $V_{IN}$  to a low value.  $D_1$  (1N914) protects  $Q_2$  from base-emitter breakdown. If an output capacitor is used,  $D_2$  protects the regulator from  $V_{IN}$

 


FIGURE 7.10. High-Voltage Regulator


shorts which would temporarily reverse  $V_{IN} - V_O$  polarity. A large input capacitor  $C_1$  should be included in the circuit to insure that  $V_G$  will rise along with  $V_{IN}$  at turn-on. Since  $Q_1$  does not switch OFF under short-circuit load, it must be a power device with heat sink adequate to handle the short circuit dissipation.

**Example:** LM340T-24

$Z_1 = 1N5359$  (24 V)  $R_1 = 300 \Omega$ , 10 W  
 $V_{IN} = 60$  V  $Q_1 = 2N3055$   $R_2 = 60 \Omega$ , 4 W  
 $V_O = 48$  V  $Q_2 = 2N3643$   $R_3 = 1500 \Omega$ , 4 W

Under short circuit conditions  $V'_{IN}$  reduces to 9 V.

### 7.1.9 Electronic Shutdown

 

\* Required if regulator far from power supply filter


**FIGURE 7.11. Electronic Shutdown Circuit**

Electronic shutdown in three-terminal regulators is done by simply opening the input circuit using a transistor switch.  $Q_1$  operates as the switch which is driven by  $Q_2$ . The control voltage  $V_C$  can be TTL compatible with the use of  $R_3 = 1K$ .  $R_1$  is a biasing resistor, and  $R_2$  can be calculated as

$$R_2 = \frac{V_{IN} - 1V}{I_O} \beta_{SAT}(Q1) \quad (7.14)$$

Figure 7.12 illustrates a short-circuit dependent power shutdown circuit with reduced heat sink requirements under short-circuit conditions.

When the power is first applied,  $Q_2$  turns ON and saturates  $Q_1$ . The regulator output ramps up to turn  $Q_3$  ON, which turns  $Q_2$  OFF ( $V_C$  should be  $> V_A$ ), thus maintaining  $Q_1$  in the ON state.

 


**FIGURE 7.12. Output Dependent Electronic Shutdown on High Voltage Regulator**

When the output is shorted,  $Q_3$  turns OFF,  $Q_4$  turns ON to clamp  $Q_2$  OFF.  $Q_1$  loses base drive and so opens to isolate the regulator from  $V_{IN}$ . When the short circuit is removed,  $Q_4$  loses some base drive and enables  $Q_2$  to re-start the regulator.  $Q_1$  always operates as a switch and needs no heat sinking.  $Q_2$  and  $Q_3$  need not be matched.  $Q_4$  may be any small signal PNP transistor. The entire circuit (less regulator) fits easily on a one-inch square PC board.

**Example:** LM340K-24

$V_{IN} = 36$  V  $Q_1 = TIP32$   $R_1 = 500 \Omega$   
 $V_O = 24$  V  $Q_2 = 2N4141$   $R_2 = 250 \Omega$ , 2 W  
 $I_O = 1$  A  $Q_3 = 2N4141$   $R_3 = 3300 \Omega$   
 $V_A = 2.5$  V  $Q_4 = 2N2906$   $R_4 = 240 \Omega$   
 $V_B = 8$  V  $R_5 = 62 \Omega$   
 $V_C = 4.8$  V  $R_6 = 2K$   
 $R_7 = 1K$   
 $R_8 = 680 \Omega$   
 $R_9 = 3.3K$

### 7.1.10 Switching Regulator

 

$$\text{Ripple} \approx V_{IN} \frac{R_2}{R_1 + R_2}$$

**FIGURE 7.13. Switching Regulator**

A switching power supply may be constructed with a three-terminal regulator, as shown in Figure 7.13. Since no reference pin is available, the positive feedback loop ( $R_1$ ,  $R_2$ ) will be connected to the ground terminal. With the supply ON, the load draws current through the regulator, which turns ON  $Q_1$  and applies power to the inductor. As the current through  $L$  increases, the regulator supplies less and less current to the load and finally turns  $Q_1$  OFF. See National Semiconductor Application Note AN-2 for further design information on switching regulator design. To optimize the efficiency of the regulator, any DC current through  $R_E$  should be minimized. This is done by appropriate choice of  $R_E$ , that is:

$$I_{RE} + I_b = \frac{V_{BE}(SAT)}{R_E} + I_b \approx \frac{V_{IN} - V_O}{2L} t_{on} \quad (7.15)$$

Capacitor  $C_3$  improves the waveform at node G to minimize ripple.

Example: LM341P05 (less heat sink)

$V_O = 5\text{ V}$	$f = 37\text{ kHz}$	$R_2 = 1\ \Omega$
$V_{IN} = 10\text{ V}$	$L = 500\ \mu\text{H}$	$R_E = 10\ \Omega$
$I_O = 300\text{ mA}$	$t_{on} = t_{off}$	$C_2 = 100\ \mu\text{F}$
	$n = 80\%$	$C_3 = 0.1\ \mu\text{F}$
	$Q = 2\text{N2905A}$	$R_1 = 500\ \Omega$
	$D = 1\text{N5807}$	

## 7.2 NEGATIVE REGULATORS

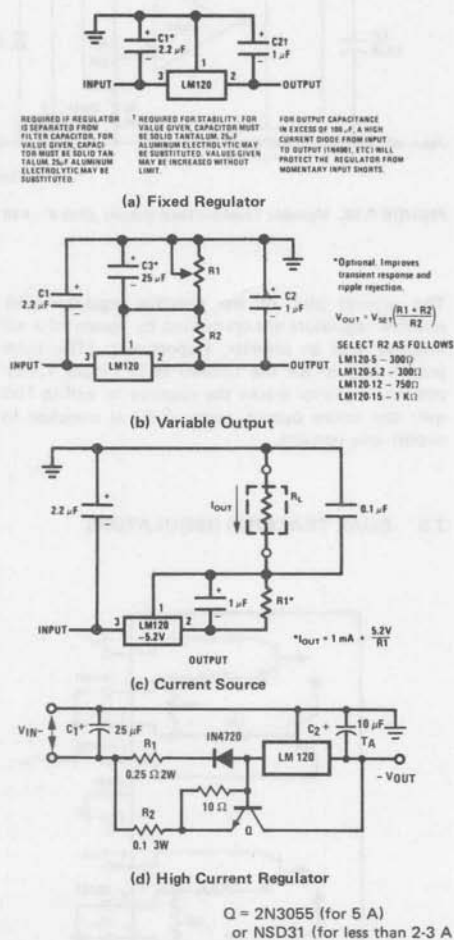


FIGURE 7.14. Negative Regulator Circuits

All the applications circuits for positive regulators can be used with the polarities inverted for the negative regulator LM320/345 series (e.g., reverse the sense of the diodes, replace PNP's with NPN's etc., etc.), as shown in Figure 7.14.

### 7.2.1 Basic Dual Power Supply

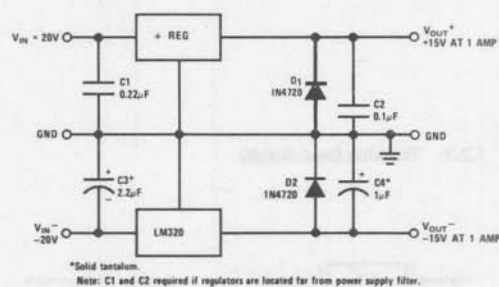


FIGURE 7.15. Dual Power Supply

A positive regulator can be connected with an LM320 to form a non-tracking dual power supply. Each regulator exhibits line and load regulation consistent with their specifications as individual devices. Protective diodes  $D_1, D_2$  allow the regulators to start under common load. They should be rated at the regulator short circuit current.

Examples:

- $\pm 15\text{ V}$  supply, 1 A common load:  
LM340T-15, LM320T-15,  $D_1, D_2$ : IN4720.
- $\pm 12\text{ V}$  supply, 1 A common load:  
LM340T-12, LM320T-12,  $D_1, D_2$ : IN4720.
- $\pm 15\text{ V}$  supply, 200 mA common load:  
LM342H-15, LM320H-15,  $D_1, D_2$ : IN4001.

### 7.2.2 Trimmed Dual Supply

Figure 7.15 may be modified to obtain a dual supply trimmed to a closer output tolerance. The trimming potentiometers are connected across the outputs so positive or negative trimming currents are available to set the voltage across the  $R_1 (R_2)$  resistors.  $R_3, R_5$  are included to linearize the adjustment and to prevent shorting the regulator ground pin to opposite polarity output voltages.

 


FIGURE 7.16. Trimmed Dual Supply

### 7.2.3 Tracking Dual Supply

 


FIGURE 7.17. Tracking Dual Supply

A tracking dual supply can be built as in Figure 7.17 where the positive regulator tracks the negative regulator.  $V_A$  is a virtual ground under steady state conditions.  $Q_2$  conducts the quiescent current of the positive regulator.

If  $-V_{OUT}$  falls,  $V_A$  follows forward biasing collector-base junction of  $Q_1$ .  $V_B$  falls, thus raising the collector voltage of  $Q_2$  and  $+V_{OUT}$  to restore  $V_A$  to desired voltage. Germanium diode  $D_1$  may be needed to start the positive regulator with a high differential load.

**Example:**  $\pm 15$  V, 1 A tracking dual supply:

LM340T-05, LM320T-15.

The 340 will track the LM320 within 100 mV.  $D_2, D_3$ : 1N4720.

### 7.2.4 Variable Tracking Dual Supply $\pm 5.0$ to $\pm 18$ V @ 1 A


 


FIGURE 7.18. Variable Tracking Dual Supply  $\pm 5.0$  V -  $\pm 18$  V

The ground pins of the negative regulator and the positive regulators are controlled by means of a voltage follower and an inverter, respectively. (The same approach is used for the LM340 as in Figure 7.18.) The positive regulator tracks the negative to within 100 mV over the entire output range if  $R_2$  is matched to  $R_3$  within one percent.


### 7.3 DUAL TRACKING REGULATORS

 

NOTE: PIN NUMBERS FOR METAL CAN PACKAGE ONLY.

(a)

FIGURE 7.19 (a). Basic Dual Regulator.

 


(b)

FIGURE 7.19b. Basic Dual Regulator for the 14-Pin Package\*
 
### 7.3.1 High Current Regulator

The basic dual regulator is shown connected in Figure 7.19. The only connections required other than plus and minus inputs, outputs, and ground are the completion of the output current paths from +RCL to +V<sub>OUT</sub> and from -RCL to -V<sub>IN</sub>. These may be direct shorts if the internal preset current limit is desired, or resistors may be used to set the maximum current at some level less than the internal current limit. The internal 300 Ω resistors from pins 3 to 1 and pins 8 to 6 should be shorted as shown when no external pass transistors are used. To improve line ripple rejection and transient response, filter capacitors may be added to the inputs, outputs, or both, depending on the unregulated input available. If a very low noise output voltage is desired, a capacitor may be connected from the reference voltage pin to ground, thus shunting noise generated by the reference zener. Figure 7.20 shows the internal current-limiting characteristics for the basic regulator circuit of Figure 7.19.



(A)

### 7.3.1 High Current Regulator


 


FIGURE 7.21. Boosted High Current Regulator

For applications requiring more output current than can be delivered by the basic regulator, an external NPN pass transistor may be added to each regulator. This will increase the maximum output current by a factor of the external transistor beta. The circuit for current boosted operation is shown in Figure 7.21.

**\*Note:** In the 14-pin package (N and S packages) the -SENSE pin (pin 6) has been brought out of the chip, and therefore should be connected to the -V<sub>O</sub> pin (pin 7). The remaining applications circuits are shown for the TO-5 package. These circuits also apply for the 14-pin N package, provided that the -V<sub>O</sub> pin is connected to the -SENSE pin (normally done at the load to eliminate effects of supply line voltage drop).

 

(B)

FIGURE 7.20. Internal Current Limiting Characteristics



In the boosted mode, current limiting is often a necessary requirement to insure that the external pass device is not overheated or destroyed. Experience shows this to be the usual cause of IC regulator failure. If the regulator output is grounded the pass device may fail and short, destroying the regulator. To limit the maximum output current, a series resistor ( $R_{CL}$  in Figure 7.21) is used to sense load current. The regulator will current limit when the voltage drop across  $R_{CL}$  equals the current limit sense voltage found in Figure 7.22. Figure 7.23 shows the external current limiting characteristics unboosted and Figure 7.24 shows the external current limiting characteristics in the boosted mode.

To ensure circuit stability at high currents in this configuration, it may be necessary to bypass each input with low inductance, tantalum capacitors to prevent forming resonant circuits with long input leads;  $C \geq 1.0\mu\text{F}$  is recommended. The same problem can also occur at the regulator output where a  $C \geq 10\mu\text{F}$  tantalum will ensure stability and increase ripple rejection.

 


FIGURE 7.22. Current Limit Sense Voltage for a 0.1% Change in Regulated Output Voltage

The 2N3055 pass device is low in cost and maintains a reasonably high beta at collector currents up to several amps. The devices 2N3055 may be of either planar or alloy junction construction. The planar devices, have a high  $f_T$  providing more stable operation due to low phase shift. The alloy devices, with  $f_T$  typically less than 1.0 MHz, may require additional compensation to guarantee stability. The simplest compensation for the slower devices is the use of output filter capacitor values greater than  $50\mu\text{F}$  (tantalum). An alternative is to use an RC filter to create a leading phase response to cancel some of the phase lag of the devices. The stability problem with slower pass transistors, if it occurs at all, is usually seen only on the negative regulator. This is because the positive regulator output stage is a

conventional Darlington while the negative output stage contains three devices in a modified triple Darlington connection giving slightly more internal phase shift. Additional compensation may be added to the negative regulator by connecting a small capacitor in the 100 pF range from the negative boost terminal to the internal reference. Since the positive regulator uses the negative regulator output for a reference, this also offers some additional indirect compensation to the positive regulator.

 


FIGURE 7.23. External Current Limiting Characteristic-Unboosted

 


FIGURE 7.24. External Current Limiting Characteristics-Boosted


### 7.3.2 7-Amp Regulator

In Figure 7.25 the single external pass transistor has been replaced by a conventional Darlington using a 2N3715 and a 2N3772. With this configuration the output current can reach values to 10A with very good stability. The external Darlington stage increases the minimum input-output voltage differential to 4.5V. When current limit protection resistor is used, as in Figure 7.25, the maximum output current is limited by power dissipation of the 2N3772 (150W at 25°C). During normal operation this is  $(V_{IN} - V_{OUT}) I_{OUT}$  (W), but it increases to  $V_{IN} I_{SC}$  (W) under short circuit conditions. The short circuit output current is then:

$$I_{SC} = \frac{P_{MAX} (T_C = 25^\circ C)}{V_{IN}}$$

$$= \frac{150W}{20V (min)} = 7.5A \text{ max.}$$

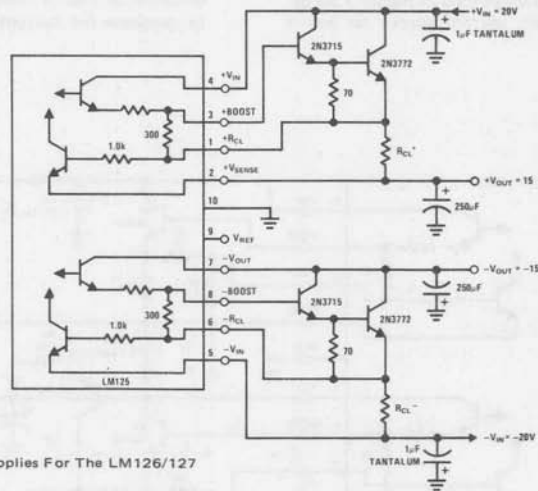$I_L$  could be increased to 10A or more only if  $I_{SC} < I_L$ . A foldback current limit will accomplish this. The typical load regulation is 40 mV from no load to a full load. ( $T_J = 25^\circ C$ , pulsed load with 20 ms  $t_{ON}$  and 250 ms  $t_{OFF}$ .)



Note: The Same Circuit Applies For The LM126/127

FIGURE 7.25. High Current Regulator Using a Darlington Pair for Pass Elements


### 7.3.3 Foldback Current Limiting

In many regulator applications, the normal operation power dissipation in the pass device can easily be multiplied by a factor of ten or more when the output is shorted. This may destroy the pass device, and possibly the regulator, unless the heat sink is oversized to handle this fault condition. A foldback current limiting circuit reduces short circuit output current to a fraction of the full load output current thus avoiding the need for larger heat sink. Figure 7.26 shows a foldback current limiting circuit on both positive and negative regulators.

The foldback current limiting, a fraction of the output voltage must be used to oppose the voltage across the current limit sense resistor. Current limiting does not occur until the voltage across the sense resistor is higher than this opposing voltage by the amount shown in Figure 7.22. When the output is grounded, the opposing voltage is no longer present so current limiting occurs at a lower level. This is accomplished in Figure 7.26 by using a programmable current source to give a

constant voltage drop across R5 for the negative regulator, and by a simple resistor divider for the positive regulator. The reason for the difference between the two is that the negative regulator current limiting circuit is located between the output pass transistor and the unregulated input while the positive regulator current limiter is between the output pass transistor and the regulated output.

The operation of the positive foldback circuit is similar to that described in NSC application note AN-23. A voltage divider R1 and R2 from  $V_E$  to ground creates a fixed voltage drop across R1 opposite in polarity to the drop across  $R_{CL}^+$ . When the load current increases to the point where the drop across  $R_{CL}^+$  is equal to the drop across R1 plus the current limit sense voltage given in Figure 7.22, the positive regulator will begin to current limit. As the positive output begins to drop, the voltage across R1 will also decrease so that it now requires less load current to produce the current limit sense voltage. With

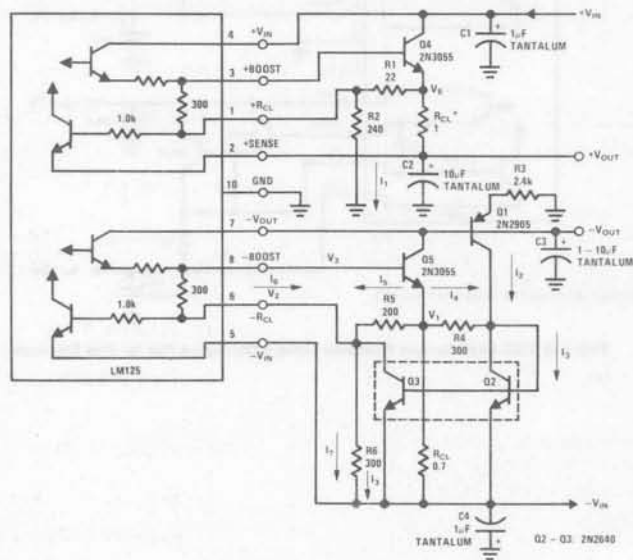

Note: For LM126 (127);  $V_{IN}^+ = 25$  (20)V,  $V_{IN}^- = 25$ V  
 $R_1 = 20$  (22),  $R_2 = 180$  (80)  
 $R_{CL}^+ = 0.9$   
 $R_3 = 1.35$  K,  $R_6 = 290$ ;  $R_{CL}^- = 0.9$   
 $I_{FB} = \pm 2$ A,  $I_{SC} = \pm 0.75$ A

FIGURE 7.26. Foldback Current Limiting Circuit

the regulator output fully shorted to ground (+V<sub>OUT</sub> = 0) the current limit will be set by the value of +R<sub>CL</sub> alone.

$$\text{If } \frac{I_{FB}}{I_{SC}} \leq 5$$

then the following equations can be used for calculating the positive regulator foldback current limiting resistors.

$$R_{CL}^+ \approx \frac{V_{SENSE}}{I_{SC}} \quad (7.16)$$

where V<sub>SENSE</sub> is from Figure 7.22.

At the maximum load current foldback point:

$$V_{R_{CL}}^+ = I_{FB} R_{CL}^+ \quad (7.17)$$

$$V_{R1} = V_{R_{CL}}^+ - V_{SENSE} \quad (7.18)$$

$$V_{R1} = I_{FB} R_{CL}^+ - V_{SENSE} \quad (7.19)$$

Then

$$R1 = \frac{V_{R1}}{I_1} \quad (7.20)$$

and

$$R2 = \frac{+V_{OUT} + V_{SENSE}}{I_1} \quad (7.21)$$

The only point of caution is to ensure that the total current (I<sub>1</sub>) through R2 is much greater than the current contribution from the internal 300Ω resistor. This can be checked by:

$$\frac{I_{FB} R_{CL}^+}{300} \ll I_1 \quad (7.22)$$

Note: The current from the internal 300Ω resistor is V<sub>3-1</sub>/300Ω, but V<sub>3-1</sub> = V<sub>BE</sub> + V<sub>R<sub>CL</sub></sub> - V<sub>SENSE</sub><sup>+</sup> assuming V<sub>BE</sub> ≈ V<sub>SENSE</sub><sup>+</sup> at the foldback point, V<sub>3-1</sub> ≈ V<sub>R<sub>CL</sub></sub> = I<sub>FB</sub> R<sub>CL</sub><sup>+</sup>.

#### Example:

Design a 2 amp regulator using LM125 and positive foldback current limiting (see Figure 7.26).

Given:

$$I_{FOLDBACK} = 2.0A$$

$$I_{SHORT-CIRCUIT} = 500 \text{ mA}$$

V<sub>SENSE</sub> (see Figure 7.22).

$$+V_{IN} = 25V$$

$$+V_{OUT} = 15V$$

$$\beta_{PASS \text{ DEVICE}} = 70$$

$$\theta_{JA} = 150^\circ C/W$$

$$T_A = 50^\circ C$$

With a beta of 70 in the pass device and a maximum output current of 2.0A the regulator must deliver:

$$\frac{2A}{\beta} = \frac{2A}{70} = 29 \text{ mA}$$

The LM125 power dissipation will be calculated ignoring any negative output current for this example.

$$\begin{aligned} P_{LM125} &= (V_{IN} - V_{OUT}) I_{OUT} \\ &= (25 - 15) 29 \text{ mA} \\ &= 290 \text{ mW} \end{aligned}$$

$$T_{RISE} @ \theta_{JA} = 150^\circ C/W = 150^\circ C \times 0.29 = 44^\circ C$$

$$T_J = T_A + T_{RISE} = 50^\circ C + 44^\circ C = 94^\circ C$$

From Figure 7.22

$$V_{SENSE} @ (T_J = 94^\circ C) = 520 \text{ mW}$$

From equation (7.17)

$$R_{CL}^+ = \frac{V_{SENSE}}{I_{SC}} = \frac{520 \text{ mV}}{500 \text{ mA}} \cong 1\Omega$$

From equation (7.18)

$$V_{R_{CL}}^+ = I_{FB} R_{CL}^+ = 2A \cdot 1\Omega = 2V$$

From equation (7.19)

$$V_{R1} = V_{R_{CL}}^+ - V_{SENSE}$$

$$V_{R1} = 2V - 520 \text{ mV} = 1.480V$$

A value for I<sub>1</sub> can now be found from equation (7.22)

$$\frac{I_{FB} R_{CL}^+}{300} = \frac{2A \cdot 1\Omega}{300\Omega} = 6.6 \text{ mA}$$

So set I<sub>1</sub> = 10 x 6.6 mA = 66 mA

Equating equation (7.28) with equation (7.29) and inserting resistor values shown in Figure 7.26,

$$I_2 + I_4 = I_5 + I_6 - I_7$$

$$I_2 + \frac{I_{FB} R_{CL}^- - V_{SENSE}}{300} = \quad (7.34)$$

$$I_5 + \frac{I_{FB} R_{CL}^- - V_{SENSE}}{300}$$

Canceling, we find:

$$I_2 = I_5 \quad (7.35)$$

This is the key to the negative foldback circuit. Current source Q1 forces current  $I_2$  to flow through resistor R5. The voltage drop across R5 opposes the normal current limit sense voltage so that the regulator will not current limit until the drop across  $R_{CL}^-$  due to load current, equals the controlled drop across R5 plus  $V_{SENSE}$  (given in Figure 7.22). This can be written as:

$$I_{FB} = \frac{V_{SENSE} + I_2 R_5}{R_{CL}^-}$$

$$I_{FB} = \frac{V_{SENSE} + 200 I_2}{R_{CL}^-} \quad (7.36)$$

#### Example:

Given:

$$I_{FOLDBACK} = 2.5A$$

$$I_{SHORT-CIRCUIT} = 750 \text{ mA}$$

$$V_{SENSE} \text{ (See Figure 7.22)}$$

$$-V_{IN} = 25V$$

$$-V_{OUT} = -15V$$

$$\beta_{PASS DEVICE} = 90$$

$$\theta_{JA} = 150^\circ\text{C/W}$$

$$T_A = 25^\circ\text{C}$$

The same calculations are used here to figure  $V_{SENSE}$  as with the positive regulator foldback example maximum regulator output current is calculated from:

$$I_{OUT} = \frac{2.5 A}{90} = 28 \text{ mA}$$

$$P_{LM125} = (V_{IN} - V_O) I_{OUT}$$

$$= 10V \times 28 \text{ mA}$$

$$= 280 \text{ mW}$$

$$T_{RISE} = 150^\circ\text{C/W} \times 0.28W = 42^\circ\text{C}$$

$$T_J = T_A + T_{RISE} = 25^\circ\text{C} + 42^\circ\text{C} = 67^\circ\text{C}$$

From Figure 7.22:

$$V_{SENSE} = 500 \text{ mV}$$

From equation (7.23):

$$R_{CL}^- = \frac{500 \text{ mV}}{750 \text{ mA}} = 0.68\Omega$$

From equation (7.36):

$$I_2 = \frac{I_{FB} R_{CL}^- - V_{SENSE}}{200\Omega} = 6.0 \text{ mA}$$

From equation (7.24):

$$R_3 = \frac{V_{OUT} - V_{BEQ1}}{I_2}$$

$$R_3 \approx \frac{14.3}{6.0 \text{ mA}} = 2.4k$$

 


FIGURE 7.28. Negative Regulator Foldback Current Limiting Characteristics

Figure 7.27 and 7.28 show the measured foldback characteristics for the values derived in the design examples. The value of R5 is set low so that the magnitude of  $I_5$  for foldback is greater than  $I_4$  through  $I_6$ . This reduces the foldback point sensitivity to the TC of the internal  $300\Omega$  resistor and any mismatch in the TC of Q2, Q3 or the pass device.

R6 can be computed from equation (7.33):

$$R_6 = \frac{V_{SENSE}^-}{I_7} = \frac{V_{SENSE}^-}{I_5 + I_6 - I_3}$$

combining (7.28) and (7.35).

$$R6 = \frac{V_{SENSE}^-}{I_6 - I_4} = \frac{V_{SENSE}^-}{I_{FB} R_{CL}^- \left( \frac{1}{300} - \frac{1}{R4} \right) + \frac{V_{BE}}{R4}} \quad (7.37)$$

Setting  $V_{BE} \approx V_{SENSE}^-$  and  $R4 = 300$  to match the internal  $300\Omega$  (22) becomes:

$$R6 = R4$$

Also setting  $\frac{I_4}{I_5} = \frac{2}{3} \rightarrow R5 = 200$

### 7.3.4 A 10-Amp Regulator

Figure 7.29 illustrates the complete schematic of a 10A regulator with foldback current limiting. The design approach is similar to that of the 2A regulator. However, in this design, the current contribution from the internal  $300\Omega$  resistor is greater due to the  $2V_{BE}$  drop across the Darlington pair. Expression (7.22) becomes:

$$\frac{I_{FB} R_{CL}^+ + V_{BE}}{300} \ll I_1; \quad (7.38)$$

and, for the negative regulator, expression (7.39) becomes:

$$R6 = \frac{V_{SENSE}^-}{I_{FB} R_{CL}^- \left[ \frac{1}{300} - \frac{1}{R4} \right] + V_{BE} \left[ \frac{1}{300} + \frac{1}{R4} \right]} \quad (7.40)$$

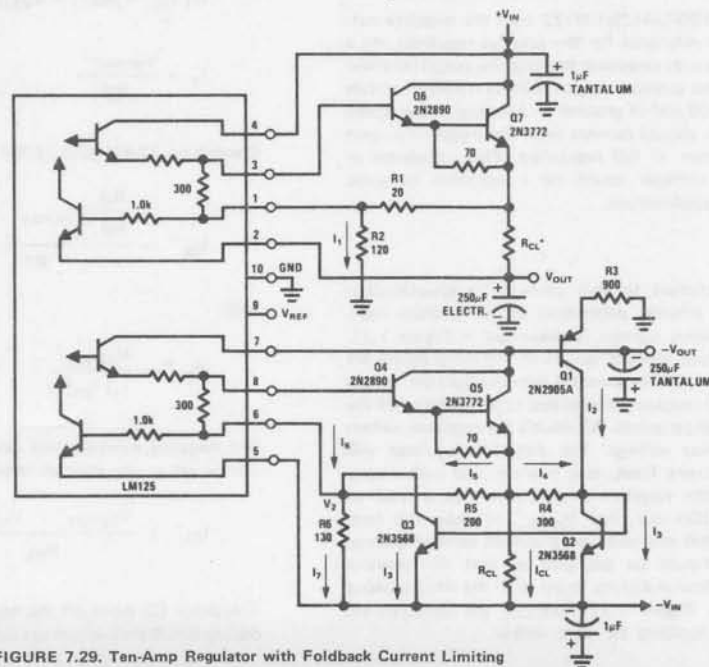


FIGURE 7.29. Ten-Amp Regulator with Foldback Current Limiting

The disagreement between the theoretical and experimental values for the negative regulator is not alarming. In fact  $R_{CL}$  was based on equation (7.23), which is correct if for zero  $V_{OUT}$ ,  $I_5$  is zero as well. This implies:

$$V_{SENSE} \text{ (at SC)} = \frac{V_{BEQ4} + V_{BEQ5}}{2} \text{ (at SC)}$$

which is a first order approximation.

Figure 7.30 illustrates the power dissipation in the external power transistor for both sides. Maximum power dissipation occurs between full load and short circuit so the heat sink for the 2N3772 must be designed accordingly, remembering that

 


FIGURE 7.30. Power Dissipation in the External Pass Transistor (Q5, Q7)

the 2N3772 must be derated according to  $0.86W/^{\circ}C$  above  $25^{\circ}C$ . This corresponds to a thermal resistance junction to case of  $1.17^{\circ}C/W$ .

### Example

Positive Side	Theoretical Value	Experimental Results
$I_{FB} = 10 \text{ A}$	$I_{125} = 13 \text{ mA}$	$I_{FB} = 9.8 \text{ A}$
$I_{SC} = 2.5 \text{ A}$	$P_{LM125} = 150 \text{ mW}$	$I_{SC} = 2.9 \text{ A}$
$V_{IN} = 22 \text{ V}$	$R_{CL}^+ = 0.26 \Omega$	$R_{CL}^+ = 0.26 \Omega$
$V_{OUT} = 15 \text{ V}$	$R1 = 21 \Omega$	$R1$ : adjusted to $20 \Omega$
$\beta = \beta1 \beta2 = 15 \times 50 = 750 \text{ min}$	$R2 = 130 \Omega$	$R2$ : adjusted to $120 \Omega$
$T_A = 25^\circ \text{C}$	$V_{SENSE}^+ = 650 \text{ mV}$	

Negative Side	Theoretical Value	Experimental Results
$I_{FB} = 10 \text{ A}$	$R_{CL}^- = 0.22 \Omega$	$I_{FB} = 10 \text{ A}$
$I_{SC} = 2.5 \text{ A}$	$R4 = 300 \Omega$	$I_{SC} = 2.9 \text{ A}$
$V_{IN} = 22 \text{ V}$	$R5 = 200 \Omega$	$R_{CL}$ : adjusted to $0.3 \Omega$
$V_{OUT} = 15 \text{ V}$	$R6 = 150 \Omega$	$R6$ : adjusted to $130 \Omega$
$\beta = 800$	$R3 = 1.6 \text{ k}\Omega$	$R3$ : adjusted to $900 \Omega$
$T_A = 25^\circ$	$V_{SENSE}^- = 550 \text{ mV}$	
$\frac{I_4}{I_5} = \frac{2}{3}$		

Note: For this example, in designing each side, the power dissipation of the opposite side has not been taken into the account.

### 7.3.5 Positive Current Dependent Simultaneous Current Limiting

The LM125/LM126/LM127 uses the negative output as a reference for the positive regulator. As a consequence, whenever the negative output current limits, the positive output follows tracks to within 200 – 800 mV of ground. If, however, the positive regulator should current limit the negative output will remain in full regulation. This imbalance in output voltages could be a problem in some supply applications.

As a solution to this problem, a simultaneous limiting scheme, dependent on the positive regulator output current, is presented in Figure 7.31. The output current causes an I-R drop across R1 which brings transistor Q1 into conduction. As the positive load current increases  $I_1$  increases until the voltage drop across R2 equals the negative current limit sense voltage. The negative regulator will then current limit, and positive side will closely follow the negative output down to a level of 700 – 800 mV. For  $V_{OUT}^+$  to drop the final 700 – 800 mV with small output current change,  $R_{CL}^+$  should be adjusted so that the positive current limit is slightly larger than the simultaneous limiting. Figure 7.32 illustrates the simultaneous current limiting of both sides.

The following design equations may be used:

$$R1 I_{CL}^+ = R3 I_1 + V_{BEQ1} \quad (7.41)$$

$$I_1 = \frac{V_{SENSE}^-}{R2} \quad (7.42)$$

Combining (7.41) and (7.42)

$$I_{CL}^+ = \frac{\frac{R3}{R2} V_{SENSE}^- + V_{BEQ1}}{R1} \quad (7.43)$$

with

$$R_{CL}^+ = \frac{V_{SENSE}^+}{1.1 I_{CL}^+} \quad (7.44)$$

The negative current limit (independent of  $I_{CL}^+$ ) can be set at any desired level.

$$I_{CL}^- = \frac{V_{SENSE}^- + V_{DIODE}}{R_{CL}^-} \quad (7.45)$$

Transistor Q2 turns off the negative pass transistor during simultaneous current limiting.

From equations (7.20) and (7.21)

$$R1 = \frac{V_{R1}}{I_1} = \frac{1.480V}{66 \text{ mA}} \cong 22\Omega$$

$$R2 = \frac{+V_{OUT} + V_{SENSE}}{I_1} = \frac{15 + 0.520}{66 \text{ mA}}$$

$$\cong 240\Omega$$

The foldback limiting characteristics are shown in Figure 7.27 for the values calculated above at various operating temperatures.

 


FIGURE 7.27. Positive Regulator Foldback Current Limiting Characteristics

The negative regulator foldback current limiting works essentially the same way as the positive side. Q1 forces a constant current,  $I_2$ , determined by  $-V_{OUT}$  and R3, through Q2. Transistors Q2 and Q3 are matched so a current identical to  $I_3$  will flow through Q3. With the output short-circuited ( $-V_{OUT} = 0$ ), Q1 will be OFF, setting  $I_2 = 0$ . The load current will be limited when  $V_1$  increases sufficiently due to load current to make  $V_2$  higher than  $-V_{IN}$  by the current limit sense voltage.

The short circuit current is:

$$I_{SC} \cong \frac{V_{SENSE}}{R_{CL}^-} \quad (7.23)$$

For calculating the maximum full load current with the output still in regulation, current  $I_2$

$$I_2 = \frac{V_{OUT} - V_{BEQ1}}{R3} \quad (7.24)$$

At the point of maximum load current,  $I_{FB}$ , where the regulator should start folding back:

$$V_1 = -V_{IN} + I_{FB} R_{CL}^- \quad (7.25)$$

and

$$V_2 = -V_{IN} + V_{SENSE} \quad (7.26)$$

The current through Q2 (and Q3) will have increased from  $I_2$  by the amount of  $I_4$  due

to the voltage  $V_1$  increasing above its no-load quiescent value. Since the voltage across Q2 is simply the diode drop of a base-emitter junction:

$$I_4 = \frac{[V_1 - (-V_{IN})] - V_{BE}}{R4}$$

Substituting in equation (7.25) gives:

$$I_4 = \frac{I_{FB} R_{CL}^- - V_{BE}}{R4} \quad (7.27)$$

$$= \frac{I_{FB} R_{CL}^- - V_{BE}}{300\Omega}$$

The current through Q2 is now

$$I_3 = I_2 + I_4 \quad (7.28)$$

and the current through Q3 is:

$$I_3 = I_5 + I_6 - I_7 \quad (7.29)$$

The drop across R5 is found from:

$$V_1 - V_2 = (-V_{IN} + I_{FB} R_{CL}^-) - [V_{SENSE} + (-V_{IN})];$$

simplifying,

$$V_1 - V_2 = I_{FB} R_{CL}^- - V_{SENSE} \quad (7.30)$$

Since  $V_{SENSE}$  is the base to emitter voltage drop of the internal limiter transistor, the  $V_{SENSE}$  in equation (7.30) very nearly equals the  $V_{BE}$  in equation (7.27). Therefore the drop across R5 approximately equals the drop across R4. The current through R5,  $I_5$ , can now be determined as:

$$I_5 = \frac{I_{FB} R_{CL}^- - V_{SENSE}}{R5} \quad (7.31)$$

Summing the currents through Q3 is now possible assuming the base-emitter drop of the 2N3055 pass device can be given by  $V_{BE} \cong V_{SENSE}$ :

$$I_6 = \frac{V_3 - V_2}{300} \quad (7.32)$$

where  $V_3 = V_1 + V_{BE} \cong V_1 + V_{SENSE}$

$$I_6 = \frac{V_1 + V_{SENSE} - V_2}{300}$$

Substituting in equation (7.30)

$$I_6 = \frac{I_{FB} R_{CL}^-}{300} \quad (7.33)$$

$$I_7 = \frac{V_2 - (-V_{IN})}{R6} = \frac{V_{SENSE}}{R6}$$



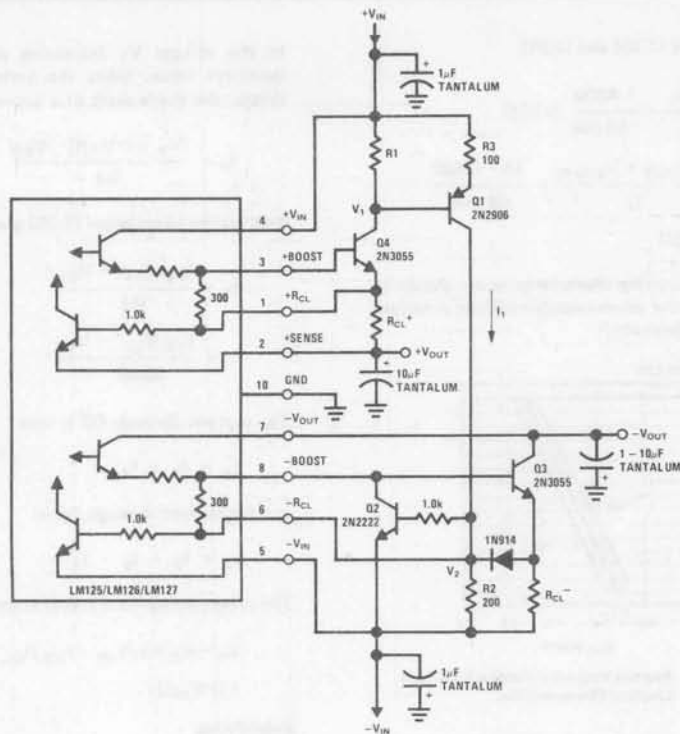


FIGURE 7.31. Positive Current Dependent Simultaneous Current Limiting

 


FIGURE 7.32. Positive Current Dependent Simultaneous Shutdown

### 7.3.6 Electronic Shutdown

In some regulated supply applications it is desirable to shutdown the regulated outputs ( $\pm V_O = 0$ ) without having to shutdown the unregulated inputs (which may be powering additional equipment). Various shutdown methods may be used. The simplest is to insert a relay, a saturated bipolar device, or some other type switch in series with either the regulator inputs or outputs. The switch must be able to open and close under maximum load current which may be several amps.

As an alternate solution, the internal reference voltage of the regulator may be shorted to ground. (See Figure 7.37)

This will force the positive and negative outputs to approximately +700 mV and +300 mV respectively. Both outputs are fully active so the full output current can still be supplied into a low impedance load. If this is unacceptable, another solution must be found.

The circuit in Figure 7.33 provides complete electronic shutdown of both regulators. The shutdown control signal is TTL compatible but by adjusting R8 and R9 the regulator may be shutdown at any desired level above  $2 V_{BE}$ , calculated as follows:

$$V_T \approx \left[ \frac{R8}{R3\beta Q4} + \frac{R9}{R3} \right] V_{BE} + 2 V_{BE} \quad (7.46)$$

Positive and negative shutdown operations are similar. When a shutdown signal  $V_T$  is applied, Q4 draws current through R3 and D2 establishing a voltage  $V_R$  which starts the current sources Q1 and Q2. Assuming that Q1 and Q2 are matched, and making  $R1 = R2 = R3$ , the currents  $I_1, I_2, I_3$  are equal and both sides of the regulator shutdown simultaneously.

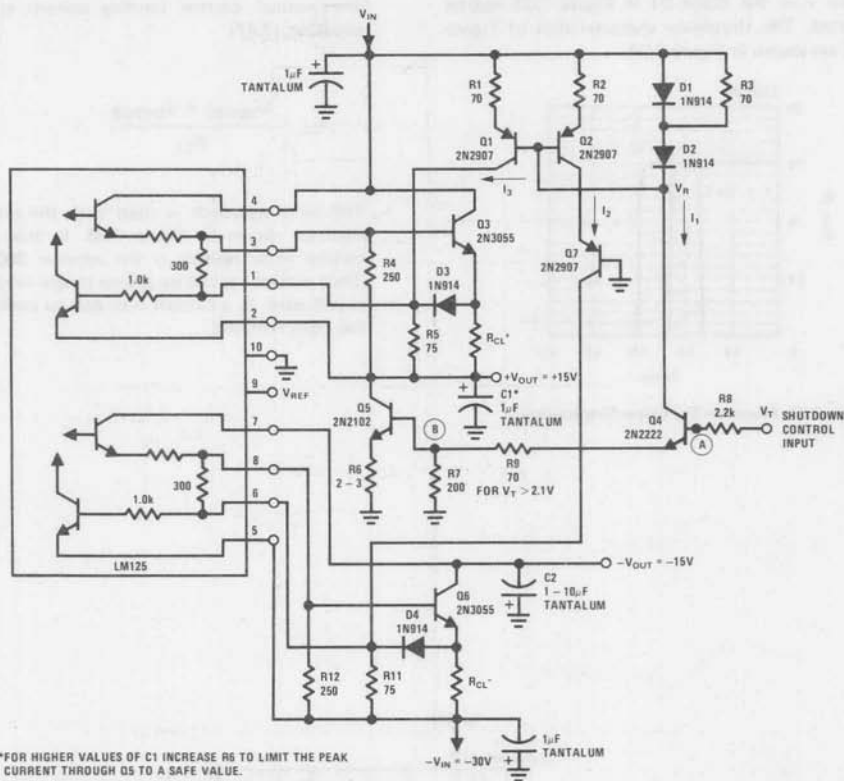


FIGURE 7.33. Electronic Shutdown for the Boosted Regulator

The current  $I_3$  creates a drop across  $R_5$ , which equals or exceeds the limit sense voltage of the positive regulator, causing it to shutdown. Since  $I_3$  has no path to ground except through the load, a fixed load is provided by  $Q_5$ , which is turned on by the variable current source  $Q_4$ .  $C_1$  also discharges through  $Q_5$  and current limiting resistor  $R_6$ . Resistor  $R_4$  prevents  $Q_3$  turn on during shutdown, which could otherwise occur due to the drop across  $R_5$  plus the internal  $300\Omega$  resistor. Diode  $D_3$  prevents  $I_3$  from being shunted through  $R_{CL}$ .

Capacitor  $C_2$  discharges through the load.  $Q_7$  shares the total supply voltage with  $Q_2$ , thus limiting power dissipation of  $Q_2$ . Another power dissipation problem may occur when the design is done for  $V_T = 2.0V$  for example, and  $V_T$  is increased above the preset threshold value.  $I_1$  is increased and  $Q_4$  has to dissipate  $(V_{IN} - 3 V_{BE} - V_T) I_1$  (W). The simplest solution is to increase  $R_8$ . If this is insufficient, a set of diodes may be added between nodes A and B to clamp  $I_1$  to a reasonable value. This is illustrated in Figure 7.34.

$$I_1 = \frac{V_{R9}}{R_9} \approx \frac{V_T - V_{BE} - [V_T - 2 V_{BE}]}{R_9}$$

$$= \frac{V_{BE}}{R_9}$$

 


FIGURE 7.34.

So  $I_1$  is made independent of  $V_T$  and by setting a minimum value of  $10 \text{ mA}$  ( $R_9 = 70\Omega$ ). The regulator will shutdown at any desired level above  $3 V_{BE}$ , without overheating transistor  $Q_4$ . Also using

Figure 7.34 the diode D1 in Figure 7.33 may be omitted. The shutdown characteristics of Figure 7.33 are shown in Figure 7.34.


 


FIGURE 7.35. Electronic Shutdown Characteristics

The normal current limiting current is set by equation (7.47)


$$I_{CL} = \frac{V_{SENSE} + V_{DIODE}}{R_{CL}} \quad (7.47)$$

 The same approach is used with the unboosted regulator shown in Figure 7.36. In this case the voltage sense resistor is the internal  $300\Omega$  one. Since output capacitors are no longer required Q3 is just used as a current sink and its emitter load has been removed.



Note: The Same Circuit Applies For The LM126/127.

FIGURE 7.36. Electronic Shutdown for the Basic Regulator

 

NOTE: PIN NUMBERS FOR METAL CAN PACKAGE ONLY  
 FIGURE 7.37. Simplified Shutdown

### 7.3.7 Power Dissipation

The power dissipation of the LM125 is:

$$P_d = (V_{IN}^+ - V_{OUT}^+) I_{OUT}^+ + (V_{IN}^- - V_{OUT}^-) I_{OUT}^- + V_{IN}^+ I_S^+ + V_{IN}^- I_S^-$$

where  $I_S$  is the standby current.

**Example:**

±1A regulator using 2N3055 pass transistors. Assuming a  $\beta = 100$ , and ±25V supply,

$$P_d = 400 \text{ mW.}$$

The temperature rise for the TO-5 package will be:

$$T_{RISE} = 0.4 \times 150^\circ\text{C/W} = 60^\circ\text{C}$$

Therefore the maximum ambient temperature is  $T_{AMAX} = T_{JMAX} - T_{RISE} = 90^\circ\text{C}$ . If the device is to operate at  $T_A$  above  $90^\circ\text{C}$  then the TO-5 package must have a heat sink.  $T_{RISE}$  in this case will be:

$$T_{RISE} = P_d (\theta_{J-C} + \theta_{C-S} + \theta_{S-A}).$$