



**4-20  
VOLTS**

# REGULATED POWER UNIT

**A. BURNETT**

**T**HE power supply described uses the same feedback principles as in closed loop control systems and is capable of delivering 1A at any voltage between 4V and 20V. A separate 45V d.c. output is also available making the power supply particularly suitable for audio amplifier work where good regulation is required for the low voltage pre-amplifier stages and a higher d.c. supply required for the power output stage, generally of the order of 45V, the regulation of this not being so critical.

Three pairs of sockets for the regulated output have been provided to enable the power supply to supply several loads with the minimum of inconvenience. These outputs have been left floating and a separate earth socket provided such that the supply can be connected to give a positive output with respect to earth or a negative output with respect to earth. The negative output of the 45V supply is connected in common with the negative output of the regulated supply.

Variable current limiting from 0.2A to 1A is included making the power supply particularly suitable for development work and also giving it protection from short-circuit surges.

## Principle

The principle of negative feedback is used in systems where accurate control is required. The system could be a positional servo as used in rudder

control of a model aircraft, speed control of an electric motor, temperature control of a blast furnace or cooker or as in this example, voltage stabilisation. In each case a sample is taken of the final output, a comparison made with some reference, then corrective adjustments made to reduce the error.

The block diagram of Fig. 1 illustrates the principle of voltage control where the controlling device is in series with the output current. The output is monitored by a sampler and the sample voltage compared to a reference voltage by a differential amplifier.

The differential amplifier amplifies the difference such as to starve the output stage of base current if the sample voltage is greater than the reference. As a transistor is basically a current amplifying device complete control of the output current can be achieved by controlling the base current of the current output transistor.

## Current Output Stage

Transistors are current amplifying devices and in general the more current they are capable of handling the less gain they have. A power transistor capable of passing 1A can have a typical  $\beta$  (current gain) of only 10 which would mean that the base current would still be rather high for the differential amplifier to handle, being in the region of 100mA. The current output stage is simply a configuration of two transistors, Tr3 and Tr4, Fig. 2, to give high output current capability with high current gain.

## Constant Current Generator

The output current of this circuit, Tr2, is constant and sufficient to supply the maximum base current of the current output stage with a little extra for the differential amplifier.

The circuit uses the principle that as the base-emitter junction of a transistor is a forward biased diode then it will present a low voltage drop (0.7V in the case of silicon transistors). The zener diode potential will therefore be applied almost completely across R6. The resulting current through R6:—

$$I = (V_z - 0.7) / R6$$

will pass through the transistor without loading the zener diode.

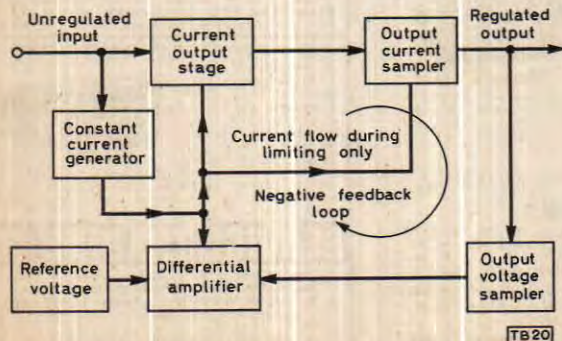


Fig. 1: Block diagram showing function of stages in the power unit.

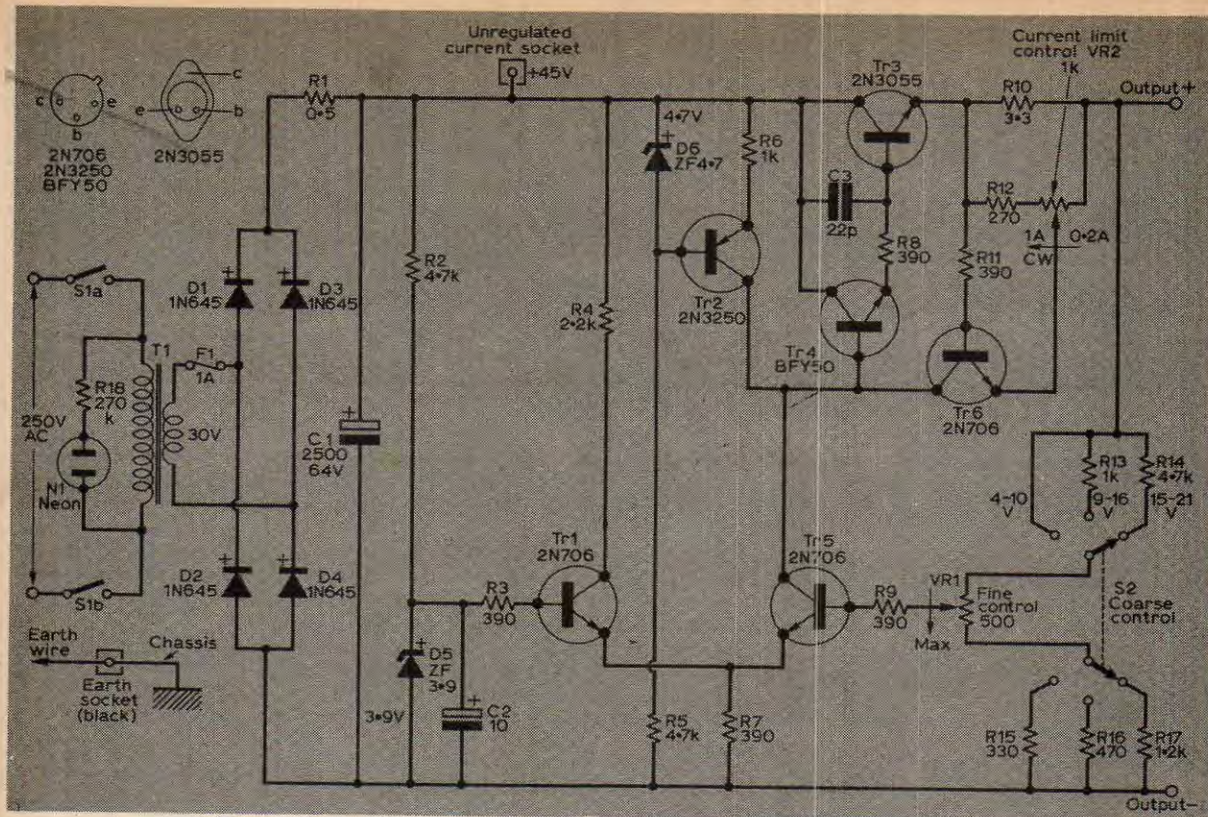


Fig. 2: Circuit of power unit. The diodes D1-4 may be replaced by a single bridge rectifier unit.

Bias current for the zener diode will be supplied by R6. A constant current output of 4mA was sufficient to supply the output stage and the differential amplifier.

stage. It takes current surplus to that required to maintain the correct amount of output current.

The amplifier amplifies the difference between its two inputs hence the term "differential amplifier." In this case it is used as a current control device.

## Differential Amplifier

The differential amplifier, Tr1 and Tr6, is coupled to the base current circuitry of the current output

## Reference Voltage

This is obtained from a zener diode, D5, an attempt being made to keep the diode current constant by connecting a capacitor across it. This is necessary as low wattage zener diodes have a high series internal resistance resulting in their output voltage varying with current.

The regulated output voltage of the power supply would normally be preferred to supply bias current to the zener but as this will be switched over wide ranges in this case, bias current has been supplied from the unregulated input through a 4.7kΩ resistor R2 giving a bias current of 10mA.

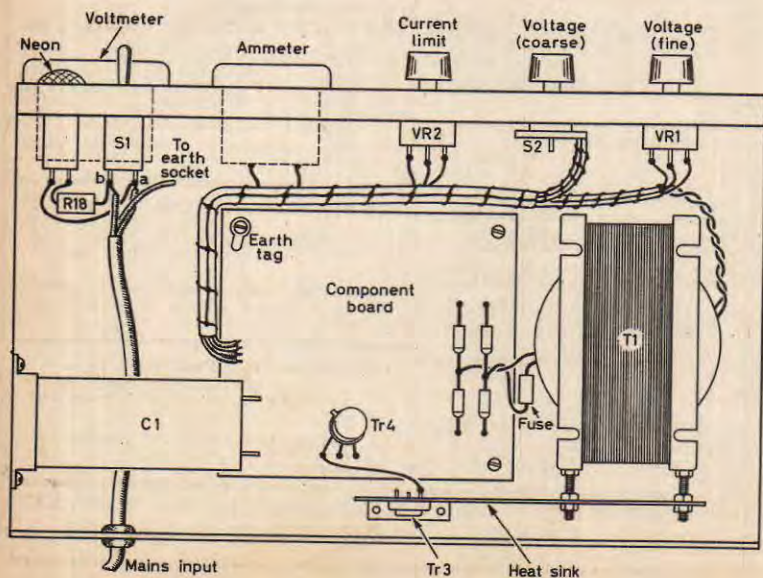


Fig. 3. Layout of unit constructed by the author. See Fig. 4: for details of the component board.

## Output Sampler

The resistor chain is strapped across the output voltage and the tapping point will always be at 3.9V. There are three separate resistor chains in order to reduce the sensitivity of VR1.

It is worth mentioning that the output of this power supply can never be less than the reference voltage generated by D5. If 3.9V is not low enough then a 2.7V zener may be used for D5 and if necessary, the sampling chain recalculated.

## Construction

Not much information need be given on the construction of this unit since much will depend upon the dimensions of the components used. Fig. 4 shows the layout of the component board and the interconnections with the remaining components.

Fig. 3 illustrates the general layout of the power unit as built by the author. Note that the transistor case of Tr3 forms the collector connection and must be insulated from the heat sink with the mica insulation kit generally supplied with the transistor. Check after assembling the transistor and heat sink that there is no conducting path between the transistor case and the heat sink.

The heat sink used here is made from aluminium sheet  $4\frac{1}{2} \times 2\frac{3}{4}$  in. bolted to the main chassis.

It is worth adding that where wire-wound resistors are used there is always a tendency for oscillation to occur. These resistors, from the nature of their construction, are slightly inductive. Often this effect can

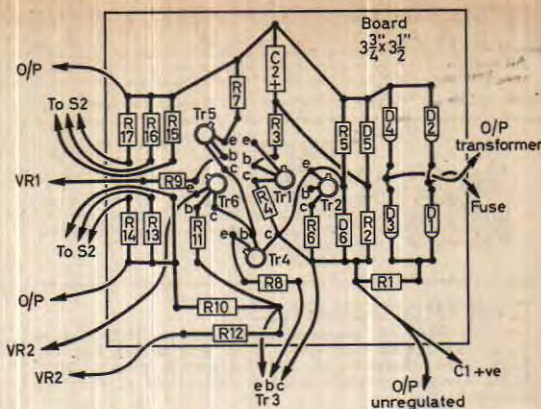


Fig. 4: Layout of component board.

be corrected by the addition of a small capacitor of 20 to 100pF coupled across the resistor to tune out the effect of the inductance. ■

## ★ components list

### Resistors

R1 0.5Ω	R7 390Ω	R13 1kΩ
R2 4.7kΩ	R8 390Ω	R14 4.7kΩ
R3 390Ω	R9 390Ω	R15 330Ω
R4 2.2kΩ	R10 3.3Ω/3W	R16 470Ω
R5 4.7kΩ	R11 390Ω	R17 1.2kΩ
R6 1kΩ	R12 270Ω	R18 270kΩ

All resistors except R10 are  $\frac{1}{4}$ W

VR1 500Ω linear carbon pot

VR2 1kΩ linear carbon pot

### Capacitors

C1 2500μF 64V	C2 10μF 25V
C3 22pF polystyrene	

### Semiconductors

Tr1 2N706 or BC107, 2N930 or 2N2484	
Tr2 2N3250 or BCY30, 31, 32 or 2N3250	
Tr3 2N3055 or BDY 38, with insulating washer etc.	
Tr4 BFY50 or 2N1711, 1613 or BFY51	
Tr5 2N706 or BC107, 2N930 or 2N2484	
Tr6 2N706 or BC107, 2N930 or 2N2484	
D1 1N645	D4 1N645
D2 1N645	D5 ZF3-9 (400mW)
D3 1N645	D6 ZF4-7 (400mW)

### Miscellaneous

Transformer 30V 2A (Type MT3AT). S1, 2 pole 2 way toggle switch. S2, 4 pole 3 way, make before break wafer switch, used as 2 pole 3 way. Sockets, red (4), black (5). Neon lamp, Q1332 (Bulgin) or equivalent; some equivalents have built-in resistor—if so delete R18. Fuse holder with 1A fuse. Vevo-board, plain,  $3\frac{1}{2} \times 3\frac{1}{2}$  in., 0.1 in. matrix. Aluminium chassis,  $10\frac{1}{2} \times 9$  in., panel  $12 \times 9$  in., heat sink  $4\frac{1}{2} \times 2\frac{3}{4}$  in. Voltmeter 20V, ammeter 1A, if required.

# TELEVISION

## DECEMBER ISSUE

### A CLOSER LOOK AT PAL

The basic principles of the PAL system are now generally understood. There is however a good deal more than meets the eye to the system. So this month we are starting a new series in which we shall be investigating the system in greater detail than previously. The account will be descriptive, not a fog of formulae!

### CONSTRUCTORS' CIRCUITS

This month we turn to the line timebase. A choice of transistor or valve line oscillator circuits, both with flywheel synchronisation, and a line output stage with optional stabilisation and optional solid-state e.h.t. and boost rectifier circuits is given.

### THE TELDEC SYSTEM

With the first demonstration of the Teldec system in colour at the recent international Berlin Radio Exhibition this remarkable disc videorecording system is again in the news. A full account of the mechanics of the system.

### RUSSIAN TV RECEIVERS

There are many novel and unusual features in the Temp single-standard receivers manufactured in the USSR and now being widely distributed in the UK. For example, an external definition control varies the vision i.f. response by means of a varicap diode, the line blocking oscillator transformer has an adjustable feed-in point for optimum a.f.c., automatic brightness control is incorporated in the video output stage and amplified negative feedback is used in the field output stage. We are taking a detailed look at this interesting chassis.

PLUS ALL THE REGULAR FEATURES

ON SALE NOVEMBER 22