

designideas

READERS SOLVE DESIGN PROBLEMS

Use an LM317 as 0 to 3V adjustable regulator

Vladimir Rentyuk, Modul-98 Ltd, Zaporozhye, Ukraine

Most engineers know that they can use an inexpensive, three-terminal adjustable regulator, such as Fairchild Semiconductor's (www.fairchildsemi.com) LM317, as an adjustable regulator to only some necessary value of voltage, such as 36 or 3V. This value cannot be less than 1.25V without employing other approaches, however. The devices' inner reference voltage is 1.25V, and their output voltage accordingly cannot be less than this value without potential bias (Reference 1). One way to solve this problem is to use a reference-voltage source based on two diodes (Reference 2). Although this approach is suitable for a 1.2 to 15V or higher-voltage regulator, it is not appropriate for an extra-low-voltage fixed- or adjustable-volt-

age regulator. The two 1N4001 diodes it employs do not provide the needed potential bias of 1.2V, and they have additional temperature instability of approximately 2.5 mV/K (Reference 3). Hence, additional temperature drifting of the output voltage is approximately 100 mV; it is more than 6% for a 1.5V output voltage and 10% for a 1V output voltage if you adjust the temperature to 20°C—a typical indoor situation. You can solve these problems by using a Fairchild Semiconductor LM185 or an Analog Devices (www.analog.com) AD589 adjustable-voltage-reference IC. These devices are expensive, however, and, in this case, they require not only additional zero adjustment but also matching. These adjustments at their reference voltages

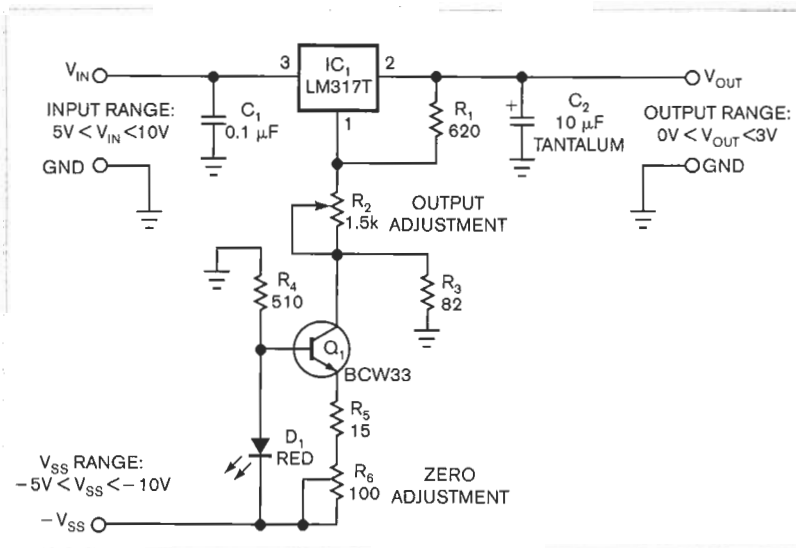


Figure 1 This circuit is an inexpensive approach using a simple 0 to 3V adjustable regulator.

DI's Inside

56 Alarm monitors rotational speed of dc motor

58 Add charging status to simple lithium-ion charger

58 555 timer drives multiple LEDs from one NiMH cell

60 Microcontroller inputs parallel data using one pin

What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

To see all of EDN's Design Ideas, visit www.edn.com/designideas.

are 1.215 to 1.255V and 1.2 to 1.25V for the LM185 and AD589, respectively. Note that the reference voltage of the LM317 is 1.2 to 1.3V.

Figure 1 shows an inexpensive approach using a simple 0 to 3V adjustable regulator. You implement the necessary potential bias using a simple temperature-stabilized constant-current source (Reference 4). You calculate this current source using the following equation: $I = (V_F - V_{EBO}) / (R_5 + R_6)$, where V_F is D_1 's forward voltage of approximately 2V and V_{EBO} is Q_1 's emitter-base voltage of approximately 0.68V. The current is approximately $1.32 / (R_5 + R_6)$. The constant-current source creates a bias voltage of approximately -1.25V on resistor R_3 . You implement the zero adjustment using resistor R_6 , which can change the current of the constant-current source. Resistor R_5 protects transistor Q_1 . You can use D_1 as a light indicator. You can adjust the output voltage using resis-

tor R_2 . Calculate the output voltage as follows: $V_{OUT} = V_{REF}(1 + R_2/R_1) - V_{R3}$, where V_{REF} is the reference voltage of IC_1 and V_{R3} is some compensative voltage of resistor R_3 . You should establish this voltage to equal the reference voltage for its compensation. In this case, $V_{OUT} = V_{REF}(R_2/R_1)$. With R_2 having a value of $1.2\text{ k}\Omega$, this circuit found use as the equivalent of a typical battery

with an output voltage of 1.56V for development projects. **EDN**

REFERENCES

- 1 "LM317 3-Terminal Positive Adjustable Regulator," Fairchild Semiconductor Corp, June 2005, www.fairchildsemi.com/ds/LM/LM317.pdf.
- 2 "LM350 3-Terminal 3A Positive Adjustable Voltage Regulator," Fairchild

Semiconductor Corp, 2001, www.fairchildsemi.com/ds/LM/LM350.pdf.

- 3 Schenk, C, and Ulrich Tietze, *Halbleiter-Schaltungstechnik*, Springer-Verlag Berlin Heidelberg, 2002, ISBN: 3540428496.
- 4 Rentyuk, Vladimir, "The Simple Temperature-Stabilized Constant-Current Source," *Electronics World*, November 2006.