

## Fixed-voltage regulator pair forms bipolar power supply

by S. K. Wong  
Torrance, Calif.

Two fixed-voltage regulators and suitable feedback circuitry can form a bipolar power supply that combines the excellent voltage regulation, trackability, and high current capacity of the three-terminal integrated-circuit voltage regulator with the voltage adjustability of more expensive supplies. This unit provides bipolar voltage from 8 to 20 volts at 1 ampere. The trackability, defined for an adjustable power supply as the voltage difference remaining between the bipolar ports at the desired output voltage, is 1%. Regulation for both line and load is about 100 millivolts.

Many IC bipolar regulators are available, but they provide only 100 milliamperes or so and their output voltages are essentially nonadjustable. Other popular regulators provide high current (up to 3 A) but are fixed-voltage devices. Although IC bipolar regulators can be modified with high-power transistors to boost the output current capability, and separate positive and negative voltage regulators can be connected directly to meet special voltage and power requirements, both designs still lack both adjustability and trackability. These

features are often needed in many applications.

Figure 1 shows the regulated supply that employs two popular three-terminal regulators and a three-transistor feedback circuit. A 115-v, 60-hertz alternating current input is transformed to approximately 40 v across its center-tapped winding, and is rectified and filtered to generate  $\pm 27$  v to the input of the respective regulators. The positive voltage output is:


$$V_P = [1 + (R_2 + R_3)/R_1] V_o + (R_2 + R_3)I_Q$$

where  $V_o$  may nominally range from 5.75 to 6.25 v for the fixed-voltage LM340-06 device and  $I_Q$  is the quiescent regulator current, which is 10 milliamperes maximum and is fairly independent of input voltage and load current. Adjustment of  $R_2$  will change the output voltage, and accordingly, the negative voltage output  $V_N$ . The negative output is:

$$V_N = (1 + R_4/R_5)V_1 + R_4(I_C + I_R)$$

where  $I_R$  is the quiescent regulator current,  $I_C$  is the collector current of transistor  $Q_3$ , and  $V_1$  is the output voltage of the negative regulator.

The LM320-05, which is a  $-5$ -v regulator, and transistors  $Q_1$  through  $Q_3$  form a slaved configuration. A differential amplifier composed of transistors  $Q_1$  and  $Q_2$  monitors the difference in magnitude between  $V_P$  and  $V_N$  through a precision voltage divider  $R_6$  and  $R_7$  and compares it to a zero reference. Normally, the voltage at this junction is zero, because  $V_P = -V_N$ . Any error voltage is amplified to cause a change in the collector

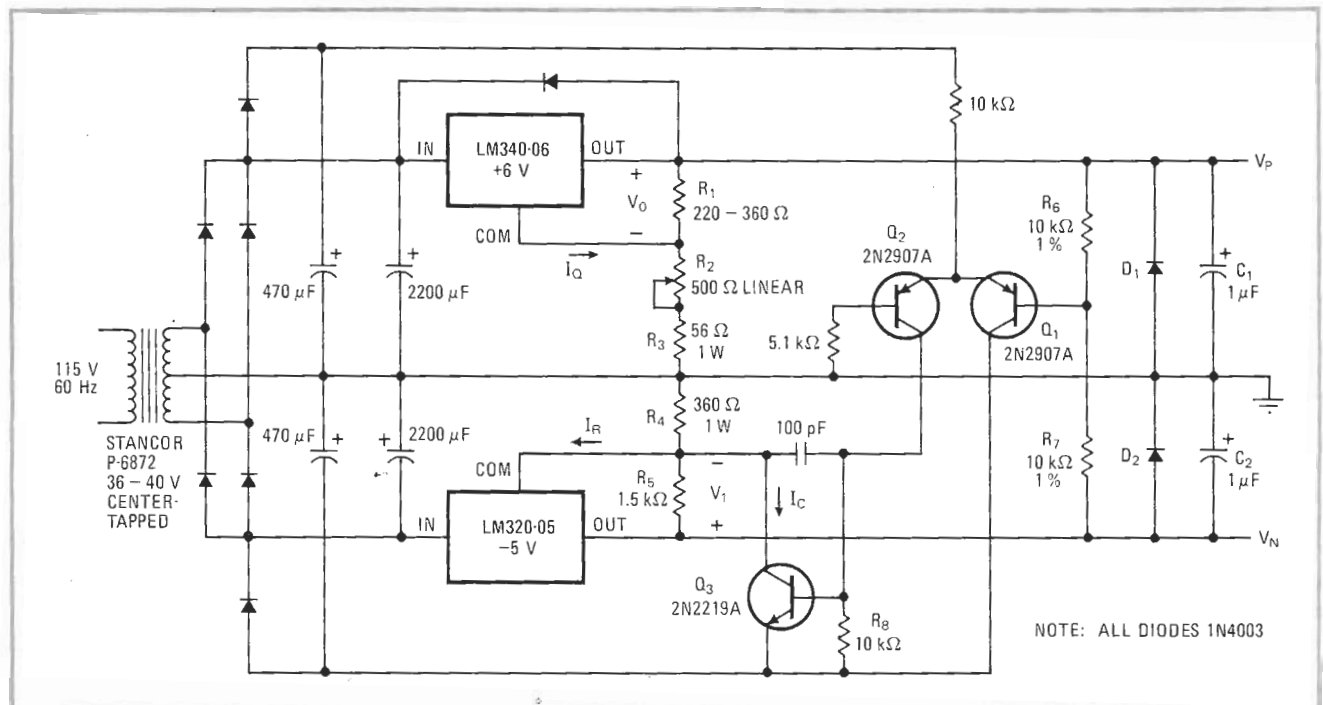

**Bipolar-tracking power supply.** Adjustable voltage output is obtained with fixed-voltage regulators if each regulator is connected back to back through current-varied networks. Circuit retains regulation properties, has high current capability, excellent trackability.

current of  $Q_3$ , which in turn changes the voltage across  $R_4$  and consequently  $V_N$ .

The high output current that can be produced by the supply generates several points where power dissipation is great. Components must be selected to ensure that those levels can be adequately handled. The maximum current through  $Q_3$  is 78 mA. The maximum power consumption is about 500 mw. The 2N2219A transistor

is used for this application. Both regulators should be mounted on suitable heat sinks. Resistor  $R_3$  prevents excessive current through  $R_2$  when its value is low.

Heavy common-mode loads may cause difficulty in the operation of the feedback network during start-up unless diodes  $D_1$  and  $D_2$  are used to clamp the circuit outputs.  $C_1$  and  $C_2$  are tantalum capacitors for improved transient response. □