

Supply derives 5 and 3.3V from USB port

Chad Olson, Maxim Integrated Products, Sunnyvale, CA

THE CIRCUIT IN **Figure 1** derives its power from a USB port and produces 5 and 3.3V supply rails for portable devices, such as digital cameras, MP3 players, and PDAs. The circuit allows the port to maintain communications while, for example, charging a lithium-ion battery. IC₂ boosts the battery voltage, V_{BATT}, to 5V, and IC₃ buck-regulates that 5V output down to 3.3V. IC₁, a lithium-ion battery charger, draws power from the USB port to charge the battery. Pulling its SELI terminal low sets the charging current to 100 mA for low-power USB ports, and pulling SELI high sets 500 mA for high-power ports. Similarly, pulling SELV

high or low configures the chip for charging a 4.2 or 4.1V battery, respectively. To protect the battery, IC₁'s final charging voltage has 0.5% accuracy. The $\overline{\text{CHG}}$ terminal allows the chip to illuminate an LED during charging.

IC₂ is a step-up dc/dc converter that boosts V_{BATT} to 5V and delivers currents as high as 450 mA. Its low-battery detection circuitry and true shutdown capability protect the lithium-ion battery. By disconnecting the battery from the output, "true shutdown" limits battery current to less than 2 μA . An external resistive divider between V_{BATT} and ground sets the low-battery trip point. Connect-

ing the low-battery output, LBO, to shutdown, SHDN, causes IC₂ to disconnect its load in response to a low battery voltage. The internal source impedance of a lithium-ion battery makes IC₂ susceptible to oscillation when its low-battery-detection circuitry disconnects a low-voltage battery from its load. As the voltage drop across the battery's internal resistance disappears, the battery voltage increases and turns IC₂ back on. For example, a lithium-ion battery with 500-m Ω internal resistance, sourcing 500 mA, has a 250-mV drop across its internal resistance. When IC₂'s circuitry disconnects the load, forcing the battery current to

zero, the battery voltage immediately increases by 250 mV.

The n-channel FET at LBO eliminates this oscillation by adding hysteresis to the low-battery-detection circuitry. The circuit in **Figure 1** has a low-battery trip voltage of 2.9V. When V_{BATT} drops below 2.9V, LBO opens and allows SHDN to switch high, turning on the FET. With the FET turned on, the parallel combination of 1.3 M Ω and 249 k Ω eliminates oscillation by setting the battery turn-on voltage to 3.3V. The turn-off and turn-on points are according to the following equations:

$$V_{BATT}(\text{TURN-OFF}) = V_{LBI} \times \frac{R_1 + R_2}{R_2},$$


where $V_{LBI} = 0.85\text{V}$, and

$$V_{BATT}(\text{TURN-ON}) = V_{LBI} \times \frac{R_1 + R'_2}{R'_2},$$

where

$$R'_2 = \frac{R_2 R_3}{R_2 + R_3}.$$

Figure 1

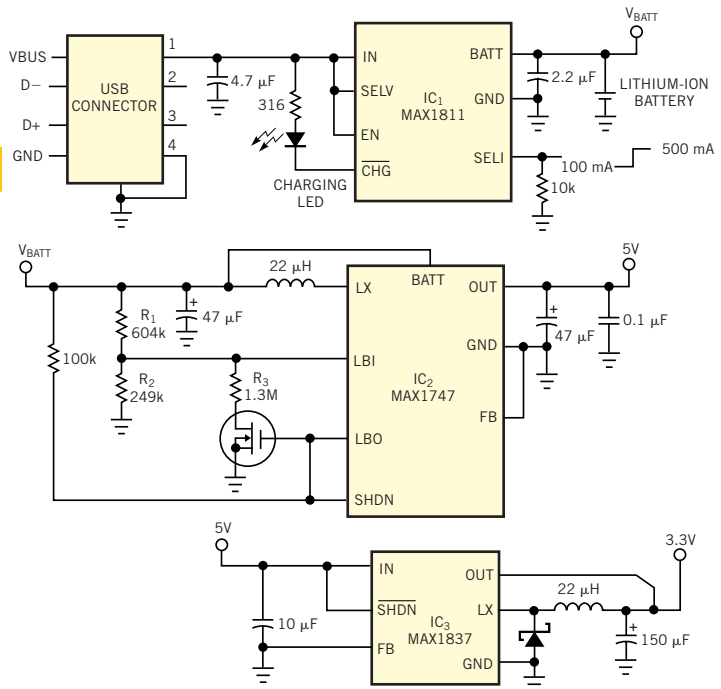

Drawing power from a USB port, this circuit generates 5 and 3.3V supply voltages for portable applications.

Finally, a step-down converter, IC₃, provides buck regulation to convert 5V to 3.3V and delivers currents as high as 250 mA with efficiency exceeding 90%.

Is this the best Design Idea in this issue? Vote at www.ednmag.com.