

Automotive switching regulators get input-transient-voltage protection

Kevin Daugherty, National Semiconductor, Novi, MI

Engineers often face difficult trade-offs when voltage regulators can encounter high-voltage transients that are well above normal input-supply operating ranges. This situation is common in automotive applications in which high-voltage transients from an alternator load dump can produce transients of 36 to 75V for durations as long as 400 msec. Designers must choose between a regulator that can withstand such maximum input voltage or use an input-protection scheme. The simple circuit in this Design Idea provides a highly cost-effective method for clamping an input voltage from a battery input with transients as high as 50V to take advantage of a 20V, 3-MHz regulator. With this

circuit, your design can achieve a small total footprint with relatively low cost because of the 3-MHz operation along with lower voltage components than might otherwise be necessary to withstand 50V.

Input-protection components consist of Q_1 , R_1 , D_1 , C_5 , and one-half of D_2 (Figure 1). At start-up, N-channel MOSFET Q_1 's source is at ground potential and turns on when R_1 applies the battery voltage to the gate. Once the input voltage is above the minimum of 2.74V on IC_1 , the LM2734Z regulator starts switching, which charges the bootstrap circuit comprising D_3 , D_4 , and C_B . This bootstrap voltage of approximately $V_{OUT} - V_{FD}$ (forward-voltage drop) of D_3 then transfers to

the gate source of Q_1 . Capacitor C_5 then maintains gate drive during the bootstrap diode's off times.

Under normal operating conditions, for example, the battery voltage is 8 to 18V, D_1 does not limit conduction of Q_1 , and the gate voltage tracks approximately 2.5V above the input-supply voltage for a low voltage drop from the battery voltage to the input voltage of the LM2734Z. However, when the input voltage increases above the threshold that D_1 sets, the input voltage to the LM2734Z regulates to the zener voltage (V_Z) of D_1 minus the threshold voltage of Q_1 , or approximately $20 - 2V = 18V$, well below the 24V absolute maximum of the LM2734Z. Selecting Q_1 requires careful consideration of maximum input voltage, gate-to-source-voltage threshold, and power dissipation under both steady-state and thermal-transient conditions.

Q_1 , the S11470DN N-channel MOSFET, provides 50V protection

with a drain-to-source voltage (V_{DS}) of $30V + 20V$ (zener diode D_1 voltage), has an on-resistance of $95\text{ m}\Omega$ at a gate-to-source voltage of $2.5V$, and comes in a thermally efficient SC70-6 package. For some applications, the

regulator's output voltage may be insufficient to fully turn on the selected protection MOSFET, so you can increase the bootstrap voltage with a separate zener reference, as the LM2734Z's data sheet shows (Reference 1).EDN

REFERENCE

■ "LM2734Z Thin SOT23 1A Load Step-Down DC-DC Regulator," National Semiconductor, www.national.com/pf/LM/LM2734Z.html.

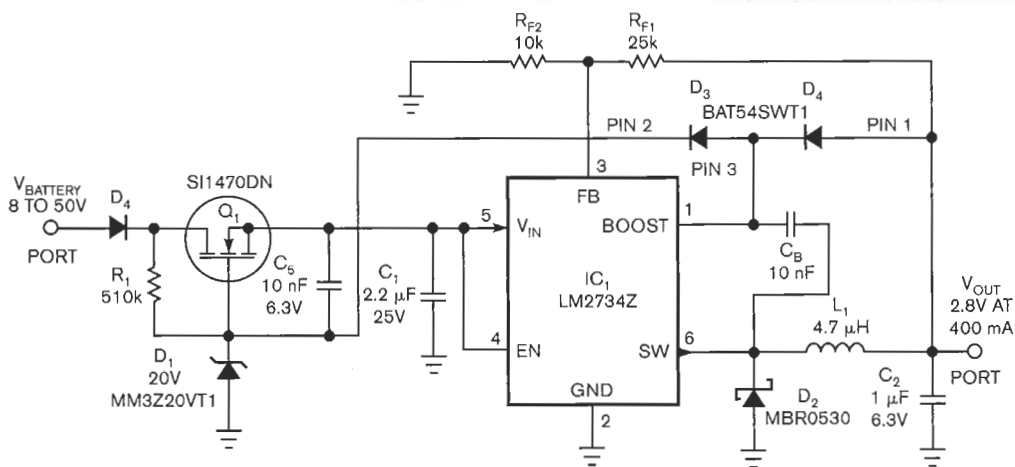


Figure 1 The N-channel MOSFET and zener diode protect the switching regulator against transient voltages as high as $50V$ in automotive applications.

Magnetic Rotary Encoder ICs

- ▶ Contactless
- ▶ 360° Angle Range
- ▶ 8 to 12-bit Resolution
- ▶ AEC-Q100 Qualified
- ▶ Harsh Environments
- ▶ High Temperature & Speed



AS5045
AS5130
AS5043
AS5030
AS5040
AS5140H
AS5046

ab austriamicrosystems

a leap ahead

West Coast (408) 345-1790 East Coast (919) 676-5292
www.austriamicrosystems.com