

**FIG. 1—SCHEMATIC OF THE 3-CHIP LOGIC ANALYZER.** It's made from two cascaded 74LS85 4-bit magnitude comparators (IC1 and IC2), and uses an 8-switch SPST DIP switch S1 and 8-resistor SIP array R3 to set the bit states compared against. The output of IC2 is fed into inverter IC3-d, which feeds into RS flip-flop IC4-a and b, which drives Q1 and LED1.

an IC test clip. The space between the PC board and the tested circuit has to be insulated with a sheet of plastic or small block of wood. At high frequencies, use a shielded enclosure. The prototype PC board operated reliably when unshielded near a 16-MHz video PC board.

### Testing

The circuit can be tested with a static input word on the test leads. When the analyzer's switches (S1-S8) match it, LED1 should light. If the switches are then changed so they no longer match, LED1 should stay lit. If S2 (RESET) is now pressed, LED1 should go out. If that doesn't happen, carefully check your work for wiring errors.


### Applications

There are three tests for which the analyzer is quite useful:

- **Data bus:** Connect the test leads in the correct order to the microprocessor data bus, and check for the desired eight-bit test word. They can be elements of the machine language program, data transmitted to the microcomputer by another device, etc.
- **Address bus:** Connect the test leads to the address bus; since it's often 16 bits long, only half can be monitored at once. The upper half will usually be the most significant, and will show what parts of the address space the system is accessing under program control.
- **Control signals:** Connect the test leads to monitor a selection of control

### PARTS LIST

- All resistors are 1/4-watt, 5%.**  
 R1, R2—10,000 ohms  
 R3-a-R3-i—10,000 ohms × 9 SIP network  
**Capacitors**  
 C1, C2—0.1 μF, ceramic disc  
**Semiconductors**  
 IC1, IC2—74LS85 magnitude comparator  
 IC3—74LS00 quad  $\overline{\text{NAND}}$  gate  
 Q1—2N2222 NPN transistor  
 LED1—light-emitting diode  
**Other components**  
 S1-a-S1-h—8-switch DIP  
 S2—subminiature, momentary, push-button SPST switch  
 TP1-TP8—Molex break-apart IC pins  
**Miscellaneous:** PC board, wire, solder, and heat-shrink tubing.

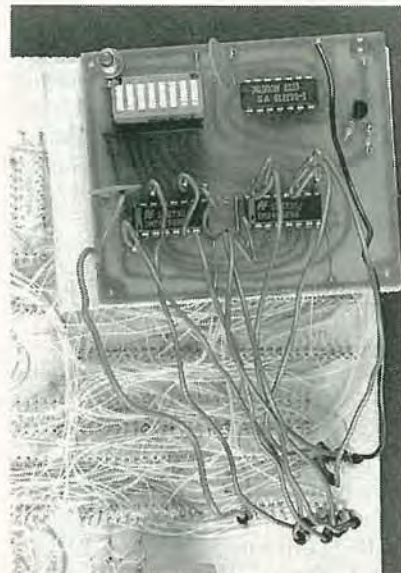

**FIG. 2—PROTOTYPE OF THE 3-CHIP logic analyzer;** note SPST DIP switch S1 and the SIP resistor array R3 at upper left. The eight pins covered with heatshrink tubing are made from Molex break-apart IC pins.

signals, like chip-, write-, and read-enable (CE, WE, and RE) pins of memory devices, I/O selects, etc. That can show whether the CE, WE, and/or RE are simultaneously active, whether multiple memories are simultaneously selected, and happens to be very useful in debugging address decoding algorithms.

To use the analyzer, connect the power and ground to the test circuit points, and the eight test leads to the appropriate signals. When a positive match is found, the LED glows. For the next test, enter a new search word and press S2.

R-E