

AUDIO OSCILLATOR

Audio oscillator utilises new design in frequency meters, giving good accuracy and fast reading rates.

THE AUDIO OSCILLATOR is an almost essential piece of test equipment in any test lab be it professional or only the home workshop. Only the multimeter would rate more highly. We first published a simple sine-square oscillator way back in 1971 and this design is still very popular and selling well. We decided however to bring the design up to date adding a few improvements, and present it again.

Design Features


This oscillator started out as a redesign, mainly mechanical, of the earlier design. It then started to evolve as a voltage controlled sweep oscillator but when it became too complex we reverted to a simple Wein bridge oscillator.

One major problem with all home made oscillators is that of scaling the frequency dial. This is not just a problem of positioning the knob but since normally available potentiometers have a tolerance of +/- 20%, the scale length will also vary. In commercial units the use of an expensive wire wound potentiometer solves most of the problems giving reasonably accurate scaling.

We then decided to build in a frequency meter, basing it on the ETI 533 display module. However the high power consumption (we wanted to allow battery operation) and the poor resolution, especially at low frequency, prompted the design of a completely new frequency meter.

This uses what is literally an analogue computer to convert a period measurement into frequency with some digital electronics controlling it and displaying the results. We based this on the Intersil ICL7106 module which, due to its liquid

Continued on page 38

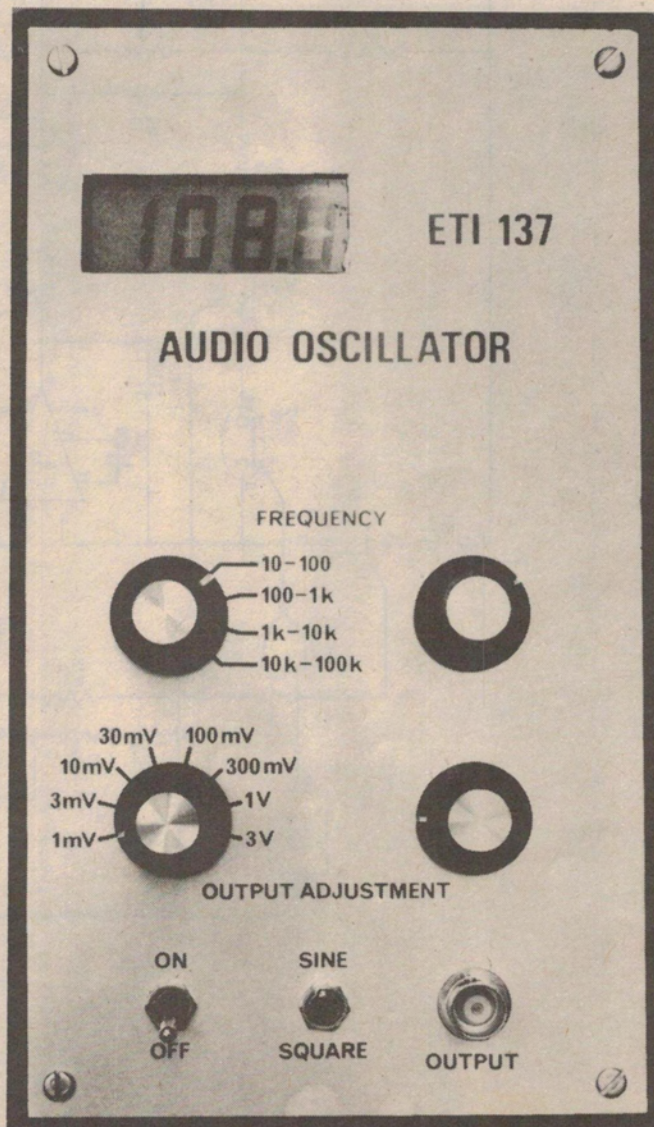

Front view of the audio oscillator. Note that this is an early prototype and the 3V range has been deleted.

HOW IT WORKS - ETI 137

Oscillator

The oscillator is the conventional Wein bridge type by Q1-Q5. Gain stabilization is done by the thermistor TH1. This type of circuit oscillates at the frequency where the impedance of the capacitors equals the resistors in the Wein bridge arms. With this feedback network the attenuation does not vary greatly like that of a twin tee but the phase shift does. The result is a sine wave oscillator with low distortion.

For frequency variation a two gang potentiometer is used to give a 20/1 continuous variation with switched capacitors giving four ranges each a decade apart.

The sine wave output is turned into a square wave by IC1 with the amplitude stabilized by D3-D6.

Frequency Meter

This section works by generating a voltage proportional to the period of one cycle and using this as the reference voltage for the Intersil voltmeter IC with a fixed voltage on the normal input. This gives the inverse function of normal operation and the display therefore is frequency.

To generate the reference voltage we use an integrator (IC6) which is controlled by IC5. Operation is as follows. Initially C3 is discharged and for one cycle of the

input signal IC5/1 turns on. As the module provides a stable voltage between pin 1 and pin 32 of about 2.8V the output of IC6 will fall linearly with time and as IC5/1 is on for exactly one cycle the voltage change will be proportional to that period.

After IC5/1 turns off the output of IC6 will stay fixed. IC5/3 is then turned on and C4 will charge to that voltage. After half a cycle IC5/3 will turn off leaving C4 at that voltage and IC5/2 will turn on. This discharges C3 to zero volts. After a short delay to allow C3 to discharge IC5/4 is turned on transferring that voltage level onto C5. After a total of two cycles the

process recommences. The voltage difference between the two capacitors is therefore the voltage change, (proportional to frequency) thus eliminating any offset errors in IC6. The pulses which control IC5 are derived from IC1/1 and IC4.

A reference voltage less than half the input voltage will result in the ICL7106 counting past 2000 (over ranging). The two inputs must also lie within the supply rails (less 1.5V). This limits the range of the instrument from 5 Hz to 200 Hz. For the higher frequency ranges, three decade dividers are provided and the necessary output selected by IC3. The correct decimal point is also selected by the other half of this IC.

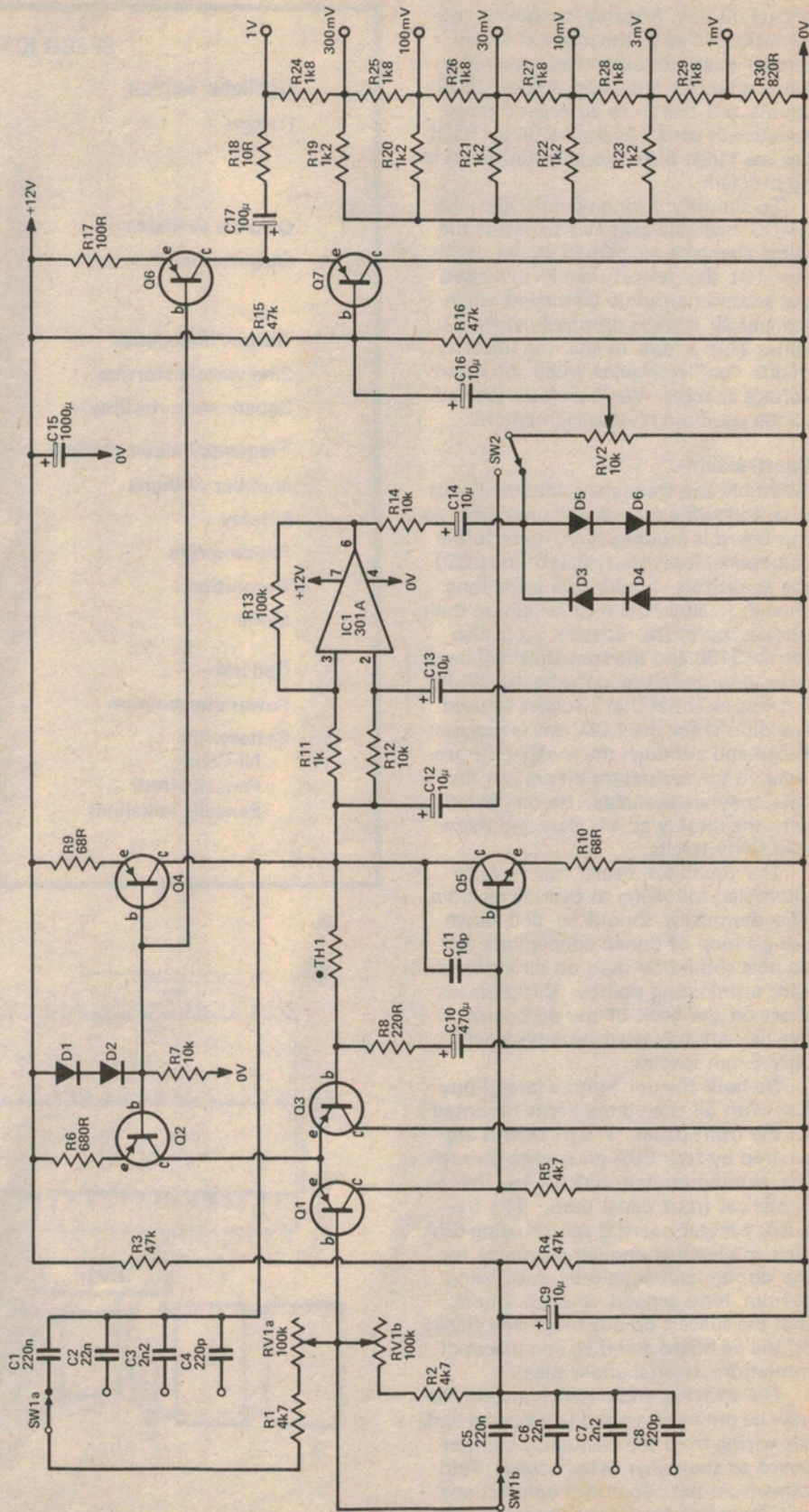


Fig. 2. The circuit diagram of the oscillator section.

Project 137

crystal display, features low power consumption. Due to the method of conversion from period to frequency the range is limited from about 50 to 1999 counts and therefore automatic range selection is used. As the oscillator itself has less range than this, this limitation is no problem.

To simplify wiring we initially used CMOS analogue switches to select the range changing capacitors in the oscillator but this unfortunately increased the second harmonic distortion when the supply voltage dropped below 12 volts. This is due to the non-linearity of the "on" resistance when the input voltage changes. We therefore reverted to the good old mechanical switch!

Construction

Assemble the frequency counter board first, following the overlay provided. As this board is mounted very close to the front panel (only the height of the LCD) the capacitors should have leads long enough to allow them to be laid on their side on top of the resistors, etc. Also the CA3130 and the transistor will have to be mounted close to the board. While it is not essential that a socket be used (we didn't) for the LCD, one is recommended and although the Molex pins provided in the evaluation kit are not the best, they are available. Be very careful with the display as it is glass and therefore fairly fragile.

The oscillator board can now be assembled following its overlay diagram. The thermistor should be tied down using a loop of tinned copper wire and pc pins should be used on all external wire terminating points. Cut all leads short on the back of the pc boards as the two are mounted back-back with only 6 mm spacing.

We built the units into a large zippy box with all the components mounted on the front panel. The pc boards are secured by four 6BA c/s screws through the aluminium but hidden by the Scotchcal front panel used. The frequency meter board is spaced using 6BA nuts to give just enough clearance for the display and is held in place using 6.4mm long tapped spacers. Check that the spacers do not touch any tracks on the pc board and if so add pieces of insulation material under them.

The switches and potentiometers can now be mounted on the front panel and the wiring from the frequency counter board to the range switch done. Add wires from the two power connections and the input for later connection to the oscillator board.

Continued on page 40.

SPECIFICATION – ETI 137

Oscillator section	
Ranges	10.0 – 100.0Hz 100 – 1000Hz 1.00 – 10.00kHz 10.0 – 100.0kHz
Outputs available	sine or square
Output level	1V maximum continuously variable plus 10dB steps down to 1mV
Output impedance	nominally 600 ohms
Sine wave distortion	<0.1%
Square wave risetime	200ns
Frequency meter section	
Number of digits	3½
Display	LCD
Reading rate	5 per second
Resolution	0.1 Hz on lowest range
Mode	Period measurement computed to read frequency
General	
Power consumption	26mA @ 12V dc
Battery life	
Ni Cads	20 hours
Pencells (red)	30 hours
Pencells (alkaline)	50 hours

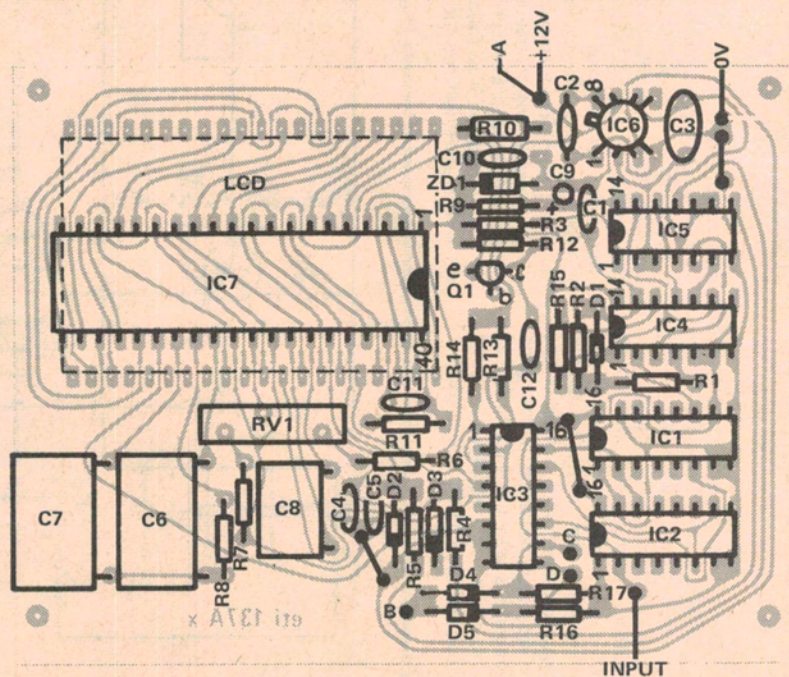


Fig. 3. Component overlay of the frequency meter board. Insert the LCD such that the +1 digit is on the left.

PARTS LIST - ETI 137

General

- Plastic box UB
- 1 One pole 12 position rotary switch
- 1 Three pole 4 position rotary switch
- 2 STDP toggle switches
- 4 knobs to suit
- 12V battery (8x dry cell or 10x Nicads)
- External power socket
- Scotchcal front panel
- Wire, screws etc.

Frequency Counter Board - ETI 137A

Resistors all 1/4W 5%

- R1 10k
- R2,3 1M
- R4,5 1k
- R6 10k
- R7 1k
- * R8 47k
- R9 1k
- R10 4M7
- * R11 100k
- R12 100k
- R13,14 4M7
- R15 1M
- R16,17 100k

Potentiometer

- * RV1 1k ten turn trim

Capacitors

- C1 330p ceramic
- C2 56p ceramic
- C3 100n polyester
- C4,5 10n polyester
- * C6 470n polyester
- * C7 220n polyester
- * C8 100n polyester
- C9 1μ0 35V tantalum
- C10 10n polyester
- * C11 100p ceramic
- C12 10n polyester

Semiconductors

- IC1,2 4518 (CMOS)
- IC3 4052 (CMOS)
- IC4 4001 (CMOS)
- IC5 4016 (CMOS)
- IC6 CA3130
- * IC7 ICL7106
- Q1 BC549
- D1-D5 1N914
- ZD1 10V 300mW Zener

Miscellaneous

- PCB ETI 137A
- * LCD display

* These parts are provided in the Intersil ICL7106 Evaluation Kit.

Oscillator Board - ETI 137B

Resistors all 1/2W 5%

- R1,2 4k7
- R3,4 47k
- R5 4k7
- R6 680R
- R7 10k
- R8 220R
- R9,10 68R
- R11 1k
- R12 10k
- R13 100k
- R14 10k
- R15,16 47k
- R17 100R
- R18 10R
- R19-R23 1k2
- R24-R29 1k8
- R30 820R

Thermistor

- TH1 type R53

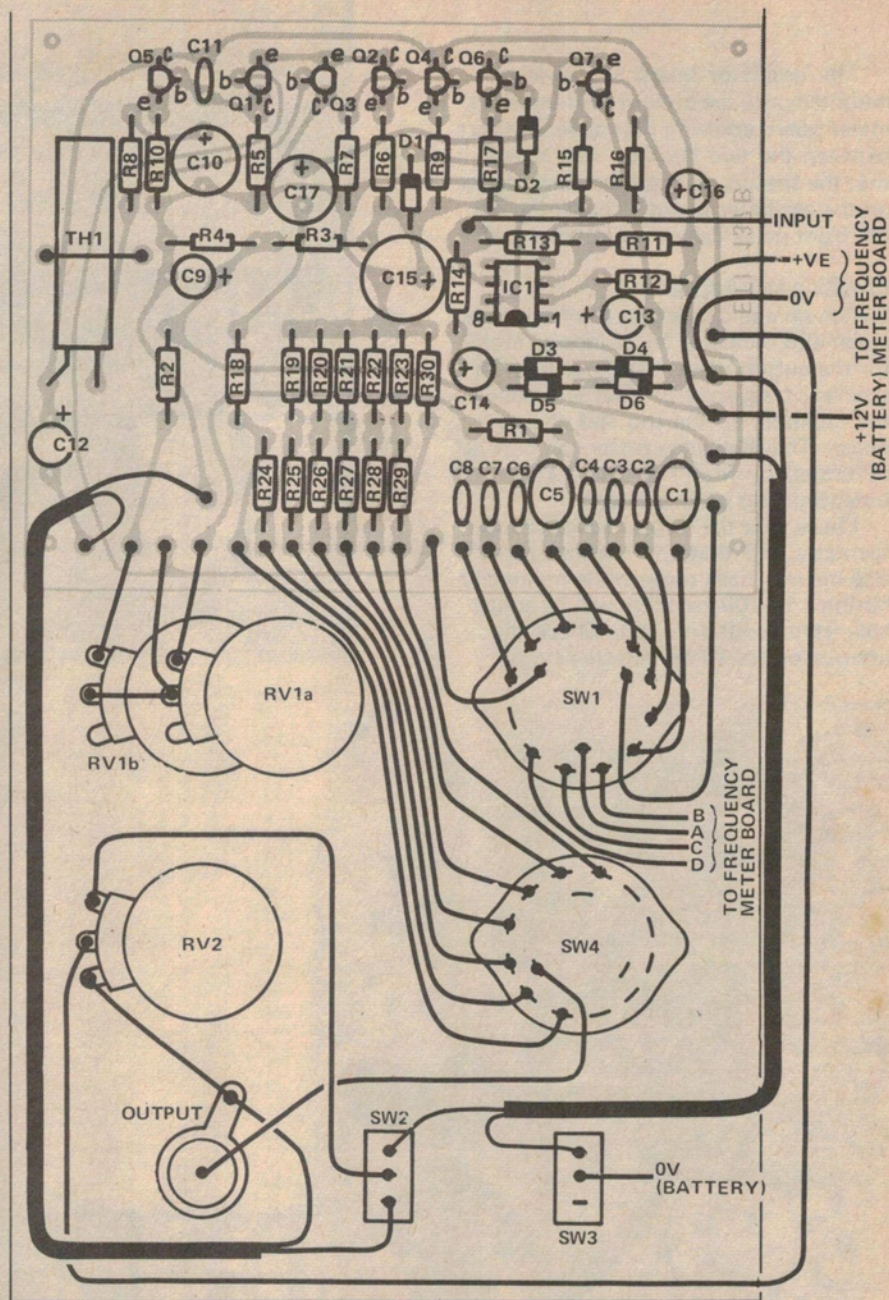


Fig. 4. The component overlay of the oscillator board and the wiring of the front panel.

Potentiometers

- * RV1 100k dual rotary
- RV2 10k lin rotary

Capacitors

- C1 220n polyester
- C2 22n polyester
- C3 2n2 polyester
- C4 220p ceramic
- C5 220n polyester
- C6 22n polyester
- C7 2n2 polyester
- C8 220p ceramic
- C9 10μ 25V electro
- C10 470μ 25V Electro
- C11 10p ceramic
- C12-C14 10μ 25V electro
- C15 1000μ 16V electro

- C16 10μ 25V electro
- C17 100μ 25V electro

Semiconductors

- IC1 301A
- Q1-Q4 BC559
- Q5 BC549
- Q6,7 BC559
- D1-D6 1N914

Miscellaneous

- PCB ETI 137B

* RV1 - the preferred curve giving best resolution is antilog. If reverse rotation is acceptable log is as good. Otherwise use a linear curve.

Project 137

The oscillator board can now be mounted onto the back of the frequency meter board ensuring that no leads short between the two boards. Also check that the spacers do not touch any tracks on the oscillator board. The wiring of the front panel can now be completed.

Checking and Adjustment

Switch on and check that the frequency meter and oscillator are working. Monitor the output of the oscillator with an accurate frequency counter and adjust the oscillator to the top end of one range. The frequency meter can now be calibrated by means of the 10 turn potentiometer on that board.

Check that the display range changes correctly and that the decimal point also moves. Each range while nominally having a 10-100 variation will be adjustable from about 7 to 150. Check the attenuator has 10 dB between steps.

