



Fig. 31 *Linear-scale ohmmeter.*

HOME OHM

Finally, to conclude, Fig. 31 shows how the 741 op-amp can be used in conjunction with a 1mA f.s.d. meter to make a linear-scale ohmmeter that has five decade ranges from 1k to 10M.

The circuit is divided into two parts, and consists of a voltage generator that is used to generate a standard test

voltage, and a readout unit which indicates the value of the resistor under test.

The voltage generator section of the circuit comprises zener diode ZD_1 , transistor Q_1 , and resistors R_1 to R_4 . The action of these components is such that a stable reference potential of 1V is developed across R_4 , but is adjustable over a limited range via RV_1 . This voltage is fed to the input of the op-amp readout unit. The op-amp is wired as an inverting d.c. amplifier, with the 1mA meter and RV_3 forming a 1V f.s.d. meter across its output, and with the op-amp gain determined by the

values of ranging resistors R_5 to R_9 and by negative feedback resistor R_x .

Since the input to the amplifier is fixed at 1V, the output voltage reading of the meter is directly proportional to the value of R_x , and equals full scale when R_x and the ranging resistor values are equal. Consequently, the circuit functions as a linear-scale ohmmeter.

CALIBRATION

The procedure for initially calibrating the Fig. 1.31 circuit is as follows. First, switch the unit to the $10k\Omega$ range and fix an accurate $10k\Omega$ resistor in the R_x position. Now adjust R_3 to give an accurate 1V across R_5 , and then adjust R_{12} to give a precise full scale reading on the meter. All adjustments are then complete, and the circuit is ready for use.