

## DMM ADD-ON

In reference to the "DMM Add-On" ("New Ideas," October 1982 issue), I must admit that, for me, the article does not compute. There was no rationale given for the "divide 4000 by the meter reading."

By my logic, I would consider the simplified circuit to be as you see it in Fig. 1.

Consider  $R_x$  to be 100 megs; then  $R$  total =  $100 + 0.5025 = 100.5025$  megs. Total current =

$$\frac{E}{R} = \frac{8}{100,502,500} =$$

0.0000000796 amperes.

The DMM should read the voltage drop across 0.5025 megs.  $E = IR = 0.0000000796 \times 502,500 = 0.039999005$  volts; that rounds out to 0.04 volts (meter reading).

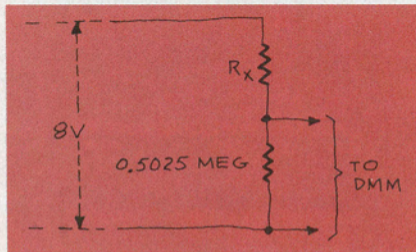


FIG. 1

According to the article,

$$R_x = \frac{4000}{0.04} = 100,000 \Omega$$

That is not 100 megohms!

100 megohms can be derived by first determining the voltage drop across  $R_x = 8V - 0.040V = 7.96V$ . Then

$$R = \frac{E}{I} = \frac{7.96}{0.0000000796} = 100,000,000$$

or 100 megohms. Or the formula could be used:

$$R_x = \frac{E_{RX}}{E_{DMM}} \times \frac{0.5025 \text{ megs}}{1}$$

JOSEPH S. RIZK  
Jacksonville, FL

*In the 200-millivolt range, the meter reading is 40—not 0.04. To obtain the correct resistance in megohms, divide 4000 by the actual meter reading—not the voltage value.—Editor.*

## AGREEMENT

I agree with Mr. Joseph W. Miller's suggestion in the "Letters" section of the January